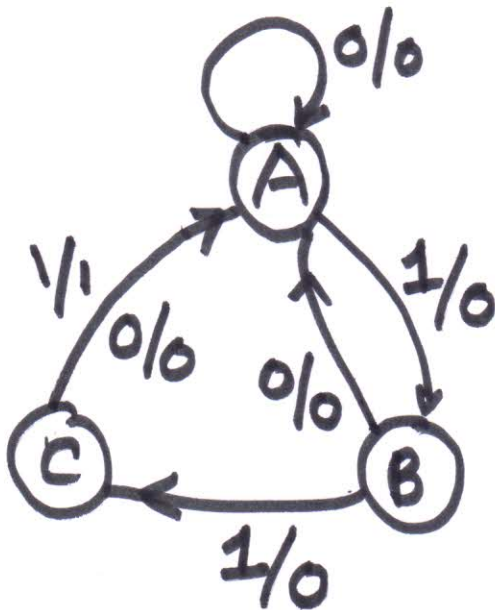


2. A Mealy system with one input  $x$  and one output  $z$  such that  $z=1$  iff  $x$  has been 1 for three consecutive clocks, but inputs are nonoverlapping.

$x$ : 0 1 0 1 1 1 1 1 0 0 1 1 1 1 0 1  
 $z$ : 0 0 0 0 0 1 0 0 0 0 0 0 1 0 0



A: no 1's

B: only one 1

C: Two ~~th. of~~ 1's  
~~more~~

### State Transition table

Present States	Next states		output(z)	
	$x=0$	$x=1$	$x=0$	$x=1$
A	A	B	0	0
B	A	C	0	0
C	A	A	0	1

A → 00  
 B → 01  
 C → 11

Present States		I/p x	Next States		I/p to D-FF		O/p (z)
q <sub>1</sub>	q <sub>0</sub>		q <sub>1</sub> <sup>+</sup>	q <sub>0</sub> <sup>+</sup>	d <sub>1</sub>	d <sub>0</sub>	
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	0	0	0	0
0	1	1	1	1	1	1	0
1	0	0	x	x	x	x	0
1	0	1	x	x	x	x	0
1	1	0	0	0	0	0	0
1	1	1	0	0	0	0	1

d<sub>1</sub>

q <sub>1</sub> q <sub>0</sub> \ x	0	1
00		
01		1
11		
10	x	x

$$d_1 = \overline{q_1} q_0 x$$


d<sub>0</sub>

q <sub>1</sub> q <sub>0</sub> \ x	0	1
00		
01		1
11		
10	x	x

$$d_0 = \overline{q_1} x$$

$$z = q_1 q_0 x$$

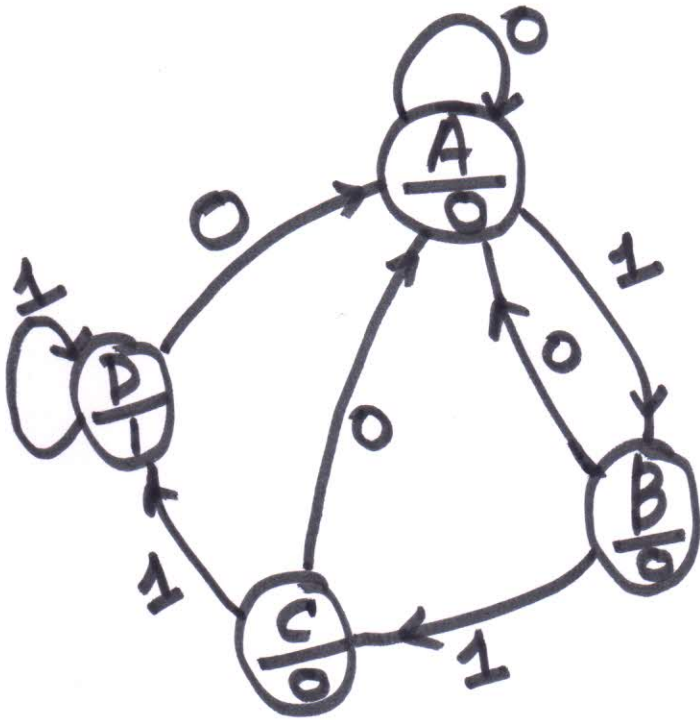3. Design a Moore system with an output of 1 iff the input has been 1 for at least three consecutive clocks.



A: no 1's

B: one 1

C: Two 1's

D: Three or more 1's

A: 00

B: 01

C: 10

D: 11

### State Transition table

Present States	Next States		output(z)
	x=0	x=1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1



TT

Present States $q_1 \ q_0$		$y_p$ $x$	Next States $q_1^+ \ q_0^+$		$y_p$ to D-FF $d_1 \ d_0$	Output ( $z$ )
0 0		0	0 0		0 0	0
0 0		1	0 1		0 1	0
0 1		0	0 0		0 0	0
0 1		1	1 0		1 0	0
1 0		0	0 0		0 0	0
1 0		1	1 1		1 1	0
1 1		0	0 0		0 0	1
1 1		1	1 1		1 1	1

$d_1$

$q_1, q_0 \backslash x$	0	1
00		
01		1
11		1
10		1

$$d_1 = q_0 x + q_1 x$$

$$= (q_0 + q_1) x$$


$$z = q_1 q_0$$

$d_0$

$q_1, q_0 \backslash x$	0	1
00		1
01		
11		1
10		1

$$d_0 = q_1 x + \bar{q}_0 x$$

$$= (q_1 + \bar{q}_0) x$$

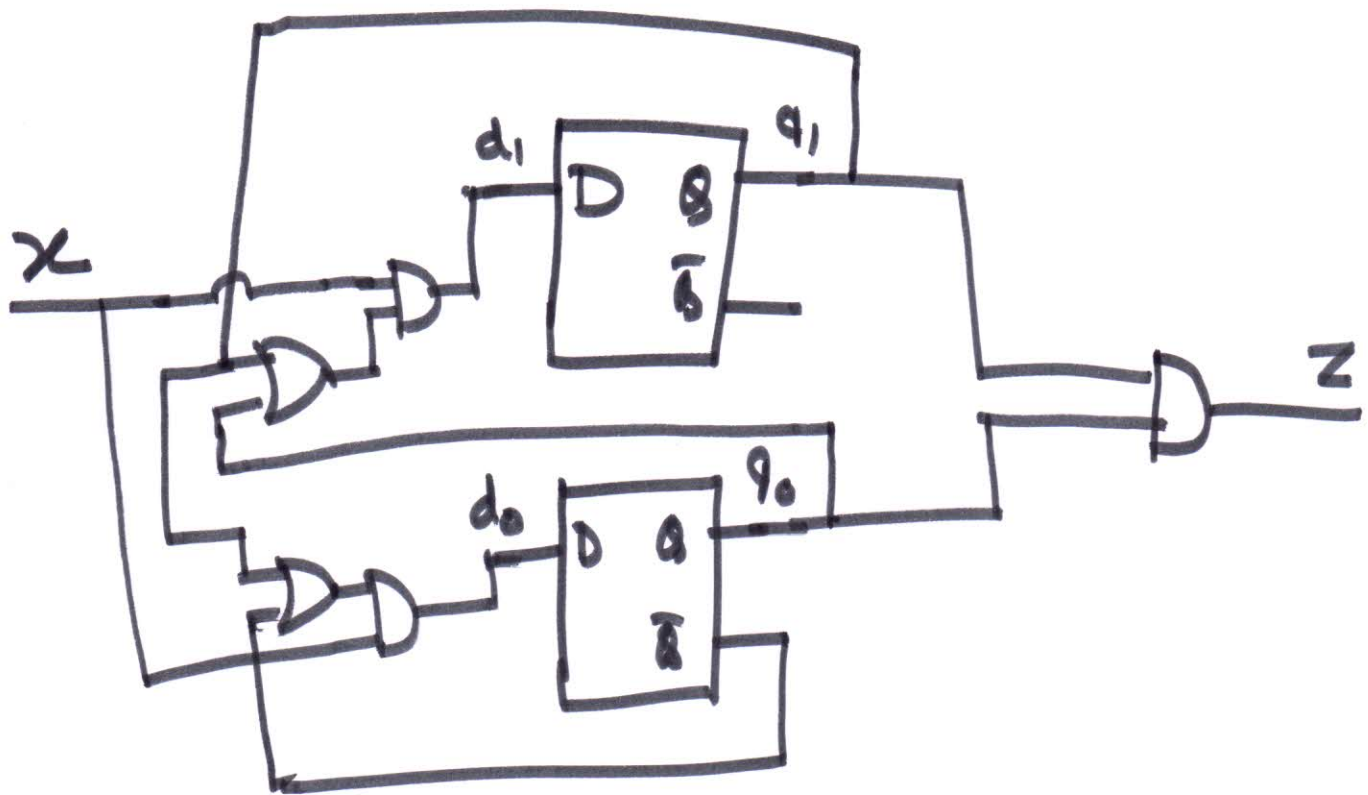


$x$ : 0 1 0 0 1 1 1 1 0 0 0 0  
 $z$ : 0 0 0 0 0 0 0 1 1 0 0 0

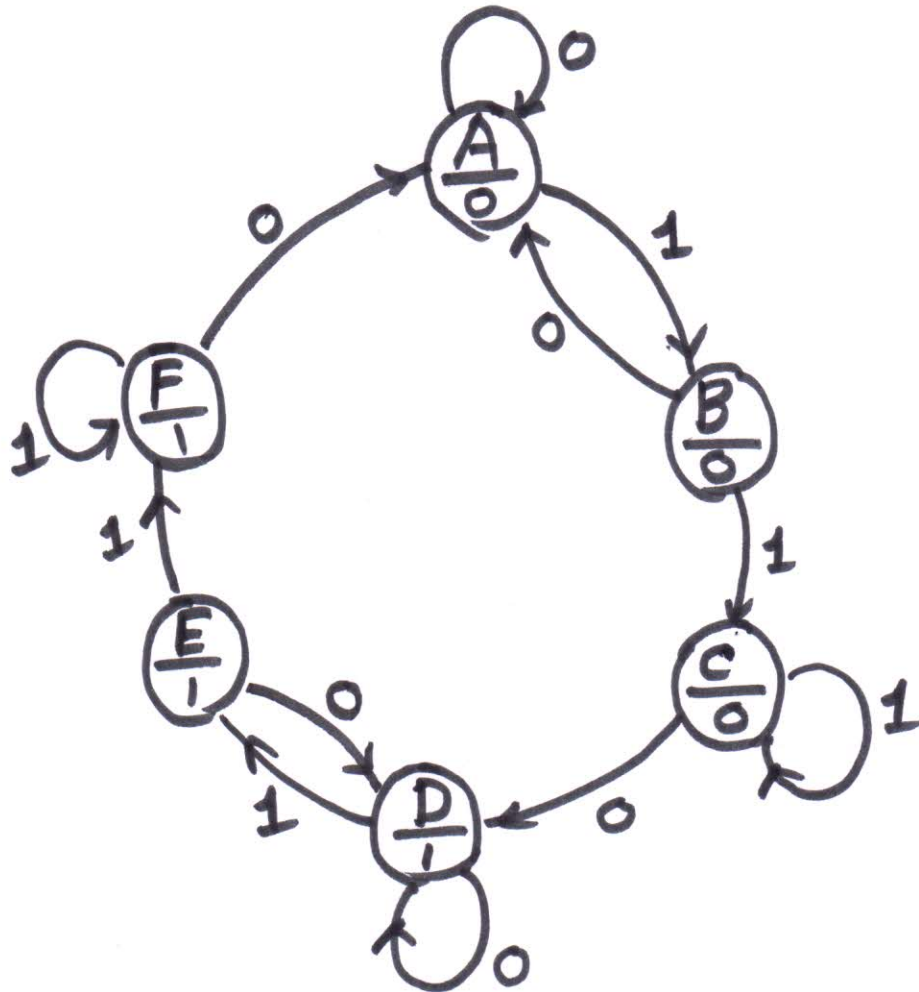4. Design a Moore system whose output changes whenever it detects a sequence 110. (Assume that initially the output is 0.)

ex

X: 0 1 1 0 0 0 1 0 1 1 0 0 1 0  
 Z: 0 0 0 0 1 1 1 1 1 1 0 0 0



A: Initial state with output 0.