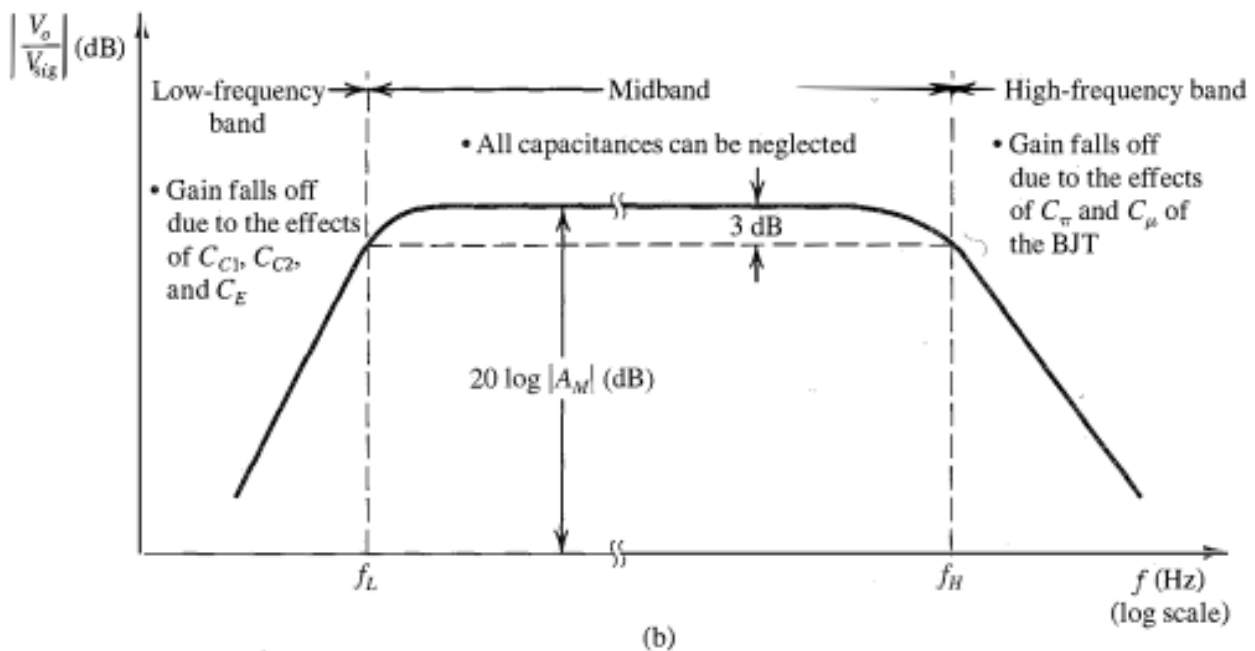


# BJT Internal Capacitances &

## HIGH FREQUENCY MODEL

(1)



behaviour of BJT as an

### BASE CHARGING or Diffusion Capacitance $C_{de}$

When BJT is in active or saturation region, minority carrier charges are stored in base region. The charge  $Q_n$  in terms of collector current  $i_c$

$$Q_n = \frac{W^2 i_c}{2 D_n} = \tau_F \cdot i_c$$

where  $\tau_F$  = device constant =  $\frac{W^2}{2 D_n}$

$W$  = effective width of Base

$D_n$  = electron diffusivity in Base

$\tau_F$  = FORWARD BASE TRANSIT TIME

of the order of 10 picoseconds to 100 picoseconds.

Since  $i_c$  is related to  $V_{BE}$  exponentially  $Q_n$  also depends upon  $V_{BE}$  nonlinearly. (2)  
 This mechanism can be represented by a SMALL SIGNAL DIFFUSION CAPACITANCE  $C_{de}$

$$C_{de} = \frac{dQ_n}{dV_{BE}} = \tau_F \frac{di_c}{dV_{BE}} = \tau_F \cdot g_m$$

$$= \tau_F \cdot \frac{I_C}{V_T}$$

Thus  $C_{de}$  increases with  $I_C$  or Bias current.  
 ————— x ————

### BASE EMITTER JN CAPACITANCE

B-E jn. depletion layer capacitance  $C_{je}$  is given by

$$C_{je} = \frac{C_{je0}}{\left(1 - \frac{V_{BE}}{V_{oe}}\right)^m}$$

← value of  $C_{je}$  at 0V

$V_{oe}$  = EBJ built-in Voltage  $\approx 0.9V$

$m$  = grading coeff.  $\approx 0.5$

$V_{BE}$  = Forward junction DC voltage or bias voltage.

Approx.  $C_{je} \approx 2 C_{je0}$


## Collector Base Jn. Capacitance $C_{\mu}$ (3)

$\therefore$  CB is reversed biased, its junction has a capacitance like effect modelled as

$$C_{\mu} = \frac{C_{\mu 0}}{\left(1 + \frac{V_{CB}}{V_{oc}}\right)^m} \rightarrow C_{\mu} \text{ at } 0V$$

$V_{oc} \rightarrow$  CBJ built-in Voltage  
 $\approx 0.75V$   
 $m \approx 0.2 \text{ to } 0.3V$

## HIGH-FREQUENCY HYBRID- $\pi$ MODEL.

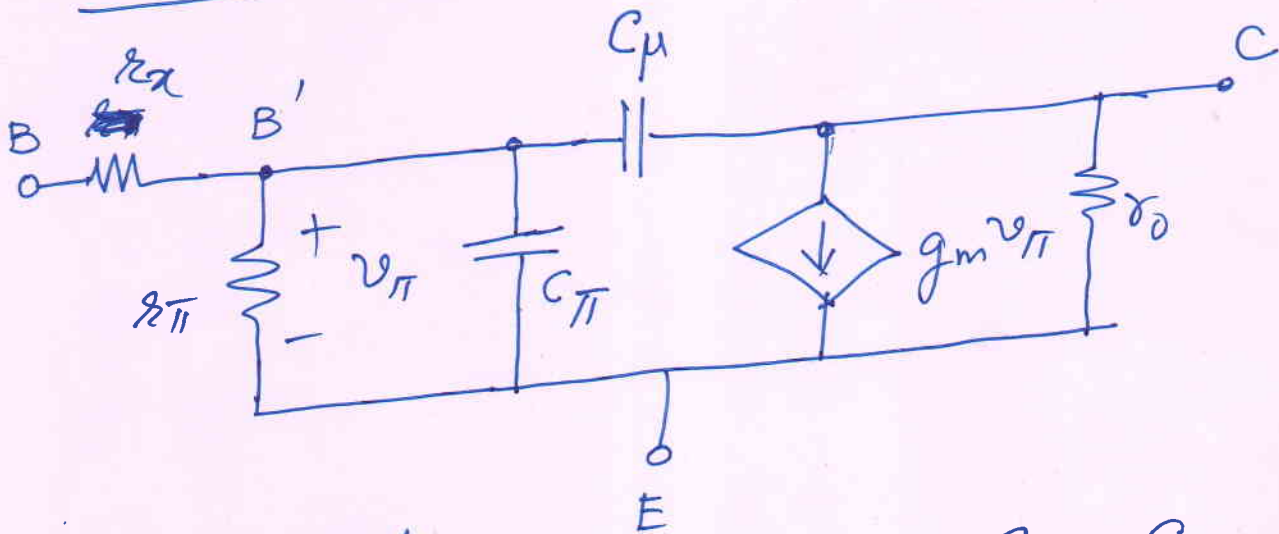

Newly Added:

$C_{\pi}$  = emitter base capacitance

$C_{\mu}$  = collector-base capacitance

$r_x$  = small value to model resistance of silicon material  $\approx$  few tens of ohms.

At low frequencies  $r_x + r_{\pi} \approx r_{\pi}$  therefore it was never considered or brought in discussion.  
 At high freq.  $C_{\pi}$  will bypass  $r_{\pi}$  &  $r_x$  will matter.




Typically  $C_{\pi}$  = few tens of Picofarads  
 $C_{\mu}$  = fraction to few Picofarads  
 $r_x$  = tens of ohms.

4

Voltages and currents described now onwards will be function of frequency hence we will use uppercase letters with lowercase subscripts like  $V_{\pi}$  or  $I_c$ .
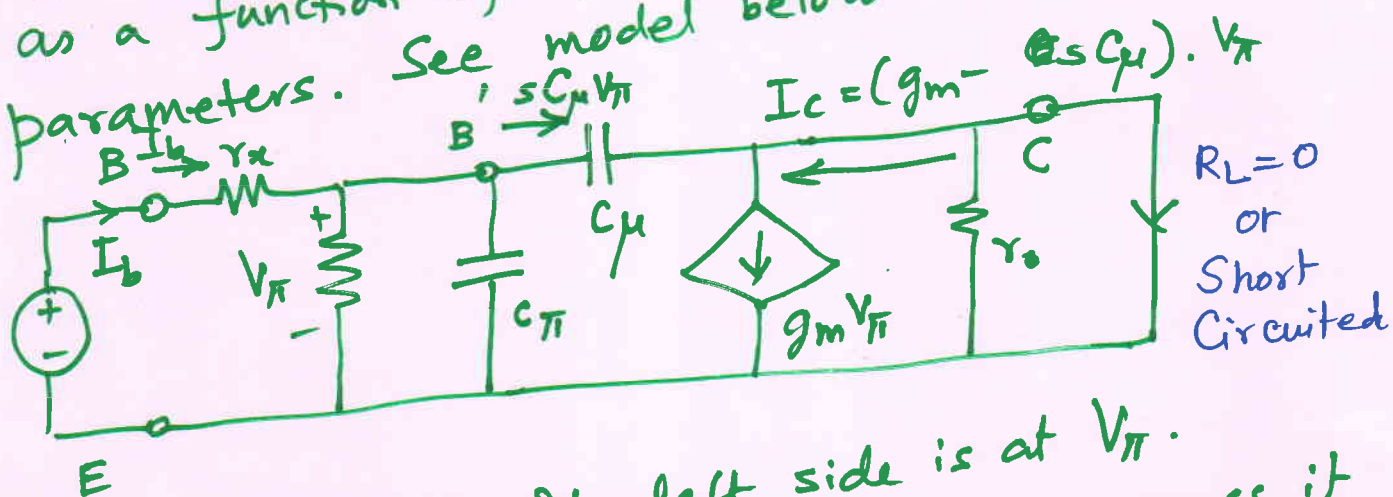
## Expression of Upper Cutoff Frequency

Derive an expression for short circuit current gain  $\beta$  (also called as  $h_{fe}$ ) or CE S.C.C. Gain as a function of frequency, in terms of model parameters. See model below with  $R_L = 0$ . S.C.



See capacitor  $C_{\mu}$ . Its left side is at  $V_{\pi}$ .  
 Its right side is at GND  $\therefore$  voltage across it is  $V_{\pi}$ .  $\therefore$  Current through  $C_{\mu} = \frac{V_{\pi}}{X_{C_{\mu}}} = \frac{V_{\pi}}{1/C_{\mu}s}$

$= C_{\mu}s \cdot V_{\pi}$   
 $\therefore r_o$  is bypassed by a short circuit, it does not matter at all in calculations

Now look at currents in Node C :

(5)

$$\begin{aligned} \text{coll. } I_c &= g_m V_{\pi} - s C_{\mu} V_{\pi} \\ \text{current} &= (g_m - s C_{\mu}) V_{\pi} \end{aligned}$$

$V_{\pi}$  is voltage across  $r_{\pi}$  due to  $I_b$ .

$$V_{\pi} = I_b (r_{\pi} \parallel C_{\pi} \parallel C_{\mu})$$

$\therefore$  voltage across  $C_{\mu}$  is also  $V_{\pi}$ .

$$V_{\pi} = \frac{I_b}{\frac{1}{r_{\pi}} + s C_{\pi} + s C_{\mu}}$$

Calculate  $h_{fe}$

$$h_{fe} = \frac{I_c}{I_b} = \frac{(g_m - s C_{\mu}) \cdot V_{\pi}}{(\frac{1}{r_{\pi}} + s C_{\pi} + s C_{\mu}) \cdot V_{\pi}}$$

Assuming that at high frequencies  $g_m \gg \omega C_{\mu}$  & we neglect  $s C_{\mu}$  in numerator.

$$\begin{aligned} h_{fe} &= \frac{g_m \cdot r_{\pi}}{1 + s(C_{\pi} + C_{\mu}) r_{\pi}} \\ &= \frac{\beta_0}{1 + s(C_{\pi} + C_{\mu}) r_{\pi}} \end{aligned}$$


where  $\beta_0 =$  low frequency  $\beta$ .  
 $= g_m \cdot r_{\pi}$

Now, we can see this expression as an STC function at a 3-db or corner freq. (6)

$$\omega = \omega_{\beta} \text{ where}$$

$$\omega_{\beta} = \frac{1}{(C_{\pi} + C_{\mu}) r_{\pi}}$$

See Bode Plot

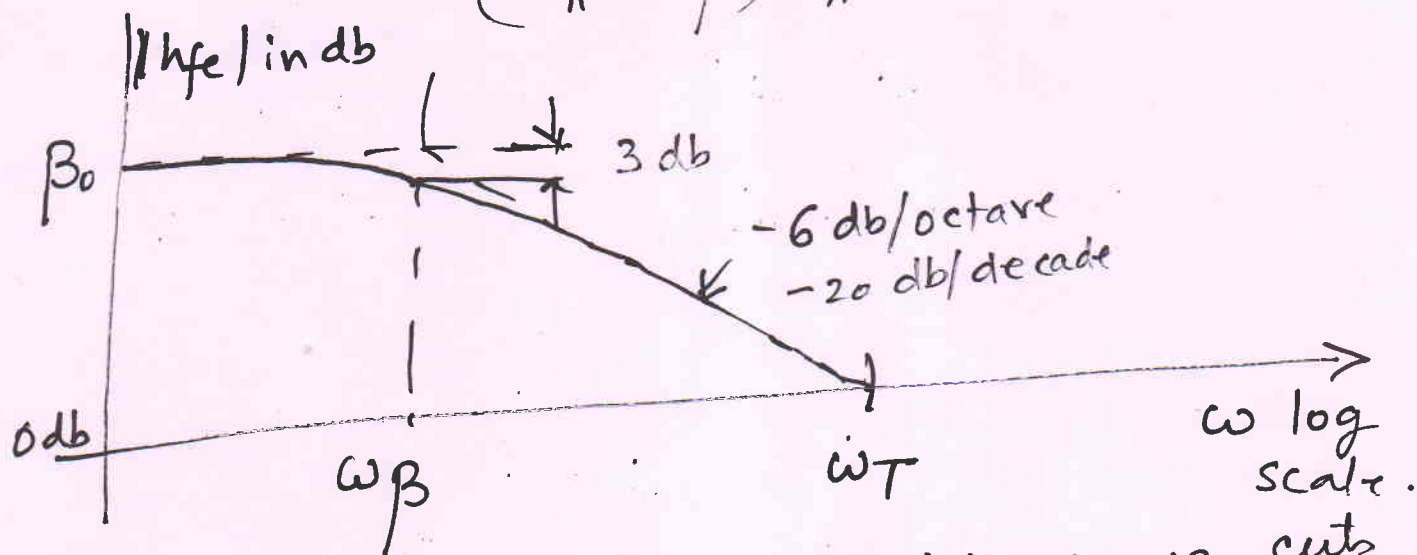

The frequency at which this curve cuts 0-dB line is called frequency where  $|h_{fe}| = 1$  or UNITY GAIN BANDWIDTH  $\omega_T$  such that  $\omega_T = (\beta_0 \cdot \omega_{\beta})$

$$\text{Thus } \omega_T = \frac{\beta_0}{(C_{\pi} + C_{\mu}) r_{\pi}} = \frac{g_m}{(C_{\pi} + C_{\mu})}$$

$$\therefore f_T = \frac{\omega_T}{2\pi} = \frac{g_m}{2\pi(C_{\pi} + C_{\mu})}$$


$f_T$  is usually specified in BJT datasheets. It is in MHz to GHz range.

From  $f_T$ , we can get  $C_\pi$  &  $C_\mu$ . (7)


We can measure practically  $C_\mu$  between B & C and get a measure of  $C_\pi$ .

This STC model we discussed, works well upto  $0.2f_T$ . At higher frequencies, we must use distributed R-C model for better estimates:

Lumped model.

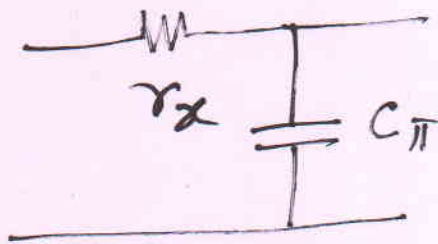

distributed model. for say 10 taps...

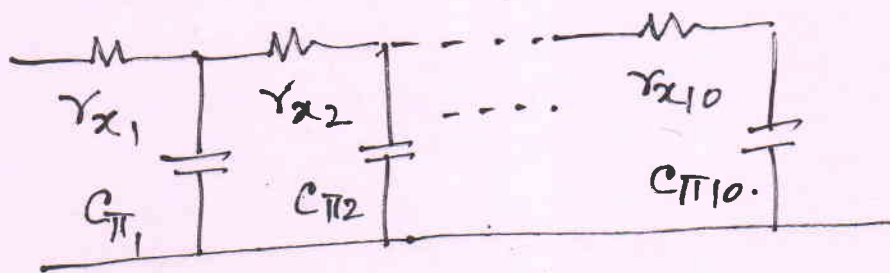



Numerical on  $C_\mu$ ,  $C_\pi$  and  $f_T$ .

3.149 Given npn BJT  $I_C = 0.5 \text{ mA}$   
 $V_{CB} = 2 \text{ V}$  ;  $\beta_0 = 100$  ;  $V_A = 50 \text{ V}$   
 $\tau_p = 30 \text{ ps}$  ;  $C_{je0} = 20 \text{ femto farad}$   
 $C_{\mu 0} = \cancel{20}^{30} \text{ femto F}$  ;  $\quad = 20 \text{ fF} = .02 \text{ pF}$   
 $V_{oc} = 0.75 \text{ V}$  ,  $m_{CBT} = 0.5$  ;  $r_x = 100 \Omega$

Draw hybrid- $\pi$  model & find  $f_T$ .

$r_x = 100 \Omega$  ;  $g_m = I_C / V_T = 0.5 \text{ mA} / 25 \text{ mV} = 20 \text{ mS}$

$r_\pi = \beta_0 / g_m = 100 / 20 \text{ mS} = 5 \text{ k}\Omega$

$r_o = V_A / I_C = 50 \text{ V} / 0.5 \text{ mA} = 100 \text{ k}\Omega$

$C_\mu = C_{\mu 0} / \left(1 + \frac{V_{CB}}{V_{oc}}\right)^m = \frac{\cancel{20}^{30} \text{ fF}}{\left(1 + \frac{2 \text{ V}}{0.75 \text{ V}}\right)^{0.5}} = 15.66 \text{ fF}$

$C_{je} \approx 2 C_{je0} = 20 \times 20 = 40 \text{ fF}$

$C_{de} = \tau_F \cdot g_m = 30 \text{ ps} \cdot 20 \text{ mS} = 600 \text{ femto F}$

$C_\pi = C_{je} + C_{de} = 40 + 600 = 640 \text{ fF} = 0.640 \text{ pF}$

$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)} = \frac{20 \text{ mS} \times 10^{-3}}{2 \times 3.14 \left(\frac{640 + 15.66}{66}\right) \times 10^{-15}} \text{ Hz}$

$\boxed{= 4.857 \text{ Giga Hz}}$



Q: 3.150 At 500 MHz signal,  $|h_{fe}| = 2.5 @ I_C = 0.2 \text{ mA}$

and at same frequency  $|h_{fe}| = 11.6 @ I_C = 1.0 \text{ mA}$  (9)

Given:  $C_\mu = 0.05 \text{ pF} \approx 50 \text{ fF}$ .

Find  $f_T$  at both Collector Currents.

What is  $r_F$  and  $C_{je}$  value?

————— x —————

Note that

$$|h_{fe}| = \frac{f_T}{\text{freq of measurement}}$$

@  $I_C = 0.2 \text{ mA}$   
 $\therefore f_T = |h_{fe}| \cdot f = 2.5 \times 500 \text{ MHz} = 1.25 \text{ GHz}$

at another  $I_C$  value @  $I_C = 1.0 \text{ mA}$

$$f_T = 11.6 \times 500 \text{ MHz} = 5.8 \text{ GHz}$$

Note: Change in bias current from 0.2 mA to 1.0 mA increases  $f_T$  from 1.25 to 5.8 GHz.

Thus if we want a higher frequency amplifier, we should keep  $I_C = \text{higher value}$ .

$$\therefore f_T = g_m / 2\pi (C_\pi + C_\mu)$$

$$\therefore C_\pi = \left( g_m / (2\pi f_T) \right) - C_\mu$$

at  $I_C = 0.2 \text{ mA} \rightarrow g_m = 0.2/25 = 8 \text{ mV}$

$$C_\pi = \left[ 8 \text{ mV} / \left( 2 \times 3.14 \times 1.25 \text{ GHz} \right) \right] - 50 \text{ fF} = 968 \text{ fF}$$

at  $I_C = 1.0 \text{ mA}$   $g_m = 40 \text{ mV}$

(10)

$$C_{\pi} = \left[ 40 \text{ mV} / (2 \times 3.14 \times 5.8 \text{ GHz}) \right] - 50 \text{ fF}$$

$$= 1047.6 \text{ fF.}$$

Note that  $C_{\pi}$  also increases with  $I_C$ .  
— x —

Next,  $C_{\pi} = C_{je} + \tau_F \cdot g_m$

②  $I_C = 0.2 \text{ mA}$

$$968 \text{ fF} = C_{je} + \tau_F \cdot 8 \text{ mV} \quad \text{--- (1)}$$

②  $I_C = 1.0 \text{ mA}$

$$1047.6 \text{ fF} = C_{je} + \tau_F \cdot 40 \text{ mV} \quad \text{--- (2)}$$

Solving (1) and (2)  $C_{je} = 950 \text{ fF}$  and  
 $\tau_F = 2.47 \text{ ps}$

Q: 3.151 Given:  $I_C = 2 \text{ mA}$ ;  $C_{\mu} = 1 \text{ pF}$ ,  $C_{\pi} = 10 \text{ pF}$   
 $\beta = 150$ . Find  $f_T$  and  $f_{\beta}$ .

$$f_T = g_m / (2\pi(C_{\mu} + C_{\pi})) = 80 \text{ mV} / (2 \times 3.14 \times (1 + 10) \text{ pF})$$

$$= \boxed{1.158 \text{ GHz}}$$

$$f_{\beta} = \frac{f_T}{\beta_0} = \frac{1.158 \text{ GHz}}{150} = \boxed{7.725 \text{ MHz.}}$$