
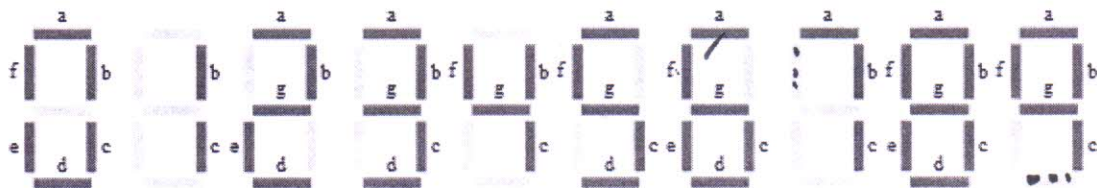


Don't-Care Conditions:

In some digital systems, certain input conditions never occur during normal operation. For those inputs, the corresponding outputs can take any value- '0' or '1'. In K-map these outputs are marked as 'X'.

Example:

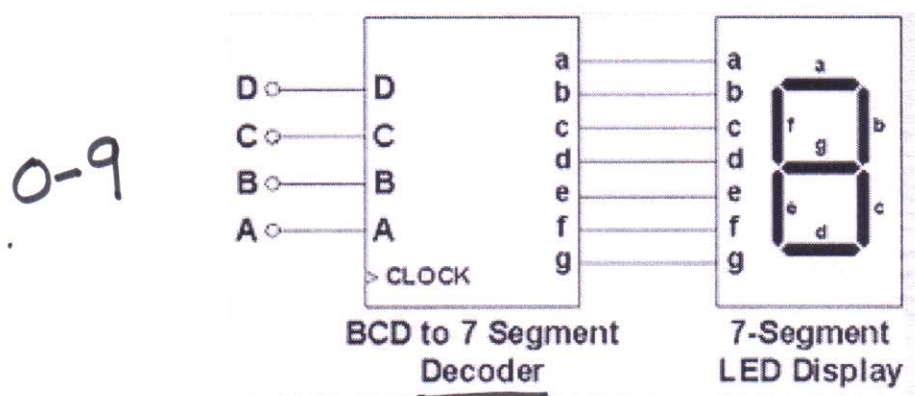

II

A	B	C	D	a	b	c	d	e	f	g
0	0	0	0							0
0	0	0	1	0			0	0	0	0
0	0	1	0			0			0	
0	0	1	1					0	0	
0	1	0	0	0			0	0		
0	1	0	1		0			0		
0	1	1	0	X	0					
0	1	1	1				0	0	X	0
1	0	0	0							
1	0	0	1				X	0		
1	0	1	0	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X
1	1	0	0	X						,
1	1	0	1	X						,
1	1	1	0	X						,
1	1	1	1	X	X	X	X	X	X	X

Ex. For LED 'a'

$$\Sigma m(0, 2, 3, 5, 7, 8, 9) +$$

$$\Sigma d(6, 10, 11, 12, 13, 14, 15)$$

Without don't-care

AB \ CD	00	01	11	10
00	1		1	1
01		1	1	
11				
10	1	1		

$$a = \bar{A}\bar{B}\bar{D} + A\bar{B}\bar{C} + \bar{A}CD + \bar{A}BD$$

With don't-care

AB \ CD	00	01	11	10
00	1		1	1
01		1	1	X
11	X	X	X	X
10	1	1	X	X

$$a = A + C + \bar{B}\bar{D} + BD$$

Product of Sums Simplification using K-map:

Ex. $F(X, Y, Z) = \sum m(0, 1, 2, 3, 6, 7)$

$$= \prod M(4, 5) = (\cancel{x} + \cancel{y} + \cancel{z})$$

$$(\bar{x} + y + z)(\bar{x} + y + \bar{z})$$

$$= (\bar{x} + y + z\bar{z}) = (\bar{x} + y)$$

$x \backslash yz$	00	01	11	10
0				
1	1	1		

$$(\bar{x} + y)$$

OR

Ex. Find minimal SOP and minimal POS for the following Boolean function:

$$F(A, B, C, D) = \sum m(2, 10, 14) + \sum d(6)$$

SOP

AB \ CD	00	01	11	10
00				1
01				X
11				1
10				1

$$F = C\bar{D}$$

POS

AB \ CD	00	01	11	10
00	0	0	0	
01	0	0	0	X
11	0	0	0	
10	0	0	0	

$$F = (C)(\bar{D})$$

Ex. Find minimal SOP and minimal POS for the following Boolean function:

$$F(A, B, C, D) = \sum m(2, 10, 14) + \sum d(3, 11)$$

SOP

AB \ CD	00	01	11	10
00			X	1
01				
11				1
10			X	1

$$F = \overline{B}C + AC\overline{D}$$

POS

AB \ CD	00	01	11	10
00	0	0	X	
01	0	0	0	0
11	0	0	0	
10	0	0	X	

$$F = C\overline{D}(A + \overline{B})$$

Digital Circuits:

1. Combinational Circuits

It consists of logic gates whose outputs at any time are determined by current inputs using logic operations.

Ex.

- a) Arithmetic circuits like binary adder, BCD adder etc
- b) Multiplexer and Demultiplexer
- c) Encoder and Decoder

2. Sequential Circuits

It consists of combinational circuits and storage elements. Therefore, its outputs depends on current inputs and previous outputs or states.

Ex.


- a) Flip-flops
- b) Registers
- c) Counters

Combinational Circuits

Binary Adders:

1. Half Adder


Inputs		Outputs	
X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

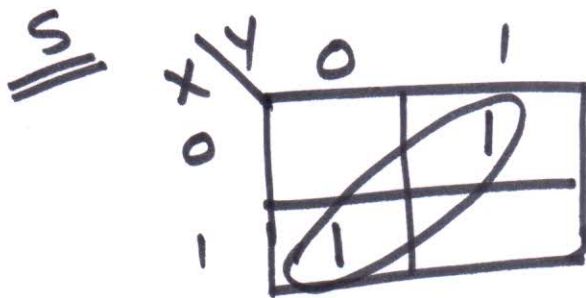

$$S = \bar{x}y + x\bar{y}$$
$$= x \oplus y$$

C

$$C = xy$$

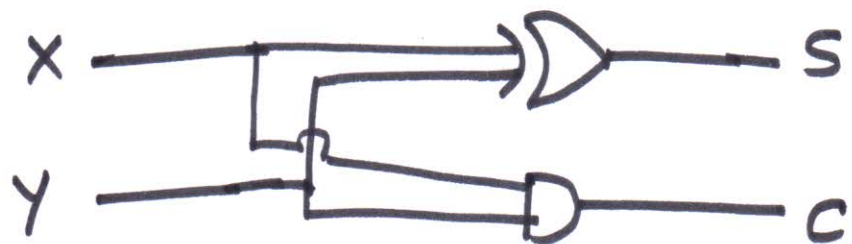


2. Full Adder

Inputs			Output	
X	Y	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

S

X \ Y C _{in}				
	00	01	11	10
0		1		1
1	1		1	

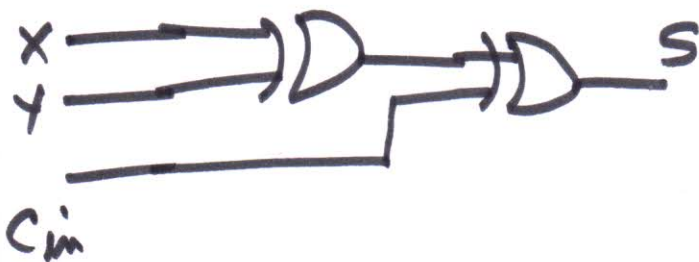

$$S = \underline{X\bar{Y}\bar{C}_{in}} + \underline{\bar{X}\bar{Y}C_{in}} + \underline{XYC_{in}} + \underline{\bar{X}Y\bar{C}_{in}}$$

$$= \bar{Y}(\underline{X\bar{C}_{in}} + \underline{\bar{X}C_{in}}) + Y(\underline{XC_{in}} + \underline{\bar{X}\bar{C}_{in}})$$

$$= \bar{Y}(X \oplus C_{in}) + Y \overline{(X \oplus C_{in})}$$

$$= Y \oplus X \oplus C_{in}$$