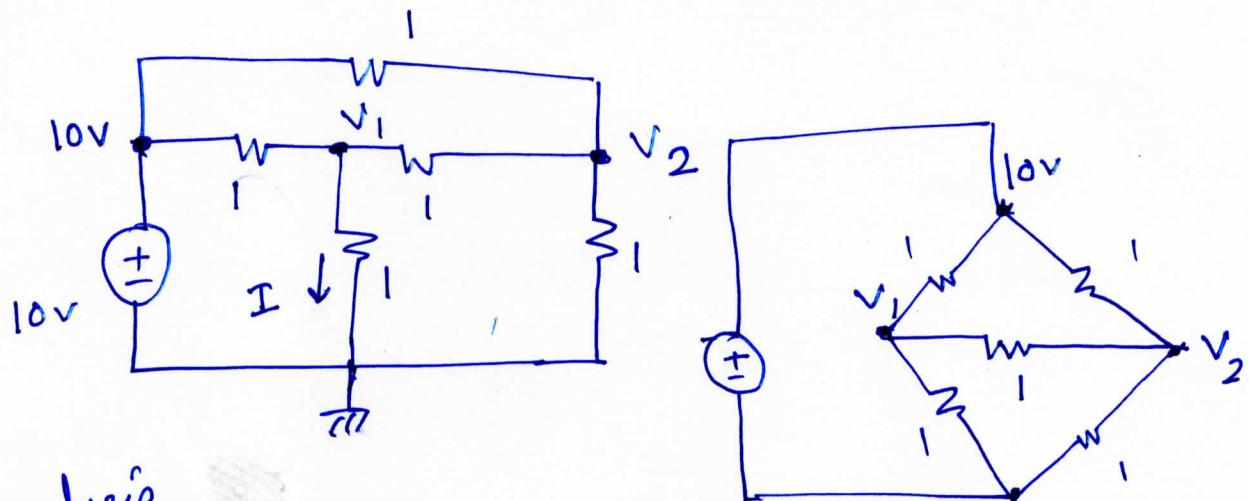


A pure Voltage Source ( $R_s=0$ ) between two nodes

ex



Node Analysis

Node  $V_1$

$$\frac{V_1 - 10}{1} + \frac{V_1 - 0}{1} + \frac{V_1 - V_2}{1} = 0$$

$$\Rightarrow 3V_1 - V_2 = 10$$



Node  $V_2$

$$\frac{V_2 - 10}{1} + \frac{V_2 - V_1}{1} + \frac{V_2 - 0}{1} = 0$$


$$\Rightarrow 3V_2 - V_1 = 10$$

Sol<sup>h</sup>:  $V_1 = V_2 = 5V$

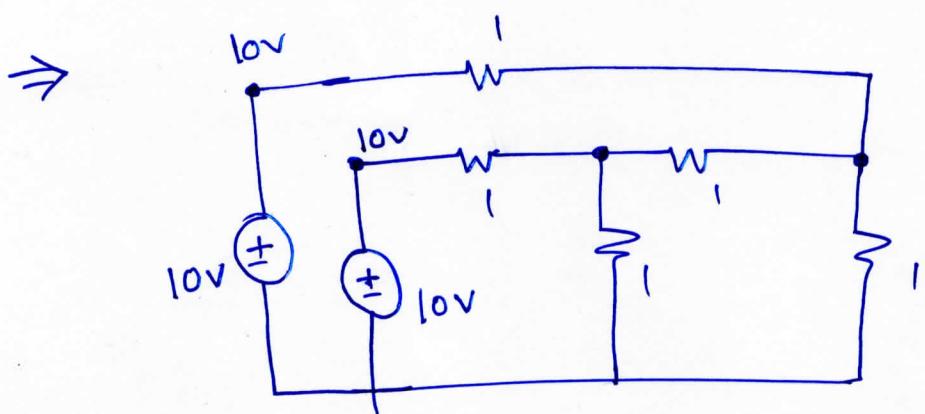
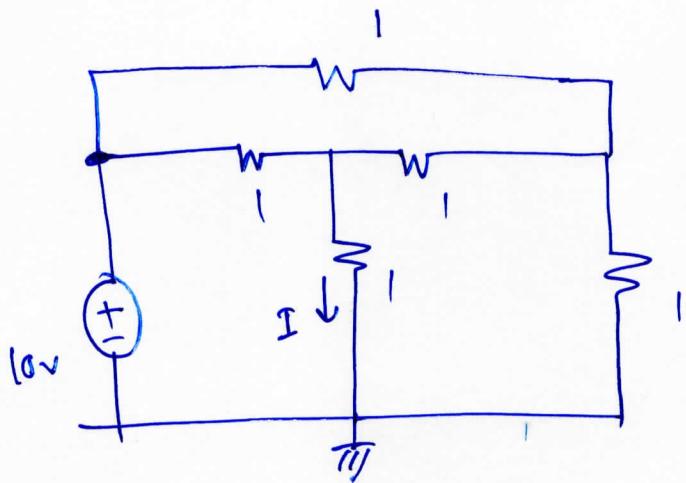
$$\Rightarrow I = \frac{V_1}{1} = \frac{5}{1} = 5A$$



Voltage Source  
Splitting

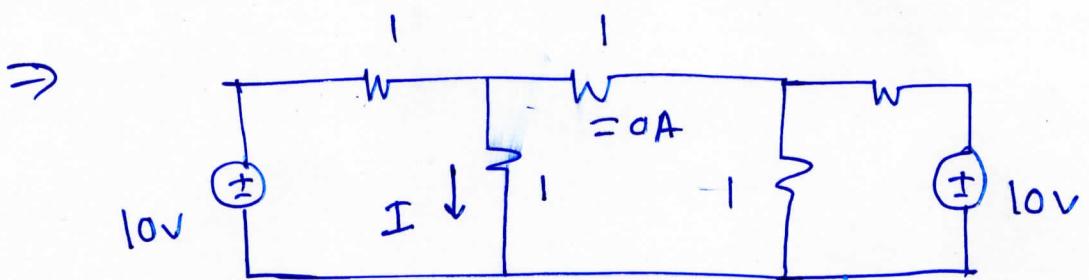


$$I = \frac{10}{2} = 5 \text{ A}$$

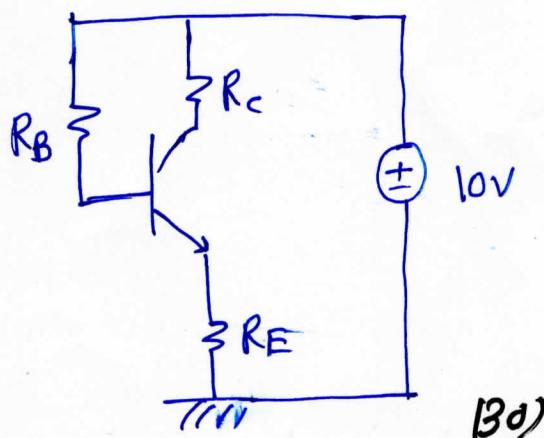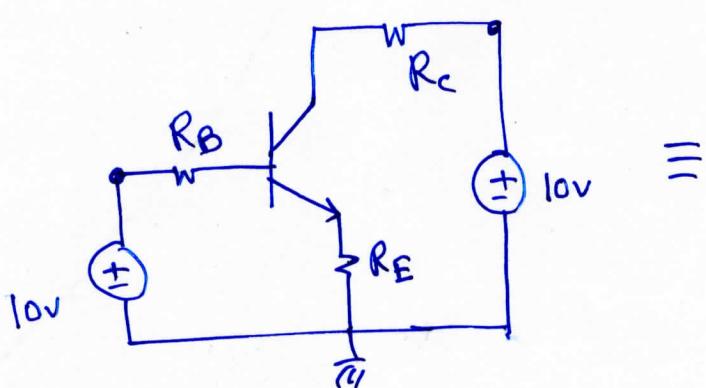

(3d)

# A Current Source between two nodes

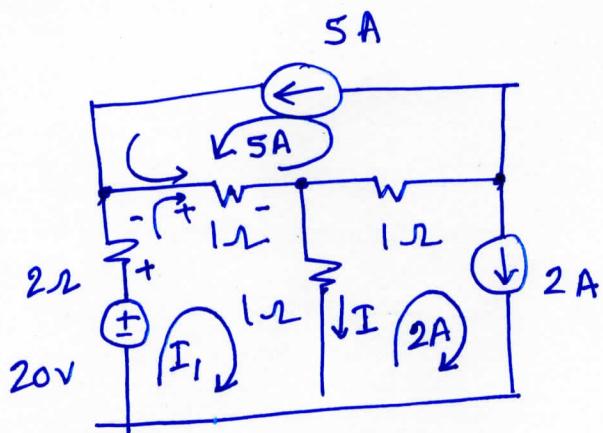

KVL


$$20 - 2I_1 - 1(I_1 + 5) - 1(I_1 - 2) = 0$$



$$\Rightarrow 20 - 4I_1 - 5 + 2 = 0$$

$$\Rightarrow 4I_1 = 17 \Rightarrow I_1 = \frac{17}{4} A$$

$$\therefore \text{So, } I = I_1 - 2 = \frac{17}{4} - 2 = \frac{9}{4} A$$



2nd App.

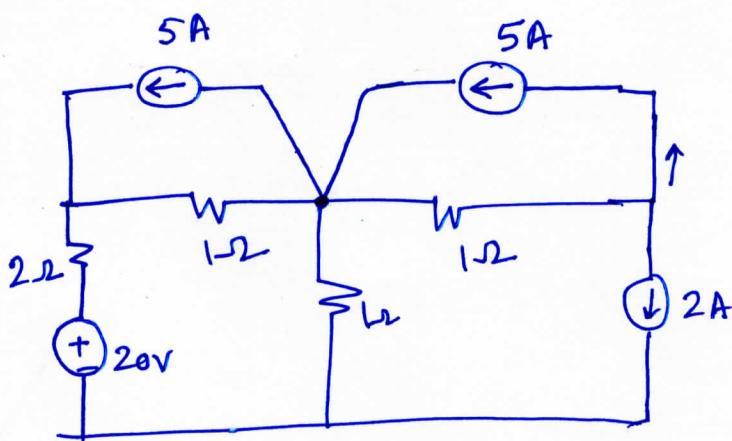

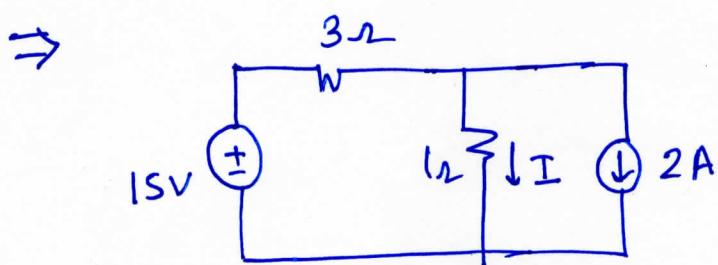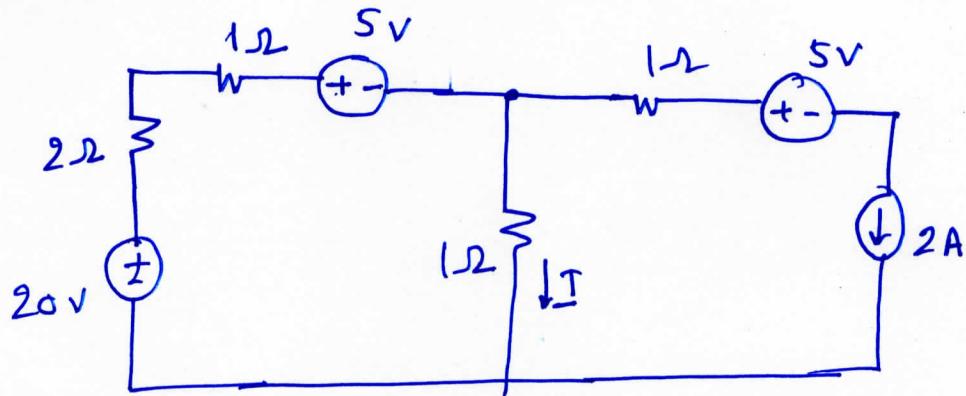

By Superposition Theorem:

$$I = I_1 + I_2$$

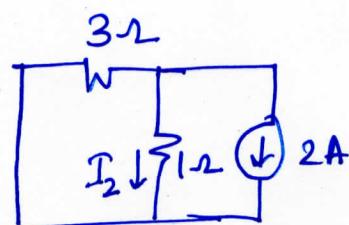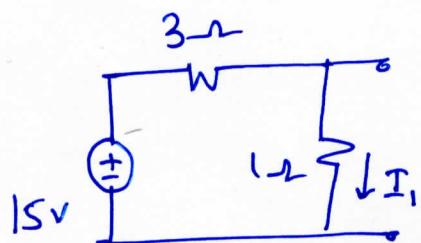


$$I_1 = \frac{15}{4}$$

$$I_2 = \frac{3}{3+1} \times (-2)$$

$$= \frac{3}{4} \times (-2) = -\frac{3}{2} A$$

$$I = \frac{15}{4} - \frac{3}{2} = \frac{15-6}{4} = \frac{9}{4} A$$

ex

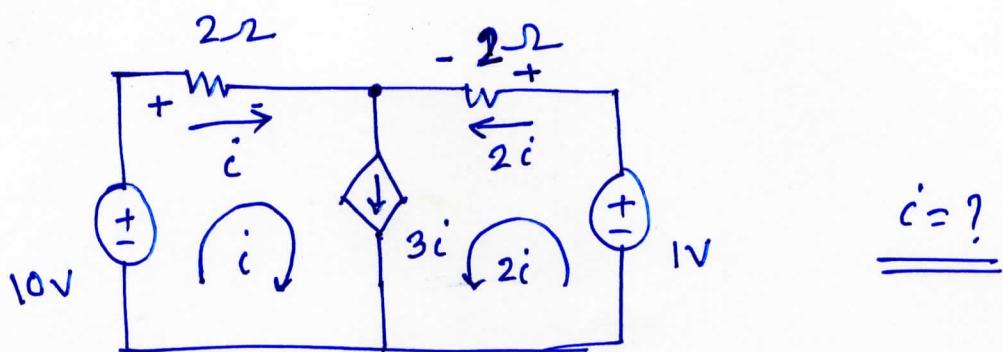

$$\underline{i = ?}$$

Super Mesh


$$10 - 2i + 2 \times 2i - 1 = 0$$

$$\Rightarrow 9 + 2i = 0$$


$$\Rightarrow i = -\frac{9}{2} A$$

Superposition Theorem

10V

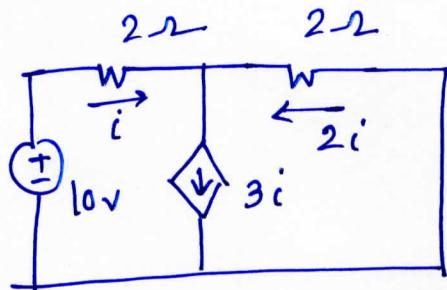

1V

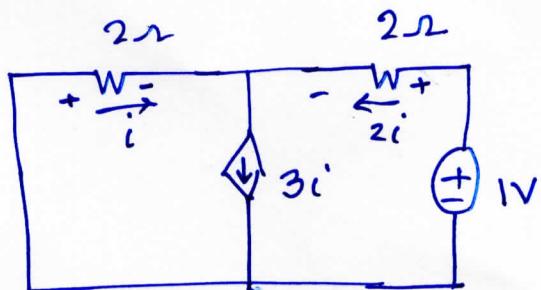

$$10 - 2i + 4i = 0$$



$$\Rightarrow i = -5 A$$

$$1 - 4i + 2i = 0$$



$$\Rightarrow 2i = 1$$

$$\Rightarrow i = \frac{1}{2}$$

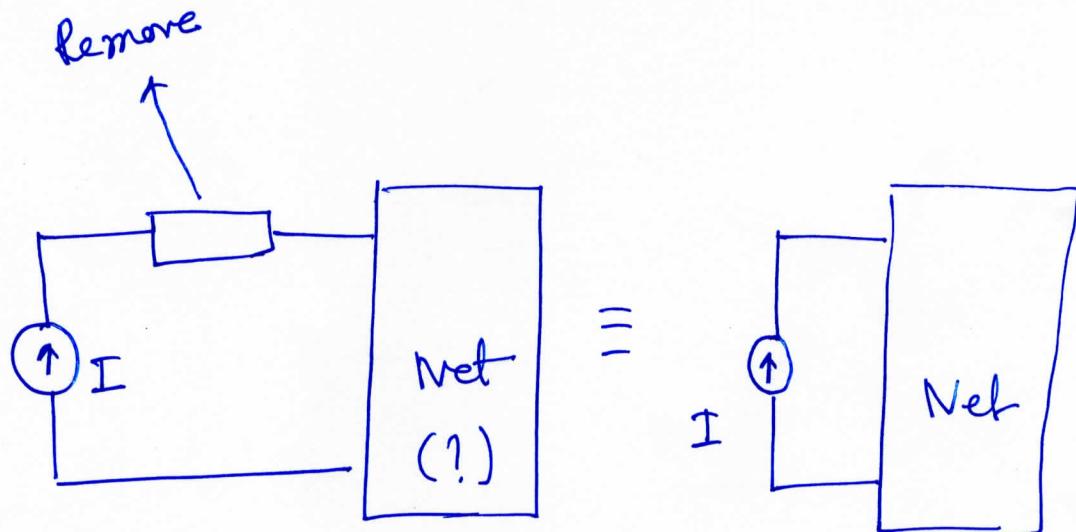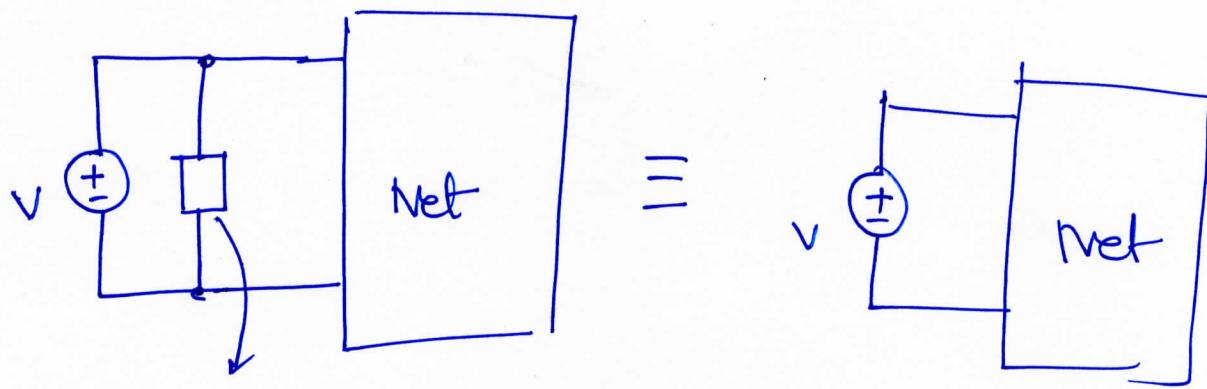
$$\text{So, } i = -5 + \frac{1}{2} = -\frac{9}{2} A$$



## Thevenin Theorem:

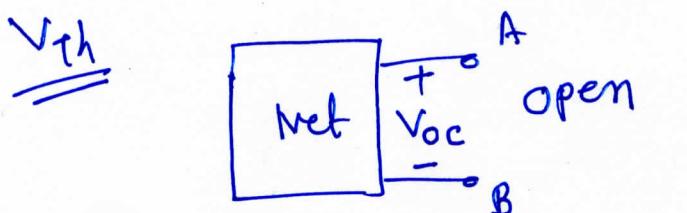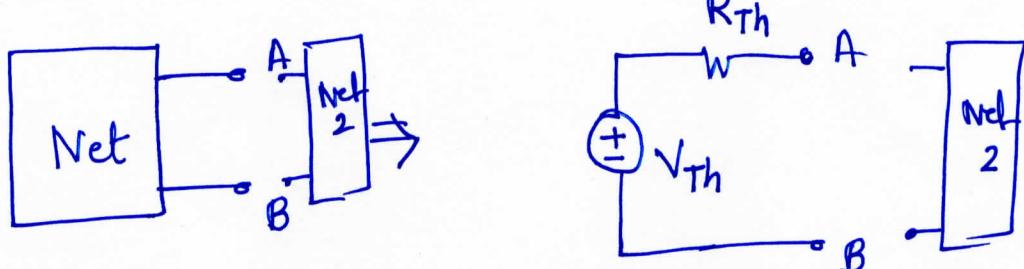

$$V_{Th} = V_{oc}$$


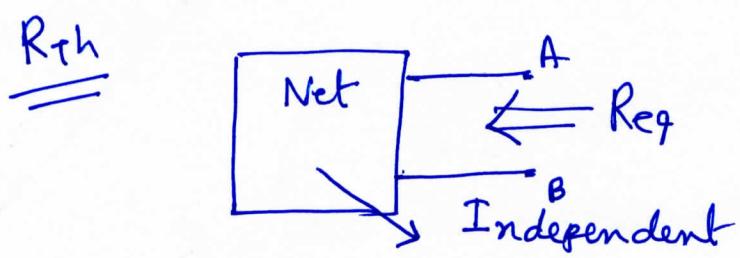


$$R_{Th} = R_{eq}$$

voltage source  $\rightarrow$  shorted  
current " "  $\rightarrow$  opened


(3)

ex

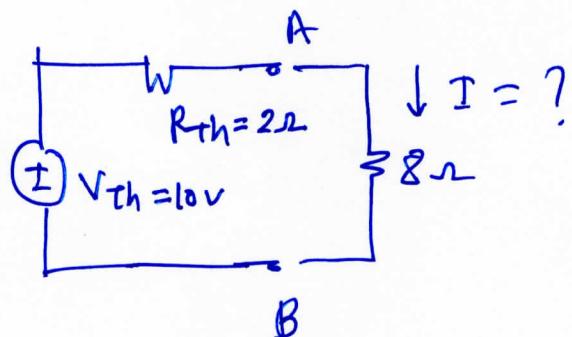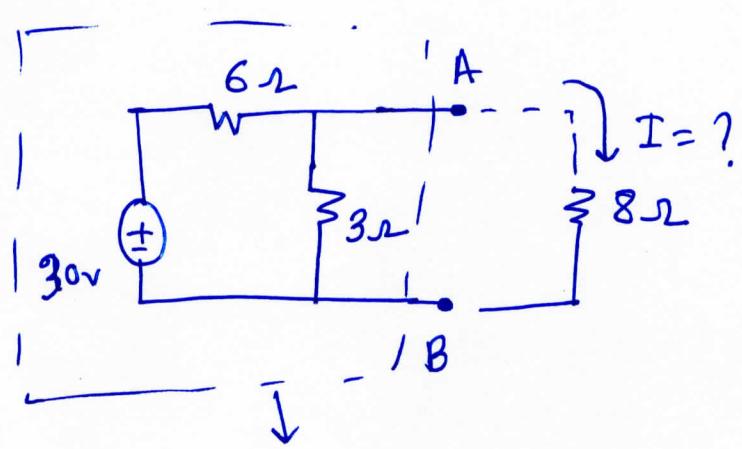

$$I = \frac{V_{Th}}{R_{Th} + 8} = \frac{10}{2+8} = 1A$$

$V_{Th}$

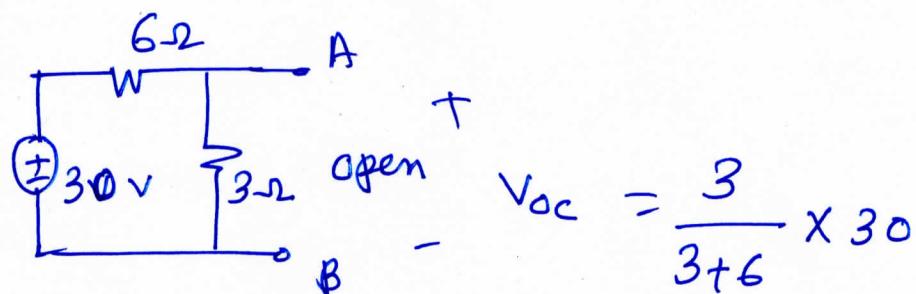


$$V_{oc} = \frac{3}{3+6} \times 30$$

$$= \frac{3}{9} \times 30 = 10V$$


$$= V_{Th}$$

$R_{Th}$

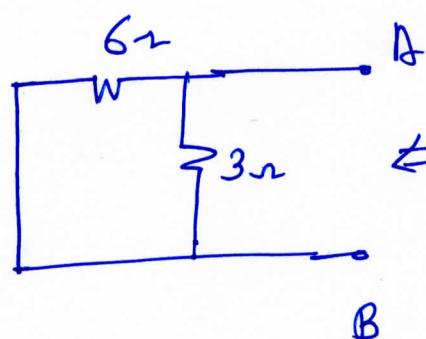


$$\Leftarrow R_{eq} = 6//3 = \frac{6 \times 3}{6+3} = 2\Omega = R_{Th}$$

Ex

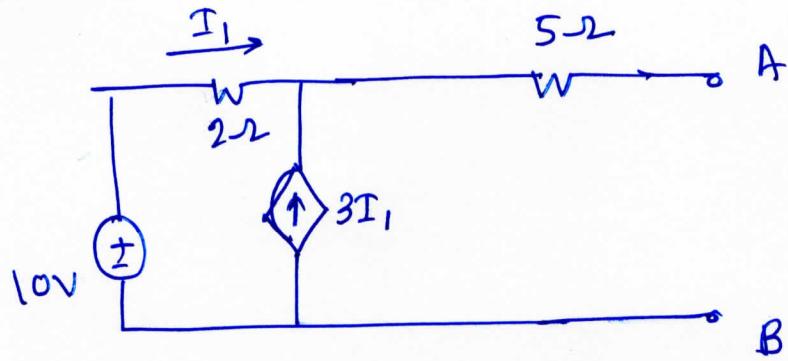

$V_{th}$  &  $R_{th}$



$V_{oc}$

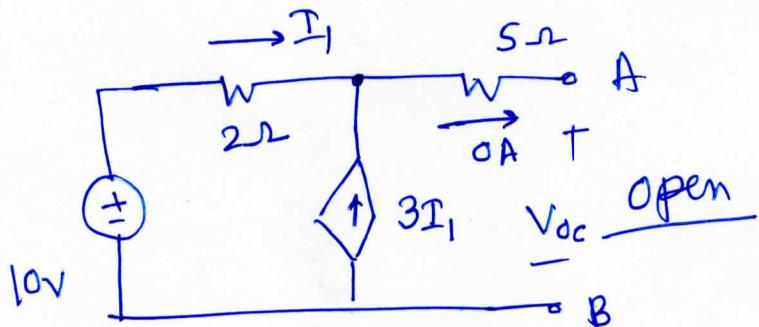

$$I_1 + 3I_1 = 0$$

$$\underline{\underline{V_{oc} = 10V = V_{th}}} \Rightarrow I_1 = 0$$

$R_{th} = ?$

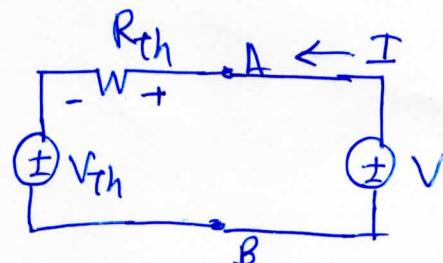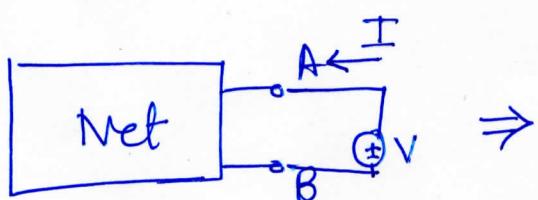

$$V - IR_{th} - V_{th} = 0$$

$$\Rightarrow \boxed{V = IR_{th} + V_{th}}$$


Ex  $V = 2I + 4$

$$V_{th} = 4V \quad \& \quad R_{th} = 2\Omega$$

✓

(36)

ex

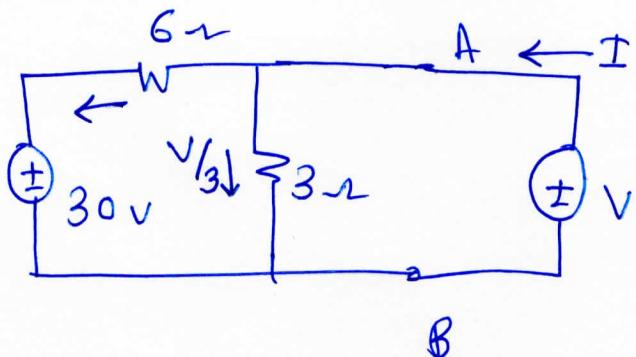

$$V - 6 \times (I - \frac{V}{3}) - 30 = 0$$


$$\Rightarrow V - 6I + 2V - 30 = 0$$

$$\Rightarrow 3V = 6I + 30$$


$$\Rightarrow V = \frac{2I}{R_{th}} + 10 \rightarrow V_{th}$$

$$\begin{cases} V_{th} = 10V \\ R_{th} = 2\Omega \end{cases}$$


ex

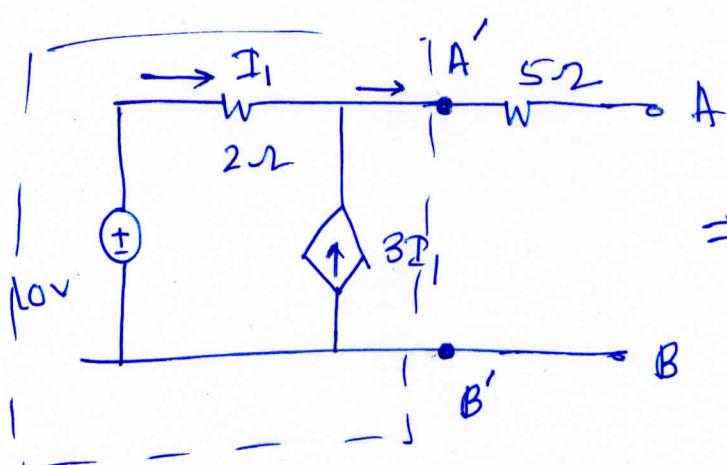

$\Rightarrow$

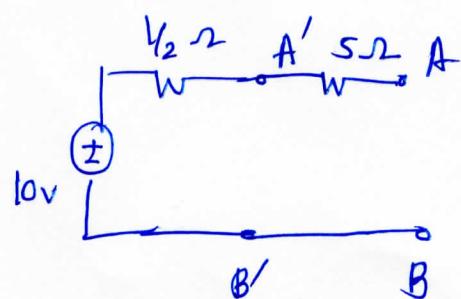
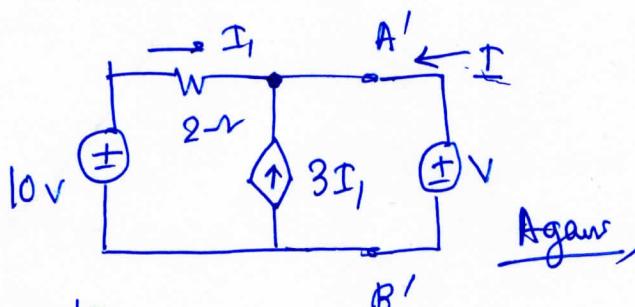
$$\begin{cases} V_{th} = 10V \\ R_{th} = 1.5\Omega \end{cases}$$



$$I_1 + 3I_1 + I = 0$$

$$\Rightarrow I_1 = -I/4$$




$$10 - 2I_1 - V = 0$$

$$\begin{aligned} \Rightarrow V &= -2I_1 + 10 = -2 \times (-I/4) + 10 \\ &= I/2 + 10 \end{aligned}$$

(37)

$$V_{th} = 10V$$

$$R_{th} = 1.5\Omega$$

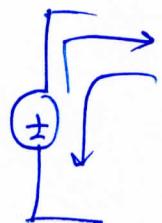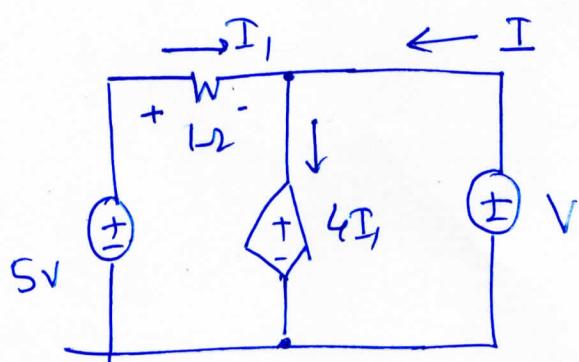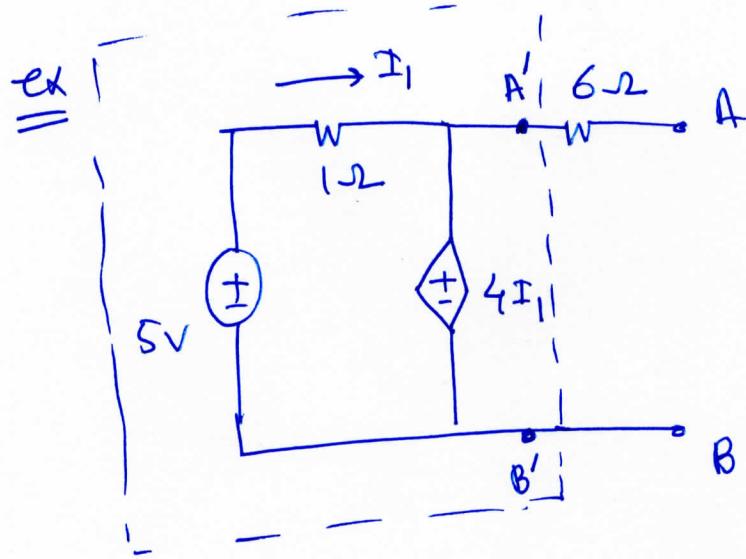

$$5 - 1 \times I_1 - 4I_1 = 0 \quad \nabla \quad V = 4I_1$$


$$\Rightarrow 5I_1 = 5$$

$$\Rightarrow I_1 = 1 \text{ A}$$

$$V = 4I_1 = 4 \times 1 = 4 \text{ V}$$

$$V = 4 + I \times 0$$





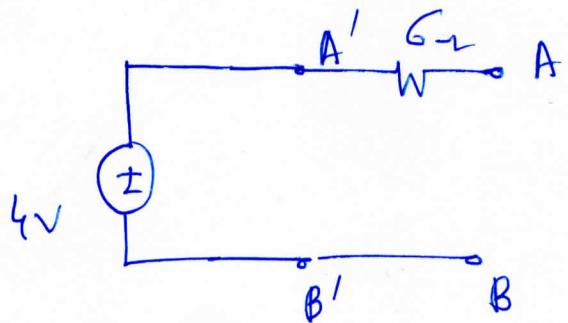
$$\begin{cases} V_{Th} = 4 \text{ V} \\ R_{Th} = 0 \Omega \end{cases}$$



$$\Rightarrow V_{Th} = 4 \text{ V}$$




$$R_{Th} > 6 \Omega$$

Ex

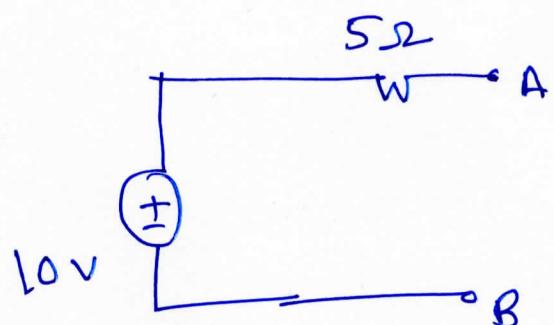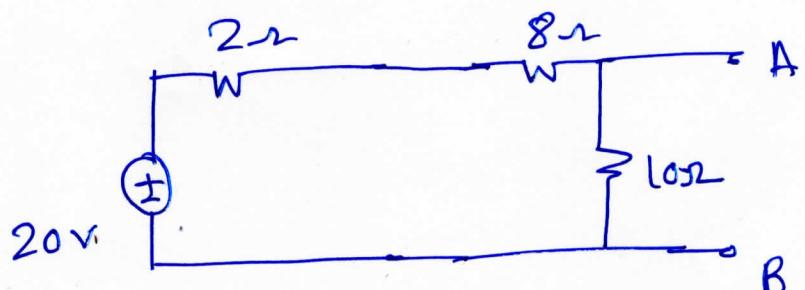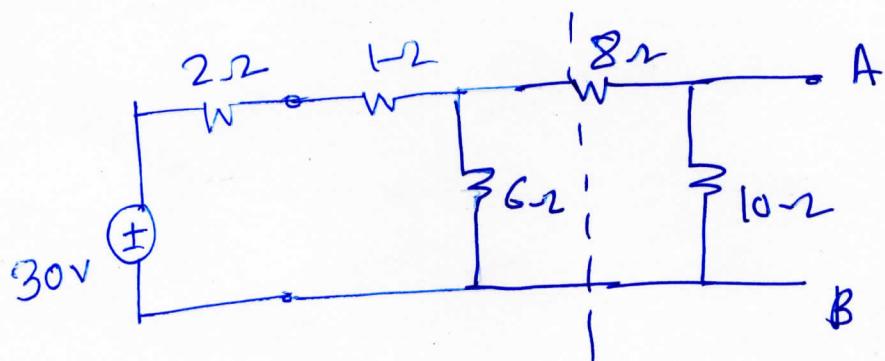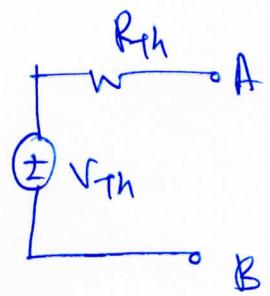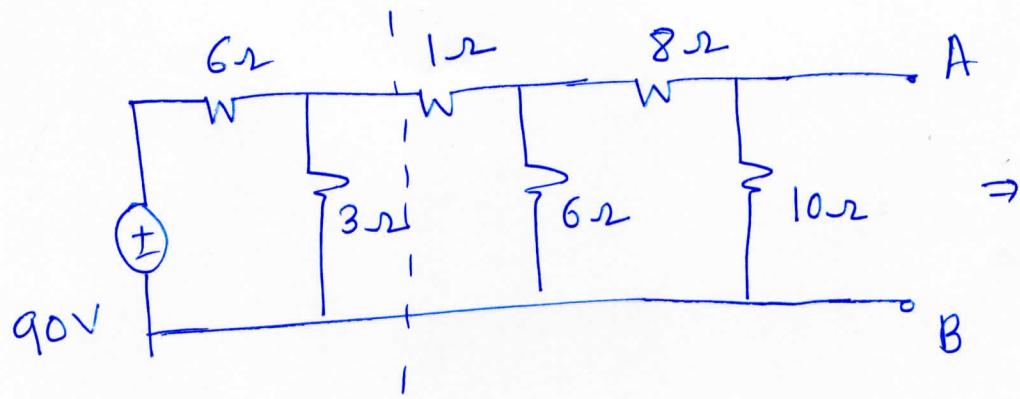


$$\left\{ \begin{array}{l} V_{Th} = 10V \\ R_{Th} = 5\Omega \end{array} \right.$$

## Wheatstone Bridge :-

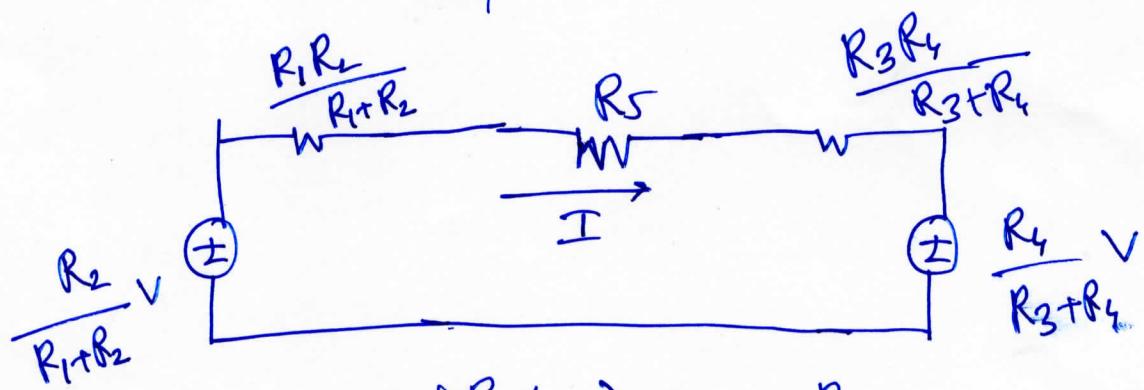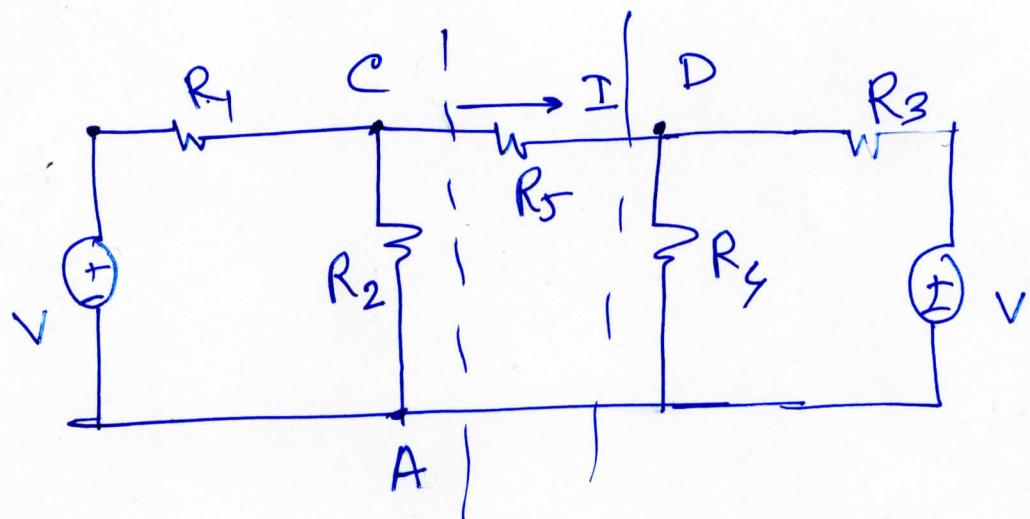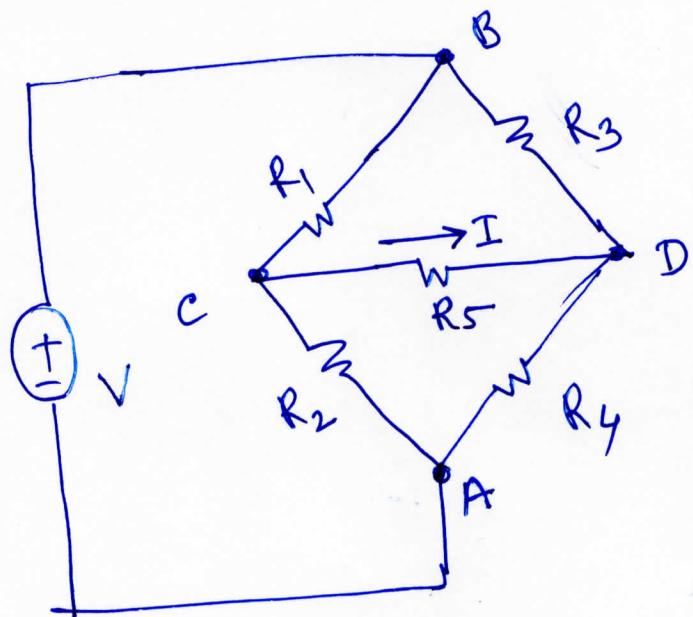


$$I = \frac{\left( \frac{R_2}{R_1+R_2} \right) V - \frac{R_4}{(R_3+R_4)} V}{\left( \frac{R_1+R_2}{R_1} \right) + R_5 + \left( \frac{R_3+R_4}{R_3} \right)}$$

## Norton's Theorem :

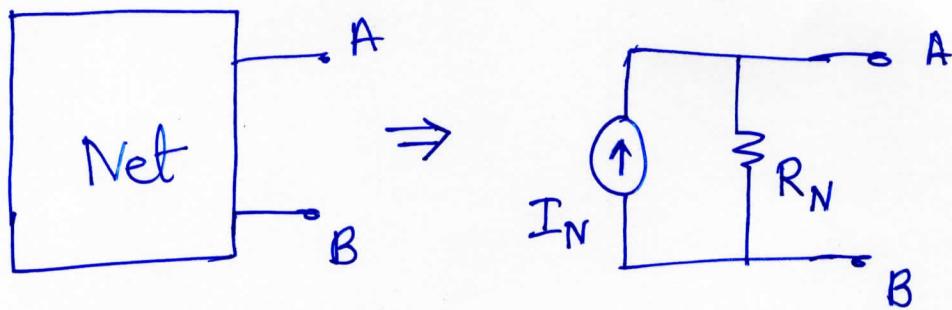


$I_N$

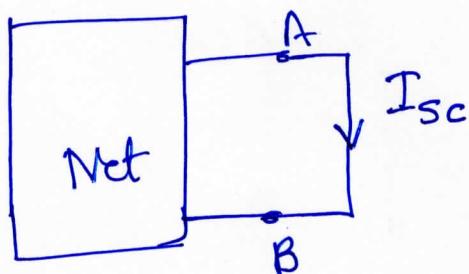

$$I_{sc} = I_N$$


$R_N$

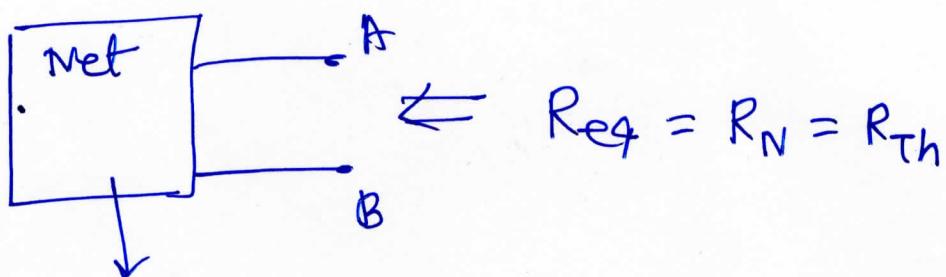

Indep. Voltage Source  $\rightarrow$  Shorted


Indep. Current  $\leftarrow \rightarrow$  Opened

ex


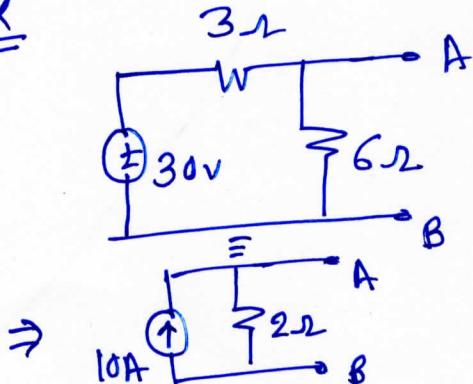


$I_N$

$R_N$

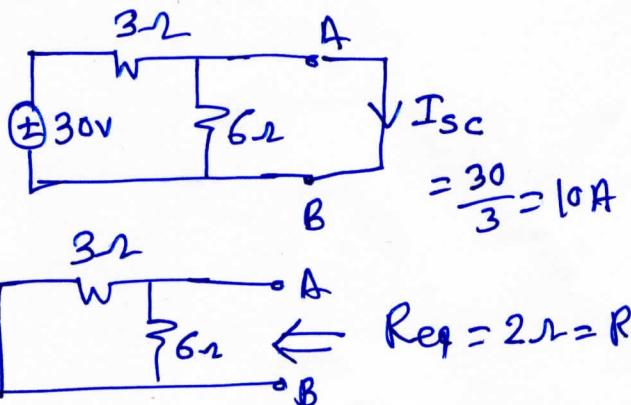



(4)

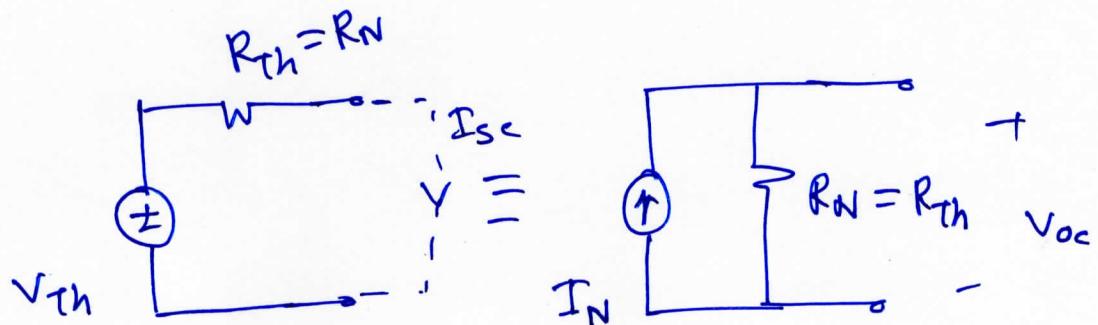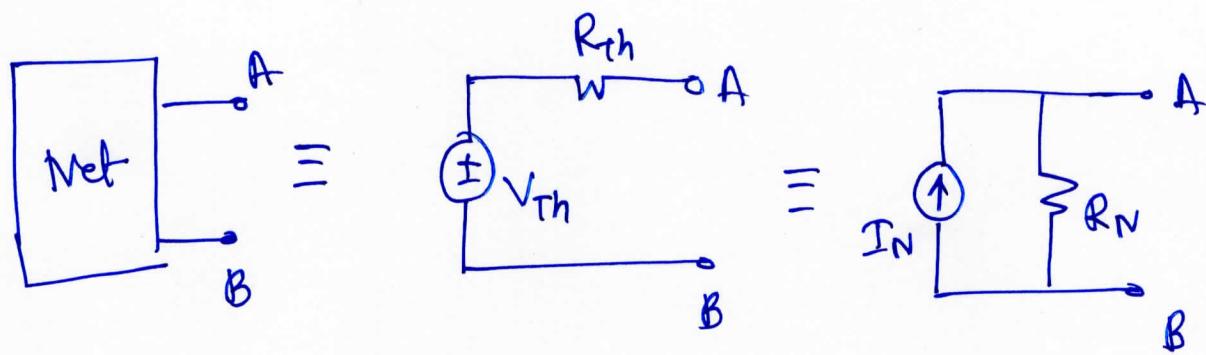

$$I_N = I_{sc} = \frac{V_{Th}}{R_{Th}}$$

$$V_{Th} = V_{oc} = I_N R_N$$
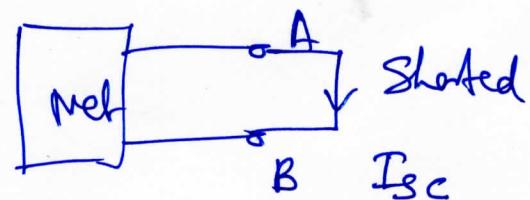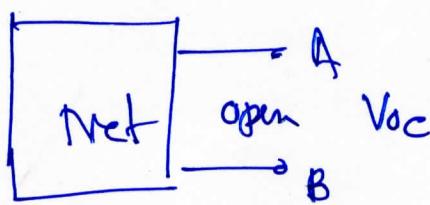
$$\begin{aligned} \frac{V_{oc}}{I_{sc}} &= \frac{I_N R_N}{(V_{Th}/R_{Th})} = \frac{I_N R_N \times R_{Th}}{V_{Th}} \\ &= \frac{I_N R_N \times R_{Th}}{I_N R_N} = R_{Th} = R_N \end{aligned}$$




$$R_{Th} = \frac{V_{oc}}{I_{sc}}$$

Power delivered / Consumed


( $P_D$ )

( $P_C$ )

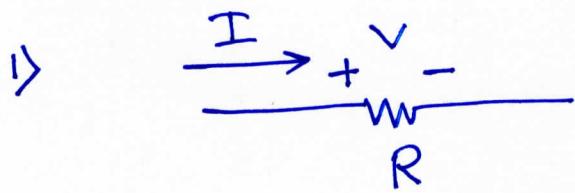


$$V = IR$$


$$P_C = VI = I^2R = \frac{V^2}{R}$$

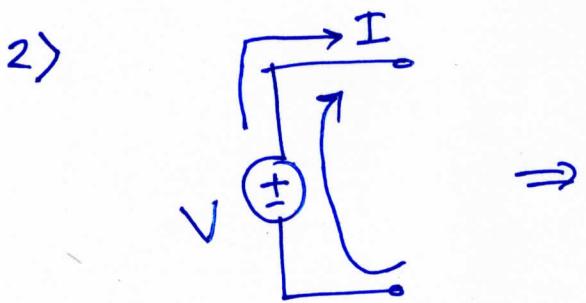


$$P_D = VI$$

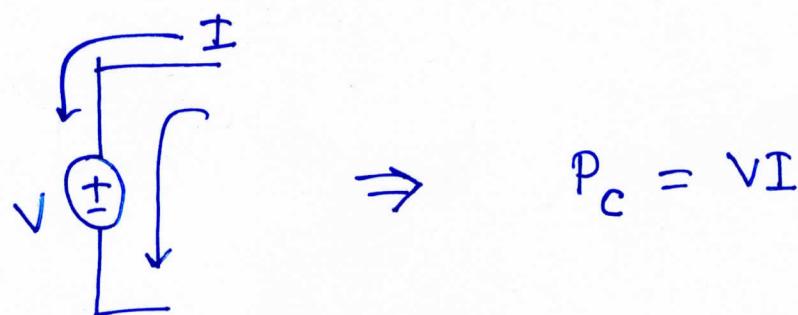

$$P_C = VI$$

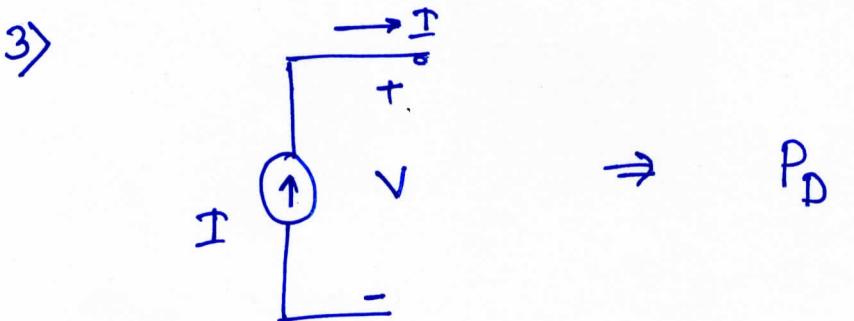


$$P_D = VI$$

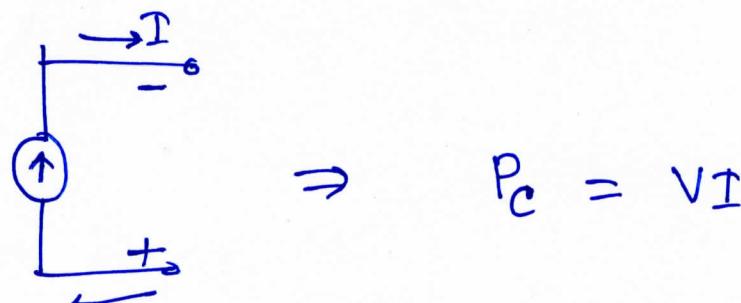

$$P_C = VI$$

ex

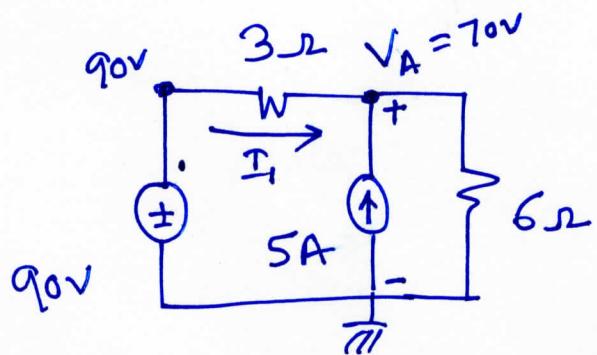

$$\frac{V_A - 90}{3} + \frac{V_A - 0}{6} = 5$$

$$\Rightarrow \frac{2V_A - 180 + V_A}{6} = 5$$

$$\Rightarrow 3V_A = 30 + 180 = 210$$

$$V_A = 70V$$

3Ω

$$I_1 = \frac{90 - 70}{3} = \frac{20}{3} A$$

$$P_{C_1} = I_1^2 \times 3 = \frac{400}{9} \times 3 = \frac{400}{3} \text{ watt}$$

6Ω

$$P_{C_2} = \frac{V^2}{R} = \frac{70^2}{6}$$

90V

$$P_{D_1} = V I = 90 \times I_1 = 90 \times \frac{20}{3} = 600 \text{ watt}$$

5A

$$P_{D_2} = V \times I = 70 \times 5 = 350 \text{ watt}$$

$$\underline{P_{C_1} + P_{C_2} = P_{D_1} + P_{D_2}}$$