
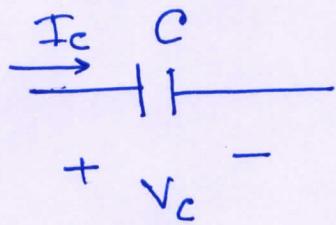


RC & RL Circuits


Capacitor

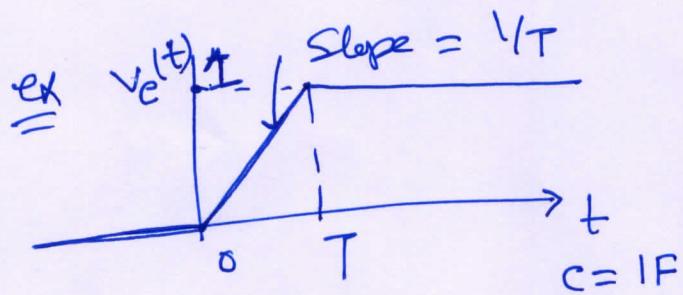




$$I_c = C \frac{dV_c}{dt}$$



Inductor

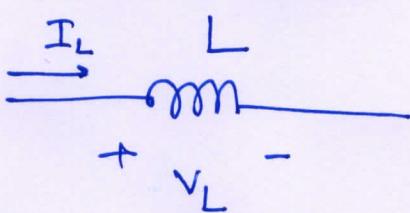

$$V_L = L \frac{dI_L}{dt}$$

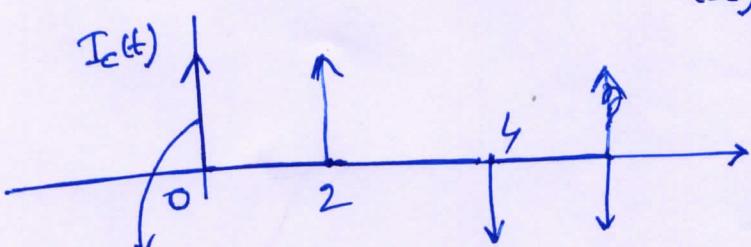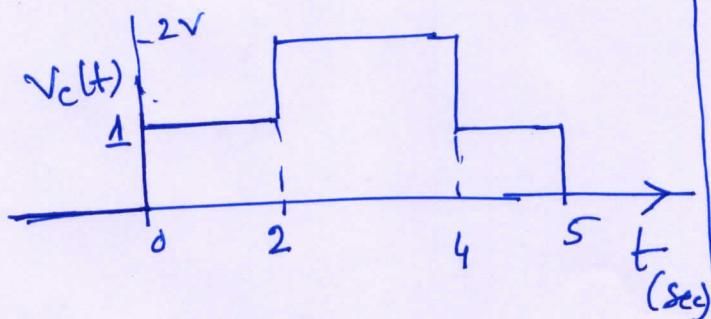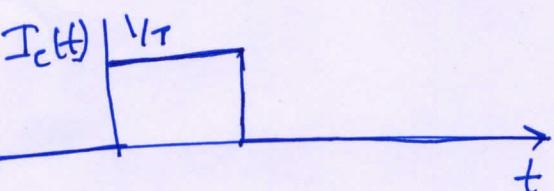

Impulse $\delta(t) = 0$ when $t \neq 0$

$$\int_{-\infty}^{\infty} \delta(t) dt = 1$$

For finite $I_c(t)$,

$V_c(t) \rightarrow$ no sudden change


$$\Rightarrow V_c(t=T_-) = V_c(t=T_+)$$

Similarly,

$$I_L(t=T_-) = I_L(t=T_+)$$

Initial condition:

$$V_c(t=0_-) = 0$$

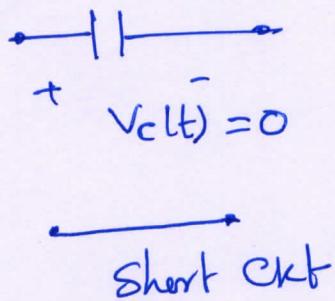

$$I_L(t=0_-) = 0 \text{ A}$$

$$\Rightarrow I_L(t=0+) = 0 \text{ A}$$

open ckt

Final Condition for DC input

$I_c(t), V_c(t) \rightarrow$ constant
at steady-state

$$I_c = \frac{dV_c(t)}{dt} = 0$$

$\overrightarrow{I_{c20}}$ open ckt


$$I_L(t), V_c(t) \rightarrow \text{constant}$$

$$\Rightarrow V_L(t) = L \frac{dI_L}{dt} = 0$$


Short ckt

(67)

Ex

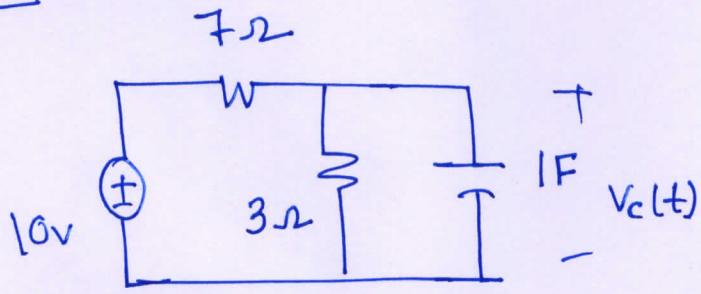


$$V_c(\infty) = ?$$

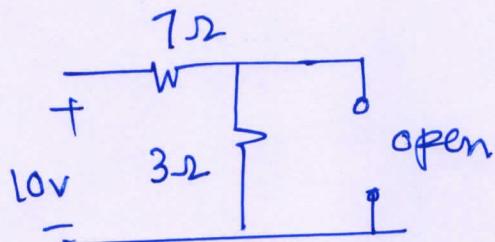

$$V_c(\infty) = \frac{3}{3+7} \times 10 = 3V$$

$$I_L(\infty) = \frac{5}{5} = 1A$$

Ex

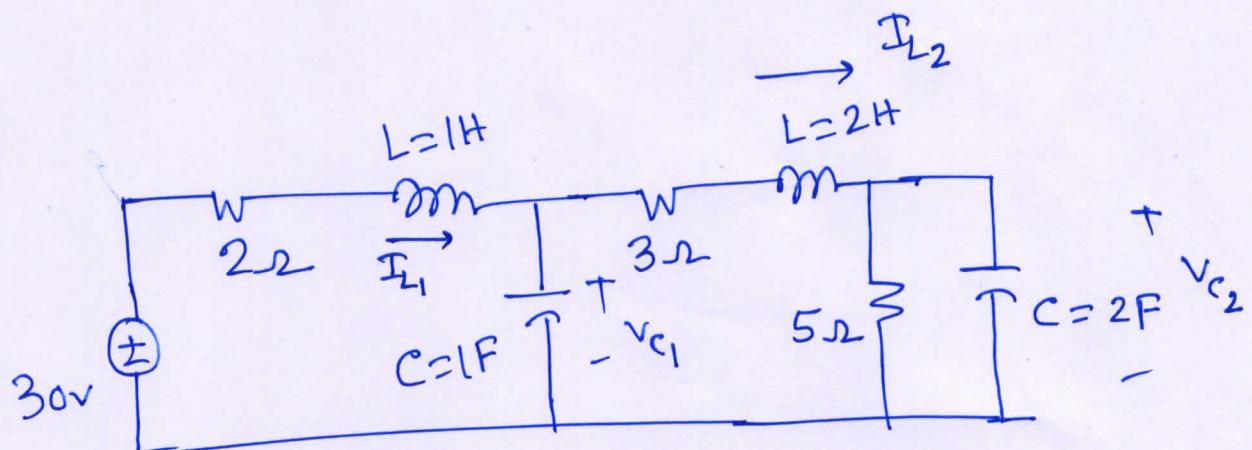



$$V_{c1}(\infty) = 24V$$

$$I_{L1}(\infty) = 3A$$

$$V_{c2}(\infty) = 15V$$

$$I_{L2}(\infty) = 3A$$

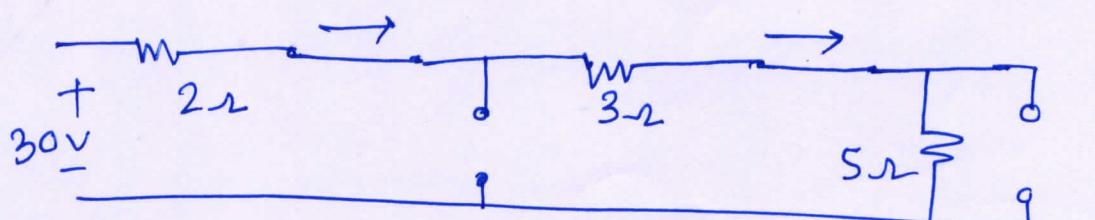


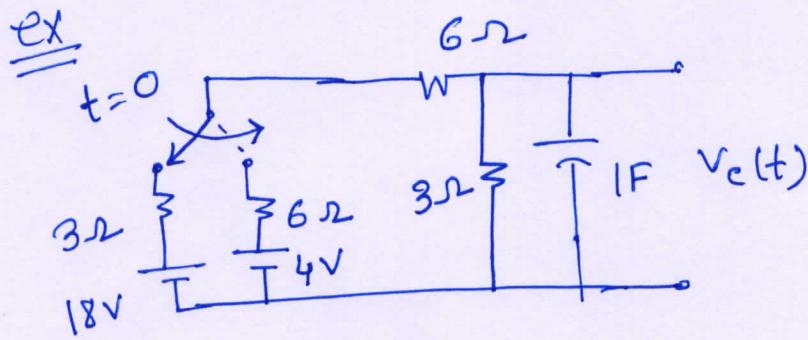

$$V_c(0+) = ?$$

$$V_c(\infty) = ?$$


$t < 0$

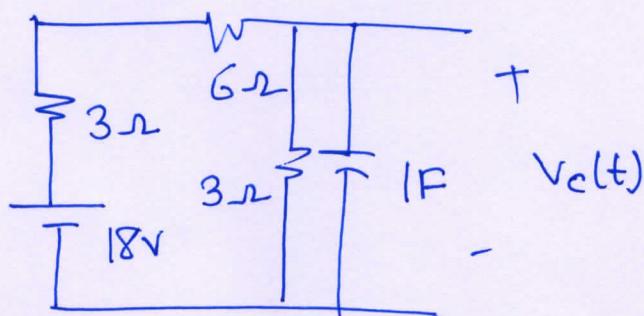

$$V_c(0-) = \frac{3}{3+6+3} \times 18 = \frac{3}{12} \times 18 = 4.5V$$

So, $V_c(0+) = V_c(0-) = 4.5V$


$t > 0$

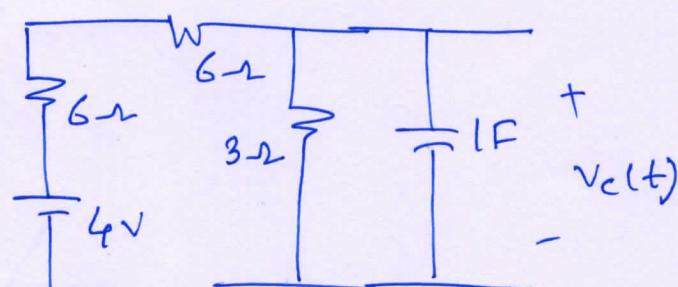

$$V_c(\infty) = \frac{3}{6+6+3} \times 4 = \frac{3}{15} \times 4 = 0.8V$$

$$= \frac{3}{15} \times 4 = 0.8V$$

RC circuit

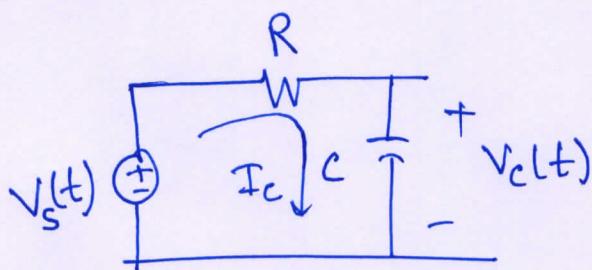

$$V_c(t=0-) = V_i$$

(initial voltage
across capacitor c)

$$I_c(t) = C \frac{dV_c}{dt}$$

KVL

$$V_s(t) = I_c(t) R + V_c(t)$$

$$= RC \frac{dV_c(t)}{dt} + V_c(t)$$

$$\boxed{V_c(t) + RC \frac{dV_c(t)}{dt} = V_s(t)}$$

$$V_c(t) = C.F + P.I$$

C.F (Natural response)

$$V_c(t) + RC \frac{dV_c}{dt} = 0$$

$$\Rightarrow \frac{dV_c}{dt} = -\frac{1}{RC} V_c$$

$$\Rightarrow \int \frac{dV_c}{V_c} = -\int \frac{1}{RC} dt$$

$$\Rightarrow \ln(V_c(t)) = -t/Rc + k_1$$

Put $k_1 = \ln(k)$

$$\Rightarrow \ln(V_c(t)) = -\frac{t}{Rc} + \ln(k)$$

$$\Rightarrow \ln_e\left(\frac{V_c(t)}{k}\right) = -\frac{t}{Rc}$$

$$\Rightarrow \frac{V_c(t)}{k} = e^{-\frac{t}{Rc}}$$

$$\Rightarrow V_c(t) = k e^{-t/Rc}$$

P.I. (Forced response)

$$V_c(t) + R_c \frac{dV_c(t)}{dt} = V_s(t)$$

For DC input

$$\frac{V_s(t)}{V_u(t)} = V_u(t)$$


$\Rightarrow V_c(t) \rightarrow \text{constant}$

$$\Rightarrow \frac{dV_c}{dt} = 0$$

$$\Rightarrow V_c(t) = V$$

1. $u(t) \rightarrow \text{Step input}$

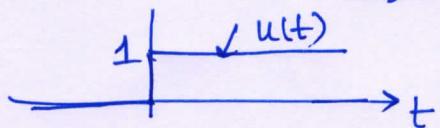1. $u(t) = 1 \text{ for } t \geq 0$
 $= 0 \text{ elsewhere}$



(71)

So, voltage across the capacitor

$$V_c(t) = C.F + P.I$$


$$= K e^{-\frac{t}{RC}} + V$$

at $t=0$, $V_c(t) = V_i = V_c(0-) = V_c(0+)$


$$\Rightarrow V_i = K \cdot e^0 + V$$

$$\Rightarrow K = (V_i - V)$$

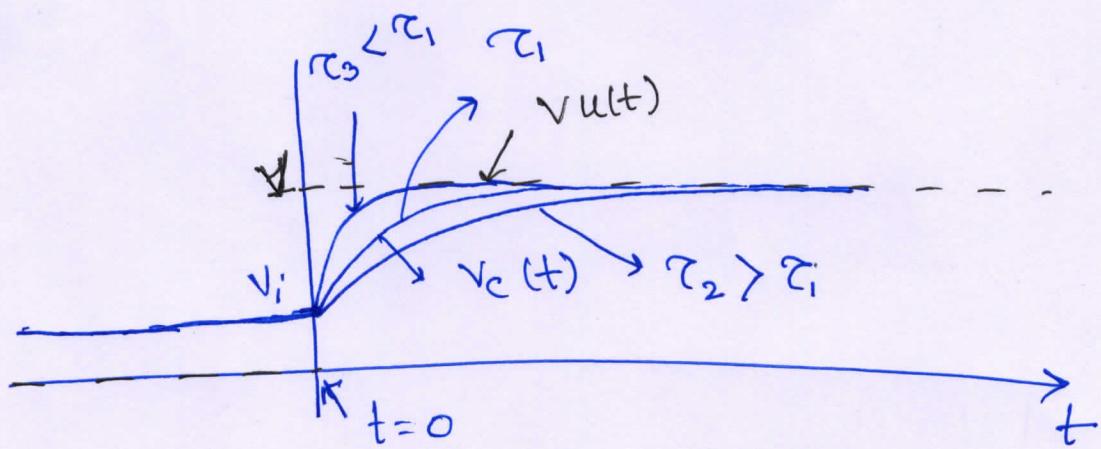So, $V_c(t) = V + (V_i - V) e^{-t/RC}$ for $t \geq 0$



$$RC = \tau = \text{time constant}$$

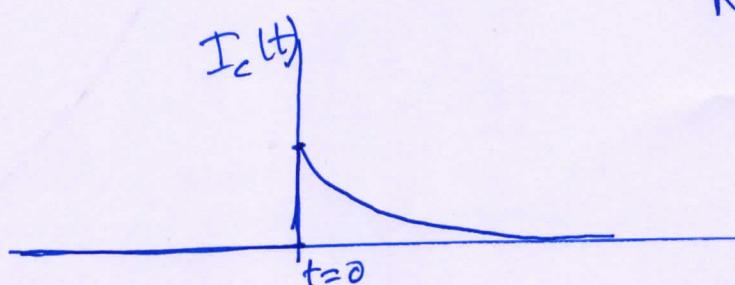


$$I_c(t) = C \frac{dV_c}{dt} = C(V_i - V) \left(-\frac{1}{RC}\right) e^{-t/RC} \quad (72)$$

For $V_i = 0$,

$$V_c(t) = V + (0 - V) e^{-t/Rc}$$

$$= V(1 - e^{-t/Rc}) = V(1 - e^{-t/\tau})$$

where $\tau = Rc$

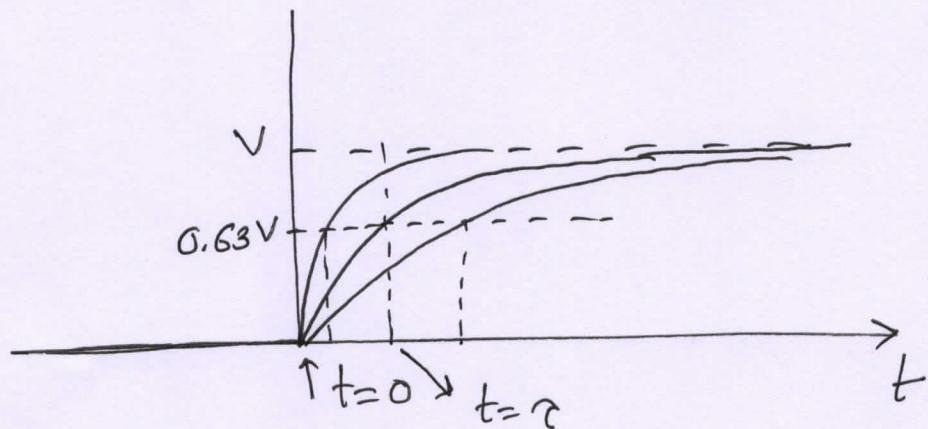


at $t = \tau$,


$$V_c(t) = V(1 - e^{-1}) = 0.63V$$

②

ex

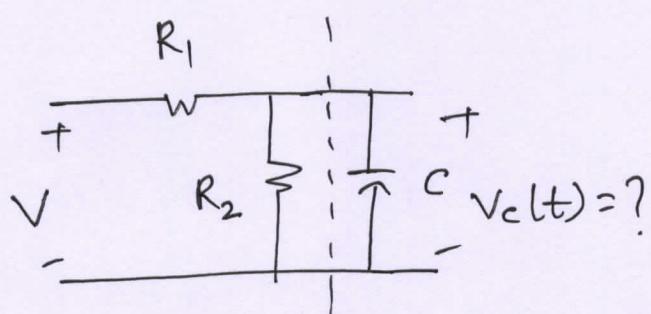

V_i = initial potential across C.

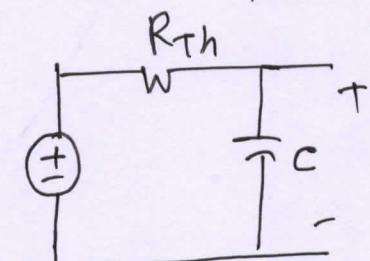

$$V_c(t) = V_{th} + (V_i - V_{th}) e^{-t/(R_{th}C)}$$


$$= \frac{R_2}{R_1+R_2} V$$

$$R_{th} = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

V_{th} = final potential across C = V_f (7.3)


$$V_C(t) = V_f + (V_i - V_f)e^{-t/(R_{eq}C)}$$
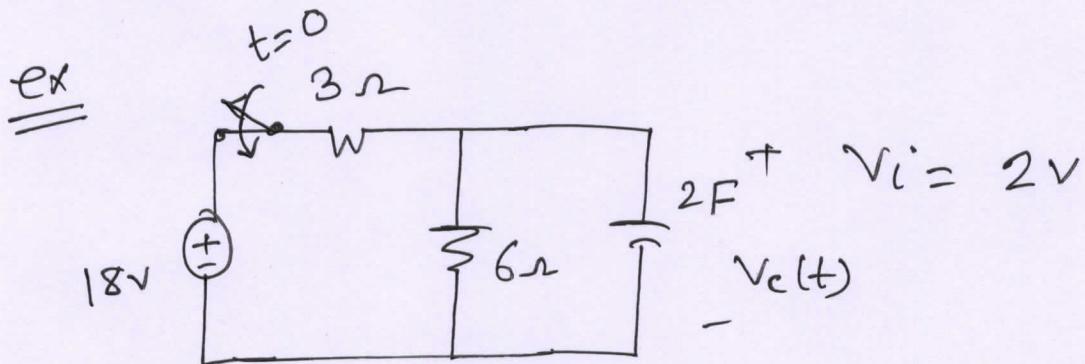
$$\begin{cases} V_C(0+) = V_i \\ V_C(\infty) = V_f \end{cases}$$



$$R_{eq} = 3||6 = 2\Omega$$

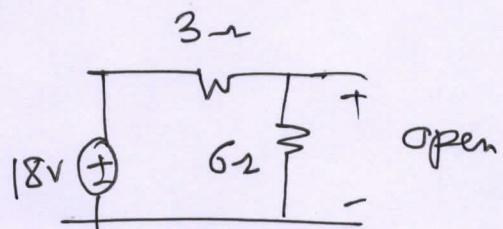
$$V_f = \frac{6}{3+6} \times 18 = 12\text{V}$$




$$V_C(t) = V_f + (V_i - V_f)e^{-t/(R_{eq}C)}$$

$$= 12 + (2 - 12) e^{-t/4}$$

$$= 12 - 10 e^{-t/4}$$

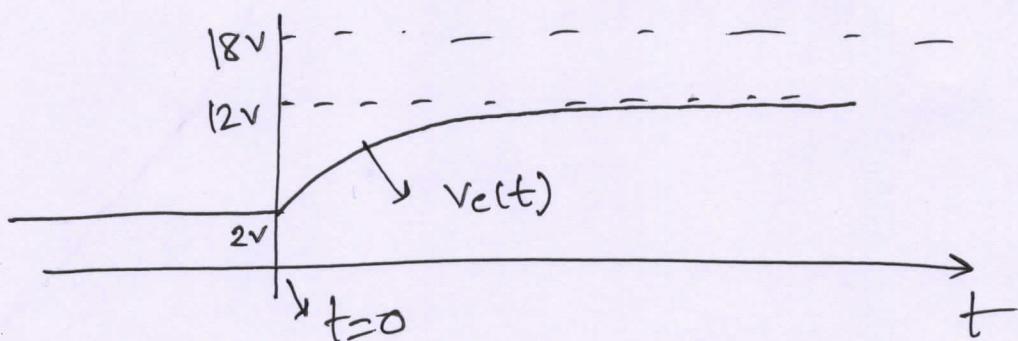


Ex

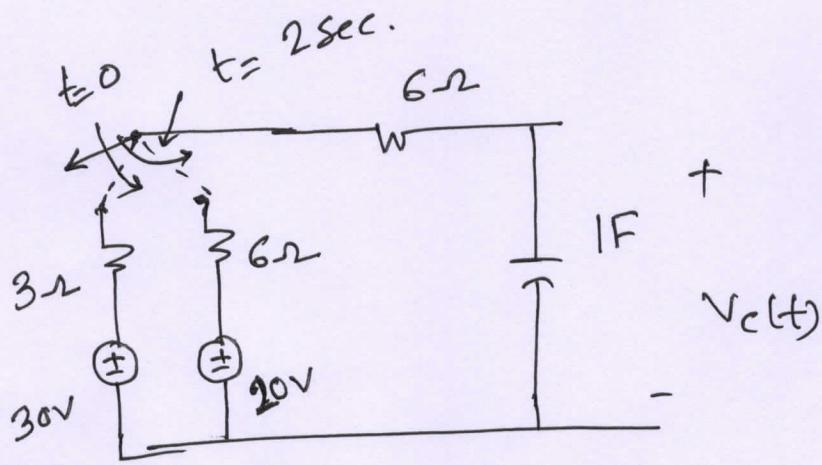

$$V_i(t) = V_c(0^-) \\ = 5V$$

$0 \leq t \leq 2$

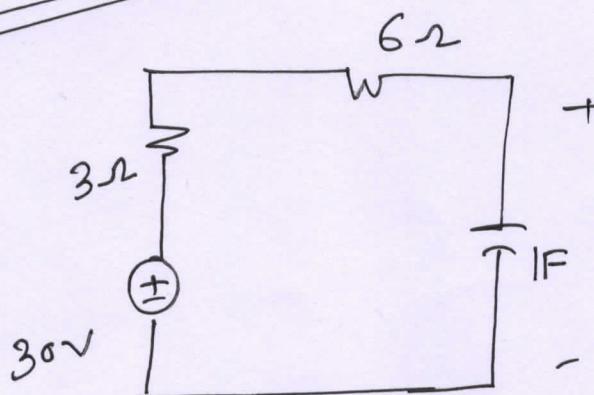

$$V_i = 5V$$


$$V_c(t) = V_f + (V_i - V_f) e^{-t/R_{eq}C}$$

$$= 30 + (5 - 30) e^{-t/9}$$

$$= 30 - 25 e^{-t/9}$$

$$V_c(2) = 30 - 25 e^{-2/9} = 9.98V$$

$2 \leq t < \infty$

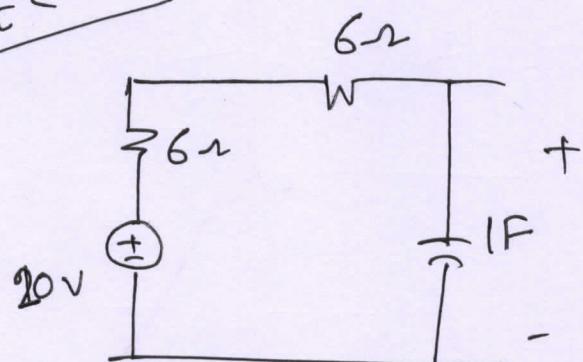



$$V_i = 9.98V$$

$$V_f = 20V$$


$$V_c(t) = V_f + (V_i - V_f) e^{-\frac{(t-2)}{R_{eq}C}}$$

$$= 20 + (9.98 - 20) e^{-\frac{(t-2)}{12}}$$


$$= 20 - 10.02 e^{-\frac{(t-2)}{12}}$$

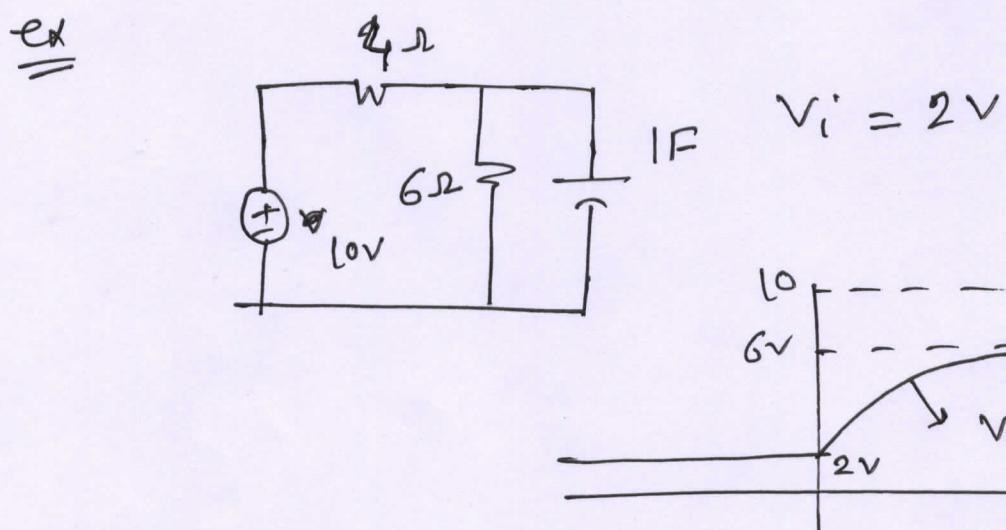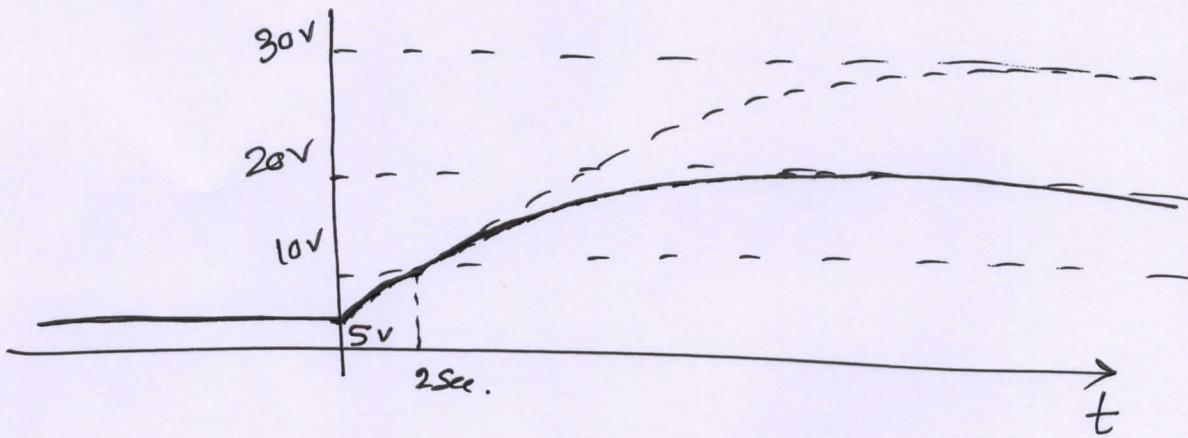

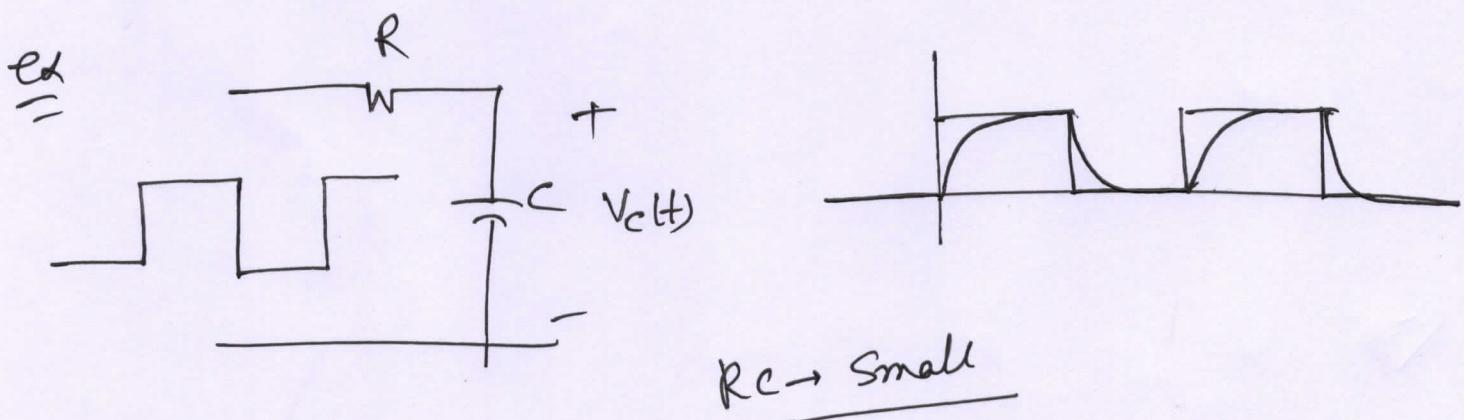
$$R_{eq} = \frac{4 \times 6}{4+6} = 2.4$$



ex

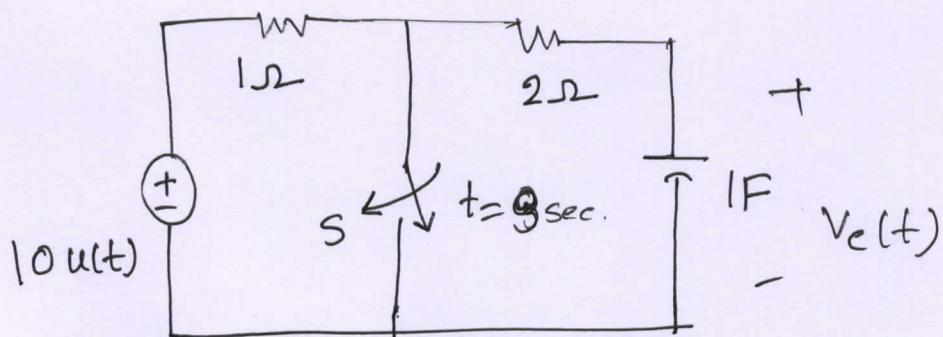


$t < 0$

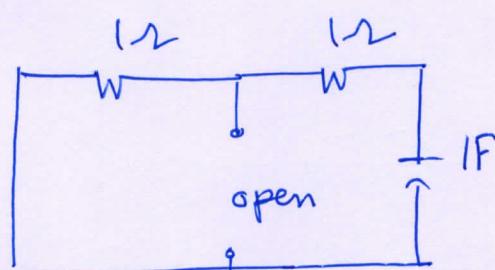

$$V_c(0-) = 0V = V_i$$

$0 \leq t \leq 3\text{sec.}$

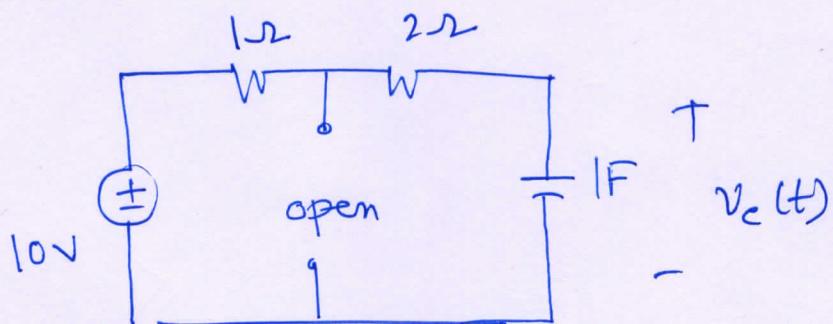

$$V_f = 10V$$

$$V_c(t) = V_f + (V_i - V_f) e^{-t/R_C}$$


$$= 10 + (0 - 10) e^{-t/(3 \times 1)}$$

$$= 10(1 - e^{-t/3})$$

$$\text{At } t = 3\text{sec}; \quad V_c(t) = 10(1 - e^{-1}) = 6.3V$$

(77)

3) $t > 3 \text{ Sec}$

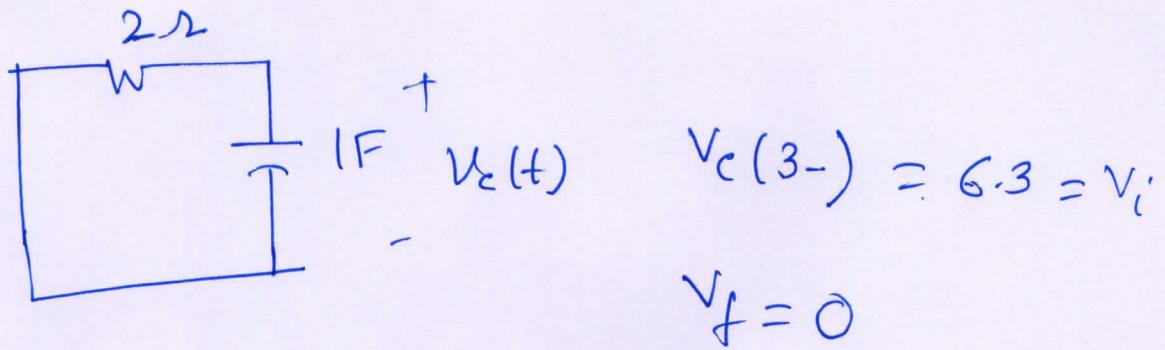

$$V_c(t) = V_f + (V_i - V_f) e^{-(t-3)/RC}$$


$$= 0 + (6.3 - 0) e^{-\frac{(t-3)}{2}}$$

$$= 6.3 e^{-(t-3)/2}$$


$$V_c(t) = 0 \quad \text{for } t \leq 0$$

$$= 10(1 - e^{-t/3}) \quad \text{for } 0 \leq t \leq 3$$
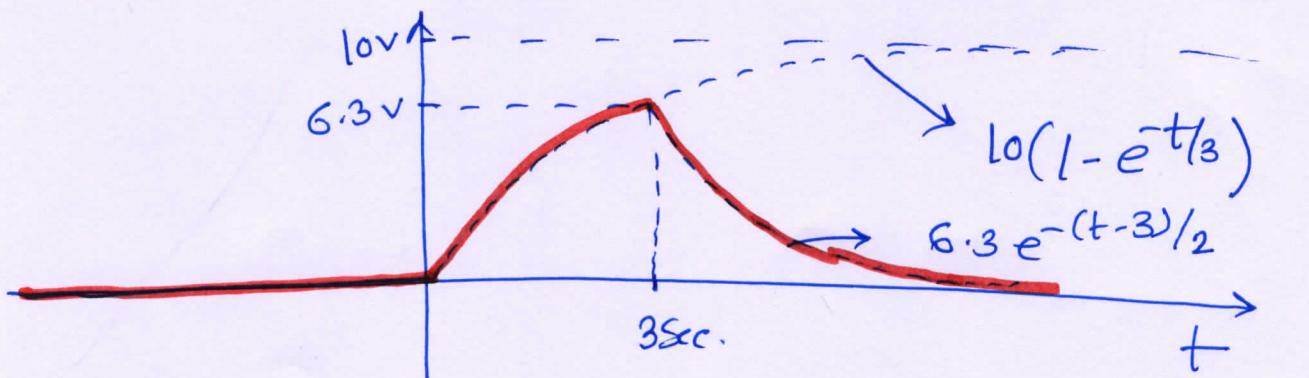
$$= 6.3 e^{-(t-3)/2} \quad \text{for } t \geq 3$$



ex

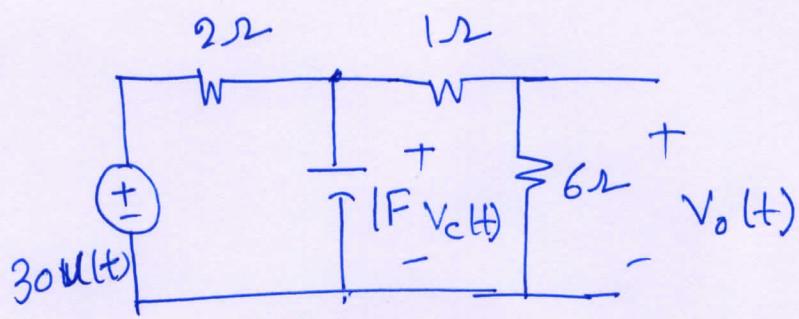


$$V_o(t) = \frac{6}{1+6} V_c(t)$$


$$= \frac{6}{7} V_c(t)$$

$$V_i = 0$$
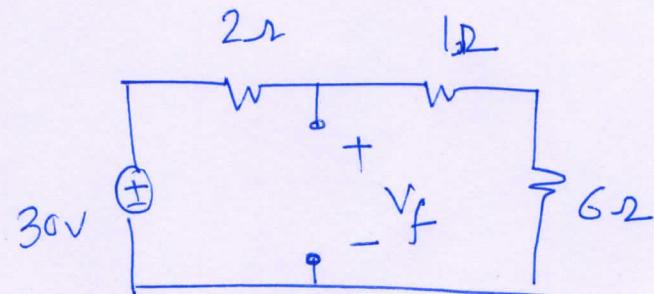
$$\begin{aligned} V_f &= \frac{7}{7+2} \times 30 \\ &= \frac{70}{3} \text{ v} \end{aligned}$$



R_{eq}

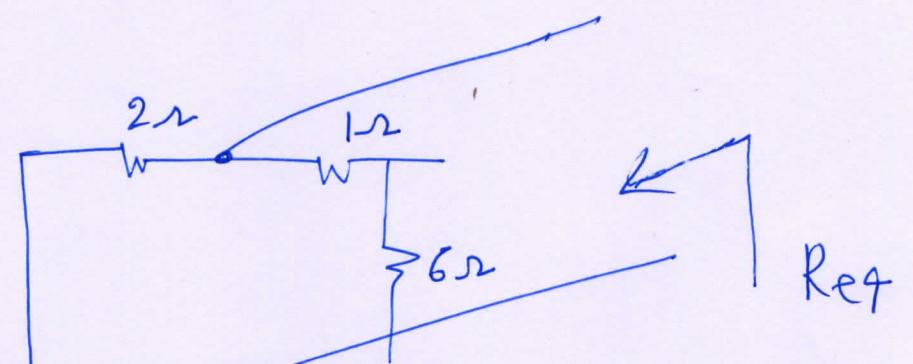

$$= 2 + 1$$

$$= \frac{2+1}{2+1} = \frac{14}{9} \Omega$$


$$V_c(t) = \frac{70}{3} + \left(0 - \frac{70}{3}\right) e^{-t/(14/9)}$$

$$= \frac{70}{3} \left(1 - e^{-9t/14}\right)$$

$$\Rightarrow V_o(t) = \frac{6}{7} V_c(t) = 20 \left(1 - e^{-9t/14}\right); t \geq 0$$

(79)

Series Connection of Capacitors

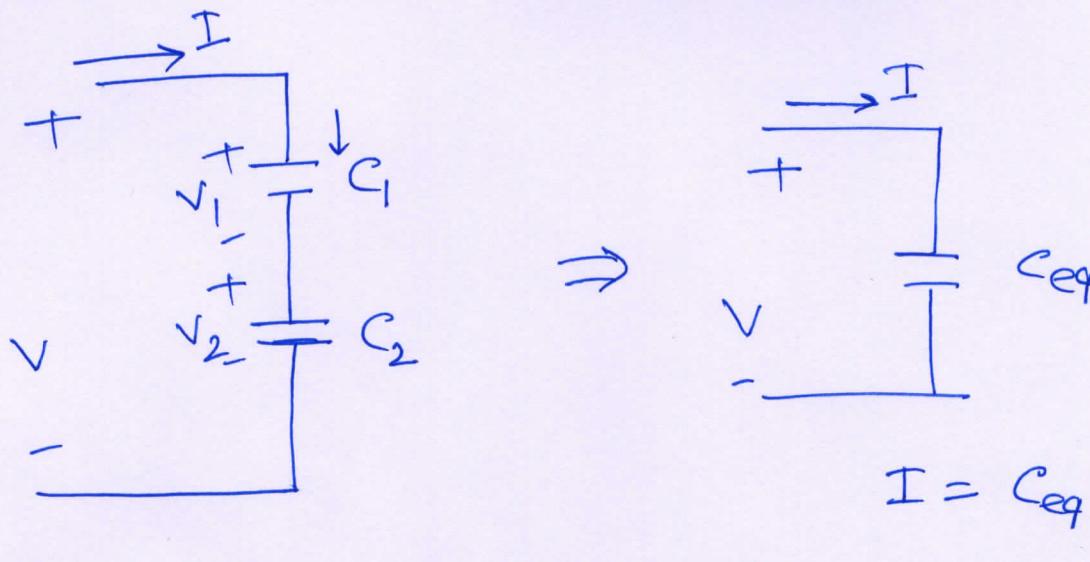

$$I = C_1 \frac{dV_1}{dt} \Rightarrow \frac{dV_1}{dt} = \frac{1}{C_1} I$$

$$I = C_2 \frac{dV_2}{dt} \Rightarrow \frac{dV_2}{dt} = \frac{1}{C_2} I$$

$$V = V_1 + V_2$$



$$\Rightarrow \frac{dV}{dt} = \frac{dV_1}{dt} + \frac{dV_2}{dt} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$= \left[\frac{1}{C_1} + \frac{1}{C_2} \right] I = \frac{1}{C_{eq}} I$$

$$\Rightarrow \boxed{I = C_{eq} \frac{dV}{dt}}$$

$$\text{where } C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

ex

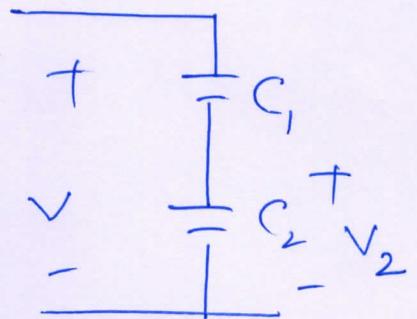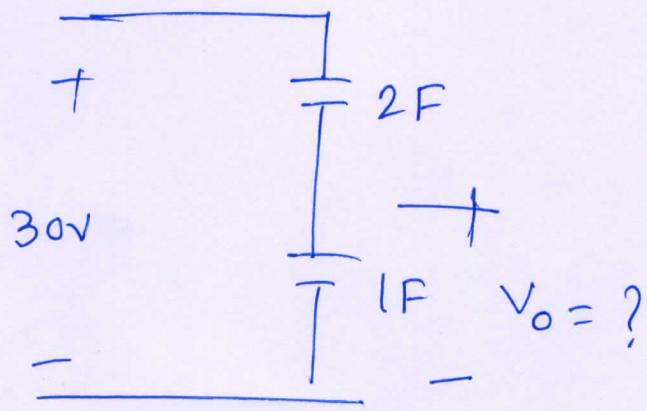


$$V = \frac{2}{3} \times 30$$


$$= \underline{\underline{20V}}$$

$$V_2 = \frac{C_1}{C_1 + C_2} V$$

ex

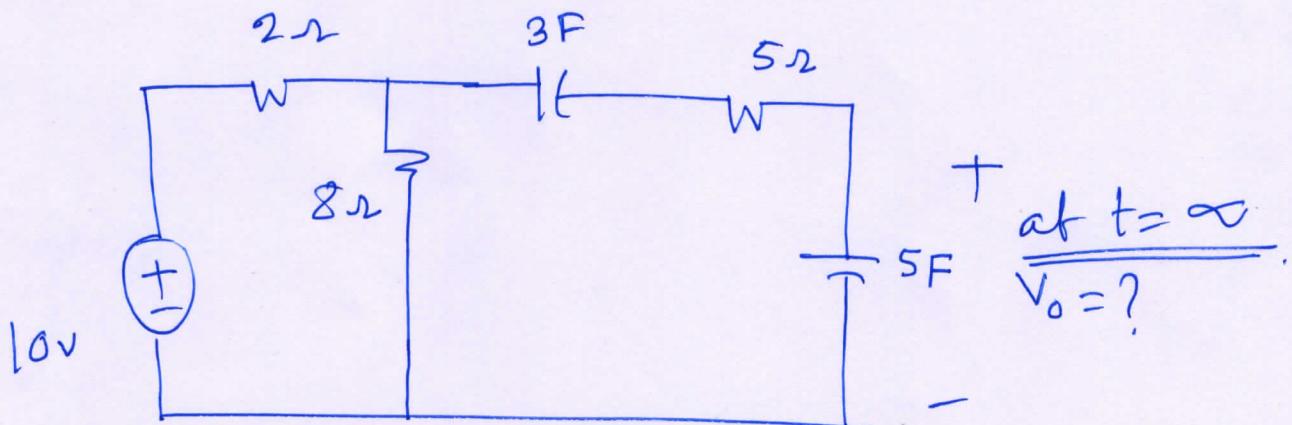

At $t = \infty$

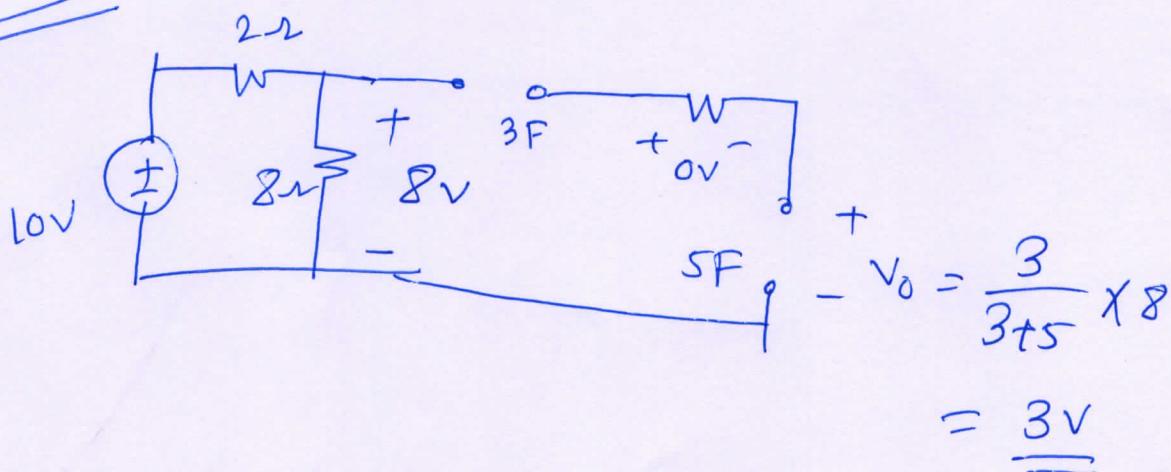

(81)