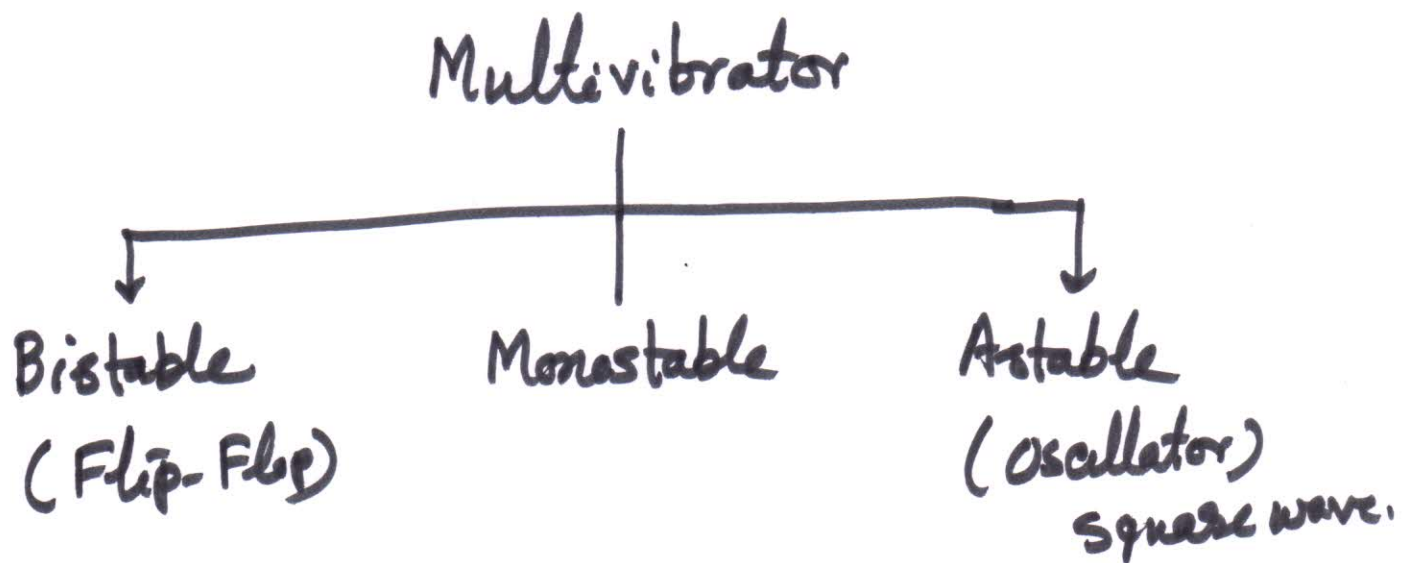


SEQUENTIAL CIRCUITS

Combinational logic \rightarrow Logic gates
are building blocks

Sequential logic \rightarrow Flip-Flop is
the building block.




states \rightarrow '0' and '1'
(LOW) (HIGH)

Bistable : Both the states are stable

Monostable : Only one state is stable

Astable : Both the states are not stable


Bistable Multivibrator

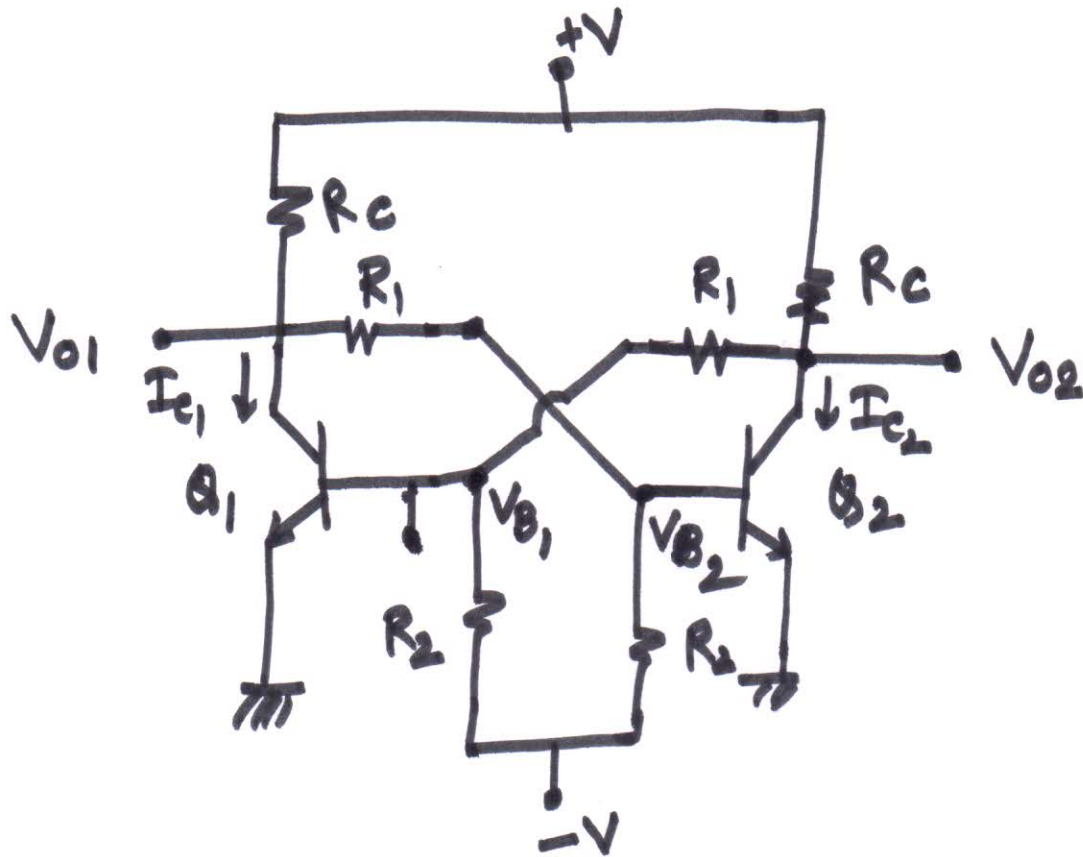

One transistor will be in 'saturation' region & other will be in 'cut-off' region.

$$V_{01} \Rightarrow V_{CE1} \quad \& \quad V_{02} = V_{CE2}$$

Suppose
 $I_{C2} > I_{C1}$

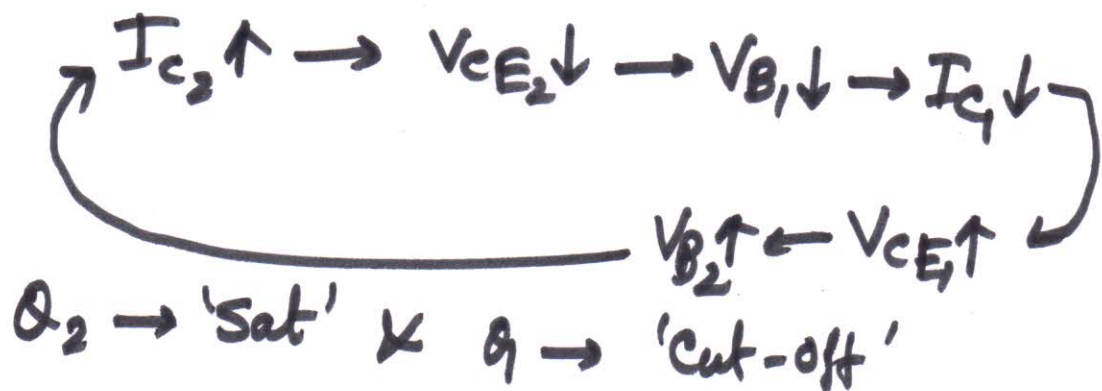

when, $\theta_2 \rightarrow \text{'Sat'}$ & $\theta_1 \rightarrow \text{'Cut-off'}$


then

$V_{o2} \rightarrow \text{Low ('0')}$

$V_{o1} \rightarrow \text{High ('1')}$

By triggering we can change the states.

RC Circuit

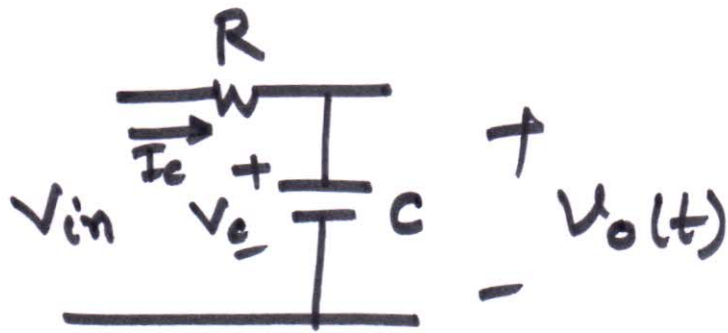

$$V_o(t) = V_c(t)$$

$$V_c(0^-) = V_i$$

$$V_{in} = R \cdot I_e(t) + V_c(t)$$

$$= R C \frac{dV_c}{dt} + V_c(t)$$

Solve for $V_c(t)$.

$$V_c(t) = C.F + P.I$$

C.F

$$RC \frac{dV_c(t)}{dt} + V_c(t) = 0$$

$$\Rightarrow \frac{dV_c(t)}{dt} = -\frac{1}{RC} V_c(t)$$

$$\Rightarrow \int \frac{dV_c(t)}{V_c(t)} = -\int \frac{1}{RC} \cdot dt$$

$$\Rightarrow \ln(V_c(t)) = -\frac{1}{RC} \cdot t + \ln(K)$$

$$\Rightarrow \ln(V_c(t)) - \ln(K) = -t/RC$$

$$\Rightarrow \ln\left(\frac{V_c(t)}{K}\right) = -t/RC$$

$$\Rightarrow V_c(t) = K \cdot e^{-t/RC}$$

P.I (Steady state)

If V_{in} is a D.C Signal.

$$V_{in} = 0 + V_c(\infty)$$

$$\Rightarrow V_c(\infty) = V_{in} = V_f$$

Therefore

$$\begin{aligned} V_c(t) &= V_c(\infty) + K e^{-t/RC} \\ &= V_f + K e^{-t/RC} \end{aligned}$$

$$\text{At } t=0, V_c(0) = V_i = V_c(0^-)$$


$$\Rightarrow V_i = V_f + K \cdot e^{0}_{(=1)}$$

$$\Rightarrow K = (V_i - V_f)$$


So,

$$V_c(t) = V_f + (V_i - V_f) e^{-t/RC}$$

$RC = \tau = \text{time constant}$

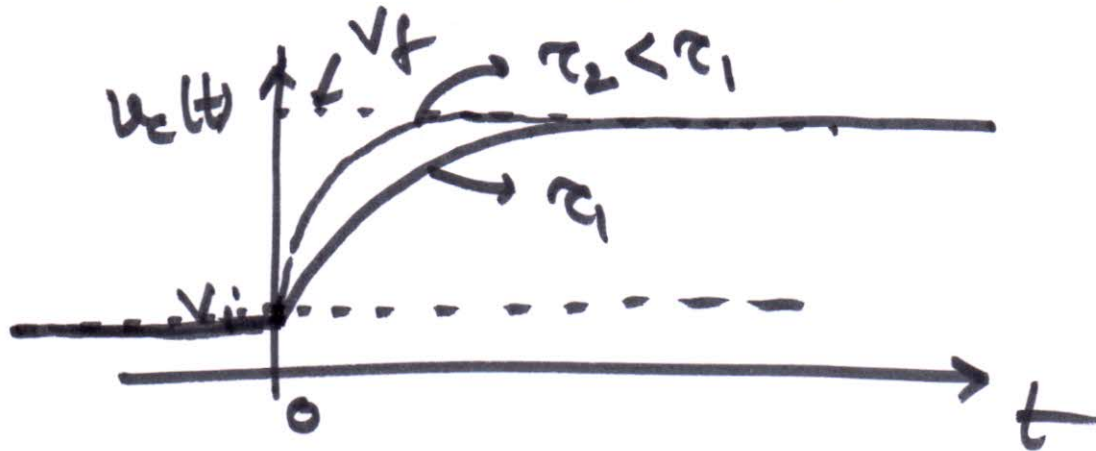

ex

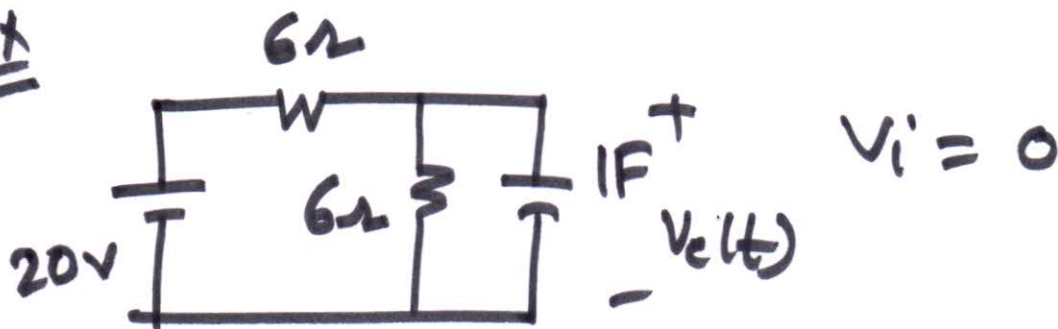


At steady state



$$V_f = \frac{6}{6+6} \times 20$$


$$= 10\text{V}$$

Req

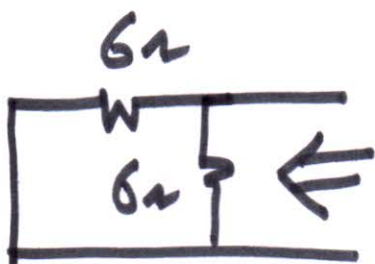

$$R_{eq} = \frac{6 \times 6}{6+6} = 3\Omega$$

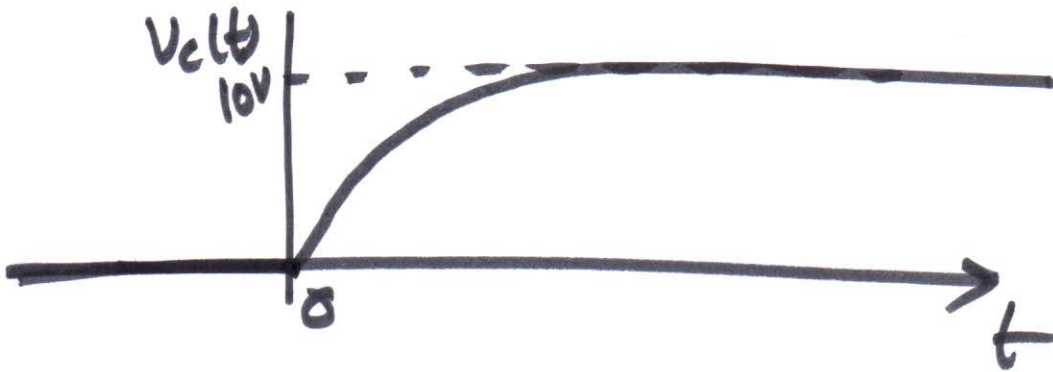
$$\begin{aligned}
 v_c(t) &= v_f + (v_i - v_f) e^{-t/R_{eq}C} \\
 &= 10 + (0 - 10) e^{-t/(3.1)} \\
 &= 10(1 - e^{-t/3})
 \end{aligned}$$



Mono-stable Multivibrator


One state \rightarrow ~~state~~ stable

Other state \rightarrow Quasi-stable

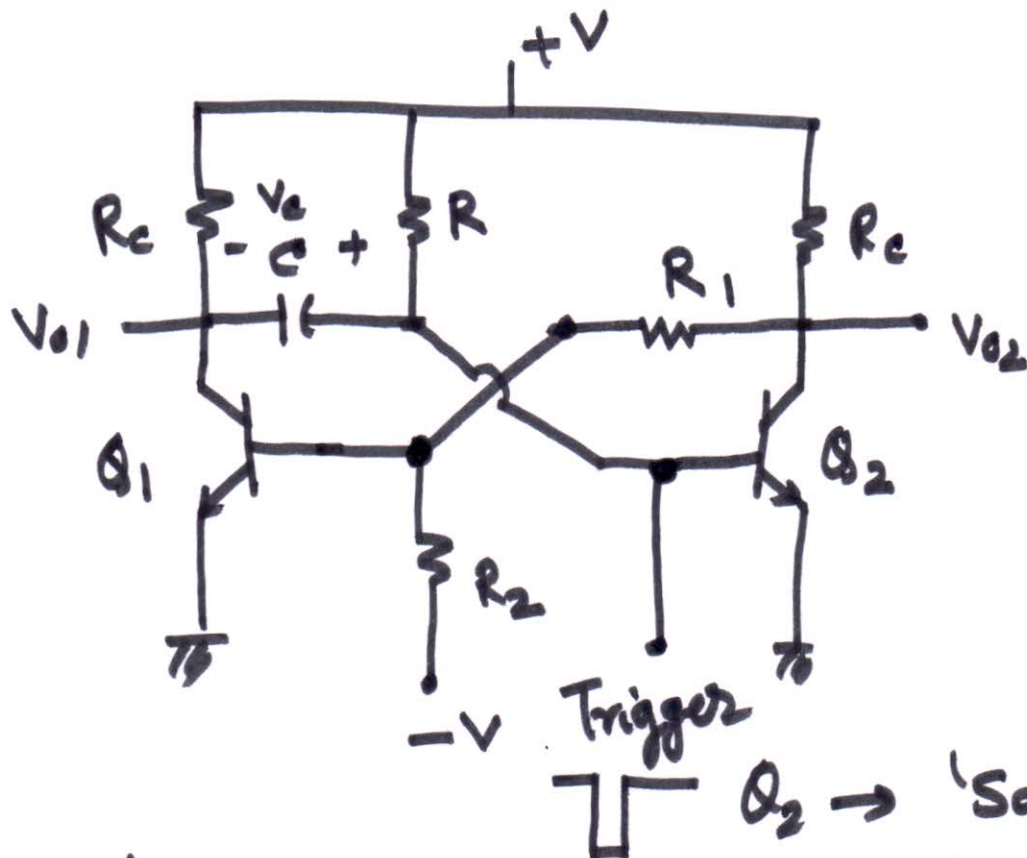

$Q_2 \rightarrow$ 'Sat'
 $Q_1 \rightarrow$ 'Cut-off'

Capacitor

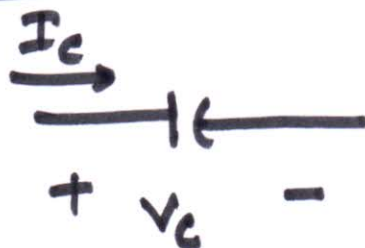

$$I_c = \frac{dq}{dt} \frac{dq}{dt}$$

$$= \frac{d}{dt} (C V_c)$$

$$= C \frac{dV_c}{dt}$$


Under steady-state,

$V_c(t) \rightarrow$ constant

$$I_c(t) = C \frac{dV_c(t)}{dt} = 0$$

(open ckt)

At Steady state

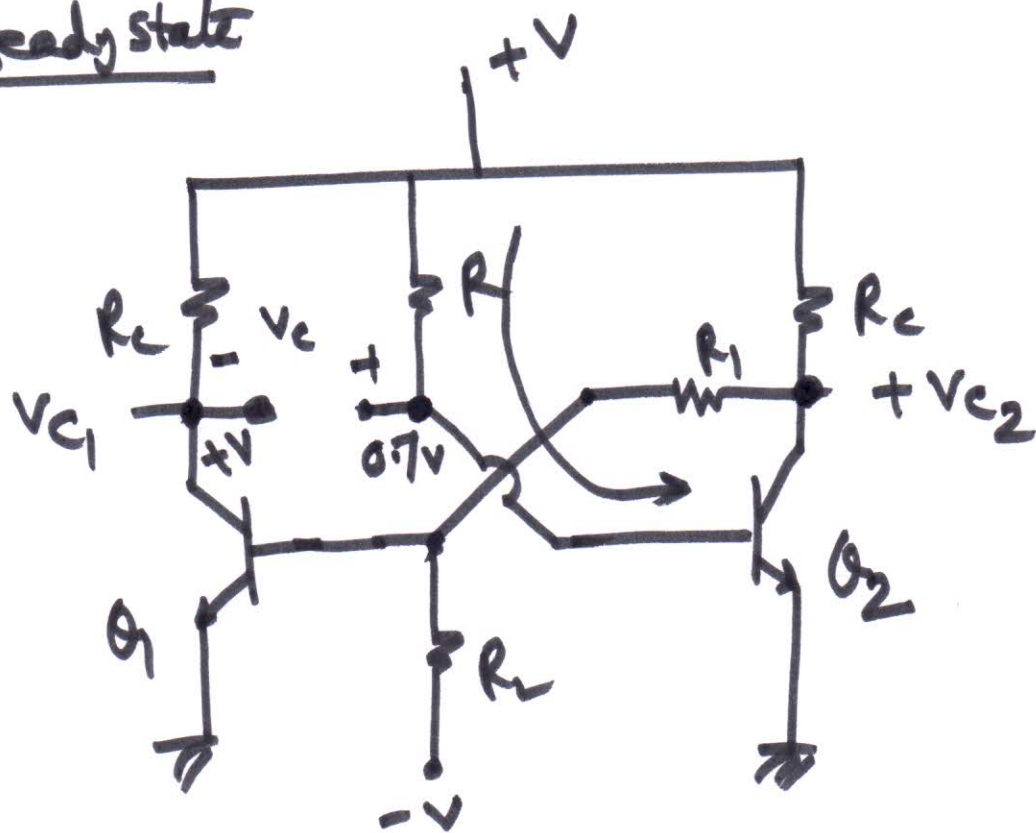

$Q_2 \rightarrow \text{'Sat'} \Rightarrow V_{C2} = 0V$

$Q_1 \rightarrow \text{'Cut-off'} \Rightarrow$


$$V_{C1} \approx +V$$

$$V_C = 0.7 - V$$

when trigger (-ve) is applied,


$\theta_2 \rightarrow$ 'cut-off'

$\theta_1 \rightarrow$ 'Sat'

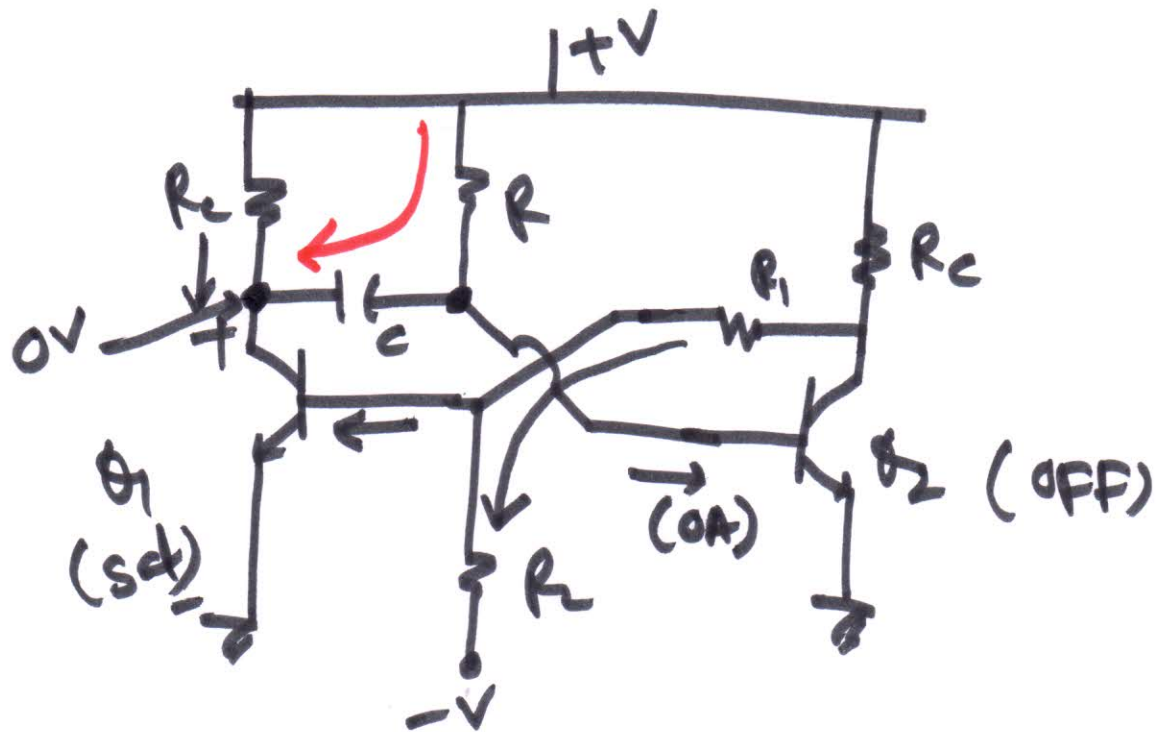

$$V_f = V$$

$$V_i = (0.7 - V)$$

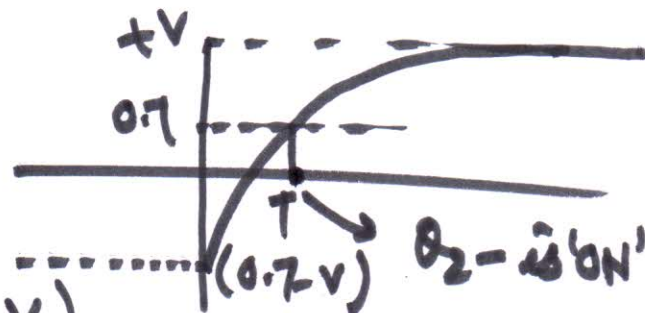

$$V_c(t) = V_f + (V_i - V_f) e^{-t/RC}$$

at $t = T$

$$V_c(t) = 0.7$$

$$\Rightarrow \underline{0.7} = V + (\underline{0.7} - V - V) e^{-T/RC}$$

$$\Rightarrow 0 = V + (-2V) e^{-T/RC}$$

$$\Rightarrow e^{-T/RC} = \frac{V}{2V} = \frac{1}{2}$$

$$\Rightarrow e^{+T/RC} = 2$$

$$T = RC \ln 2$$

$$= 0.69 RC$$

