
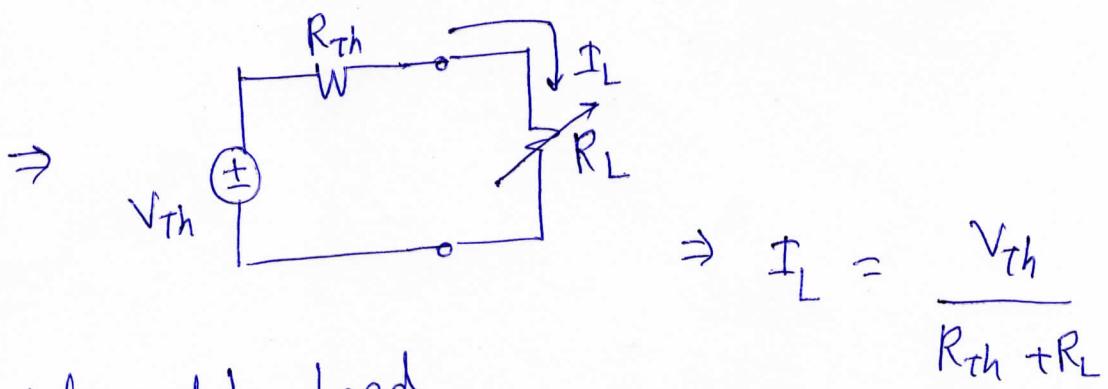


Maximum Power Transfer Theorem;

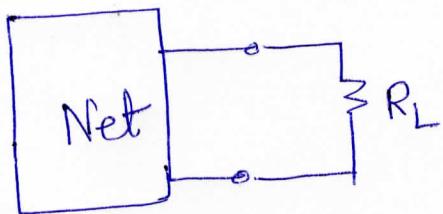

Power delivered to Load

$$P_L = I_L^2 R_L \quad R_L = ?$$

$$= \frac{V_{Th}^2 R_L}{(R_{Th} + R_L)^2}$$

$$\Rightarrow \frac{\partial P_L}{\partial R_L} = V_{Th}^2 \left[\frac{(R_{Th} + R_L)^2 \times 1 - R_L \times 2(R_{Th} + R_L) \times 1}{(R_{Th} + R_L)^4} \right]$$

$$= \frac{V_{Th}^2 \times (R_{Th} + R_L) [R_{Th} + R_L - 2R_L]}{(R_{Th} + R_L)^4}$$


$$= \frac{V_{Th}^2 (R_{Th} - R_L)}{(R_{Th} + R_L)^3}$$

For maximum Power to the load

$$\frac{\partial P_L}{\partial R_L} = 0$$

$$\Rightarrow R_{Th} - R_L = 0$$


$$\Rightarrow \boxed{R_L = R_{Th}}$$

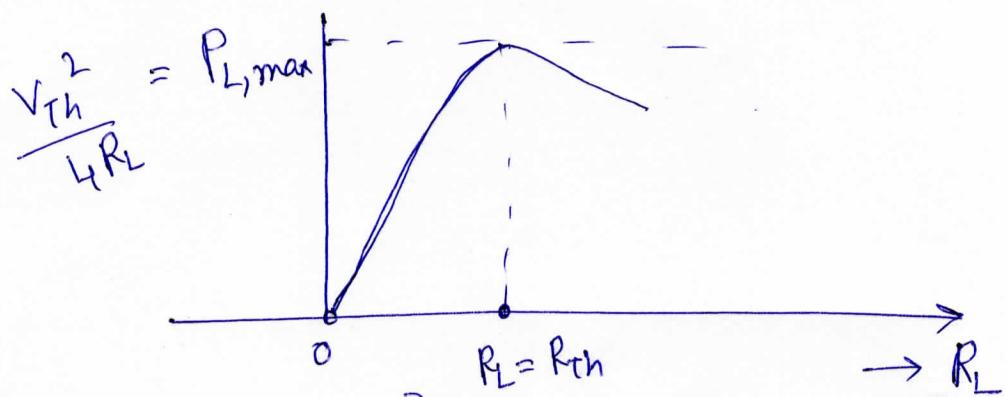

$$P_L \Big|_{max} = \frac{\frac{V_{Th}^2}{4} R_L}{(R_{Th} + R_L)^2} \Big|_{R_L = R_{Th}}$$

$$= \frac{V_{Th}^2}{4 R_{Th}}$$

Operational Amplifier (OPAMP)

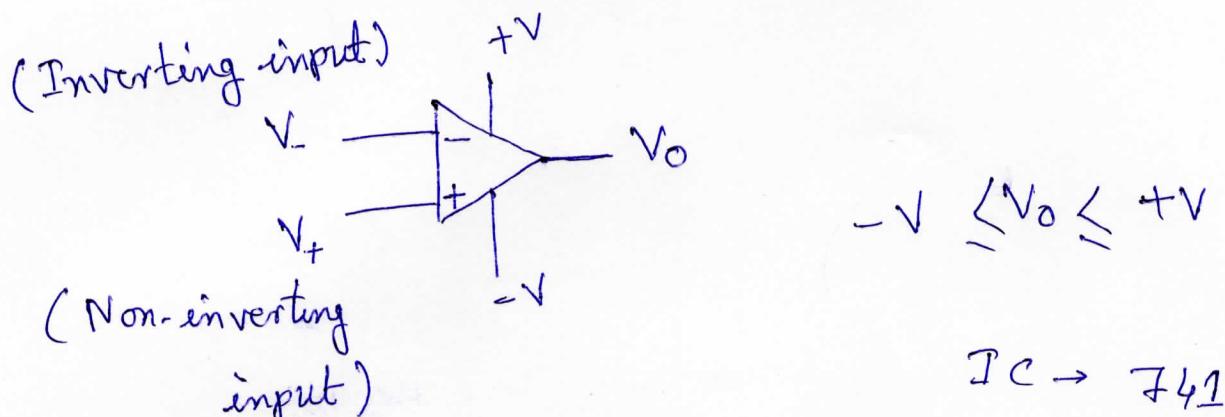


- High gain differential amplifier
- $A \rightarrow$ voltage gain (large)

$$A \rightarrow 10^6$$

$$\Rightarrow V_0 = A(V_+ - V_-)$$

Applications :-

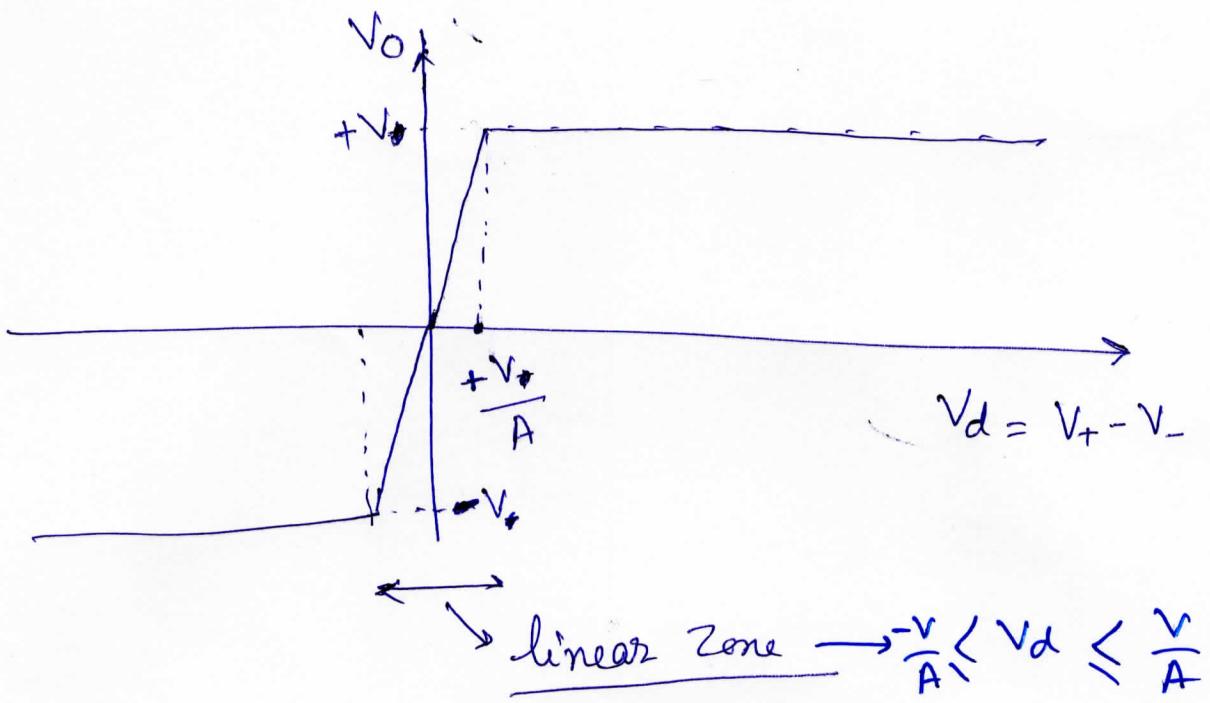1. Voltage Amplifiers
2. Math. operations \rightarrow Addition, Sub., Multiplication, Log, Integration, Differentiation,
3. To design oscillator (Square wave)



• Op-Amp is used with -ve feedback



Adv. \rightarrow System Stability \uparrow

Disadv. \rightarrow gain \downarrow

$$\boxed{-V_{\text{sat}} \leq V_o \leq +V_{\text{sat}}}$$

$$\Rightarrow V_o = A (V_+ - V_-)$$




finite

$$\Rightarrow V_+ - V_- = \frac{V_o}{A} \approx 0$$



$$\boxed{V_+ \approx V_-}$$

practical Op-Amp

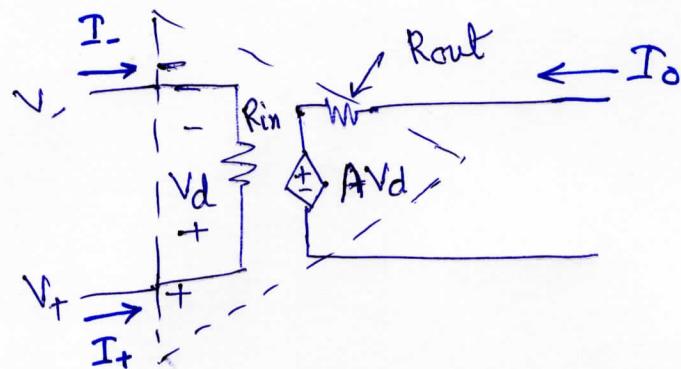

$$R_{in} \rightarrow M_\Omega \Rightarrow I_+, I_i \rightarrow (\text{low})$$

$$R_{out} \rightarrow \Omega \rightarrow I_o$$


$$A \rightarrow 10^6$$

ideal Op-Amp :

$$R_{in} \rightarrow \infty$$


$$R_{out} \rightarrow 0$$

$$A \rightarrow \infty$$

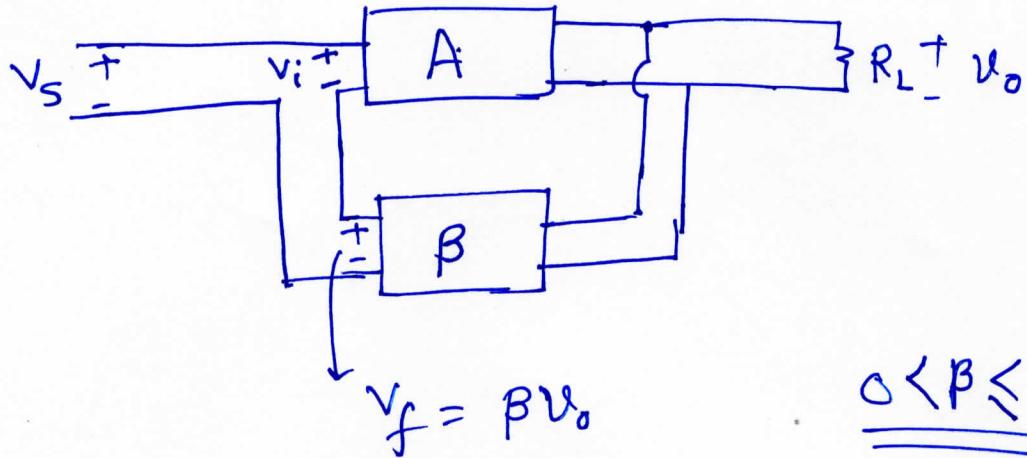

$$v_s = v_i + v_f$$
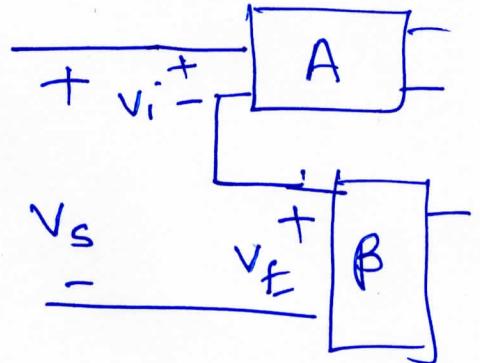
$$\Rightarrow v_i = \underline{\underline{v_s - v_f}}$$



$$v_o = A v_i = A (v_s - v_f)$$

$$= A v_s - A v_f$$

$$= A v_s - A (B v_o)$$



$$\Rightarrow v_o + A B v_o = A v_s$$

$$\Rightarrow v_o (1 + AB) = A v_s$$

$$\Rightarrow \frac{v_o}{v_s} = \frac{A}{1+AB} = A_f < A$$

$A \rightarrow \text{large}$ $A_f \approx \frac{A}{AB} = \frac{1}{\beta}$

(50)

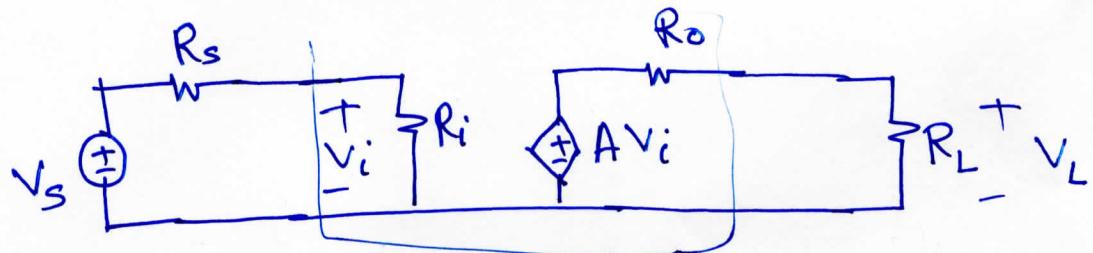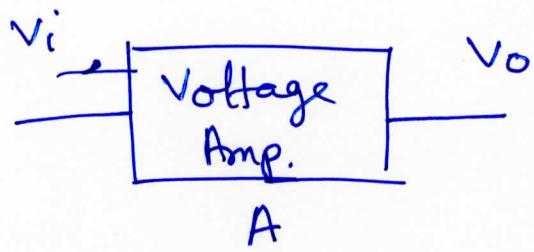

$$\frac{V_L}{V_s} = ?$$


$$V_i = \frac{R_i}{R_s + R_i} \times V_s$$

$$\Rightarrow V_L = \frac{R_L}{R_o + R_L} \times A V_i$$

$$\frac{V_L}{V_s} = \left(\frac{R_L}{R_o + R_L} \right) \times \left(\frac{R_i}{R_s + R_i} \right) \times A < A$$

$$\left\{ \begin{array}{l} R_i \gg R_s \\ R_o \ll R_L \end{array} \right.$$

1) Inverting Amplifier

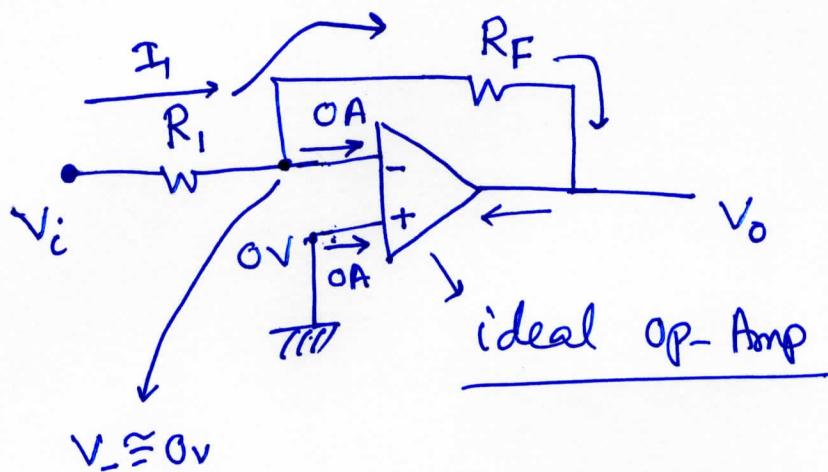

KCL


$$\frac{0 - V_i}{R_1} + \frac{0 - V_o}{R_F} = 0$$

$$\Rightarrow -\frac{V_i}{R_1} = \frac{V_o}{R_F}$$


$$\Rightarrow V_o = -\frac{R_F}{R_1} V_i$$

$$\Rightarrow \boxed{\frac{V_o}{V_i} = -\frac{R_F}{R_1}}$$

Ex

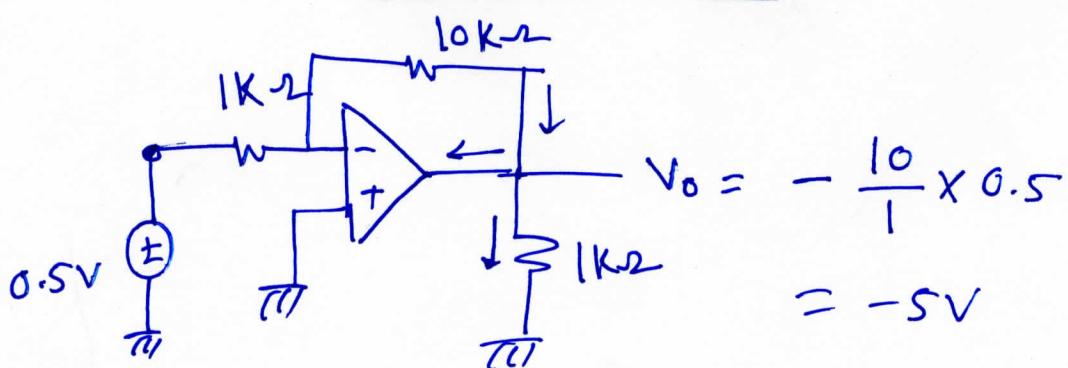

2) Non-inverting Amp.

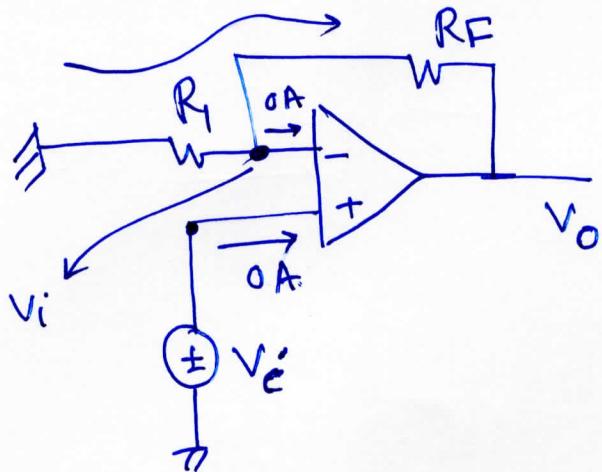

$$\underline{\underline{KCL}} \quad \frac{V_i - 0}{R_1} + \frac{V_i - V_o}{R_F} = 0$$

$$\Rightarrow \frac{V_i}{R_1} + \frac{V_i}{R_F} - \frac{V_o}{R_F} = 0$$

$$\Rightarrow \frac{V_o}{R_F} = V_i \left[\frac{1}{R_1} + \frac{1}{R_F} \right]$$



$$V_o = V_i \left[\frac{1}{R_1} + \frac{1}{R_F} \right] \times R_F$$

$$= \left(1 + \frac{R_F}{R_1} \right) V_i$$

$$\Rightarrow \boxed{\frac{V_o}{V_i} = 1 + \frac{R_F}{R_1}}$$

3> Summing Amplifiers or Adder

a) Inverting type:

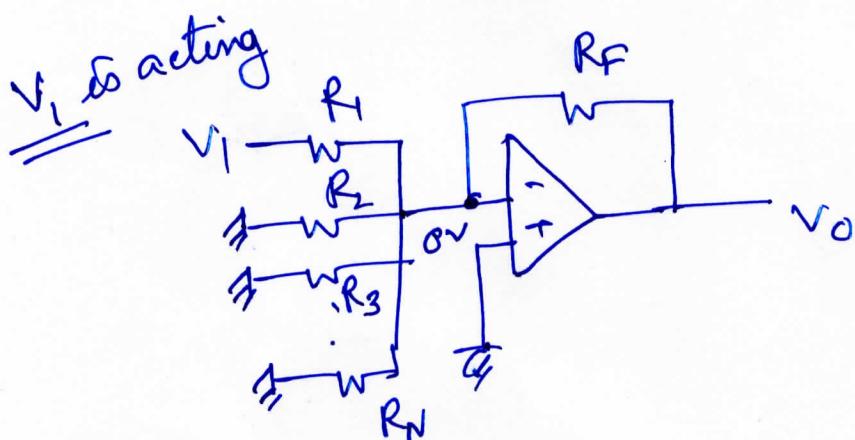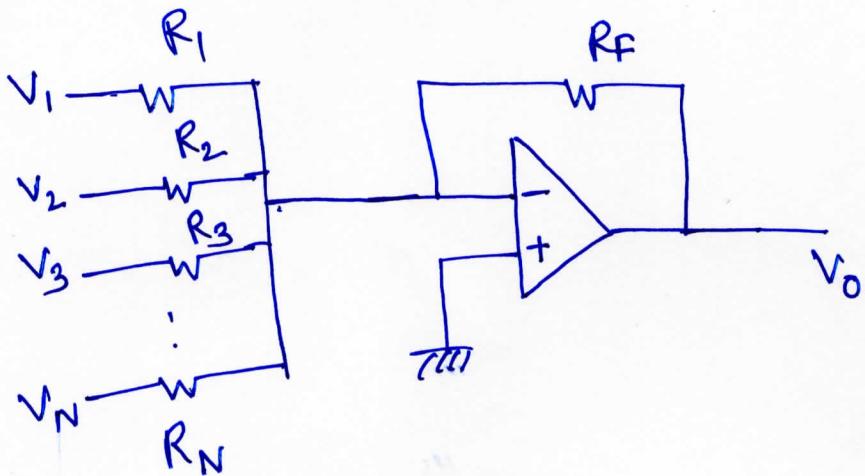

$$v_{o,1} = -\frac{R_F}{R_1} v_1$$

$$\vdots$$

$$v_{o,N} = -\frac{R_F}{R_N} v_N$$

$$v_o = -\frac{R_F}{R_1} v_1 - \frac{R_F}{R_2} v_2 - \frac{R_F}{R_3} v_3 - \dots - \frac{R_F}{R_N} v_N$$


$$= (-R_F) \times \sum_{i=1}^N \frac{v_i}{R_i}$$

When $R_1 = R_2 = R_3 = \dots = R_N = R$


$$\Rightarrow v_o = \left(-\frac{R_F}{R}\right) \times \sum_{i=1}^N v_i$$

(54)


b) Non-inverting type

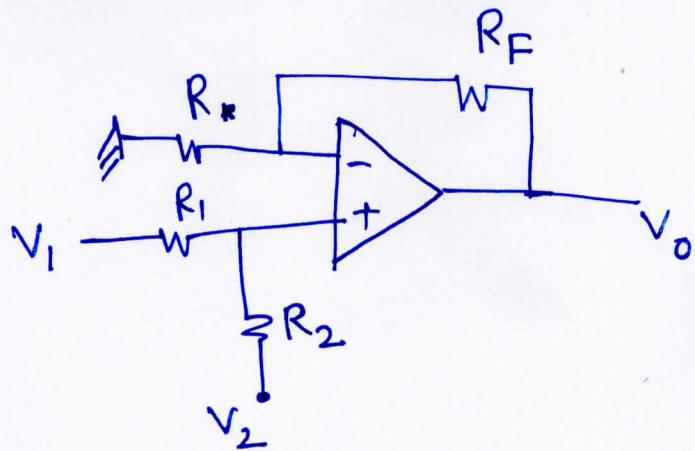

V_1 is acting

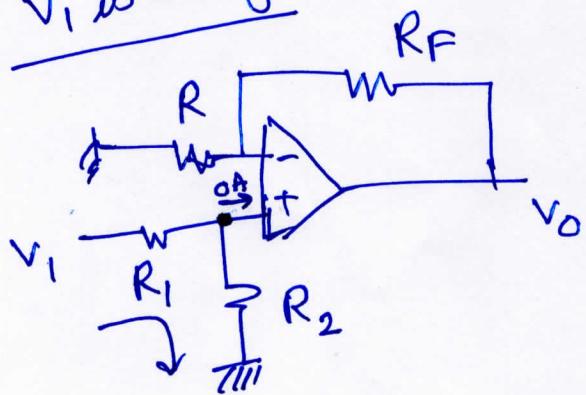


V_2 is acting

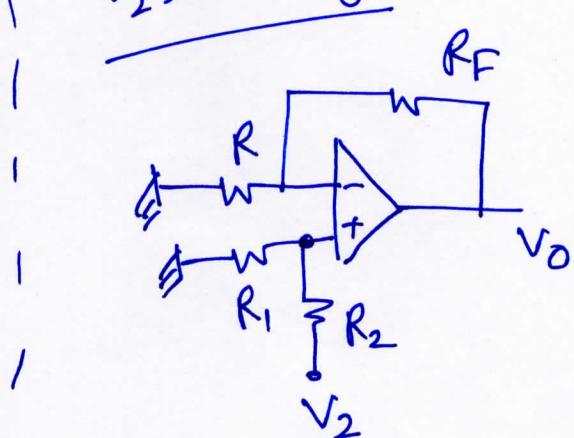


$$V_{o,1} = \left(1 + \frac{R_F}{R}\right) \times \left(\frac{R_2}{R_1 + R_2}\right) \times V_1$$
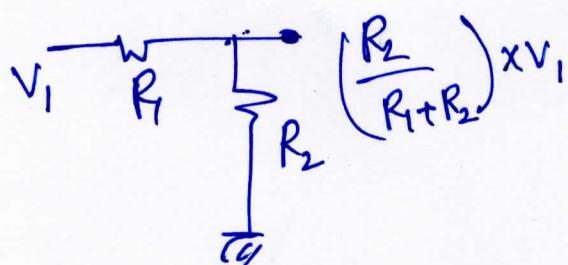
$$V_{o,2} = \left(1 + \frac{R_F}{R}\right) \times \left(\frac{R_1}{R_1 + R_2}\right) \times V_2$$



$$\Rightarrow V_o = \frac{\left(1 + \frac{R_F}{R}\right) \times \left[\underline{\underline{R_2 V_1 + R_1 V_2}}\right]}{(R_1 + R_2)}$$

4) Difference Amplifier

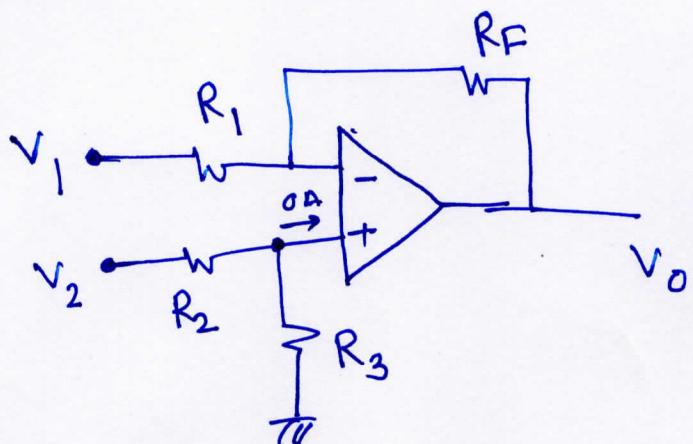

$$V_0 = K(V_2 - V_1)$$

$$V_0 = \left(-\frac{R_F}{R_1} \right) \times V_1 + \left(1 + \frac{R_F}{R_1} \right) \times \left(\frac{R_3}{R_2 + R_3} \right) \times V_2$$


$$= -\frac{R_F}{R_1} \times V_1 + \frac{\frac{R_F}{R_1} \times \left(1 + \frac{R_1}{R_F} \right)}{\left(1 + \frac{R_2}{R_3} \right)} \times V_2$$

when $\frac{R_1}{R_F} = \frac{R_2}{R_3}$

$$\Rightarrow V_0 = -\frac{R_F}{R_1} (V_1) + \frac{R_F}{R_1} \times V_2$$

$$V_0 = \frac{R_F}{R_1} (V_2 - V_1)$$


~~ex~~

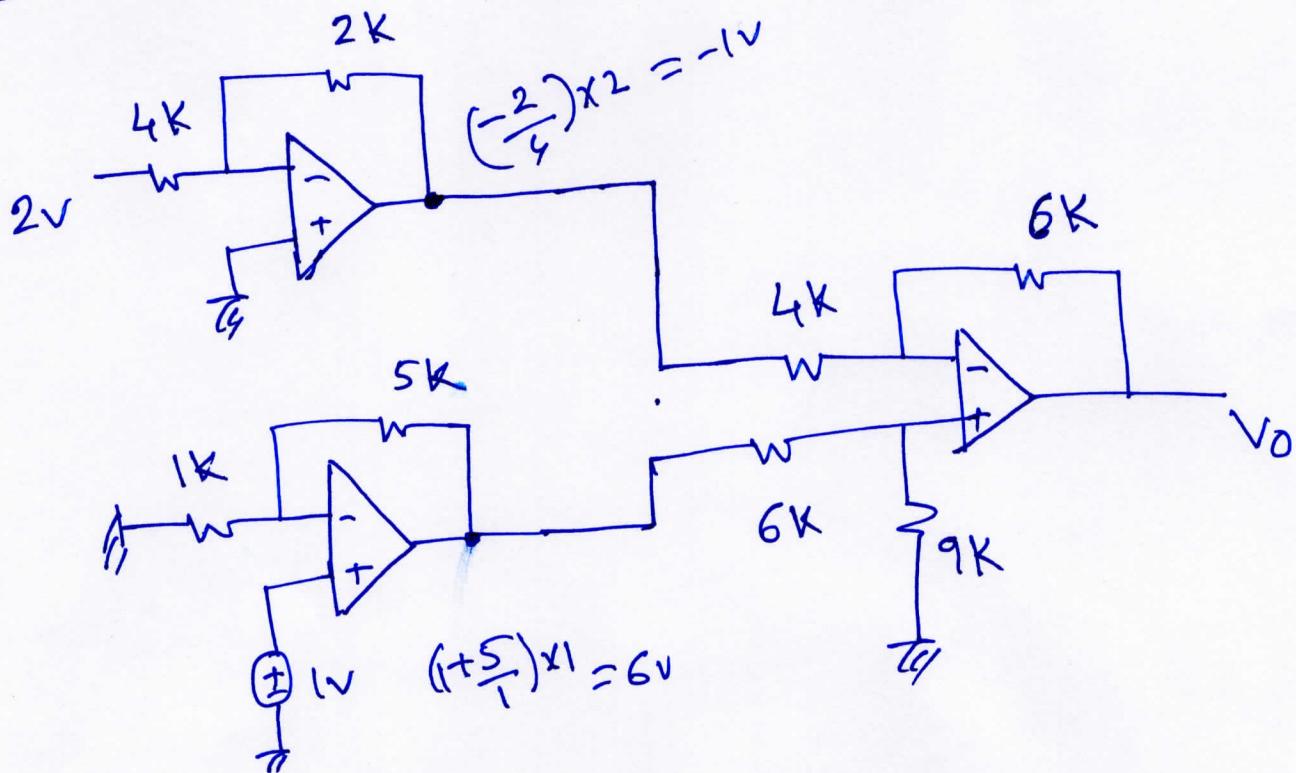


$$V_o = \frac{3}{1} \times (6 - (-1))$$

$$= \frac{21}{2} = \underline{\underline{10.5V}}$$

5) Voltage follower or Voltage Buffer :-

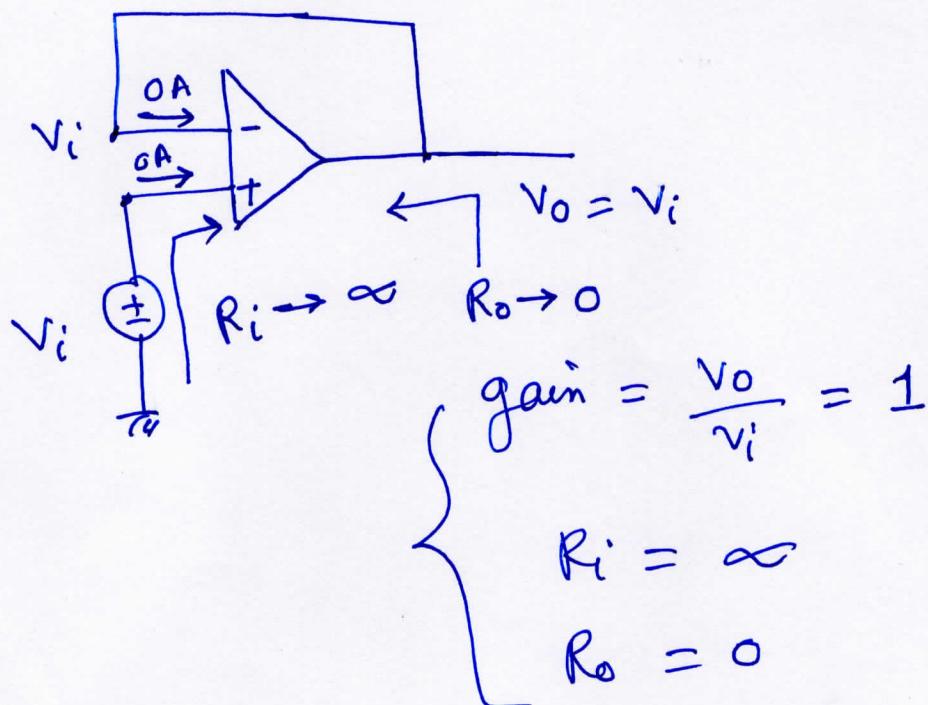


- It reduces loading effect

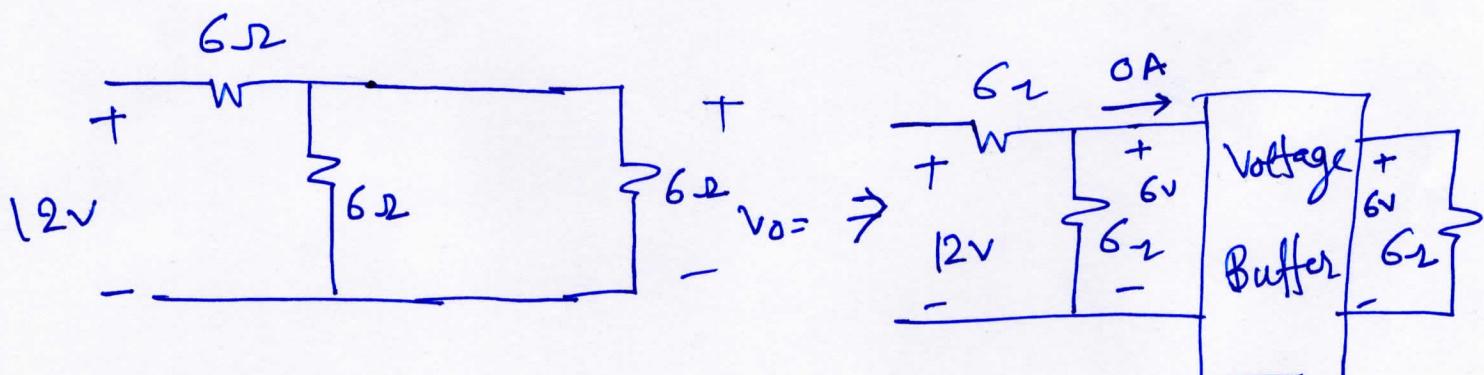

$$V_o = \frac{3}{6+3} \times 12 = 4V$$

Input impedance


A)

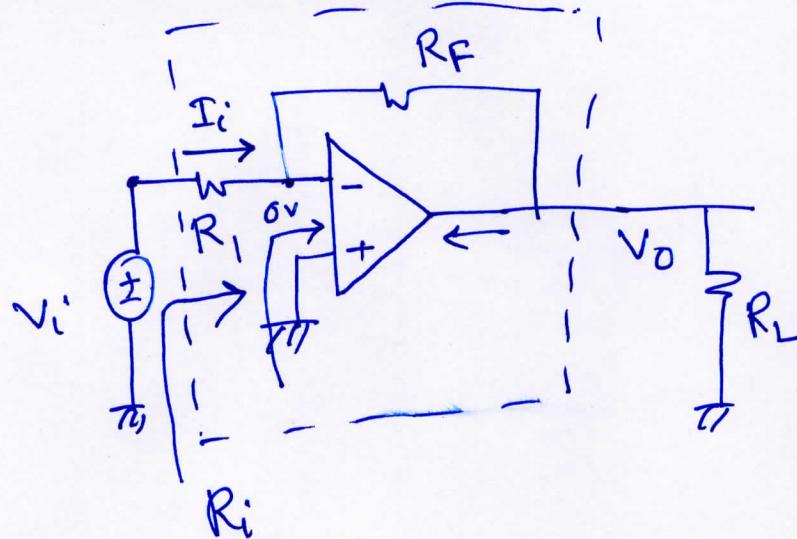

$$I_i = \frac{V_i - 0}{R_1} = \frac{V_i}{R_1}$$

$$\Rightarrow R_i = \frac{V_i}{I_i} = R_1$$

B)

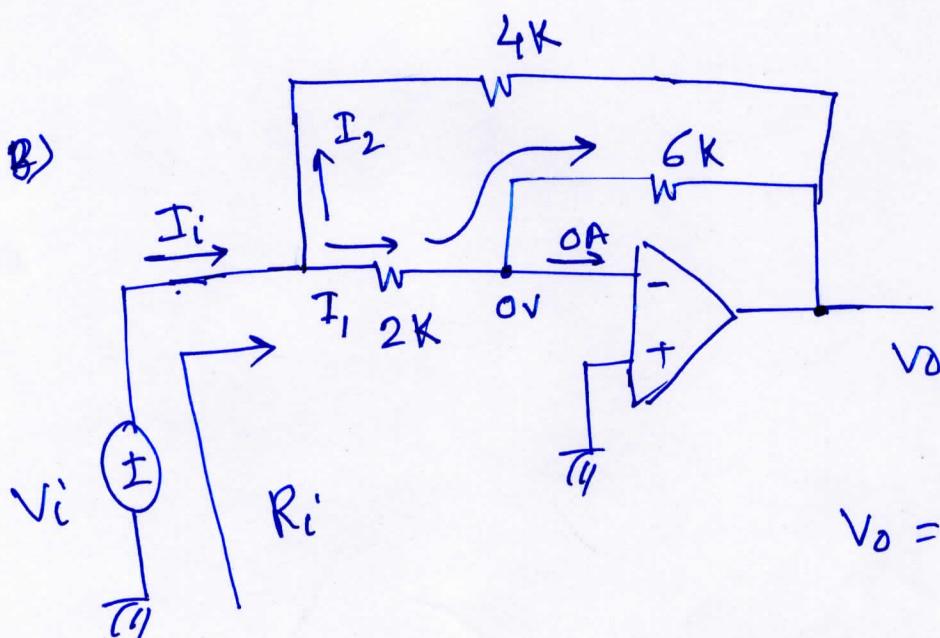

$$V_o = \left(-\frac{6}{2} \right) V_i = -3V_i$$

$$I_1 = \frac{V_i}{2 \times 10^3}$$

$$\Rightarrow I_2 = \frac{V_i - V_o}{4 \times 10^3} = \frac{V_i + 3V_i}{4 \times 10^3}$$


$$\Rightarrow I_i = I_1 + I_2 = \frac{(1.5) \times V_i}{10^3}$$

$$= \frac{V_i}{10^3}$$


$$\text{So, } R_i = \frac{V_i}{I_i} = 10^3 / 1.5 = \frac{2}{3} \text{ k}\Omega$$

(59)

⑤

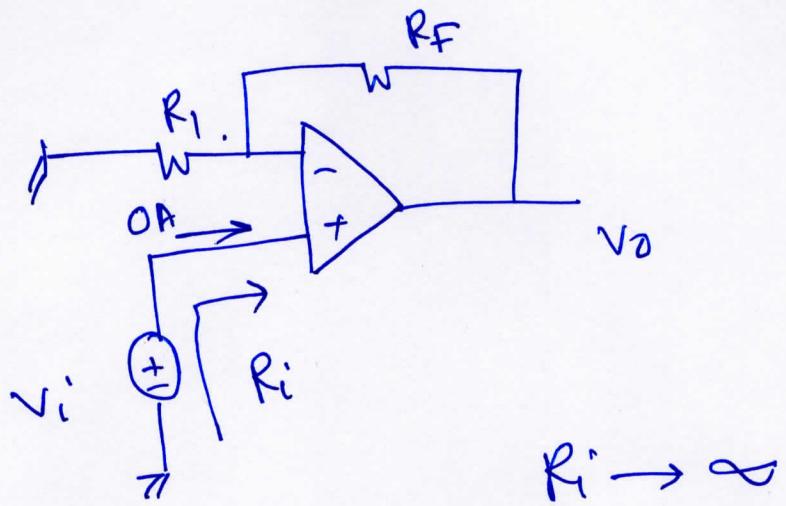

6) Instrumentation Amplifiers

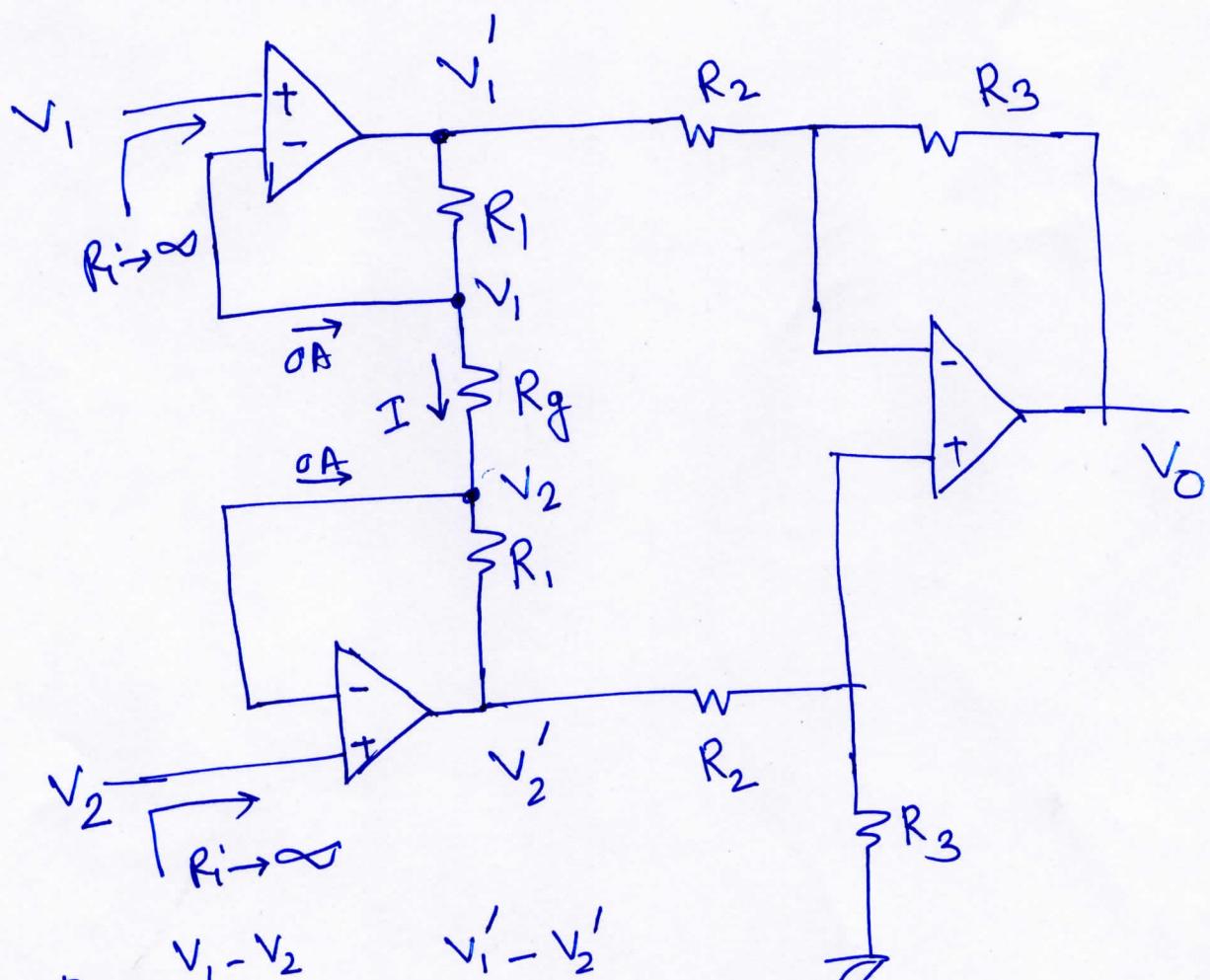

$$I = \frac{V_1 - V_2}{R_g} = \frac{V'_1 - V'_2}{2R_1 + R_g}$$

$$\Rightarrow V'_1 - V'_2 = \left(\frac{2R_1 + R_g}{R_g} \right) \times (V_1 - V_2)$$

(60)

Again

$$V_o = \frac{R_3}{R_2} (V'_2 - V'_1)$$

$$\boxed{V_o = \frac{R_3}{R_2} \times \left(1 + \frac{2R_1}{R_g}\right) (V_2 - V_1)}$$

(61)