

16 | 9 | 19



classmate

Date _____

Page _____



Periphery of region

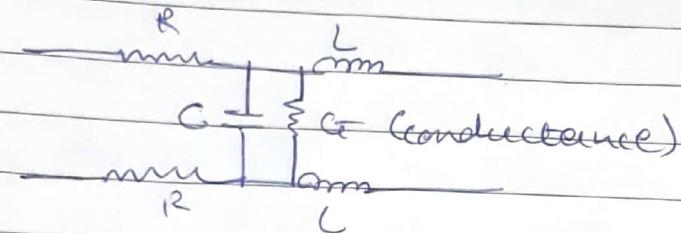
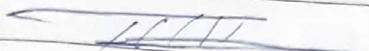



$R \rightarrow$ due to material by conductance.

$L \rightarrow$ required magnetic flux generated by current on T_x line.


$C \rightarrow$ Capacitance (due to 2 conductors separated by dielectric)

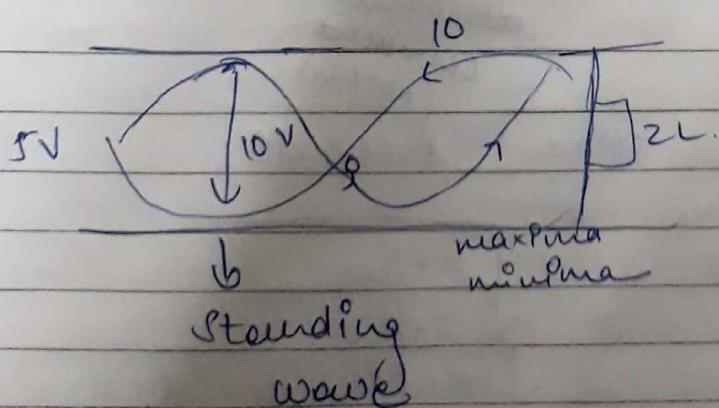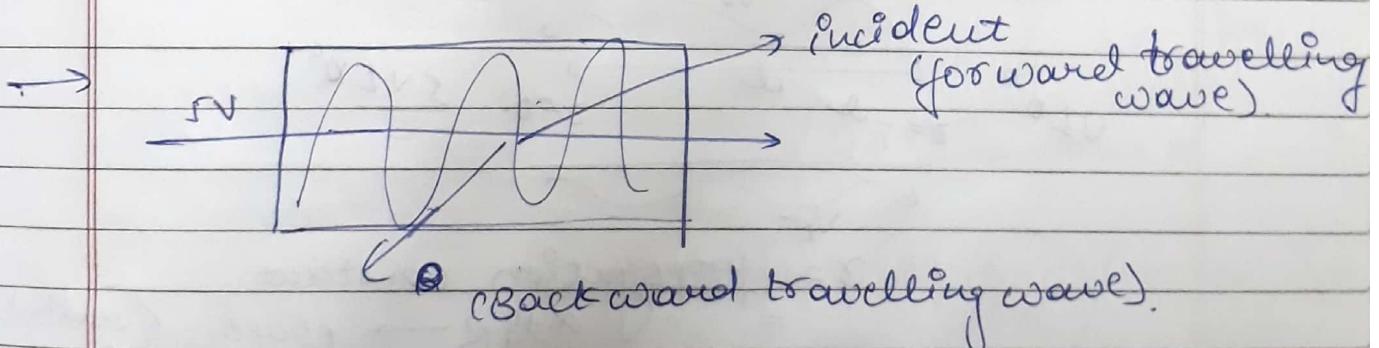$G \rightarrow$ Conductance because of coupling.
($\neq 1/R$) b/w 2 conductors.



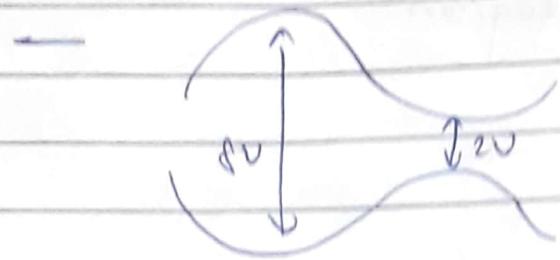


$V(z)$

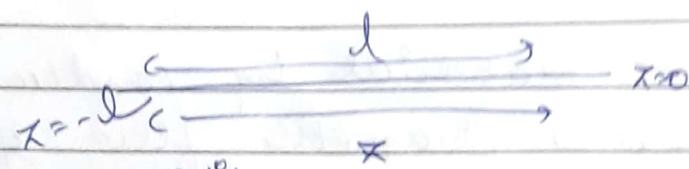

(characteristic impedance)
 $Z_0 = 50 \Omega$

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$
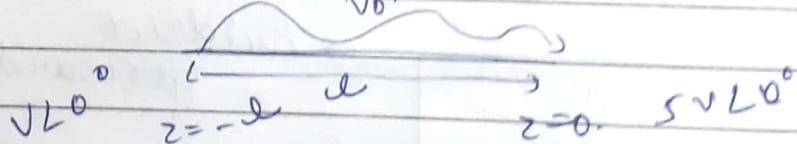
$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$



$\gamma = \text{propagation constant.}$

\downarrow
 $\alpha + j\beta \rightarrow \text{phase constant}$
 \downarrow
 $\text{attenuation constant.}$

(NP/m)

$$(\text{NP}) = 8.686 \text{ dB}$$

$$\rightarrow Z_0 = \frac{R_0 + jX_0}{\alpha + j\beta} =$$

$$\sqrt{R + j\omega L}$$

$$\gamma = \alpha + j\beta =$$

$$\sqrt{(R + j\omega L)(G + j\omega C)}$$

$$V_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

→ case-1

Lossless line (ideal) - $R=0, G=0$

$$\gamma = j\omega \sqrt{LC} = \alpha + j\beta$$

$\therefore \alpha=0, \beta = j\omega \sqrt{LC}$

$$Z_0 = \sqrt{\frac{L}{C}} = R_0 + jx_0$$

$$\therefore R_0 = \sqrt{\frac{L}{C}}, x_0 = 0$$

→ case-2

Low loss line. - $R \ll \omega L, G \ll \omega C$

$$\begin{aligned} \gamma &= \alpha + j\beta = \sqrt{(R+j\omega L)(G+j\omega C)} \\ &= j\omega \sqrt{LC} \left(\frac{i+R}{j\omega L} \right)^{1/2} \left(\frac{1+G}{j\omega C} \right)^{1/2} \\ &\quad \left\{ (1+x)^n = 1+nx+\dots \right\} \\ &= j\omega \sqrt{LC} \left(1 + \frac{R}{2j\omega L} \right) \left(1 + \frac{G}{2j\omega C} \right) + \dots \\ &= j\omega \sqrt{LC} \left[1 + \frac{1}{2} \left(\frac{R}{L} + \frac{G}{C} \right) \right] + \dots \\ &= \underbrace{j\omega \sqrt{LC}}_{\beta} + \underbrace{\frac{1}{2} \frac{R}{\sqrt{LC}}}_{\alpha} + \underbrace{\frac{1}{2} \frac{G}{\sqrt{LC}}}_{\alpha} \end{aligned}$$

$$Z_0 = R_0 + jx_0 = \frac{R + j\omega L}{G + j\omega C}$$

DH for ~~losses~~

~~losses~~ of electric field = losses ~~Rate~~ ~~date~~ ~~current~~
 $R_C = \alpha L$ $B = \frac{G}{C}$ magnetic f.

$$= \frac{R}{j\omega L} + j$$

$$\frac{G}{j\omega C} + j \frac{B}{j\omega L}$$

$$= \sqrt{\frac{L}{C}} \left(1 + \frac{R}{j\omega L} \right)^{1/2} \left(1 + \frac{G}{j\omega C} \right)^{1/2}$$

$$\approx \sqrt{\frac{L}{C}} \left(1 + \frac{1}{2j\omega} \cdot \left(\frac{B}{L} - \frac{G}{C} \right) \right)$$

$$\therefore R_0 = \sqrt{\frac{L}{C}}, X_0 = \sqrt{\frac{L}{C}} \cdot \frac{1}{2j\omega} \left(\frac{B}{L} - \frac{G}{C} \right) \approx 0$$

$$\gamma_p = \frac{\omega}{B} \approx \frac{1}{\sqrt{LC}}$$

$$\gamma = \alpha + j\beta = \sqrt{(R+j\omega L)(G+j\omega C)}$$

$$= \sqrt{(R+j\omega L)(\frac{R}{L} + j\omega C)}$$

$$= \sqrt{\frac{R^2 C}{L} - \omega^2 LC + j\omega RC + j\omega LC}$$

$$= \sqrt{\frac{R^2 C}{L} - \omega^2 LC + 2j\omega CR}$$

$$= \sqrt{\frac{C}{L} (R^2 - \omega^2 L^2 + 2j\omega RL)}$$

$$= \sqrt{\frac{C}{L} (R + j\omega L)^2}$$

$$= \sqrt{\frac{C}{L} (R + j\omega L)} = \gamma = \alpha + j\beta$$

$$\therefore \alpha = \frac{R}{\sqrt{L}} = \sqrt{RG} \quad (\because G = \frac{B}{L})$$

$$R_c = \omega \sqrt{Lc}$$


$$\Psi = \frac{\omega}{\beta} = \frac{1}{\sqrt{Lc}}$$

$$Z_0 = R_0 + jx_0 = \sqrt{\frac{(R+j\omega L)}{(G+j\omega C)}} \\ = \sqrt{\frac{R+j\omega L}{(R_C)^{-1} + j\omega C}}$$

$$R_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{R}{G}}$$

$$x_0 \approx 0.$$

~~19/9/19~~

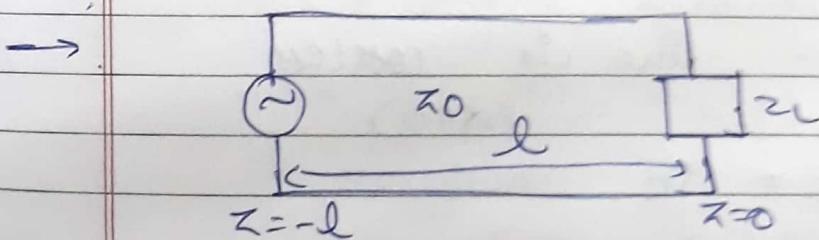

$$\gamma = \alpha + j\beta = \sqrt{(R+j\omega L)(G+j\omega C)}$$

propagation constant (m^{-1})
 attenuation constant (Np/m)

phase constant (rad/m)

$$Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} \quad \text{characteristic impedance}$$

(complex)

- KOMERS Line, ($\rho = 0, \alpha = 0$)
- RAYLEIGH Line, ($\rho = \alpha z, \alpha < 0$)
- DISTANCE LAW Line ($\rho = \text{const}$)

$$V_p = \frac{V_0}{\beta} \quad , \quad \beta = \frac{2\pi}{\lambda}$$

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

\downarrow
forward
(incident)
 \downarrow
backward
(reflected)

$$I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z}$$

$$= \frac{V_0^+}{Z_0} e^{-j\beta z} + \frac{V_0^-}{Z_0} e^{+j\beta z}$$

$$\left[\because Z_0 = \frac{V_0^+}{I_0^+} = \frac{-V_0^-}{I_0^-} \right]$$

→ Assumption:- Line is lossless ($\rho = 0$)

$$\gamma = \alpha + j\beta = j\beta$$

$$\left[\begin{array}{l} V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z} \\ I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z} \end{array} \right] \quad \textcircled{A}$$

→ Voltage reflection co-efficient ($r_{\text{or} c}$)
(load is at $z=0$)

$$(A) \quad V_L \text{ (Voltage at load)} = V(z=0) = V_0^+ + V_0^-$$

$$(B) \quad I_L \text{ (Current at load)} = I(z=0) = \frac{V_0^+ - V_0^-}{Z_0} = \frac{V_0^+ - V_0^-}{Z_0}$$

$$z_L = \frac{v_L}{I_L}$$

$$z_L = \frac{v_0^+ + v_0^-}{\frac{1}{2} [v_0^+ - v_0^-]}$$

$$\Rightarrow v_0^- = \left(\frac{z_L - z_0}{z_L + z_0} \right) v_0^+$$

$$\Rightarrow \frac{v_0^-}{v_0^+} = \frac{z_L - z_0}{z_L + z_0}$$

$$\Rightarrow r = \frac{v_0^-}{v_0^+} = \frac{z_L - z_0}{z_L + z_0} \quad (z_0 = 50 + j0)$$

complex quantity.

$$\boxed{\frac{I_0^-}{I_0^+} = -\frac{v_0^-}{v_0^+} = r}$$

r = complex quantity.

($\because z_L$ is complex).

$$= |r| e^{j\theta_r} = |r| \angle \theta_r$$

Magnitude

of reflection

co-efficient.

angle of

ref. co-efficient.

→ Matched Line - ($z_L = z_0$)

$$r = \frac{z_L - z_0}{z_L + z_0} = 0.$$

- short-circuited line. ($z_L = 0$)

$$r = \frac{z_L - z_0}{z_L + z_0} = -1 = 1 \angle 180^\circ$$

- open-circuited line : $Z_L = \infty$.

$$|\Gamma| = 1 \quad = 1 \angle 0^\circ.$$

→ TDR (Time Domain Reflectometer).
OTDR (Optical ").

$$-1 < |\Gamma| < 1$$

$$0 \leq |\Gamma| \leq 1$$

- VSWR (Voltage Standing Wave Ratio)

$$\text{VSWR} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

(Matched load)

$$Z_L = Z_0$$

$$S_C = \infty$$

$$O_C = \infty$$

$$1 \leq \text{VSWR} \leq \infty$$



→ Standing wave (lossless $\alpha=0 \Rightarrow \gamma=j\beta$)

$$(A) : V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$(B) : I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z}$$

$$\Rightarrow \begin{cases} V(z) = V_0^+ (e^{-j\beta z} + r e^{j\beta z}) \\ I(z) = I_0^+ (e^{-j\beta z} - r e^{j\beta z}) \end{cases}$$

$$\left[\because \frac{V_0^-}{V_0^+} = r \Rightarrow V_0^- = r V_0^+ \right]$$

$$|V(z)| = [v(z) - v^*(z)]^{1/2} \rightarrow \text{complex conjugate}$$

$$= \left[\left(V_0^+ \right) \left(e^{-j\beta z} + r e^{j\beta z} \right) \right]^{1/2} \left[\left(V_0^+ \right)^* \left(e^{j\beta z} + r e^{-j\beta z} \right) \right]^{1/2}$$



$$= \left[\left(V_0^+ \right) \left(e^{-j\beta z} + |r| e^{j\theta_r} e^{j\beta z} \right) \right]^{1/2} \left[\left(V_0^+ \right)^* \left(e^{j\beta z} + |r| e^{-j\theta_r} e^{-j\beta z} \right) \right]^{1/2}$$

$$\therefore r = |r| e^{j\theta_r}$$

$$= |V_0^+| \left[1 + |r|^2 + |r| e^{j(2\beta z + \theta_r)} + e^{-j(2\beta z + \theta_r)} \right]$$

$$|V(z)| = |V_0^+| \left[1 + |r|^2 + 2|r| \cos(2\beta z + \theta_r) \right]^{1/2}$$

$$\because e^x + e^{-jx} = 2 \cos x.$$

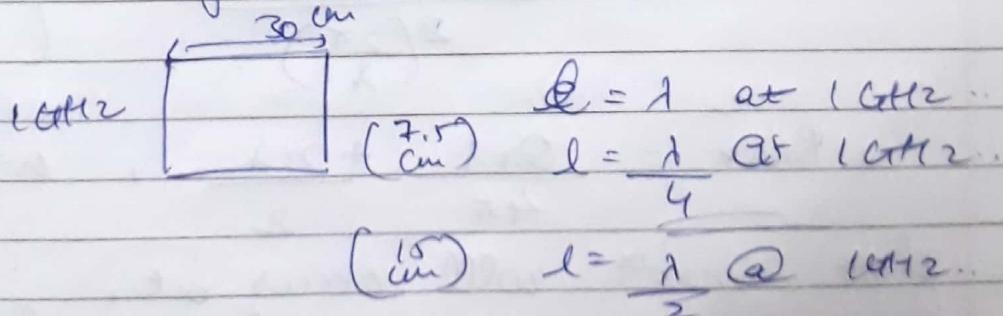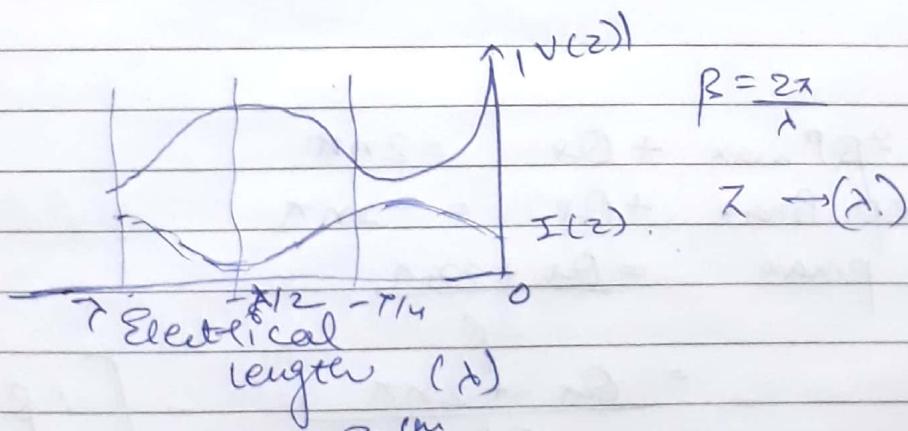

20/9/19

classmate

Date _____

Page _____

* Standing waves (condition):

$$\rightarrow |v(z)| = |v_0| \sqrt{[1 + [r]^2 + 2[1] \cos(\beta z + \phi_i)]}^{\frac{1}{2}}$$
$$\beta = \frac{2\pi}{\lambda}, \text{ or } \phi_i = \text{angle of reflection}$$

Co-efficient (β)

- Our objective:-

- ① To find positions of maxima & minima.
- ② To find amplitudes of maxima & minima.

→ Maxima :- The max^o value of standing wave pattern of $|v(z)|$ corresponds to positions on line at which incident +

$$\rightarrow 2\beta P_{max} + \phi_i = 2n\pi$$

$$\rightarrow -2\beta P_{max} + \phi_i = -2n\pi$$

$$\Rightarrow P_{max} = \underline{\phi_i + 2n\pi}$$

$$- \frac{\phi_i + 2n\pi}{2\left(\frac{2\pi}{\lambda}\right)}$$

$$\left[\because \beta = \frac{2\pi}{\lambda} \right]$$


$$P_{max} = \frac{\phi_i \lambda}{4\pi} + \frac{n\lambda}{2}, \quad n=0, 1, 2, \dots$$

first max will occur at,

$$\frac{\phi_i \lambda}{4\pi} \quad (\text{for } n=0)$$

$$2^{nd} \dots \dots \dots \frac{\phi_i \lambda}{4\pi} + \frac{\lambda}{2} \quad (\text{for } n=1)$$

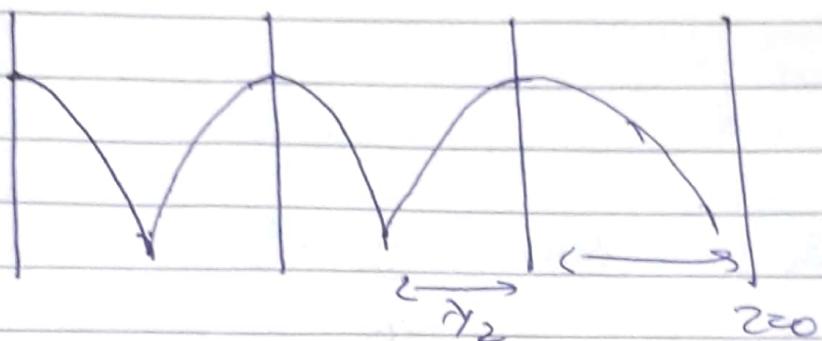grd $\frac{\alpha_2 z}{4\pi} + \lambda$ (for $n=2$)



Distance b/w 2 successive maxima = $\lambda/2$

→ M Pulma :-

$$(2\beta z + \alpha) = (2n+1)\pi, n = \\ \downarrow \\ p_{\min}$$

$$\lambda_{\min} = \frac{Q_{ext}}{4\pi} + (2n+1)\frac{\pi}{ka/\lambda}$$

= 9B

1st min =


$$\lambda_{\min 1} = \frac{Q_{ext}}{4\pi} + \frac{\pi}{ka/\lambda} \quad (n=0)$$


$$\lambda_{\min} = \frac{Q_{ext}}{4\pi} + \frac{\pi}{4} \quad (n=0)$$

$$\lambda_{\min 2} = \frac{Q_{ext}}{4\pi} + \frac{3\pi}{4} \quad (n=1)$$

Distance b/w 2 successive minima = $\lambda/2$

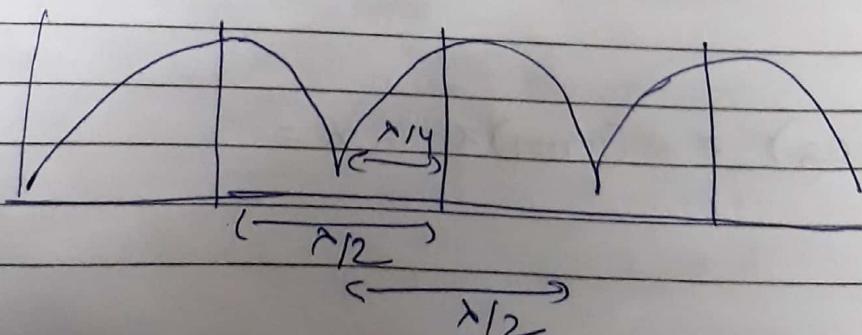
Distance min b/w max & subsequent
 $= \lambda/4$



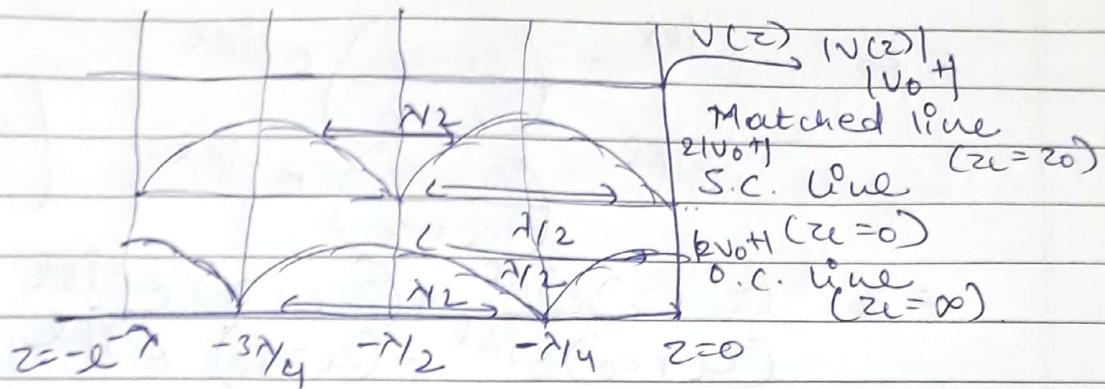

$$r = \frac{z_L - z_0}{z_L + z_0}$$

$\rightarrow z_{in}$

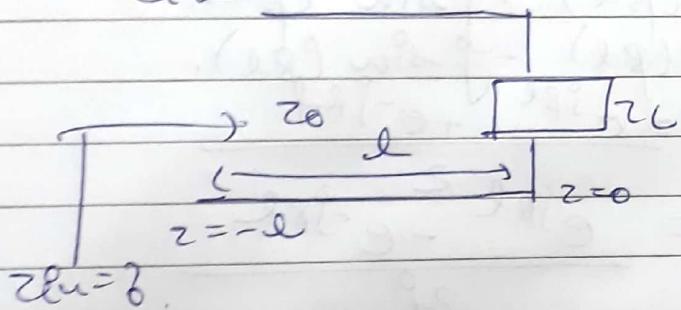

(A) $V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$
 (B) $I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z}$

$$z_{in} (z = -l) \text{ from load} = \frac{V(z = -l)}{I(z = -l)}$$

$$\begin{aligned} z_{in} &= z_0 \frac{V_0^+ e^{j\beta l} + V_0^- e^{-j\beta l}}{V_0^+ e^{j\beta l} - V_0^- e^{-j\beta l}} \\ &= z_0 \frac{V_0^+ (e^{j\beta l} + \frac{V_0^-}{V_0^+} e^{-j\beta l})}{V_0^+ (e^{j\beta l} - \frac{V_0^-}{V_0^+} e^{-j\beta l})} \end{aligned}$$

$$= z_0 \frac{e^{j\beta l} + r e^{-j\beta l}}{e^{j\beta l} - r e^{-j\beta l}} \quad \left[\frac{v_0^-}{v_0^+} = r \right]$$

$$= z_0 \cdot \frac{e^{j\beta l} + \left(\frac{z_L - z_0}{z_L + z_0} \right) e^{-j\beta l}}{e^{j\beta l} - \left(\frac{z_L - z_0}{z_L + z_0} \right) e^{-j\beta l}} \quad \left[\begin{array}{l} r = z_L - z_0 \\ z_L + z_0 \end{array} \right]$$

$$= z_0 \cdot \frac{(z_L + z_0)e^{j\beta l} + (z_L - z_0)e^{-j\beta l}}{(z_L + z_0)e^{j\beta l} - (z_L - z_0)e^{-j\beta l}}$$

$$= z_0 \cdot \frac{z_L(e^{j\beta l} + e^{-j\beta l}) + z_0(e^{j\beta l} - e^{-j\beta l})}{z_L(e^{j\beta l} - e^{-j\beta l}) + z_0(e^{j\beta l} + e^{-j\beta l})}$$

$$\left\{ \begin{array}{l} e^{j\beta l} = \cos(\beta l) + j \sin(\beta l) \\ e^{-j\beta l} = \cos(\beta l) - j \sin(\beta l) \\ \rightarrow \cos(\beta l) = \frac{e^{j\beta l} + e^{-j\beta l}}{2} \end{array} \right.$$

$$\therefore R_L(\beta l) = \frac{e^{j\beta l} - e^{-j\beta l}}{2j}$$

$$Z_{in} = z_0 \cdot \frac{z_L \cos(\beta l) + j z_0 \sin(\beta l)}{j z_L \sin(\beta l) + z_0 \cos(\beta l)}$$

$$Z_{in}(z_L - l) = z_0 \cdot \frac{z_L + j z_0 \tan(\beta l)}{z_0 + j z_L \tan(\beta l)}$$

$$\beta = \frac{2\pi}{\lambda}$$

$$\left\{ \begin{array}{l} \rho = \beta / m \\ L = m \lambda / m \end{array} \right.$$

distributed elements.
wired elements.

If line is lossy. ($\alpha \neq 0, \gamma = \alpha + j\beta$)

$$\frac{Z_{in}}{(j\omega)} = \frac{Z_0 - Z_L + jZ_0 \tan h(\gamma l)}{Z_0 + Z_L + \tan h(\gamma l)}$$

$$\tan h(\gamma l) = \tan h(j\beta l) = j \text{ temp } \downarrow \text{for lossless } (\sigma = j\beta)$$

23/9/19

classmate

Date _____


Page _____



$$f = \frac{z_L - z_0}{z_L + z_0}$$

$$Z_{in} = z_0 \cdot \frac{z_L + j z_0 \tan(\beta l)}{z_0 + j z_L \tan(\beta l)}$$

(lossless)

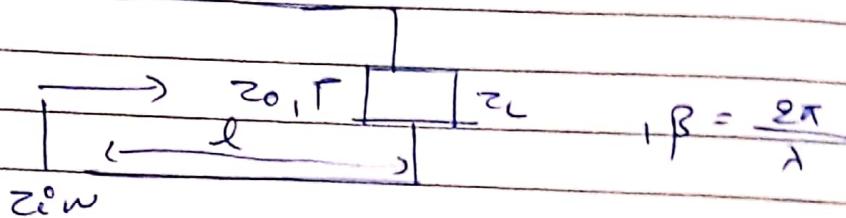

Case-5 lossless short-circuited line:-

$Z_L = 0$ (short-circuited).

(b) (i)

$$Z_{in}^{sc} = z_0 \cdot \frac{j z_0 \tan \beta l}{z_0}$$

$$Z_{in}^{sc} = j z_0 \tan \beta l$$

purely reactive.
(loss).



At $l=0$, $Z_{in}^{sc}=0$ ($\because \tan 0=0$).

$$l = \frac{\lambda}{4} \rightarrow \beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4}$$

$$\tan(\beta l) = \tan\left(\frac{\pi}{2}\right) = \infty$$

$$l = \frac{\lambda}{2} \rightarrow \beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} = \pi.$$

Der Rgn -



meander.




mm mm mm

classmate

Date _____

Page _____



$$\tan(\beta \cdot l) = \tan \pi = 0.$$

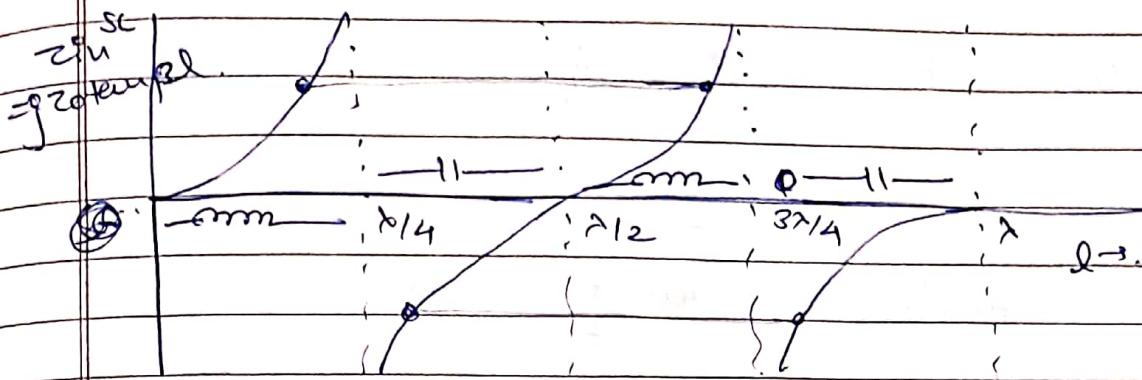

→ Case-2 - lossless O.C. line.
($z_0 = \infty$)

$$(b) : z_{in}^{OC} = -\frac{jz_0}{\tan \beta l} = -jz_0 \cot \beta l.$$

lossy case

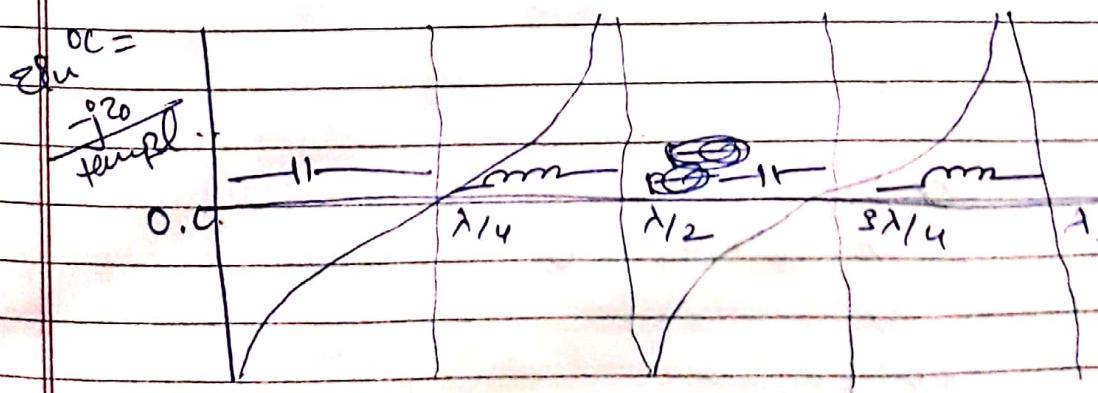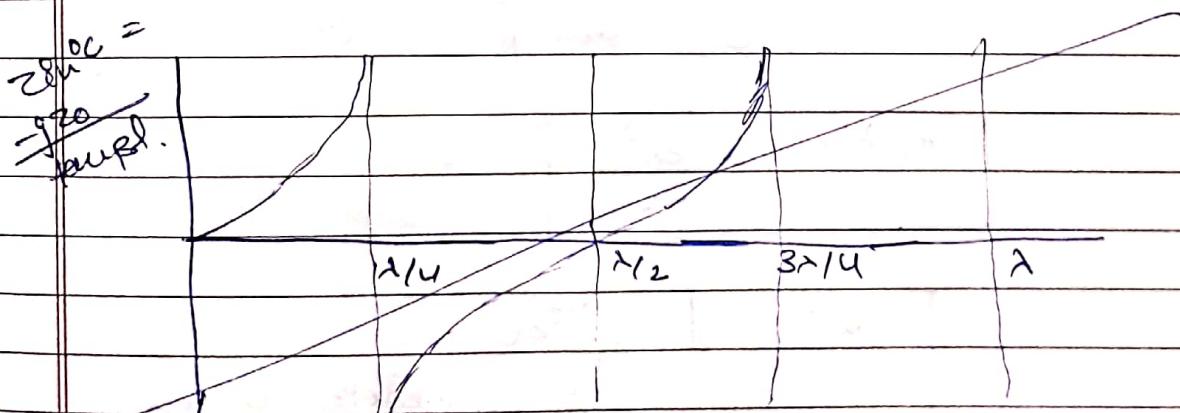

Case - 3 - $l = \frac{\lambda}{4}$

$$\textcircled{D} : \beta l = 2\pi \cdot \frac{1}{4}$$

$$= \frac{\pi}{2}$$

$$\tan(\beta l) = \tan \frac{\pi}{2} = \infty$$

$$\textcircled{D} : Z_{in}^{1/4} = Z_0 \left[\frac{Z_L + j Z_0}{Z_0 + j Z_L} \right]$$


$$Z_{in}^{1/4} = Z_0 \left[\frac{j Z_0}{j Z_L} \right]$$

$$\left[\because \frac{1}{\tan \beta} \rightarrow 0 \right]$$

$$\boxed{Z_{in}^{1/4} = \frac{Z_0^2}{Z_L}}$$

$$Z_0 = \sqrt{Z_{in} Z_L}$$

geometric mean.

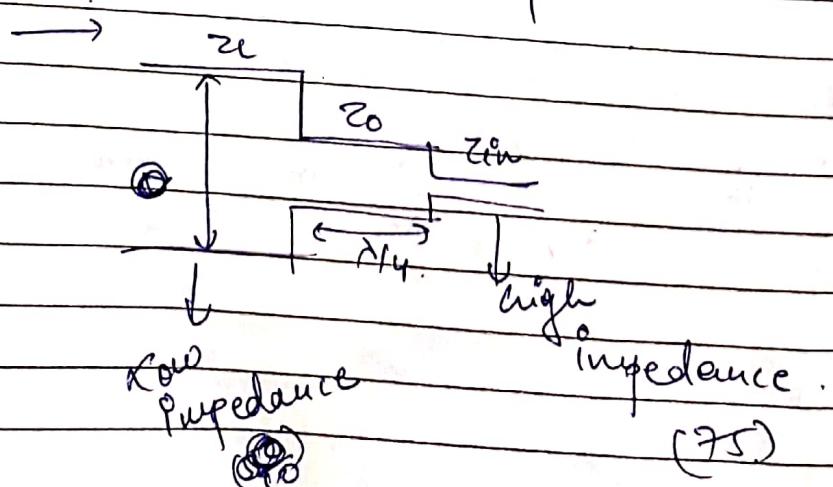

(75)

$$\begin{aligned}
 r &= \frac{z_u - z_o}{z_u + z_o} \\
 &= \frac{75 - 50}{75 + 50} \\
 &= \frac{25}{125} \\
 &= 20\%
 \end{aligned}$$

$$\begin{aligned}
 z_0 &= \sqrt{z_u z_o} \\
 &= \sqrt{50 \times 75} \\
 &= 65.52
 \end{aligned}$$

— Impedance Transformer,
 (Quarter Wave Transformer), ($\lambda/4$).
 (Impedance inverter).
 $OC \rightarrow SC$
 Induction \rightarrow capacitive.

$$\rightarrow \text{Circ-4} - l = \frac{\lambda}{2}$$

$$\beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{2}$$

$$\tan(\beta l) = \tan \alpha = 0$$

$$(b): z_u^{\lambda/2} = z_0, \frac{z_u + 0}{z_0 + 0}$$

$$\frac{z_u^{\lambda/2}}{z_0 + 0} = \frac{z_u}{z_0}$$

Half wave transformer.

30/9/19

$$\rightarrow Z_{in}^{cc} = jZ_0 \tan \beta l$$

$$Z_{in}^{cc} = \frac{jZ_0 \tan \beta l}{\tan(\beta l)}$$

$$\frac{1}{4} : Z_0 = \sqrt{Z_{in}^{cc}}$$

$$\lambda/2 : Z_0 = \sqrt{Z_{in}^{cc}}$$

* Equivalent Reactive Elements (L1)

→

$$Z_0 \quad | \quad \text{c.c.}$$

Equivalent L

$$\text{Equivalent } Z_{in}^{cc} = jZ_0 \tan \beta l$$

$$\Rightarrow jX_{in}^{cc} = jZ_0 \tan \beta l$$

$$\Rightarrow j\omega_{eq} = jZ_0 \tan \beta l$$

$$\Rightarrow \omega_{eq} = \frac{Z_0 \tan \beta l}{j} \text{ rad/s}$$

$$Z = R + jX_L$$

$$X = j\omega_{eq}$$

$$0 \leq \beta l \leq \pi/4$$

$$\frac{\lambda}{2} \leq \beta l \leq 3\pi/4$$

$$\omega = 2\pi f, \beta = \frac{2\pi}{\lambda}$$

$$l = \frac{1}{\beta} \tan^{-1} \left(\frac{\omega_{eq}}{Z_0} \right) \text{ m.}$$

Equivalent C

$$Z_{in}^{cc} = jZ_0 \tan \beta l$$


$$\Rightarrow jX_{in}^{cc} = jZ_0 \tan \beta l$$

$$\Rightarrow -j\frac{1}{\omega_{eq}} = jZ_0 \tan \beta l = \frac{1}{j\omega_{eq}}$$

$$\downarrow \frac{\pi}{4} \leq \beta l \leq \pi/2, \frac{3\pi}{4} \leq l \leq \pi,$$

$$d = \frac{-1}{\beta} \text{ cm}^{-1} ()$$

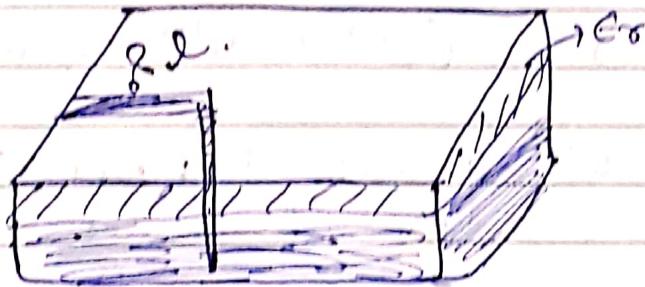eg $C_{eq} = 41 \mu F$ @ 2.25 GHz.
 using a short-circuited Tx line
 wave velocity = $\frac{c}{\sqrt{\epsilon_r}} = 0.75 c$.
 (or phase velocity)



$$Z_{in}^{(0)} = j Z_0 + \text{impedance} = \frac{-j}{c \omega C_{eq}} = j Z_0 \text{ termal.}$$

$$\Rightarrow \frac{1}{j c \omega C_{eq}} = \text{impedance}$$

$$\Rightarrow \text{impedance} = \frac{-1}{Z_0 c \omega C_{eq}}$$

$$\omega = 2\pi f.$$

$$f = 2.25 \times 10^9$$

$$\text{Imp} = 0.75 c = 0.75 \times 3 \times 10^8 = 2.25 \times 10^9 \text{ m/s.}$$

$$\lambda = \frac{v_p}{f}$$

$$\beta = \frac{2\pi}{\lambda} = \frac{2\pi f}{v_p} = \frac{2\pi \times 2.25 \times 10^9}{2.25 \times 10^8} = 20 \pi$$

$$\beta = 62.8 \text{ radian.}$$

$$\tan\beta_l = \frac{-1}{z_0(\omega) c_{eq}}$$

$$\tan\beta_l = 1$$

$$50 \times 2\pi \times 2.25 \times 10^9 \times 4 \times 10^{-12}$$

$$\underbrace{\omega = 2\pi f}_{C=}$$

$$\tan\beta_l = -0.03054$$

$\tan(-ve)$ (2nd & 4th quadrant)

Solⁿ in 2nd quadrant : $\beta l_1 = 2.8$ rad.

or, $l_1 = \frac{2.8}{2\pi} = \frac{2.8}{6.28} = 0.45$ cm

Solⁿ in 4th quadrant : $\beta l_2 = 5.94$ rad.

$$\Rightarrow l_2 = \frac{5.94}{6.28} = 0.946$$
 cm

$$l_2 > l_1 = 5\text{cm} \quad (=\lambda/2)$$

$$l = 10\text{cm..}$$

$$l = 4.46\text{cm} + \frac{n\lambda}{2}$$

$$n=0, 1, 2, \dots$$

* Analysis of E.C. and o.c. mean:

$$\rightarrow Z_{in}^{sc} = j z_0 + \tan\beta_l \quad \text{--- (1)}$$

$$Z_{in}^{oc} = j z_0 \cot\beta_l = \frac{-j z_0}{\tan\beta_l} \quad \text{--- (2)}$$

$$\textcircled{1} + \textcircled{2} \rightarrow Z_0 = \sqrt{Z_{in}^{sc} Z_{in}^{oc}}$$

$$\frac{\textcircled{1}}{\textcircled{2}} \Rightarrow \tan\phi_l = \sqrt{\frac{-Z_{in}^{sc}}{Z_{in}^{oc}}}$$

$$\beta = \frac{2\pi}{\lambda}$$

~~$$Z_{in}^{sc} = 940.42 \Omega$$~~

~~$$Z_{in}^{oc} = -j121.1024 \Omega$$~~

~~$$Z_0 = ?$$~~

$$\rightarrow Z_0 = \sqrt{Z_{in}^{sc} Z_{in}^{oc}}$$

$$= \sqrt{(940.42) (-j121.1024)}$$

$$= 70 \Omega$$

$$\tan\phi_l = \sqrt{\frac{-Z_{in}^{sc}}{Z_{in}^{oc}}} = \sqrt{\frac{1}{3}}$$

$$\beta = \frac{2\pi}{\lambda}$$

$\Rightarrow |r| = ?$ for a purely reactive load.
(inductive).

$$X_L = j X_L$$

$$r = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{j X_L - Z_0}{j X_L + Z_0}$$

$$= \frac{-(Z_0 - j X_L)}{Z_0 + j X_L}$$

$$T = \frac{\sqrt{Z_0^2 + X_L^2}}{\sqrt{Z_0^2 + X_L^2}} e^{-j\theta} \\ = -e^{-j20^\circ}$$

$$\theta = \tan^{-1} \frac{X_L}{Z_0}$$

$$|T| = |1 - e^{j20^\circ}|$$

$$= [(ce^{-j20}) (e^{-j20})^*]^{1/2}$$

$$\boxed{|T| = 1}$$

~~Eq~~

A $100\ \Omega$ Tr line is connected (terminated)

to a load consisting of $50\ \Omega$ resistor in series with 10 pF capacitor. Find Γ for 100 MHz freq.

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$Z_0 = 100\ \Omega$$

$Z_L = 50\ \Omega$ in parallel with 10 pF

$$= 50 \cdot \frac{1}{2\pi \times 10^{-11} \times 10^{-11}} \\ = 10 - j119\ \Omega$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = -0.76 e^{j119.3^\circ}$$

$\left(\begin{array}{c} R + jX \\ R Z_0 \\ e^{\theta} \end{array} \right)$

$$r = 0.76 e^{j119.3} e^{-j180^\circ}$$

$$= 0.76 e^{-j60.7}$$

$$= 0.76 \angle -60.7^\circ$$

$$|r| = 0.76$$

* powerflow \circ in a π line \therefore (lossless)

$$\rightarrow A \quad V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$B \quad I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z}$$

forward wave backward wave.

At load. $(z=0)$, incident and reflected voltages & currents.

$$V^{in} = V_0^+$$

$$V^{ref} = V_0^-$$

Θ

→ Definition of Time average power -

$$P_{av} = \frac{1}{2} \operatorname{Re} [V \cdot I^*] \xrightarrow{\text{complex conjugate}}$$


Incident

$$P_{av} = \frac{1}{2} \operatorname{Re} \left[V_0^+ \cdot \frac{V_0^+ *}{Z_0} \right]$$

7/10/19

→ x^{px}

$\pi-y$ plot.
 r plot.

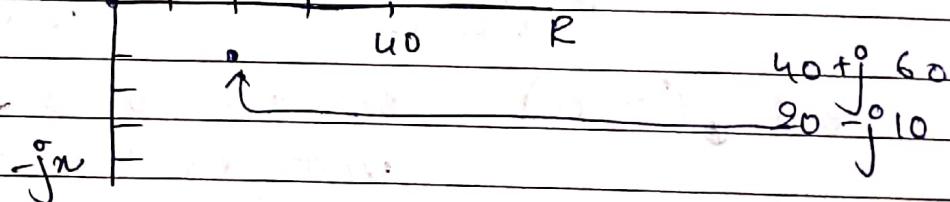

$$r = \frac{z_l - z_0}{z_l + z_0}$$

$$\begin{aligned} r_u + j r_i &= \frac{z_l - z_0}{z_l + z_0} \\ &= \frac{(z_l - z_0) / z_0}{(z_l + z_0) z_0} \end{aligned}$$

$$r_u + j r_i = \frac{g - 1}{g + 1}$$

$$r_u + j r_i = \frac{x + j n - 1}{x + j n + 1}$$

($\because z = R + j n$)

($\because j = \gamma \omega$)

$\gamma = \frac{2}{z_0}$

$\alpha = R / R_0$

$$z = z_0 \frac{1+\alpha}{1-\alpha} \rightarrow$$

$$z_0 = \frac{1+\alpha}{1-\alpha}$$

$$\alpha + j\beta = \frac{1+\alpha}{1-\alpha}$$

$$\alpha + j\beta = \frac{(1+\alpha) + j\beta}{(1-\alpha) - j\beta}$$

$$\alpha + j\beta = \frac{(1+\alpha) + j\beta}{(1-\alpha) - j\beta}, \quad \frac{(1-\alpha) + j\beta}{(1-\alpha) - j\beta}$$

$$= \frac{(1-\alpha^2 - \beta^2) + j(\alpha + \beta)}{1 + \alpha^2 - 2\alpha\beta + \beta^2}$$

$$\alpha + j\beta = \frac{(1-\alpha^2 - \beta^2) + 2j\beta}{1 + \alpha^2 - 2\alpha\beta + \beta^2}$$

$\rightarrow r(\text{real})$

$$r = \frac{1 - \alpha^2 - \beta^2}{1 + \alpha^2 - 2\alpha\beta + \beta^2}$$

$$\Rightarrow r + \sqrt{\alpha^2 - 2\alpha\beta + \beta^2} = \frac{1 - \alpha^2 - \beta^2}{1 - \alpha^2 - \beta^2}$$

$$\Rightarrow \alpha^2 + \beta^2 - 2\alpha\beta + \beta^2 = \frac{1 - \alpha^2 - \beta^2}{1 - \alpha^2}$$

$$\Rightarrow (1+\alpha)(\alpha^2 - 2\alpha\beta + \beta^2) = (1-\alpha)\beta^2 = 1 - \alpha$$

$$\Rightarrow \frac{\alpha^2 - 2\alpha\beta + \beta^2}{\alpha+1} = \frac{1 - \alpha}{1 + \alpha}$$

Add

$$\Rightarrow \frac{(\alpha^2 - 2\alpha)}{\alpha+1} + \frac{\alpha^2}{(\alpha+1)^2} + r_1^2 - \frac{\alpha^2}{(\alpha+1)^2} = \frac{1-\alpha}{1+\alpha}$$

$$\Rightarrow \left(\frac{\alpha - \alpha}{\alpha+1} \right)^2 + r_1^2 = \frac{1-\alpha}{1+\alpha} + \frac{\alpha^2}{(1+\alpha)^2}$$

$$\Rightarrow \left(\frac{\alpha - \alpha}{\alpha+1} \right)^2 + r_1^2 = \frac{1}{(1+\alpha)^2} - \alpha^2 + \alpha^2 \quad \text{--- } \textcircled{1}$$


Eqn of circle.

$$(x-a)^2 + (y-b)^2 = r^2$$

Centre (a, b) & radius r

$$\therefore (a, b) = \left(\frac{\alpha}{\alpha+1}, 0 \right)$$

$$\alpha = \frac{1}{1+\alpha}$$

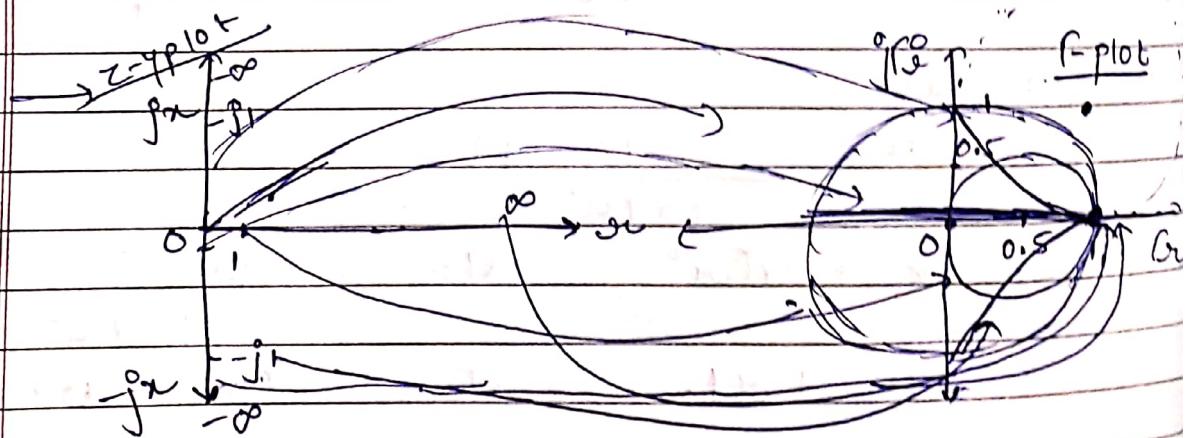for $\alpha=0$

$$\textcircled{1} \quad (r - 0)^2 + r_1^2 = 1$$

\rightarrow center $(0, 0)$, $\alpha=1$

$$\textcircled{2} \quad (r - 1/2)^2 + r_1^2 = (1/2)^2 \rightarrow \text{center } (0.5, 0), \alpha=0.5$$

for $x = \infty$

$$\textcircled{A} \left(\frac{re}{r+1}, 0 \right) \rightarrow (1, 0)$$

$$\text{radius } \frac{1}{(r+1)} \rightarrow 0$$

\Rightarrow x (Puag iway)

$$x = 2r^{\circ}$$

$$(1 + r^{\circ 2} - 2r^{\circ} + r^{\circ 2})$$

$$\Rightarrow x + xr^{\circ 2} - 2r^{\circ} + r^{\circ 2} = 2r^{\circ}$$

$$\Rightarrow 1 + r^{\circ 2} - 2r^{\circ} - r^{\circ 2} = 2r^{\circ}/x$$

$$\Rightarrow r^{\circ 2} - 2r^{\circ} - 1 + r^{\circ 2} - \frac{2r^{\circ}}{x} = 0.$$

$$\Rightarrow r^{\circ 2} - 2r^{\circ} + 1 + r^{\circ 2} - \frac{2r^{\circ}}{x} + \frac{1}{x^2} - \frac{1}{x^2} \geq 0.$$

Add Subtract.

$$\Rightarrow (r^{\circ} - 1)^2 + \left(\frac{r^{\circ} - 1}{x} \right)^2 = \frac{1}{x^2} \quad \text{LR}$$

Eq of circle:

$$(9_{16}) = \left(1 + \frac{1}{x} \right)$$

$$x = \frac{1}{n}$$

for $x = \infty$

$$\textcircled{B} \text{ center } (9_{16}) = \left(1 + \frac{1}{n} \right), \text{ radius } x = \frac{1}{n} 20.$$

for $x = 1$

(B) center $(a_1, b) = (1, 1)$, radius, $\delta = 1$

for $x = -1$

(B) $C = (1, -1)$, $\delta = 1$

for $x = 0$

$C = (1, \infty)$

$\delta = \infty$.

$\Rightarrow Z_L \rightarrow \text{complex}$

$$r = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$VSWR = \frac{1+r}{1-r} = (1, \infty)$$


10 | 10 | 9

$\rightarrow \text{Return Loss (dB)} = -20 \log (r)$

\downarrow
Voltage reg. constant.

$$\frac{Z_L - Z_0}{Z_L + Z_0}$$

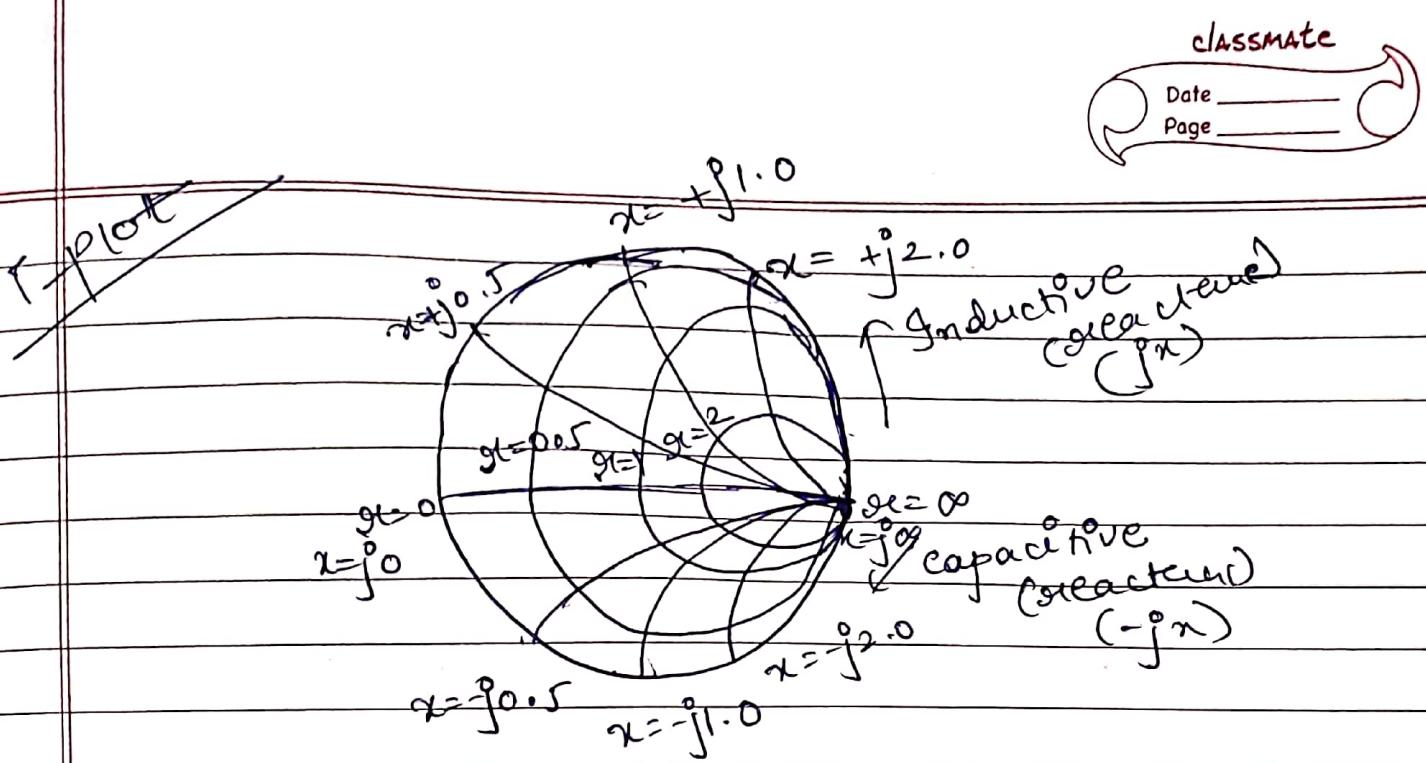$\rightarrow Z - \gamma \text{ Smith Chart.}$



$$Z = R + jx$$

$$\rightarrow f = \frac{z_1 - z_0}{z_1 + z_0}$$

$$z_t = z_0 \frac{(1+r)}{(1-r)}$$

$$\frac{Z_L}{Z_0} = \frac{1+r}{1-r}, \quad Z_L = \frac{1+r}{1-r}, \quad r = 1 - \frac{Z_L}{1+r}$$

$$[-r = (c) \exp(j\theta)]$$

It can now be

* Antenna :-

→ Radiation Eq. :-

$$\ddot{q}_i = \frac{d\dot{q}_i}{dt} \rightarrow \text{acceleration of charge.}$$

\downarrow \downarrow


Coulomb (m/s^2)

length of antenna
(m)


time changing current
(Afs)

- Time - changing current radiation
- accelerated charge radiation.

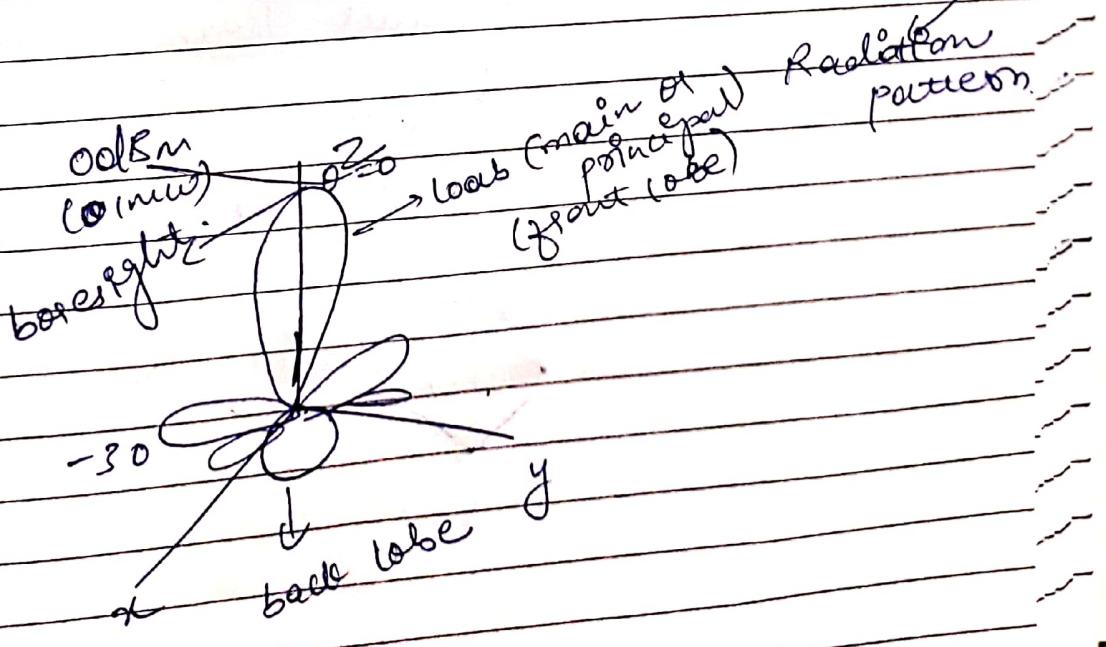- ① Antenna should be able to search. → detect track
- ②
- ③



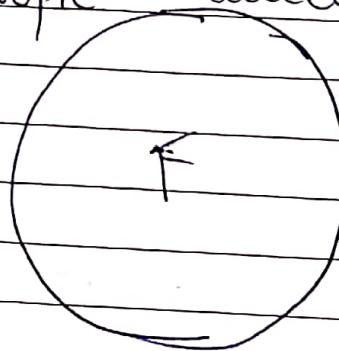→ Omni directional antenna -
 ↳ Isotropic antenna.



BW


$$\Delta f \text{ Hz}$$

$$Q = \frac{f_0}{\Delta f}$$

Beamwidth


angle dependent -

Beamwidth.

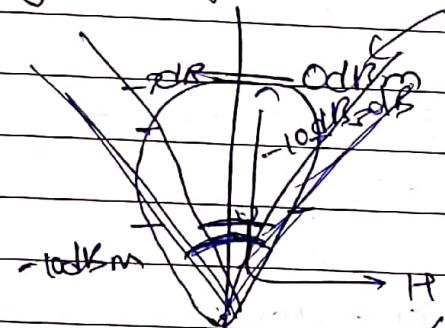

(Half power beam width)

FN BW (First null Beam width)

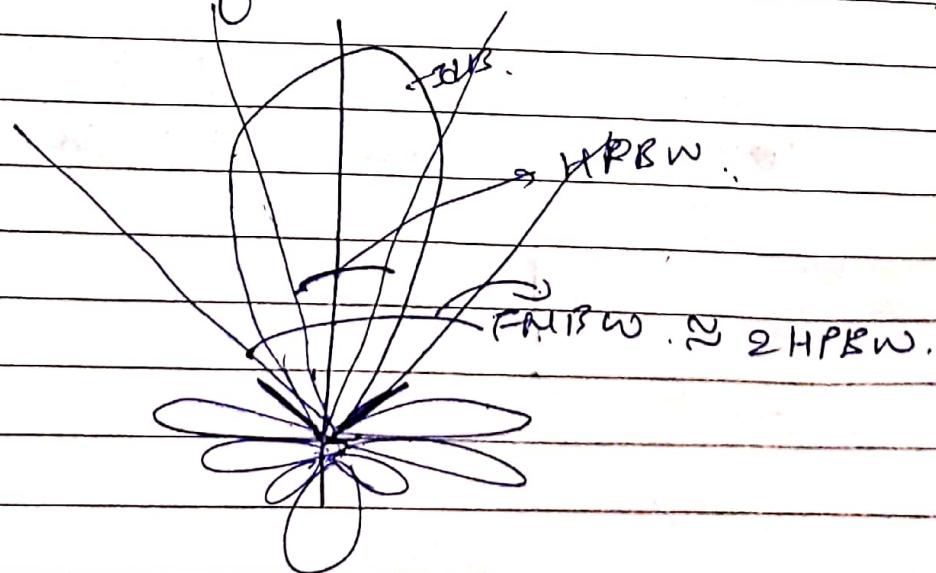

2/11/19

diagram



side
top

- Antennas -
- Radiators.
- Sensors (Temperature)
- Transducers
- Impedance matching device
($Z_{out} = 377 \Omega$)

Classification of antenna


↳ Radiation response.

$$I_L = 0.3 \text{ (A/m}^2\text{)}$$

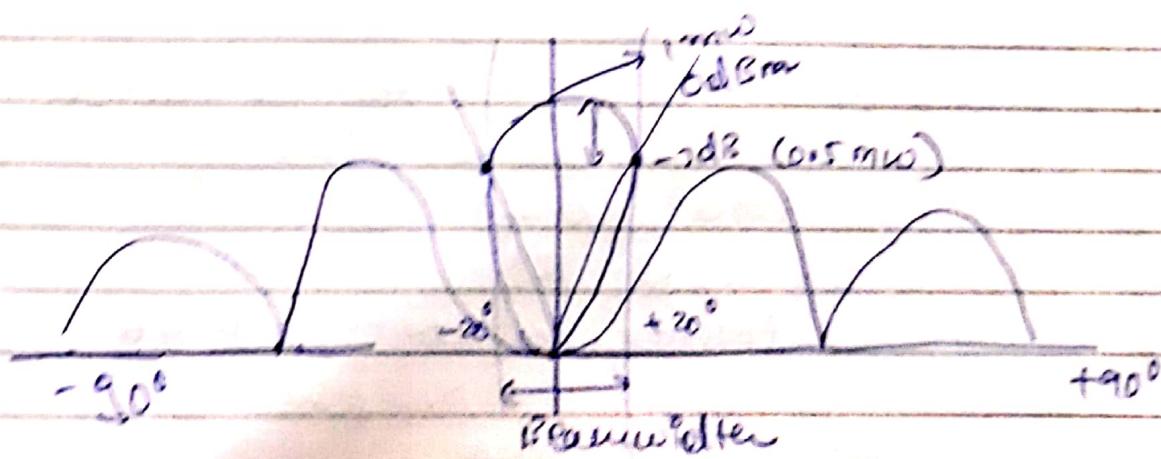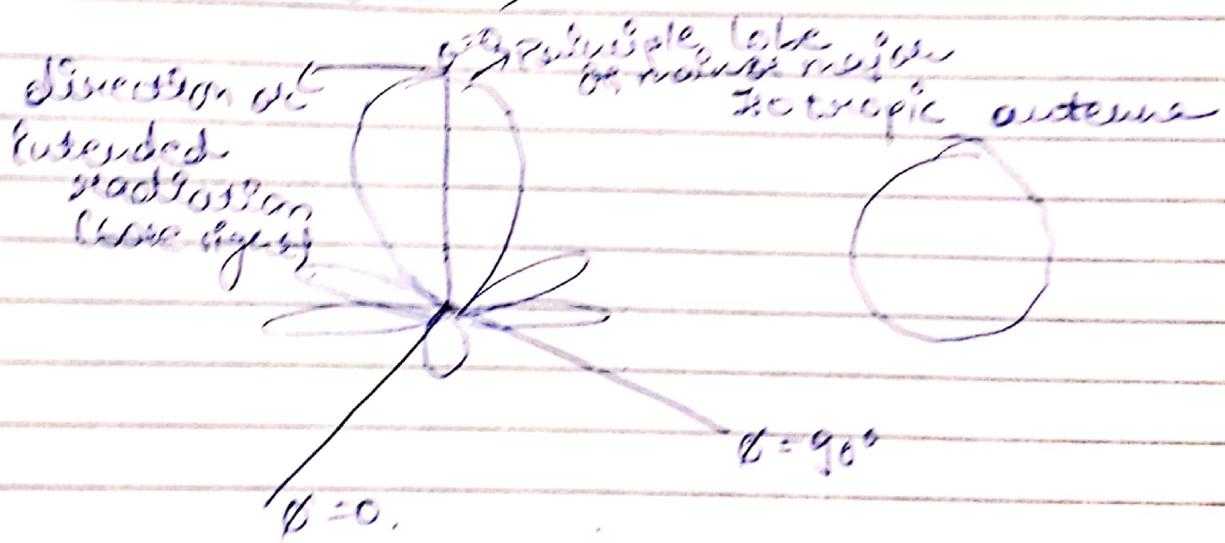

$$3dB BW \text{ (HPBW)} = 40^\circ.$$


E vs Θ

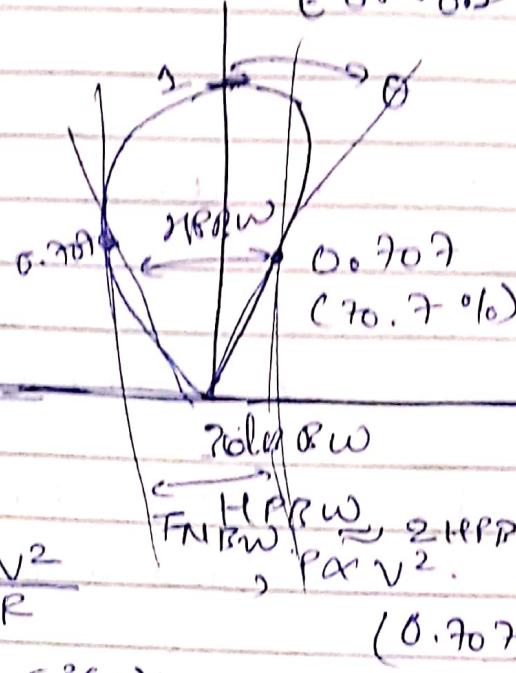

$$P = VI = \frac{V^2}{R}$$

$$P(\Theta) = E^2(\Theta)$$

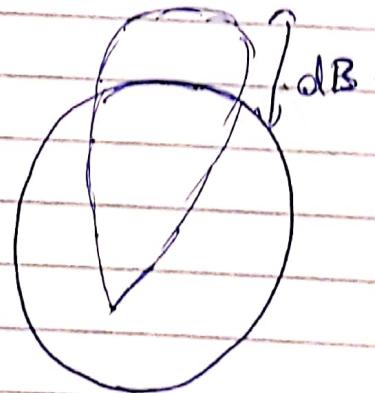$\frac{d\theta}{d\theta}$
dB w.r.t. Isotropic antenna



$$E(\Theta) = \cos^2 \Theta \quad \text{for } 0^\circ \leq \Theta < 90^\circ$$

$$\cos \Theta = \sqrt{0.707} \quad \text{HPPW ?}$$

$$\Theta = 33^\circ$$

$$\text{HPPW} = 20 = 2(33) = 66^\circ$$

$$E(\Theta) = \cos \Theta \cos 2\Theta$$

$$\text{HPBW} = ?, \quad \text{for } 0^\circ \leq \Theta \leq 90^\circ$$

$$\cos \Theta \cos 2\Theta = 0.707 = \frac{1}{\sqrt{2}}$$

$$\cos \theta = \frac{1}{\sqrt{1 + \tan^2 \theta}}$$

$$20 = \cot^{-1} \left(\frac{1}{\sqrt{1 + \tan^2 \theta}} \right)$$

$$\theta = \frac{1}{2} \cot^{-1} \left(\frac{1}{\sqrt{1 + \tan^2 \theta}} \right)$$

$$\theta = 0^\circ \Rightarrow \alpha = 0^\circ$$

$$\alpha = 22.5^\circ \Rightarrow \theta = 22.5^\circ$$

$$\alpha = 90^\circ \Rightarrow \theta = 45^\circ$$

\Rightarrow Beam Area = (beam solid angle) (σ)

Steradigm (σ) = solid angle subtended

by sphere $\frac{4\pi}{4}$


$$= 120\text{d}^2$$

$$= \frac{(150)^2}{\pi} \text{deg}^2$$

$$= 3282.606 \text{ deg}^2$$

$$= 3282 \frac{\text{square degrees}}{32.64}$$

\rightarrow σ (polo angle)

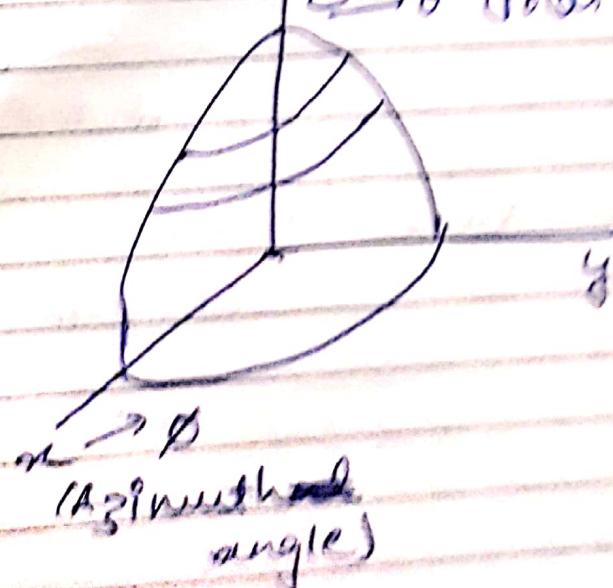

$$\text{Area of sphere} = 2\pi r^2 \int_{0}^{\pi} \sin\theta d\theta$$

$$= 2\pi r^2 \left[-\cos\theta \right]_0^\pi$$

$$= 4\pi r^2$$

↓
Solid angle subtended by
Sphere (sr)

$$1 \text{ srad}^2 = 1 \text{ sr} = 328 \text{ sr}$$

$$4\pi \text{ sr} = 328 \text{ sr} \times 4\pi$$

$$4\pi \text{ sr} = 41,257 \text{ sr}$$

\Rightarrow
Solid angle in sphere

Beam area (or solid angle) =
Integral of normalized power
pattern over a sphere (47.3)

$$S_A = \iint_{0}^{2\pi} P_n(\theta, \phi) \sin\theta d\phi d\Omega$$


$$S_A = \iint_{\phi=0}^{2\pi} \int_{\theta=0}^{\pi} P_n(\theta, \phi) d\theta d\phi$$

$$d\Omega = \sin\theta d\phi$$

$$\text{Beam Area} = S_A$$

$$= \text{OHP} \times \text{HP}$$

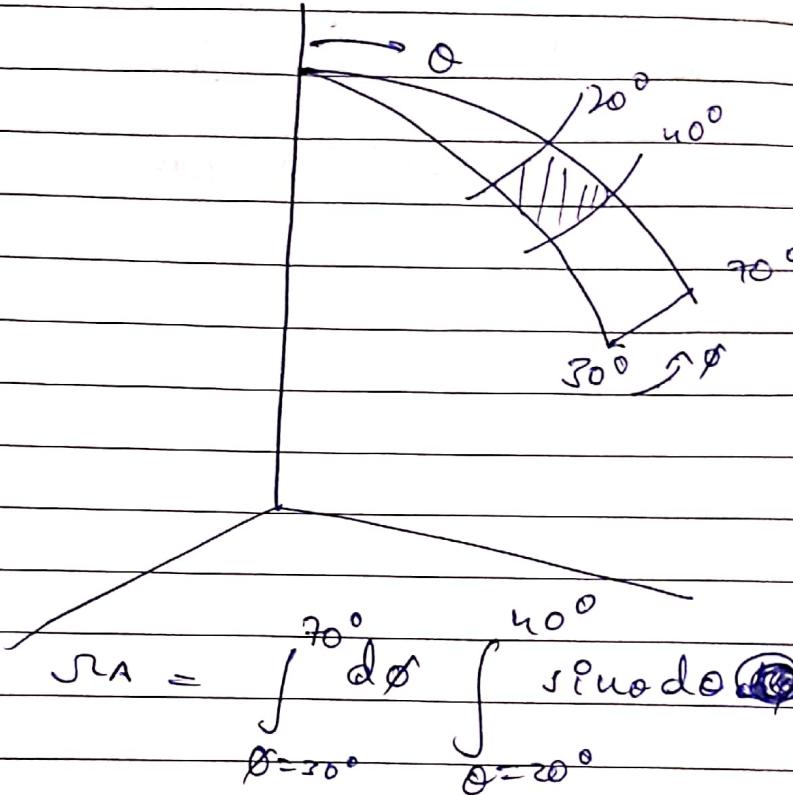→ solid angle Ω_A on a spherical surface between $\theta = 20^\circ$ & 40° and $\phi = 30^\circ$



$$\Omega_A = \int_{\theta=20^\circ}^{70^\circ} d\theta \int_{\phi=20^\circ}^{40^\circ} \sin \theta d\phi$$

$$\Omega = \iint \sin \theta d\theta d\phi$$


$$= \frac{40}{360} \cdot 2\pi \left[-\cos \theta \right]_{20}^{40}$$

$$= 0.222 \times 0.173 \text{ sr}$$

$$= 0.121 \text{ sr}$$

$$= 0.121 \times 22.83 \text{ sq deg.} = 397 \text{ } \square$$

→ Beam efficiency -

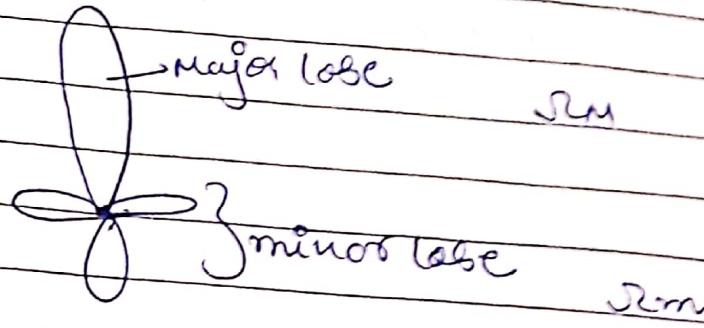

$$\text{Beam efficiency, } \eta = \frac{R_M}{R_A} \times 100\%$$

→ Directivity - (dB) ratio of max power density $P(\theta, \phi)_{\max}$ (W/m²) to its average value over a sphere,

$$D = \frac{P(\theta, \phi)_{\max}}{P(\theta, \phi)_{\text{avg}}} \geq 1$$

$D = 1$
(0dB)

$$P(\theta, \phi)_{\text{av}} = \frac{1}{4\pi} \int_0^{2\pi} \int_0^{\pi} P(\theta, \phi) \sin\theta d\theta d\phi$$
$$= \frac{1}{4\pi} \iint_{\text{sr}} P(\theta, \phi) d\Omega \quad (\text{W/m}^2)$$

$$\therefore D = \frac{P(\theta, \phi)_{\max}}{\frac{1}{4\pi} \iint_{\text{sr}} P(\theta, \phi) d\Omega}$$

$$= \frac{1}{\frac{1}{4\pi} \iint_{\text{sr}} d\Omega} \left[\frac{P(\theta, \phi)}{P(\theta, \phi)_{\max}} \right] d\Omega$$

$$= \frac{4\pi}{\int_{4\pi}^{} P(\theta, \phi) d\Omega}$$

$$D = \frac{4\pi}{S_A}$$

for an antenna radiation over
any half a sphere.


$$S_A = 2\pi \text{ sec}$$

$$\text{D} = \frac{4\pi}{2\pi} = 2$$


↓
3dB
2dBd

→ Gain. -

→ RF or radio link - (freespace)

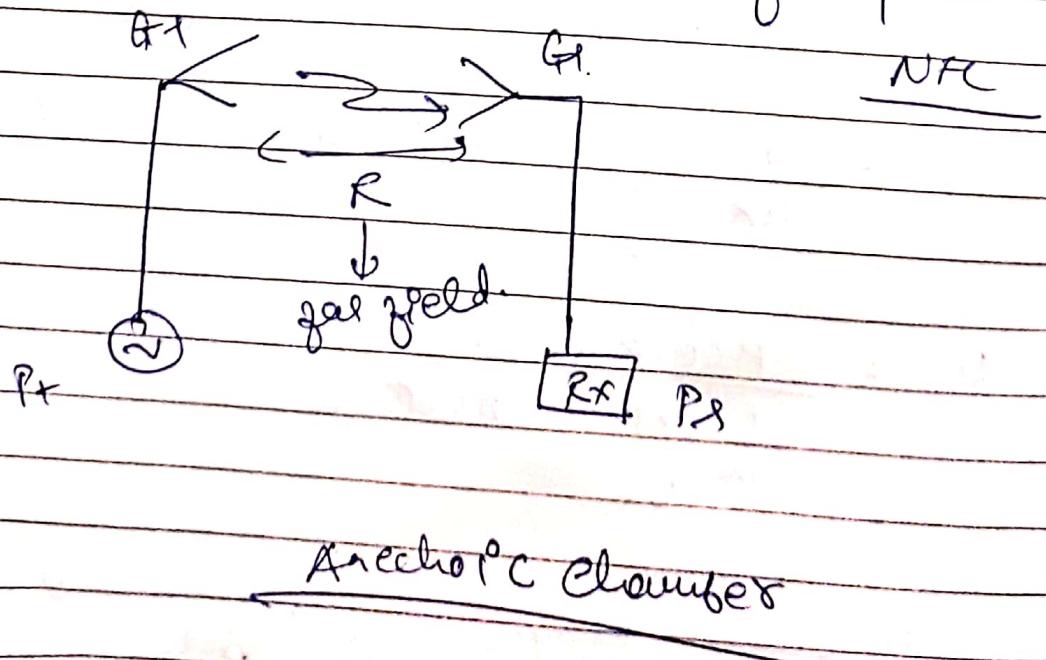

Gain : ?

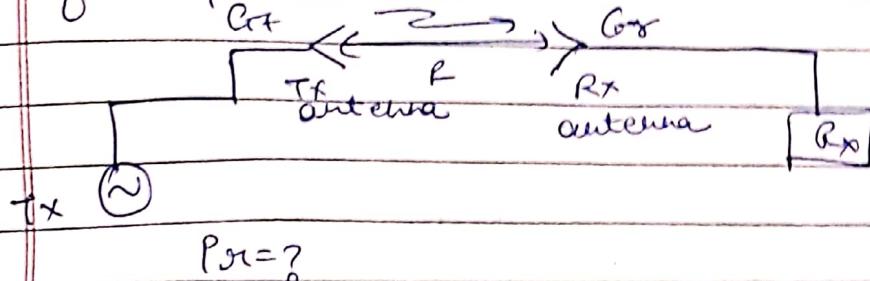RF link / comm^a link / MW link / satelliteFree-space link -

$$P_r = ?$$

Surface area of sphere of radius R is

$$A = 4\pi R^2$$

But as sphere expands (i.e. R increases)
power decreases, i.e.

$$S_{av} = \frac{P_t}{A} = \frac{P_t}{4\pi R^2} \text{ W/m}^2 \quad \text{--- (1)}$$

If it is gain of T_x antenna, power density radiated by T_x antenna is given by,

$$S_{av} = \frac{P_t G_{tx}}{4\pi R^2} \text{ W/m}^2 \quad \text{--- (2)}$$

This power is incident on Rx antenna, we use concept of effective aperture area of antenna (capture area).
(A_e)

As is related to gain by

$$\dots 4\pi A_e / \lambda^2$$

$$\Rightarrow Ae = \frac{G_F \lambda^2}{4\pi} \quad (2)$$

$$P_A = ?$$

$$P_A = Ae \cdot 8au$$

(2) & (3)

$$P_A = \frac{P_t G_F}{4\pi R^2} \cdot \frac{G_F \lambda^2}{4\pi} \quad (w)$$

$$P_A = P_t G_F C_{\lambda} \left(\frac{\lambda}{4\pi R} \right)^2$$

↓
approx equation.

$$P_A \propto \frac{1}{R^2}$$

→ Geostationary orbit,
 $R = 36,900 \text{ km.}$

$$P_A = \frac{P_t G_F G_F}{(4\pi)^2 R^2} \frac{c^2}{f^2}$$

$$= \frac{P_t G_F G_F (3 \times 10^8)^2}{157 \times (10^3)^2 R^2 \times (10^6)^2 f^2}$$

$f \rightarrow \text{MHz}$
 $R \rightarrow \text{km.}$

$$P_A = P_t G_F G_F \left[\frac{0.057 \times 10^{-2}}{f^2 R^2} \right]$$

$\downarrow \text{MHz}$ ↓ 1cm.

$$P_A |_{\text{dBm}} = P_t \left| \frac{dBm}{dB} + G_F | dB + G_F | dR \right| - \left(10 \log (F^2) + 10 \log (R^2) \right)$$

$$P_A |_{\text{dBm}} = P_t \left| \frac{dBm}{dB} + G_F | dB + G_F | dR \right| - \left[20 \log 20 \log F + 20 \log R \right]$$

$20 \log R \text{ law. or } 20 \log D \text{ (cm)} \leftarrow \text{free space path loss calc}$

f (in GHz), R (km)

$$F \text{ SPL} = 92.5 + 20 \log f + 20 \log R.$$

11/11/19

$$\rightarrow P_{tx} = P_t (G_t + G_r) \left(\frac{\lambda}{4\pi R} \right)^2$$

↓ free space path loss

$$EIRP = P_t G_t$$

↓

Effective Isotropic Radiated power (eirp)

$$EIRP \left|_{\text{dBm}} \right. = P_t \left|_{\text{dBm}} \right. + G_t \left|_{\text{dB}} \right.$$

$$D = \frac{4\pi}{\lambda^2} = \iint_0^\pi$$


$$D = \frac{4\pi A_e}{\lambda^2}$$

$$G = \frac{4\pi A_e}{\lambda^2}$$

$$G = k D$$

↓ Efficiency

→ A_e for an ideal isotropic antenna -

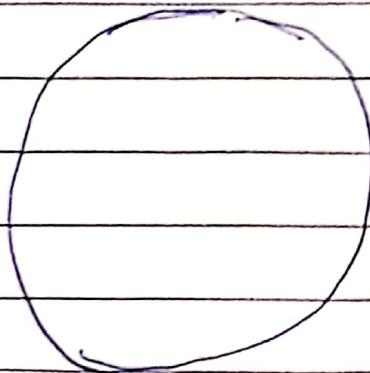


$$D = 1$$

$$A_c = \frac{D\lambda^2}{4\pi} = \frac{\lambda^2}{4\pi} = 0.0796\lambda^2$$

2 identical antennas

$$G_f = G_t = G$$
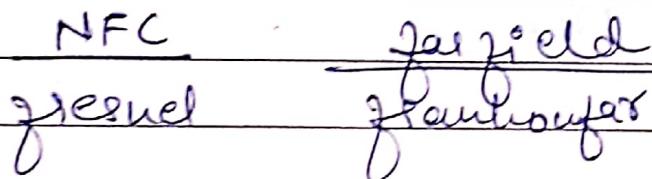
$$P_f = P_t G^2 \left(\frac{\lambda}{4\pi d}\right)^2$$





- Near field = Reactive in nature
(non-radiative)

- Far field = Radiative in nature.

$$G_f = G_t$$

$$G_f = G_t$$

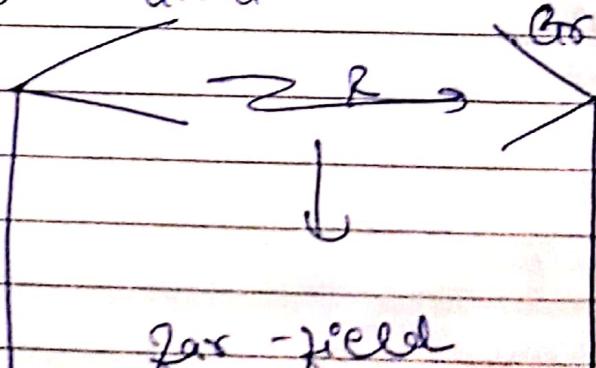

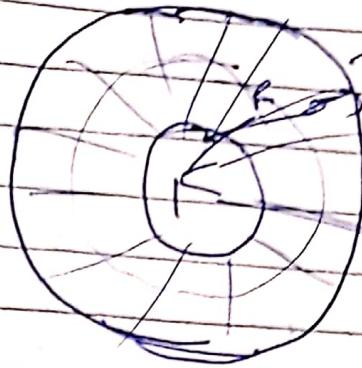

$$P > \frac{2D^2}{\lambda}$$

classmate
Date _____

~~largest dimension
of antenna~~

far field
or
frankowfair.

near
or
near-field.

* ~~Microstrip~~ or patch Antenna: (Radiator)


planar
↳

permitted


shorted
antenna

Aluminum

$$\epsilon_r = 10$$

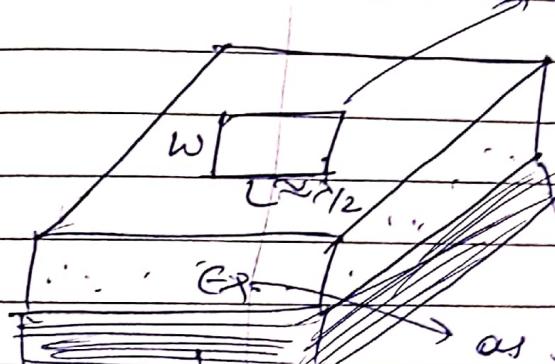

tried,

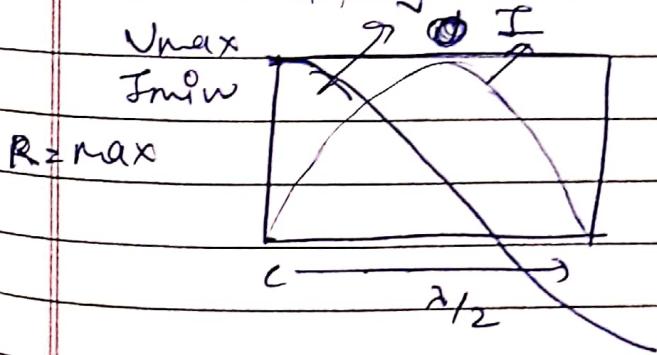

Vmax
Imin
R = max

Ideal Resonant antenna

→ DR's advantage → Limited Bandwidth.
(1-3%)

- ② Low power handling
- ③ Low power gain. (Radiate in half plane)

