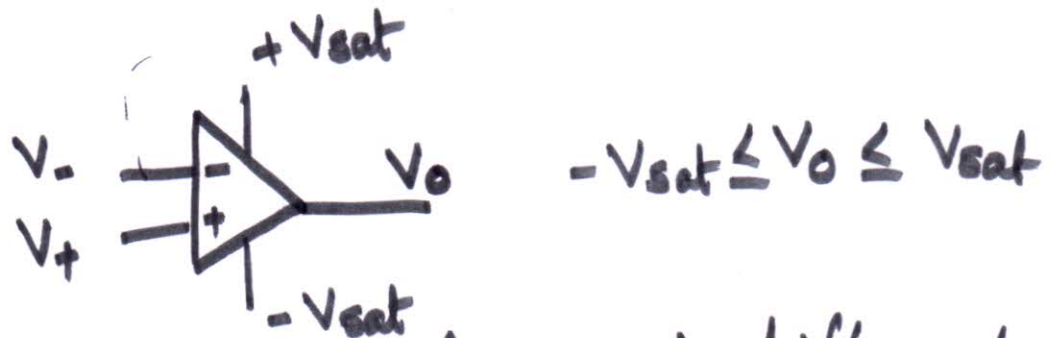


D/A AND A/D CONVERSION

- Digital-to-analog converter (DAC): used to translate digital information to analog information.
- Analog-to-digital converter (ADC): used to change analog signal to its equivalent digital signal.

Brief Discussion on OPERATIONAL AMPLIFIER (OP-AMP):




- Op-Amp is a very high gain differential Amplifier.

$A_d \rightarrow$ diff. gain

$$V_d = V_+ - V_-$$

$$\Rightarrow V_0 = A_d V_d$$

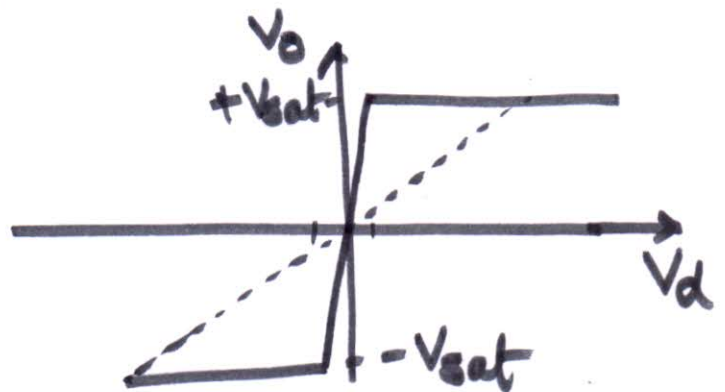

ex

$$V_{sat} = 15V$$

$$A_d = 10^6$$

$$\Rightarrow V_d = \frac{15}{10^6} V = 15 \mu V$$

Use -ve feedback,


$$V_o \rightarrow \text{finite}$$

$$\Rightarrow V_o = A_d V_d$$

$$\Rightarrow V_d = \frac{V_o}{A_d} \approx 0 \text{ V}$$

$$\Rightarrow V_+ - V_- \approx 0 \text{ V}$$

$$\Rightarrow \boxed{V_+ \approx V_-}$$

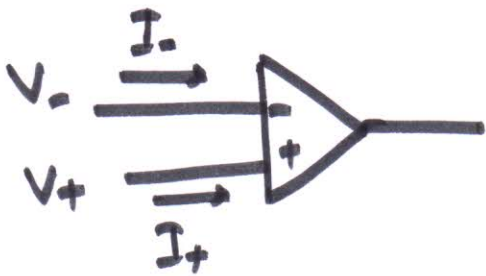


1/p impedance is very large.

$$I_- = I_+ = 0 \text{ A}$$

Applications

1) Inverting Amp

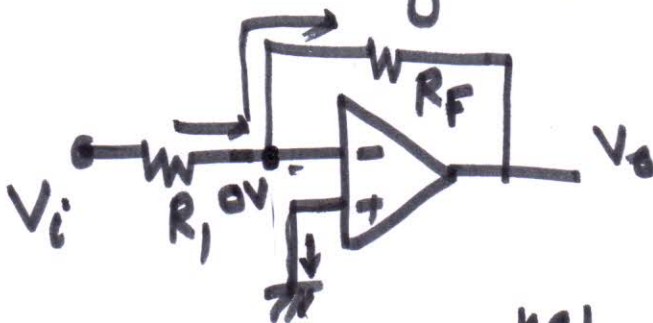


KCL

$$V_o = \left(-\frac{R_F}{R_1} \right) \cdot V_i$$

$$\frac{V_i - 0}{R_1} = \frac{0 - V_o}{R_F}$$

1) Non-inverting

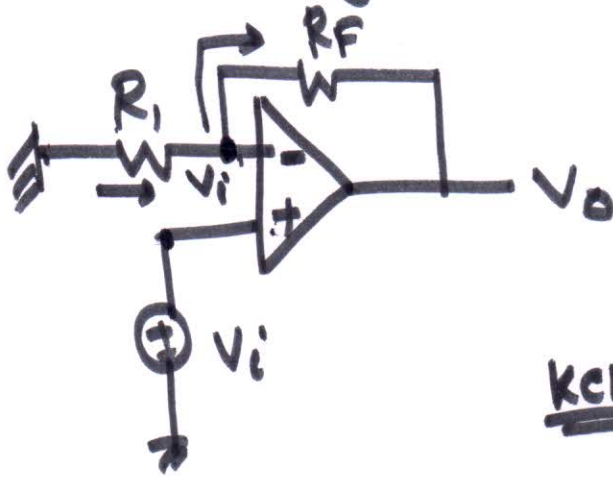

KCL


$$\frac{0 - V_i}{R_1} = \frac{V_i - V_o}{R_F}$$

$$\Rightarrow V_o = \left(1 + \frac{R_F}{R_1}\right) V_i$$

DAC:

1. Variable Resistor Network
2. Binary Ladder Network

Variable Resistor Network:

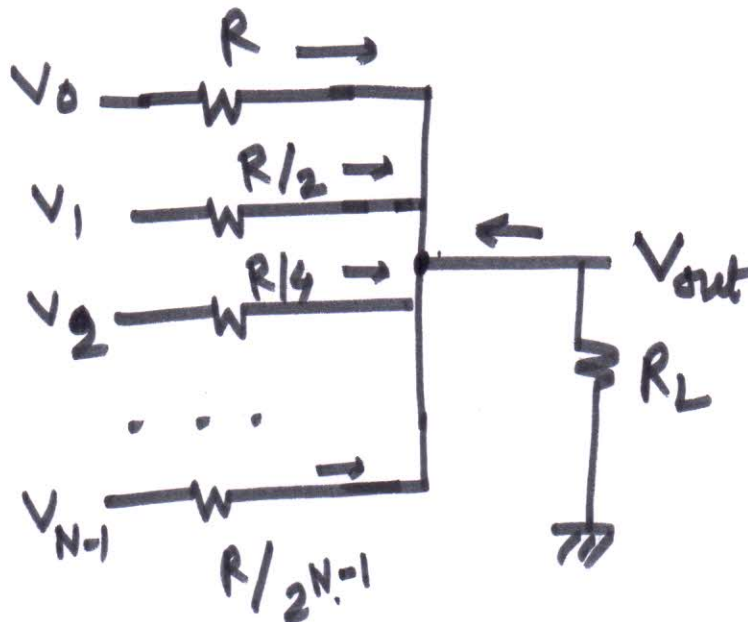

$$R_L \gg R$$

$$K = \frac{1}{1+2+4+\dots+2^{N-1}}$$

$$= \frac{1}{2^N - 1}$$


KCL

$$\frac{V_0 - V_{out}}{R} + \frac{V_1 - V_{out}}{R/2} + \dots + \frac{V_{N-1} - V_{out}}{R/2^{N-1}} + \frac{0 - V_{out}}{R_L} = 0$$

$$\Rightarrow V_{out} = \frac{\frac{V_0}{R} + \frac{V_1}{R/2} + \dots + \frac{V_{N-1}}{R/2^{N-1}}}{\frac{1}{R} + \frac{1}{R/2} + \dots + \frac{1}{R/2^{N-1}} + \frac{1}{R_L}}$$

$$= K \left[\underset{\text{LSB}}{V_0 + 2V_1 + 4V_2 + \dots + 2^{N-1}V_{N-1}} \right] \text{MSB}$$

Using Op Amp

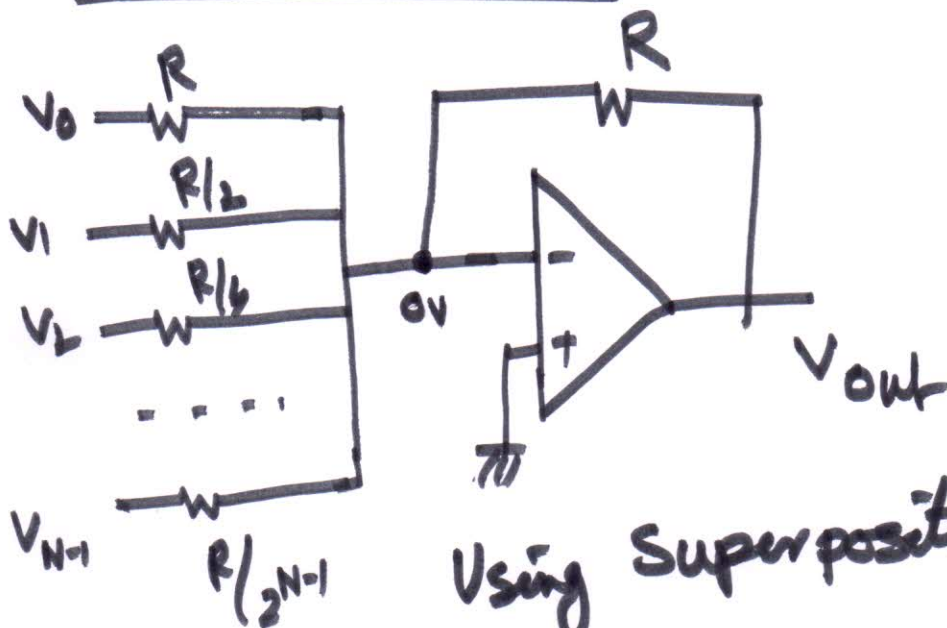


Using Superposition Theorem,

$$V_{out} = -\frac{R}{R} \cdot V_0 - \frac{R}{R/2} \cdot V_1 - \frac{R}{R/4} \cdot V_2$$




$$- + \dots - \frac{R}{R/2^{N-1}} \cdot V_{N-1}$$


$$= - \left(V_0 + 2V_1 + 4V_2 + \dots + 2^{N-1} V_{N-1} \right)$$

2. Binary Ladder (R-2R) D/A Converter :

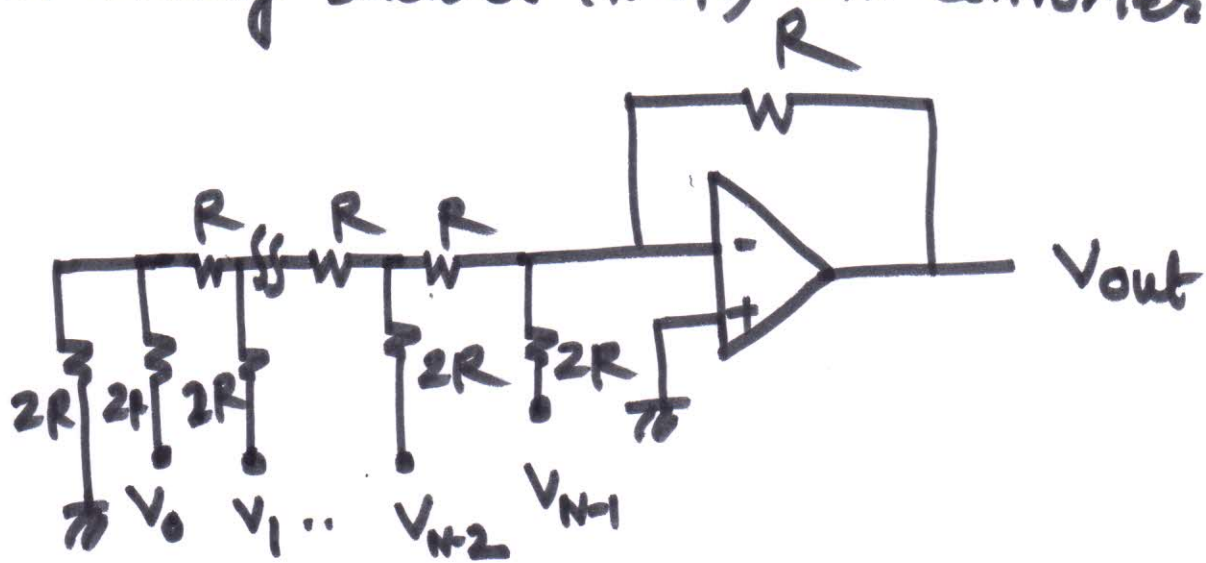




Only V_0 is acting

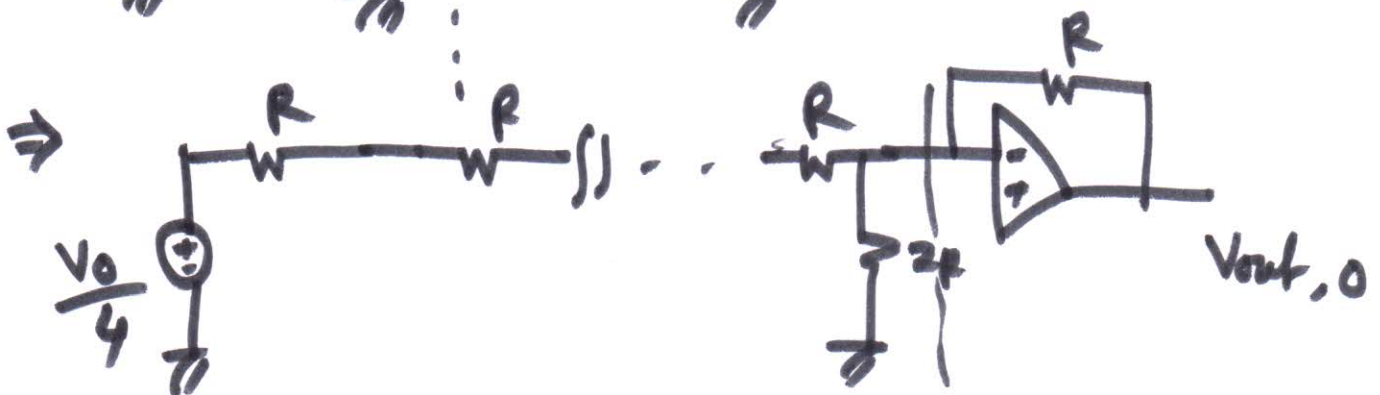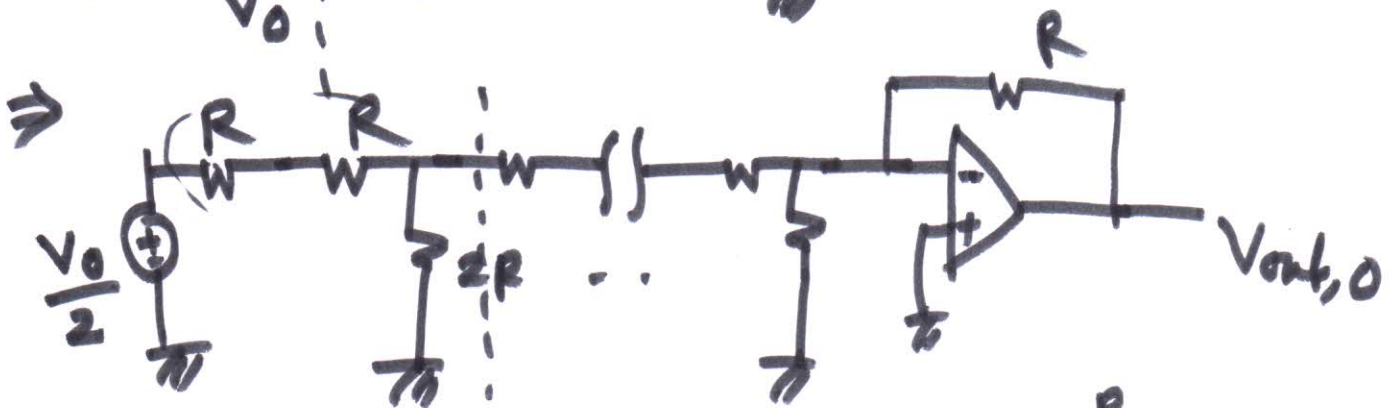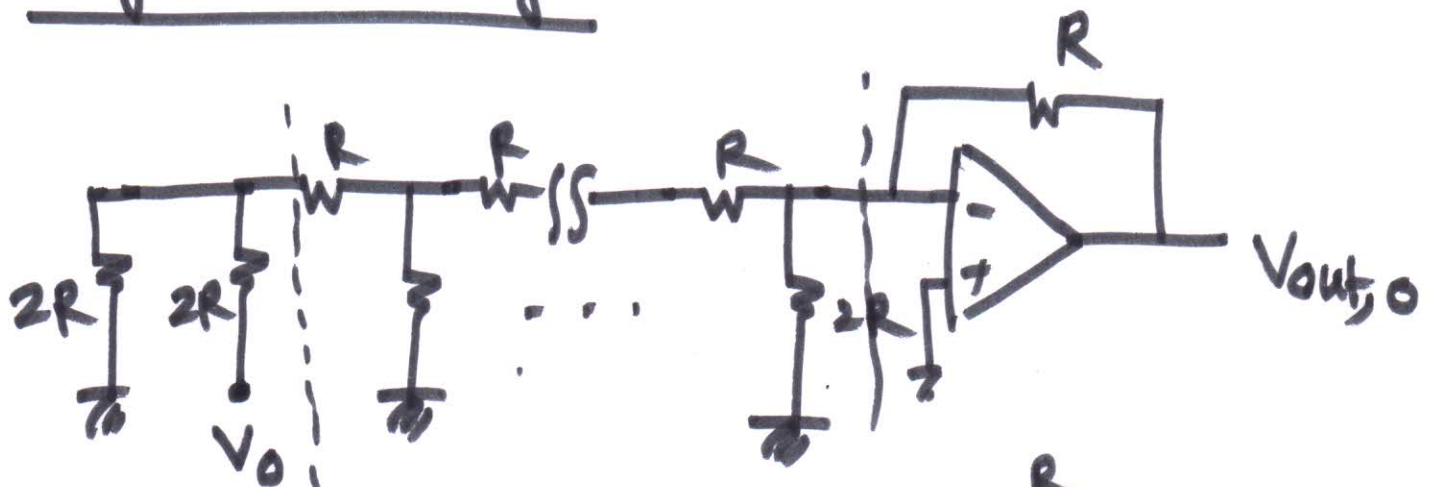

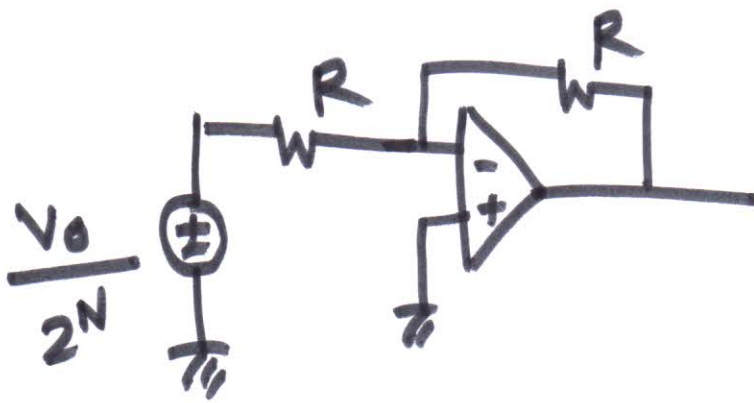

$$V_{out,0} = \left(-\frac{R}{R}\right) \times \frac{V_0}{2^N}$$

V_1 is acting

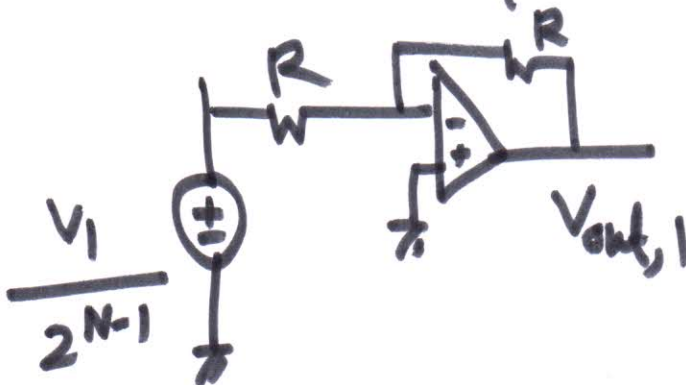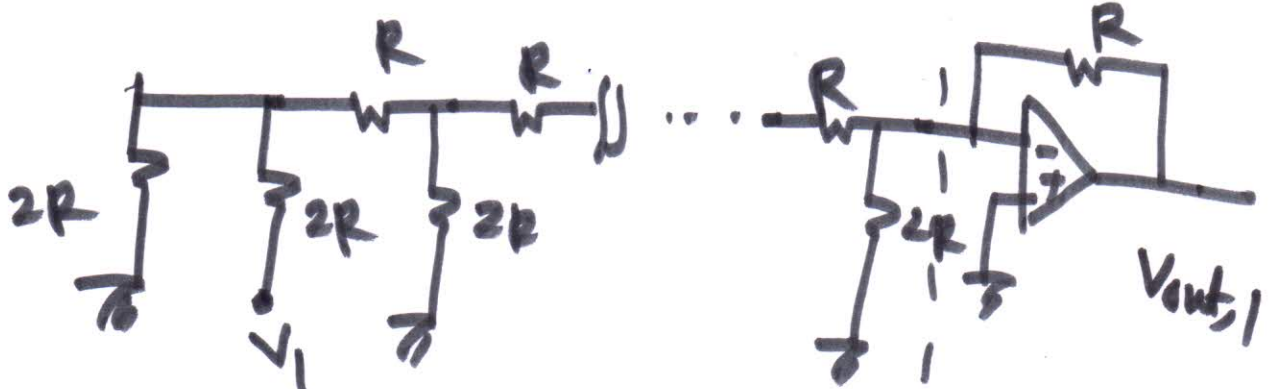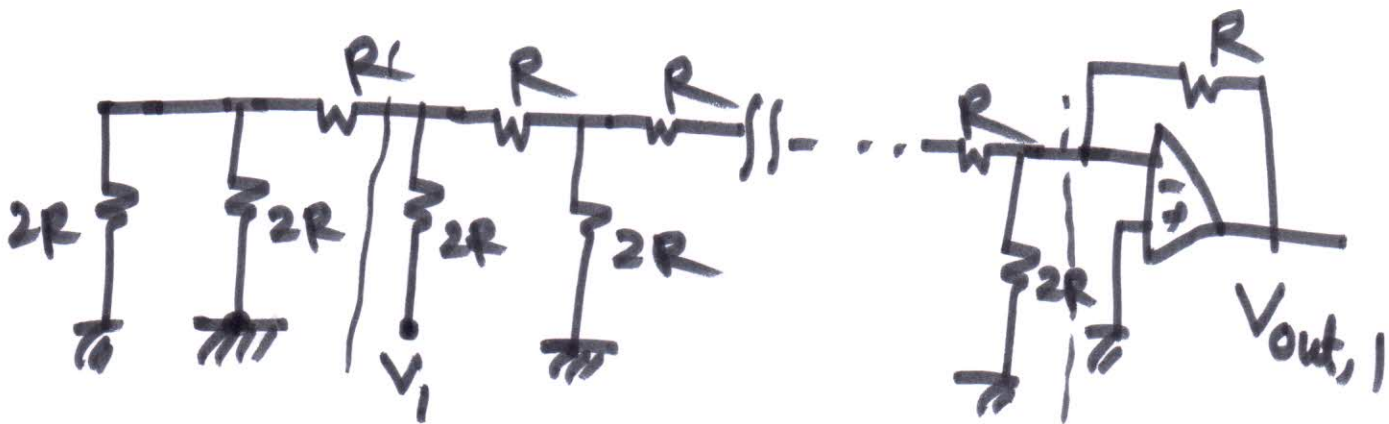

$$V_{out,1} = \left(-\frac{R}{R}\right) \frac{V_1}{2^{N-1}}$$

Therefore,

$$V_{out} = \left(-\frac{R}{R}\right) \times \frac{V_0}{2^N} + \left(-\frac{R}{R}\right) \times \frac{V_1}{2^{N-1}} + \dots$$

$$+ \left(-\frac{R}{R}\right) \times \frac{V_{i'}}{2^{N-i'}} + \left(-\frac{R}{R}\right) \times \frac{V_{N-1}}{2}$$

$$= -\frac{1}{2^N} [V_0 + 2V_1 + 2^2V_2 + \dots + 2^{N-1}V_{N-1}]$$

If, $V_0 = V_1 = \dots = V_{N-1} = V$

$$\Rightarrow V_{out} = -\frac{V}{2^N} \times [1 + 2 + 4 + \dots + 2^{N-1}]$$

$$= -\frac{V}{2^N} \times [2^N - 1]$$

$$\underline{-\frac{V[2^N - 1]}{2^N} < V_{out} < 0}$$

A/D Converter

1) Simultaneous or Flash-type A/D Converter



Consider $1/p$ V_i ,
with $0 \leq V_i \leq V$.

$$0 \leq V_i \leq \frac{V}{4} \Rightarrow '00'$$

$$\frac{V}{4} \leq V_i \leq \frac{2V}{4} \Rightarrow '01'$$

$$\frac{2V}{4} \leq V_i \leq \frac{3V}{4} \Rightarrow '10'$$

$$\frac{3V}{4} \leq V_i \leq V = '11'$$

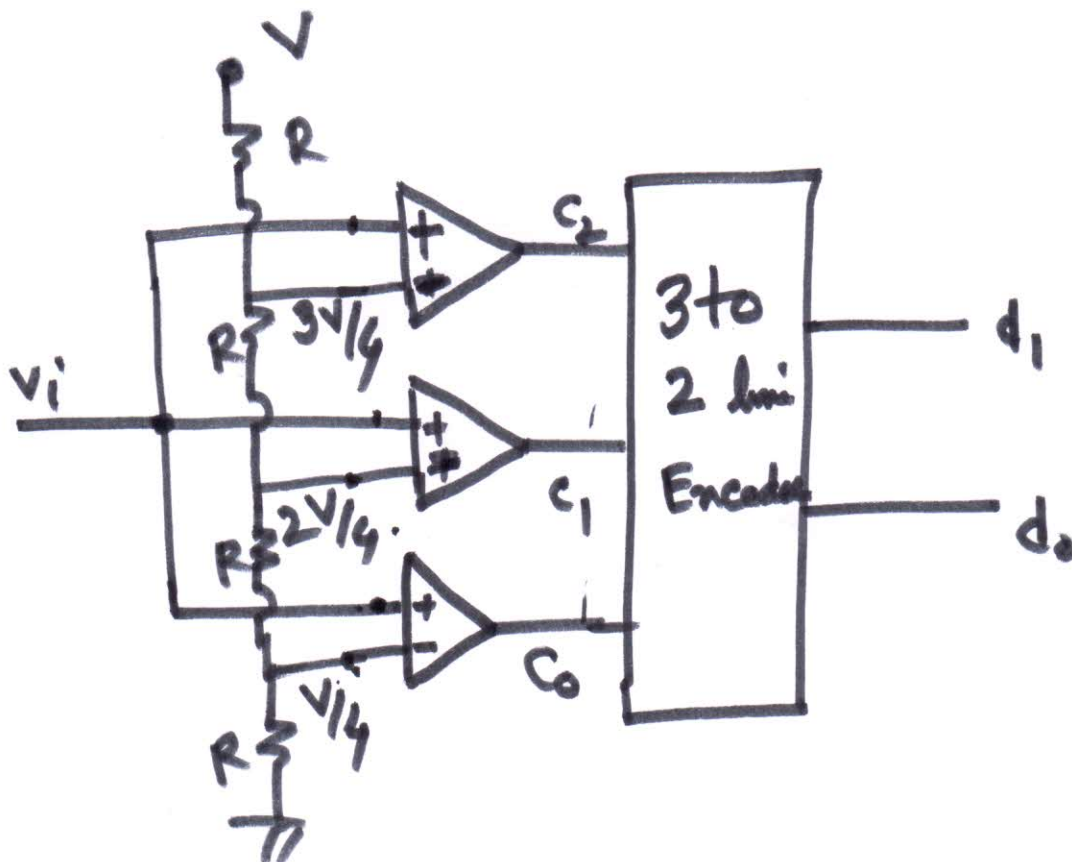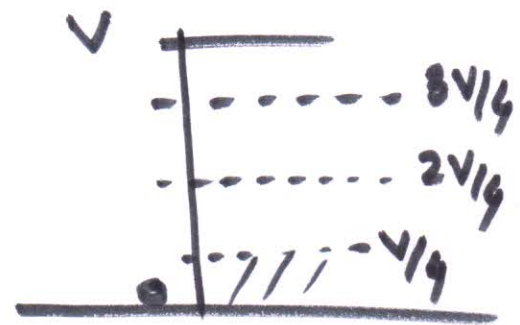

V_i	c_2	c_1	c_0	d_1	d_0
$0 \leq V_i < \frac{V}{4}$	0	0	0	0	0
$\frac{V}{4} \leq V_i < \frac{V}{2}$	0	0	1	0	1
$\frac{V}{2} \leq V_i < \frac{3V}{4}$	0	1	1	1	0
$\frac{3V}{4} \leq V_i \leq V$	1	1	1	1	1

4 bits Flash-type A/D Converter:

