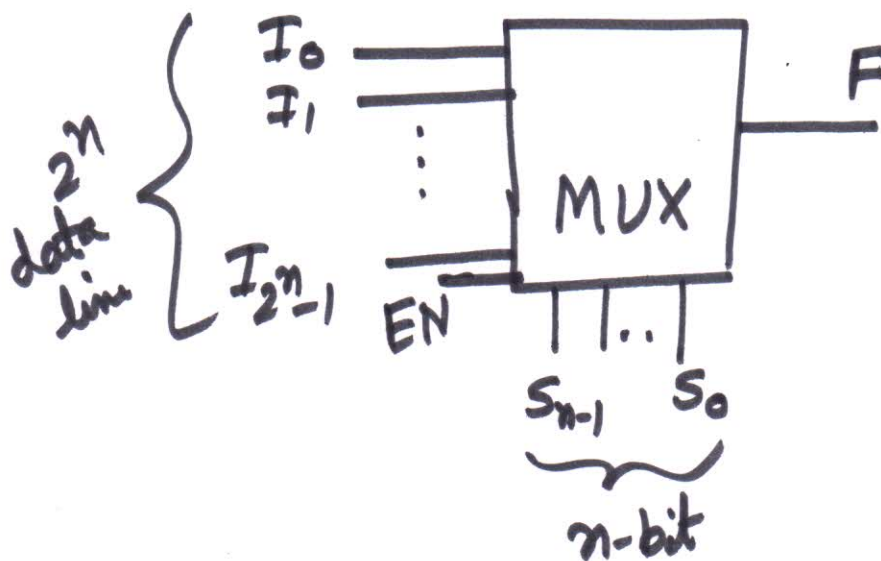





Multiplexers

- A multiplexer or MUX is a combinational circuit with more than one input line, one output line and more than one selection line.
- In general, for n selection lines, there are 2^n data lines, and the multiplexer is referred to as a 2^n -to-1 MUX or $2^n \times 1$ MUX.
- The multiplexer sends the binary information present on any of the input line to the data line depending on the binary status of the select lines.




Application
(1) TDM/FDM
(2) parallel to
Serial
Converter

Time Division Multiplexing (TDM)

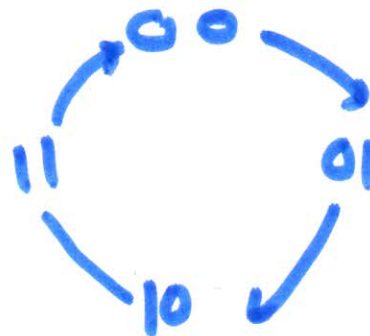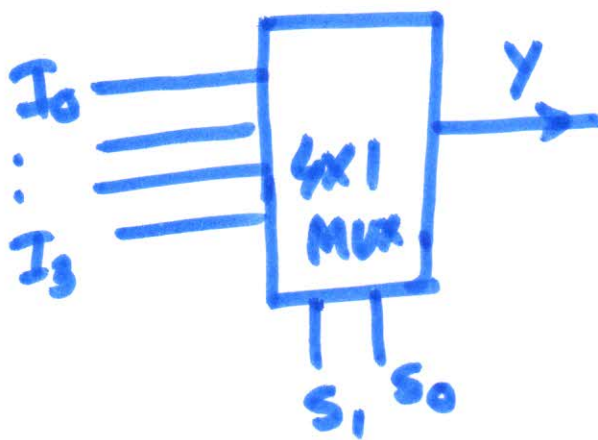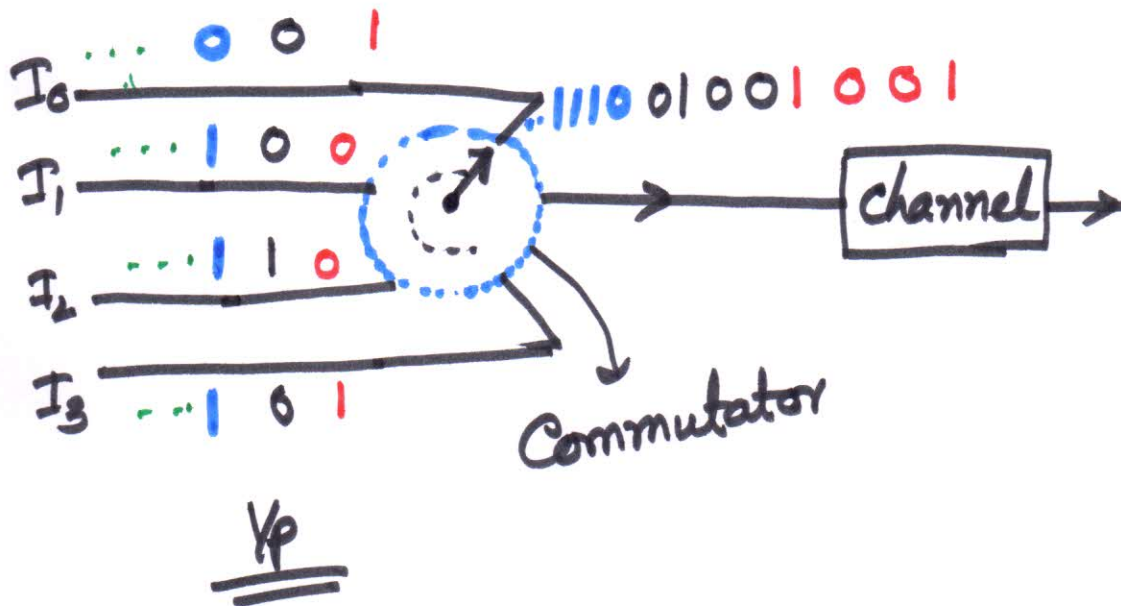


A) 2×1 MUX (with ENABLE input)

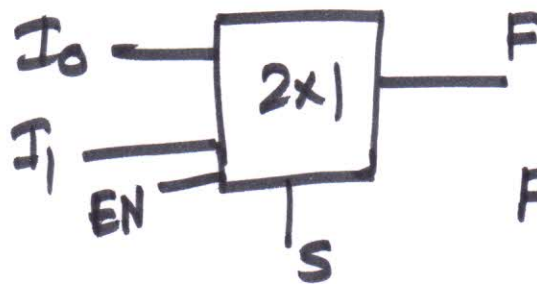


$$F = EN \cdot \bar{S} \cdot I_0 + EN \cdot S \cdot I_1$$

| S | EN | F |
|---|----|-------|
| X | 0 | 0 |
| 0 | 1 | I_0 |
| 1 | 1 | I_1 |

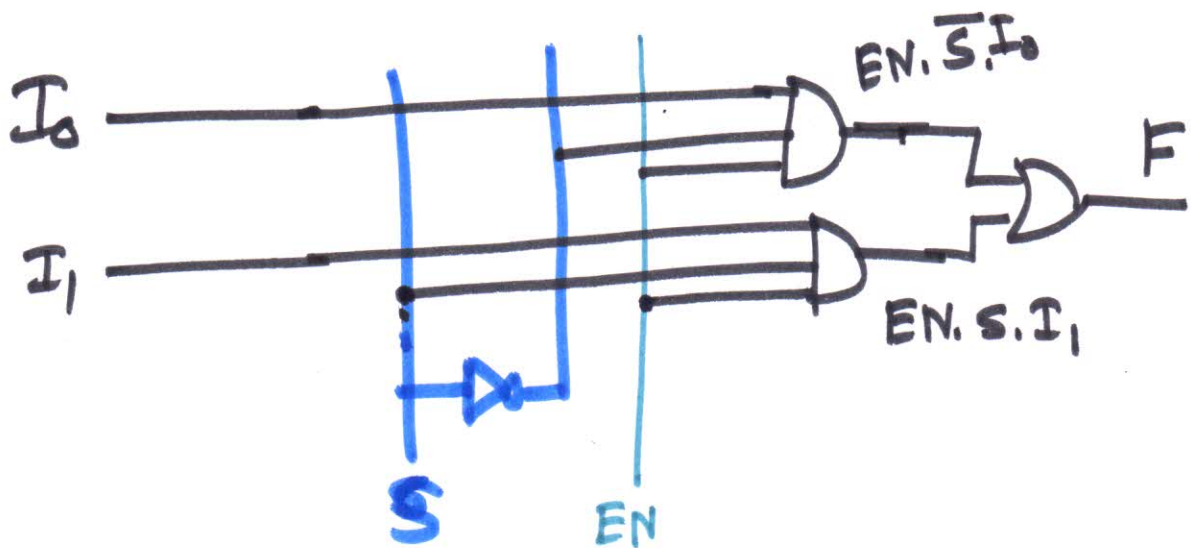

B) 4×1 MUX (with ENABLE input)

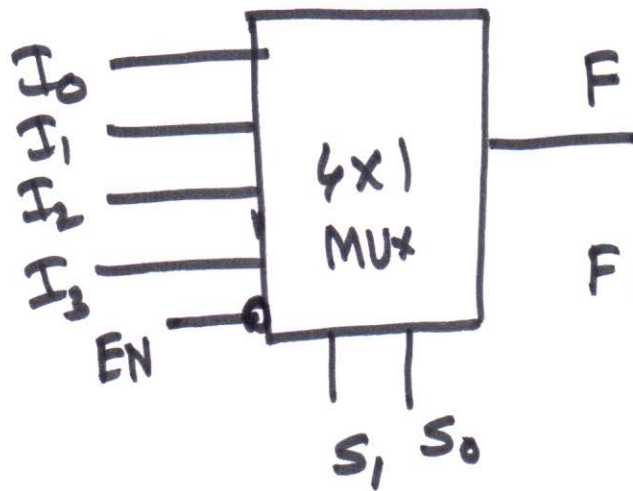


$$F = \overline{EN} \cdot \overline{S_0} \cdot \overline{S_1} \cdot I_0 + \overline{EN} \cdot S_0 \cdot \overline{S_1} \cdot I_1 + \overline{EN} \cdot \overline{S_0} \cdot S_1 \cdot I_2 + \overline{EN} \cdot S_0 \cdot S_1 \cdot I_3$$

II


| EN | S_1 | S_0 | F |
|----|-------|-------|-------|
| 1 | x | x | 0 |
| 0 | 0 | 0 | I_0 |
| 0 | 0 | 1 | I_1 |
| 0 | 1 | 0 | I_2 |
| 0 | 1 | 1 | I_3 |

Implementing Boolean Functions with Multiplexers:

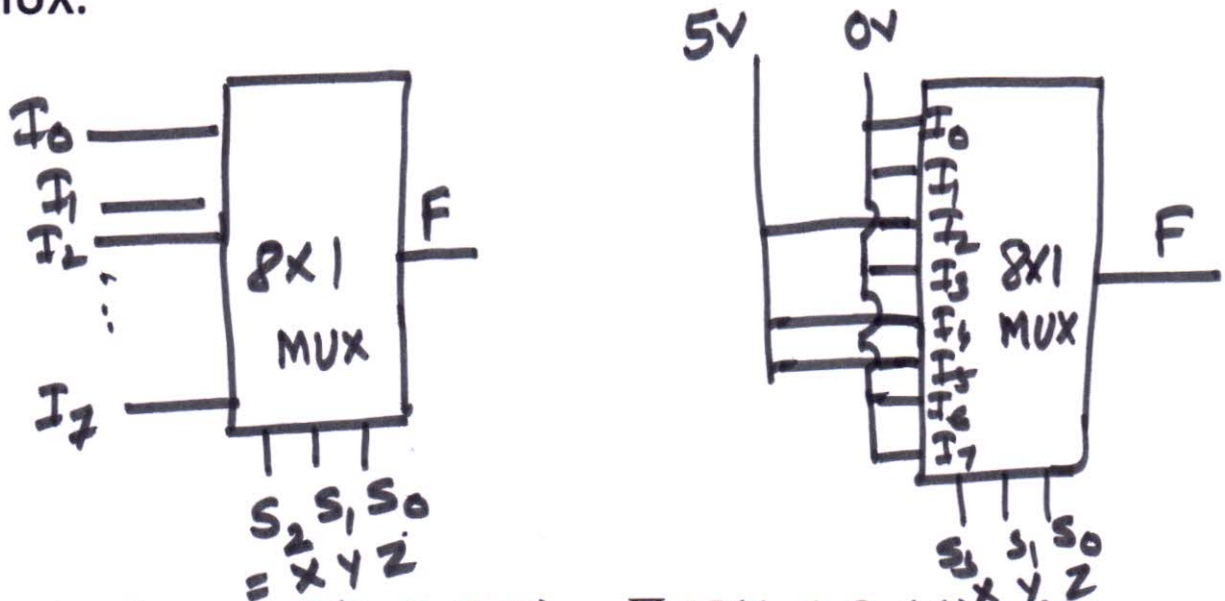
Ex. Implement $F(X, Y, Z) = \sum m(2, 4, 5)$ using 8-to-1 MUX.



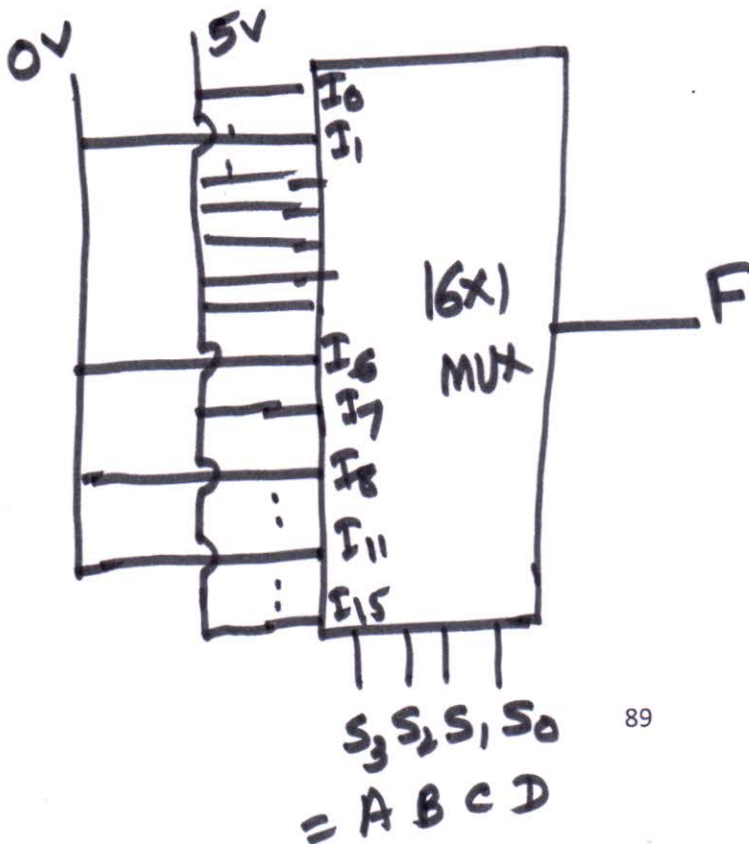Ex. Implement $F(A, B, C, D) = \prod M(1, 6, 8, 11)$ using 16-to-1 MUX.



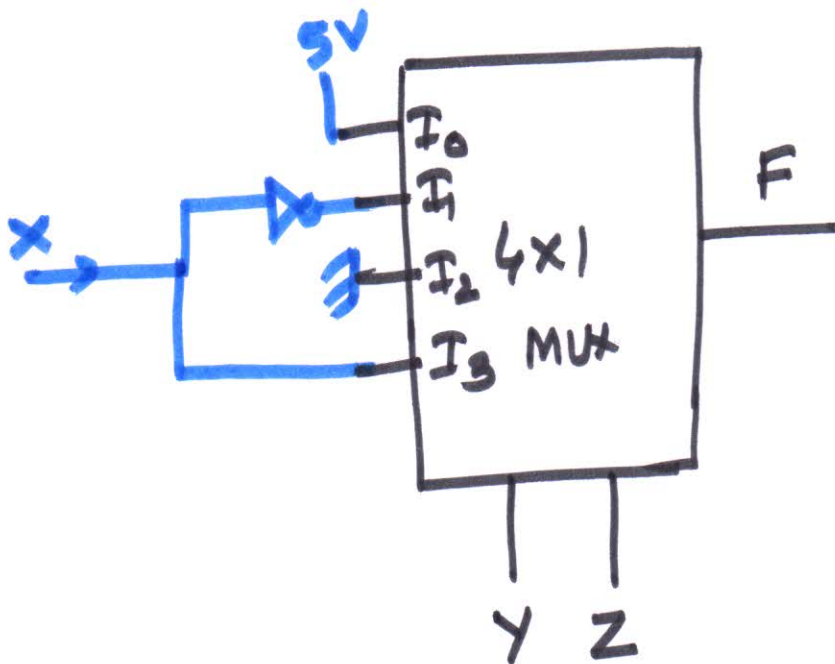Ex. Implement $F(X, Y, Z) = \sum m(0, 1, 4, 7)$ using 4-to-1 MUX.




| x \ yz | 00 | | 01 | | 10 | | 11 | |
|--------|----|-----------|----|-----|----|-----|----|-----|
| | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 1 |
| | ↓ | ↓ | ↓ | ↓ | ↓ | ↓ | ↓ | ↓ |
| | 1 | \bar{x} | 0 | x | 0 | x | 0 | x |

Ex.

Implement $F(A, B, C, D) = \sum m(3, 4, 5, 8, 9, 12, 14, 15)$
using 8-to-1 MUX.

| A \ BCD | | | | | | | | |
|---------|-----|-----|-----|-----------|-----|-----------|-----|-----|
| | 000 | 001 | 010 | 011 | 100 | 101 | 110 | 111 |
| 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 |
| | A | A | 0 | \bar{A} | 1 | \bar{A} | A | A |

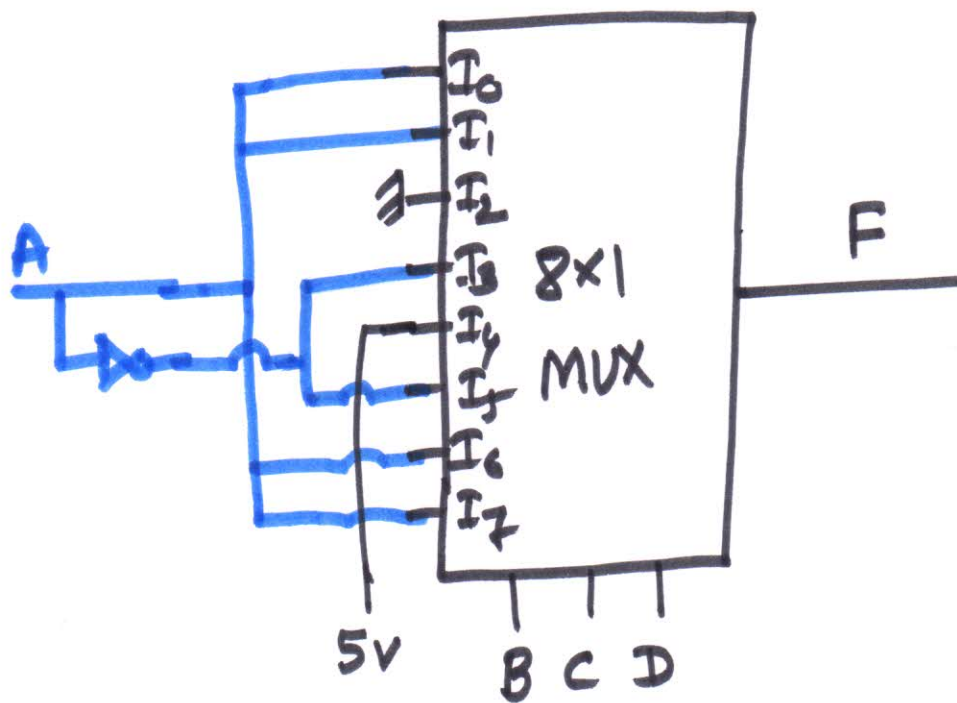

Ex. Implement $F(X, Y, Z) = \sum m(3, 5, 6)$ using 2-to-1 MUX.

