
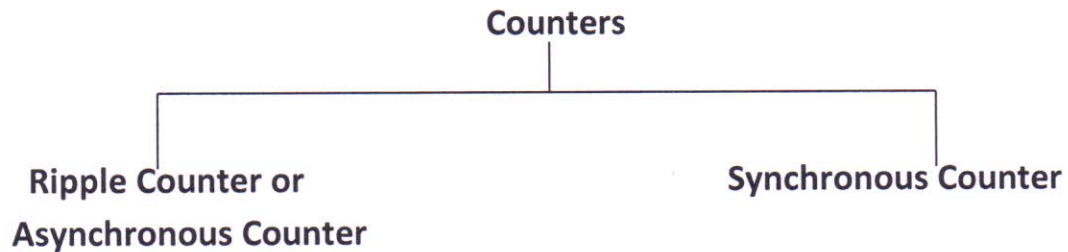

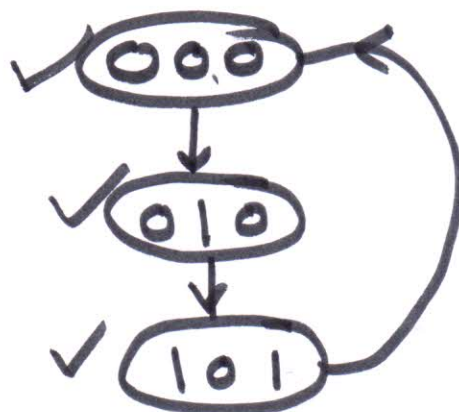
## Registers and Counters

- Registers are used for temporary storage of data.
- Counters are mainly used in counting applications, where they either measure the time interval between two unknown time instants or measure the frequency of a given signal.



- A ripple counter is a cascaded arrangement of flip-flops where the output of one flip-flop drives the clock input of the following flip-flop.
- In synchronous counter, the clock is applied to all flip-flops simultaneously, and thus, all the flip-flops change their states at the same time.
- Modulus (MOD) of a counter is the number of different logic states it goes through before it comes back to the initial state to repeat the count sequence.




$$\underline{\underline{\text{MOD} = 3}}$$



0 → 2 → 5 → 0 → 2 → 5

MOD-  $2^N$  binary ripple counter:

$N=4$

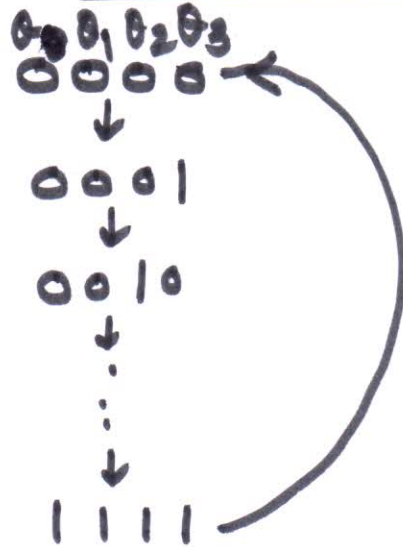

$$\text{MOD} = 2^4 = 16$$

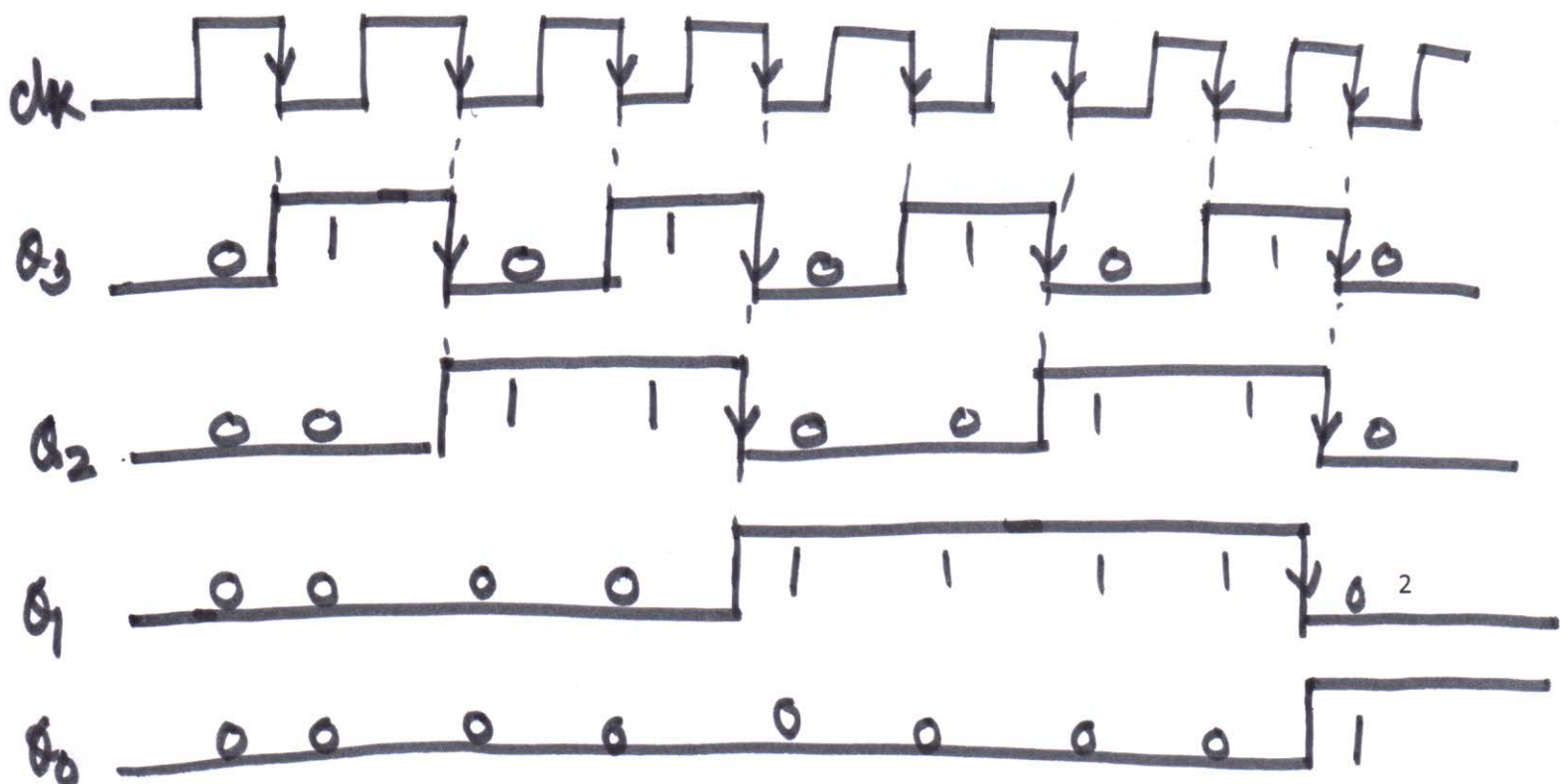
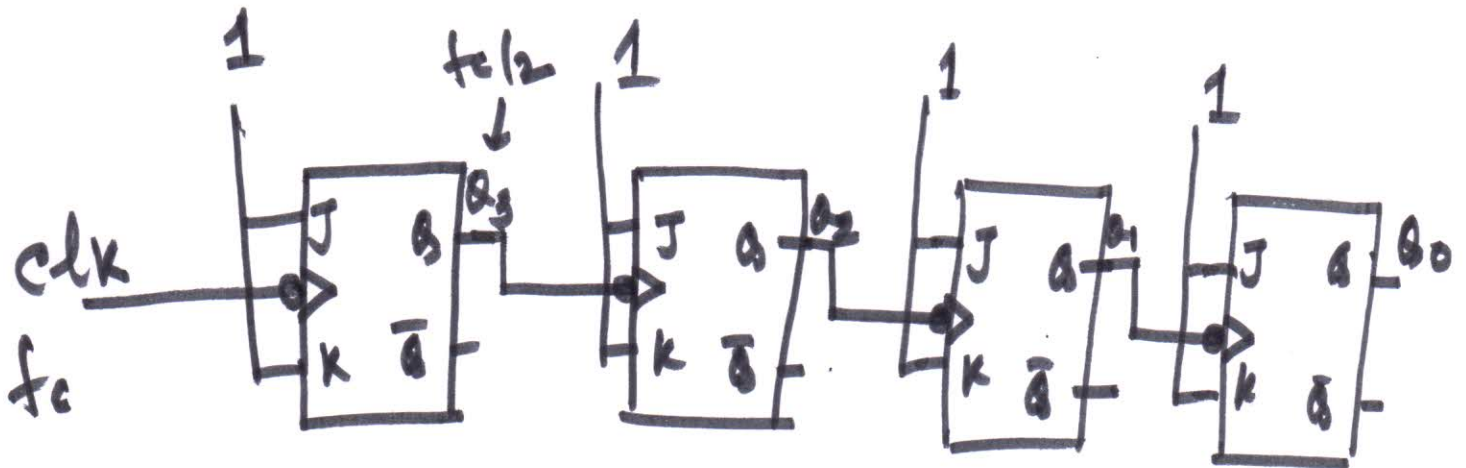


MOD- 5 binary ripple counter:

N=3

$$\underline{2^{N-1} + 1 \leq \text{MOD} \leq 2^N}$$

Preset	Clear	Q	Q'
0	1	x	1
1	0	x	0

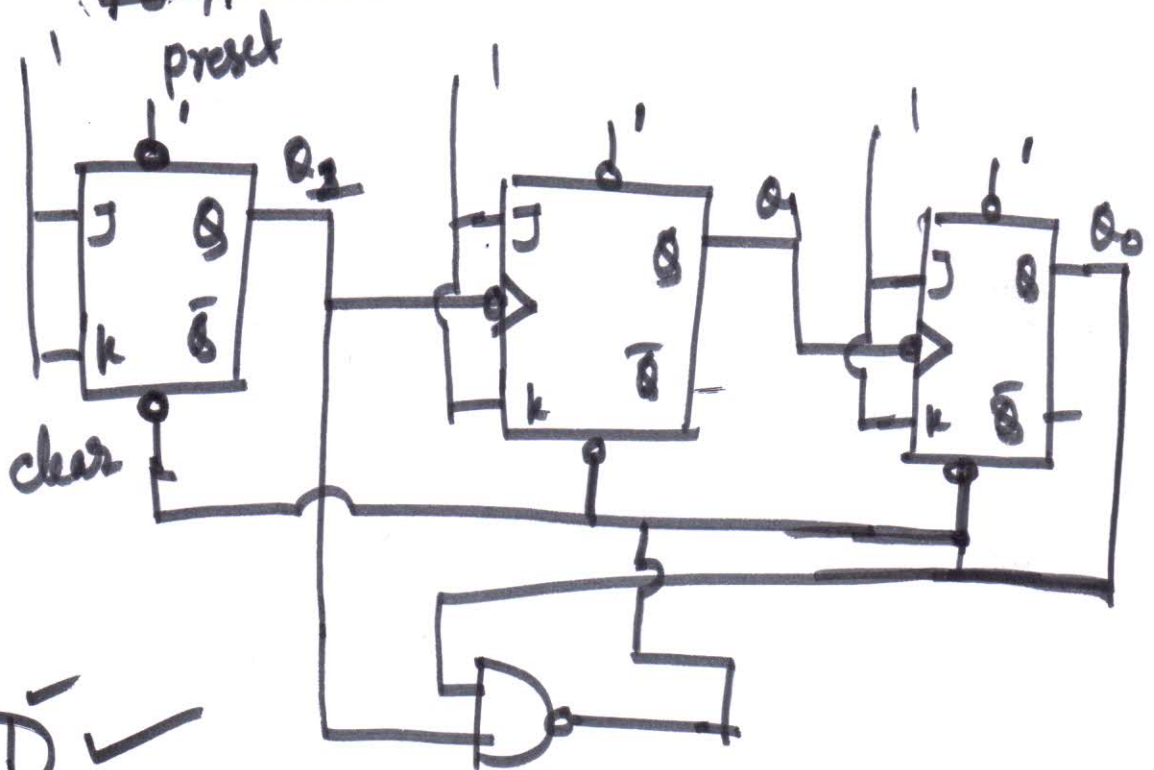
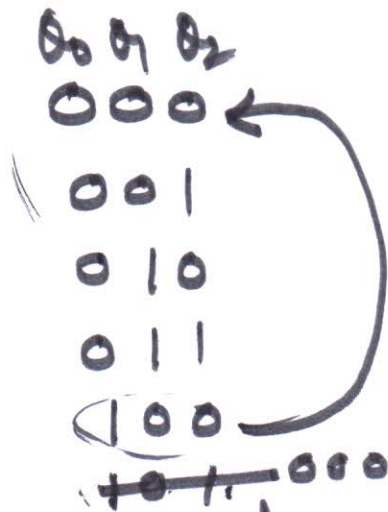


101 ✓

111 ✓

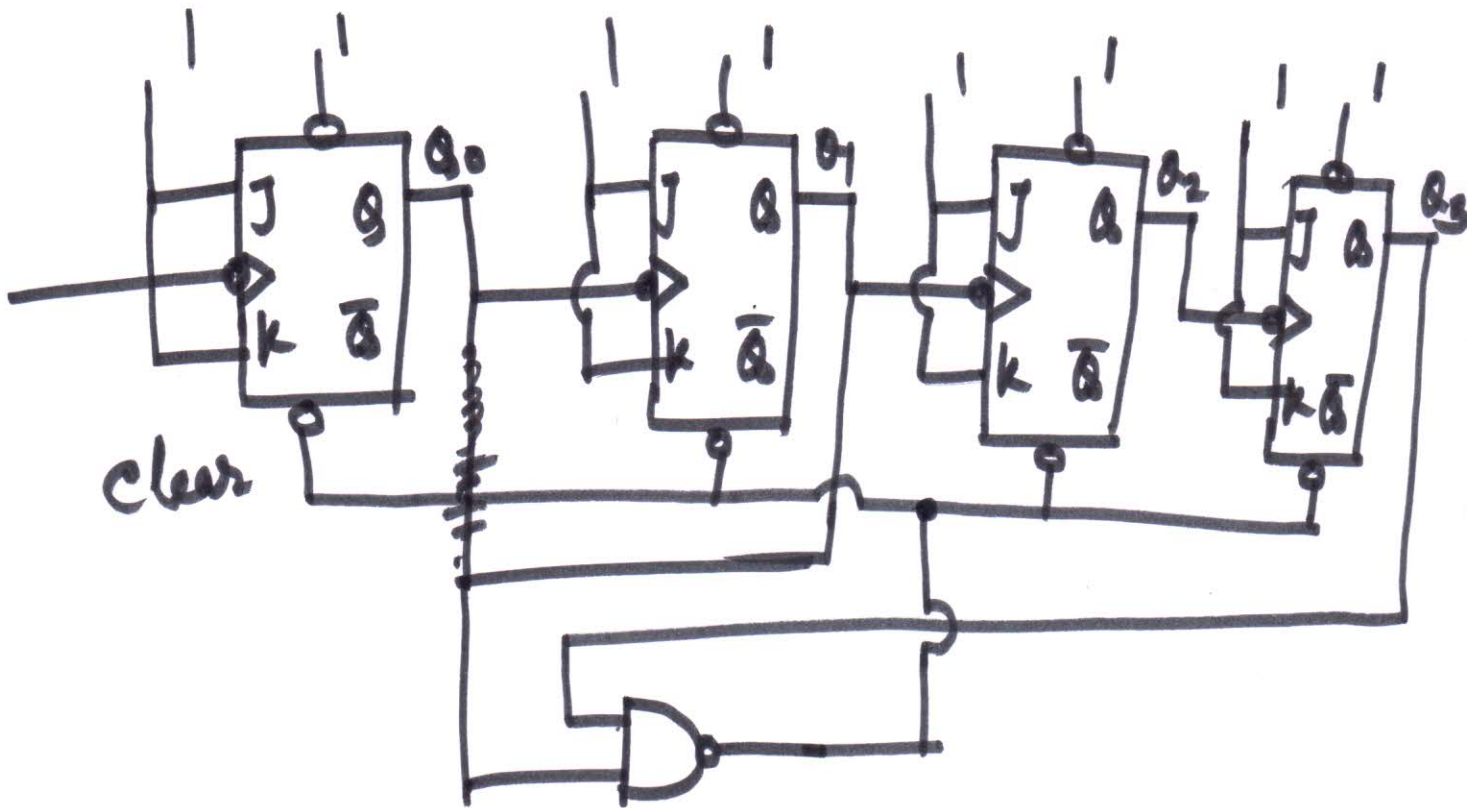
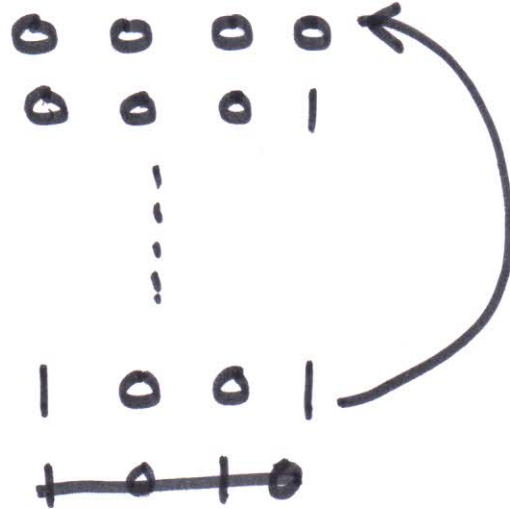
# BCD Decade Ripple Counter:

(MSB)  $Q_3$   $Q_2$   $Q_1$   $Q_0$  (LSB)







ex

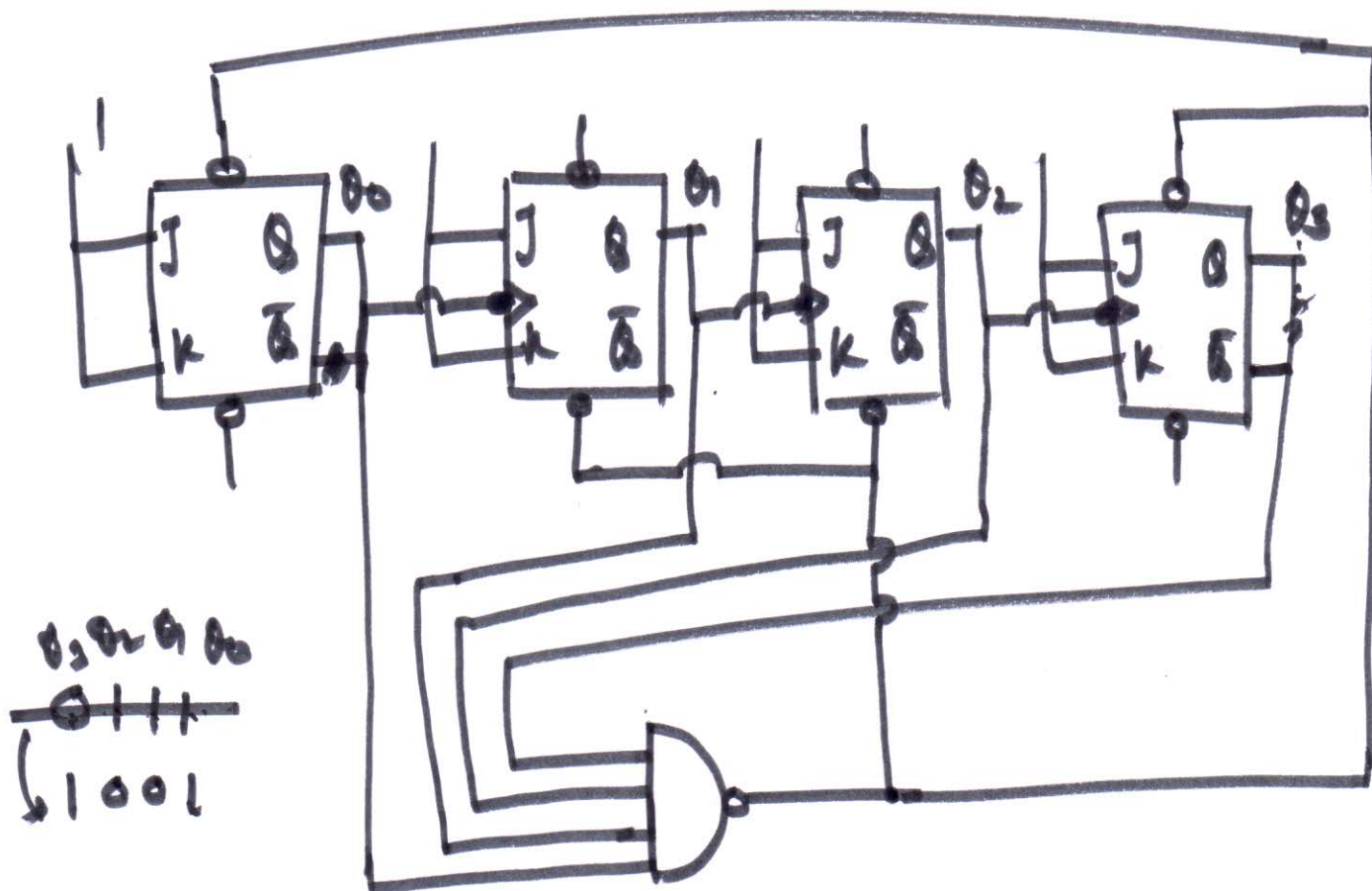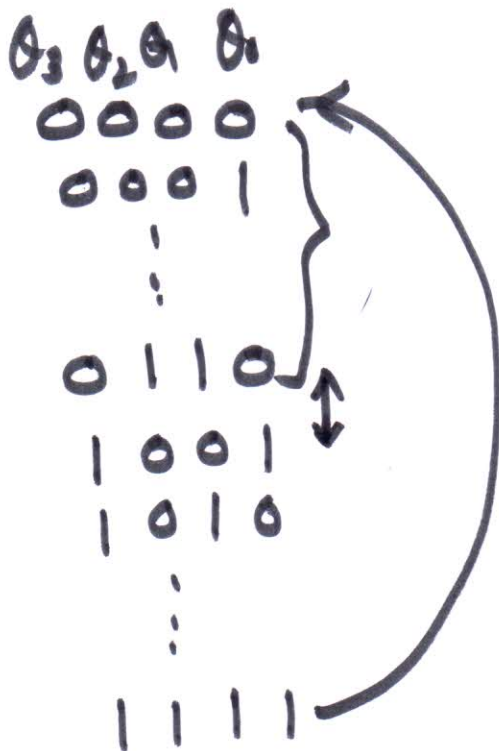


# MOD- $2^N$ DOWN Ripple Counter:

$N=4$

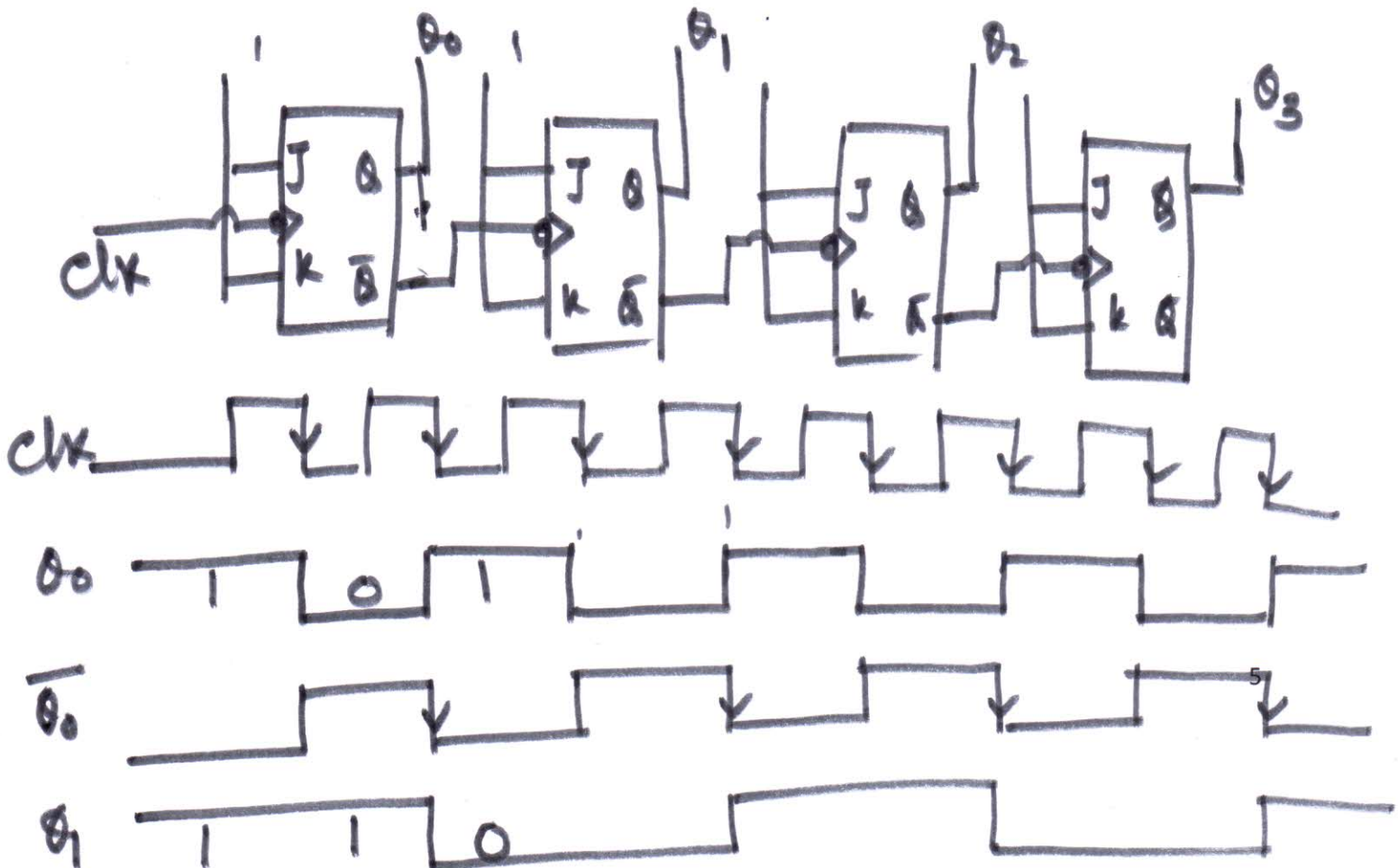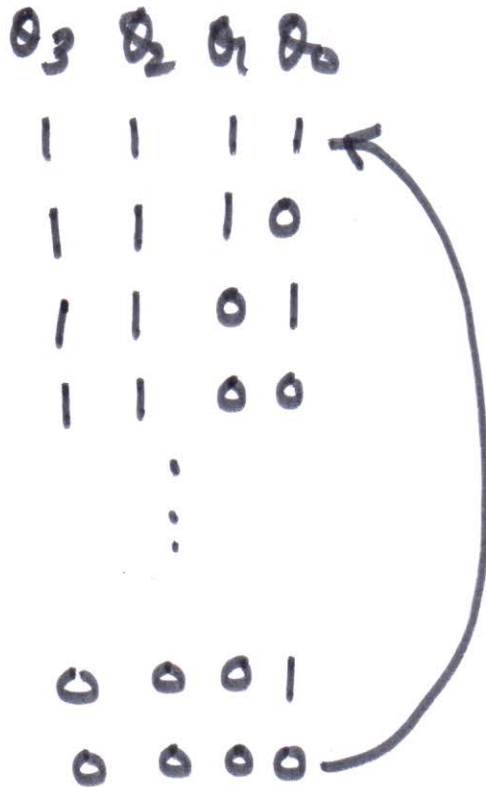



# Asynchronous Up/Down Counter:

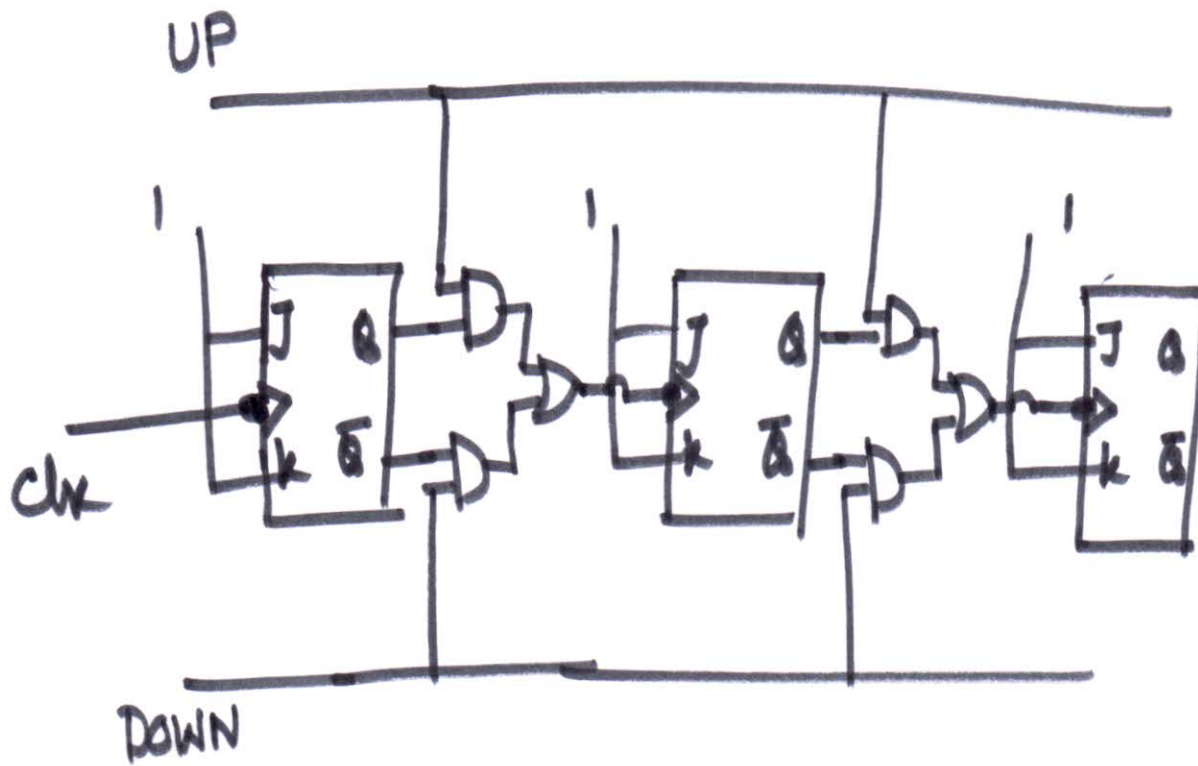

Synchronous Counters:

MOD-8 Synchronous Counter:

$$2^N = 8 \Rightarrow N = 3$$

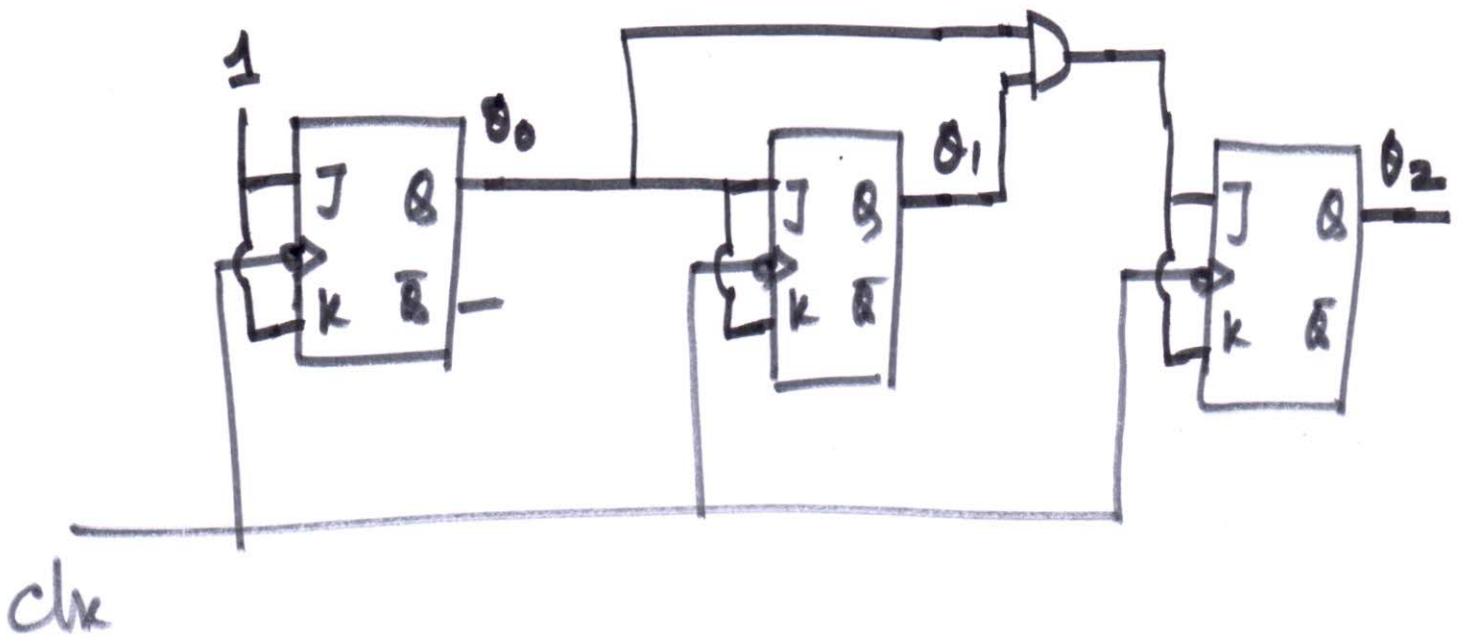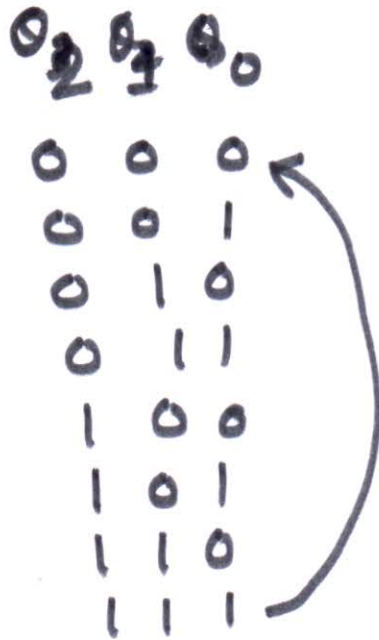



Present State			Next state			V/p					
$Q_2$	$Q_1$	$Q_0$	$Q_2^+$	$Q_1^+$	$Q_0^+$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	0	0	0	1	0	x	0	x	1	x
0	0	1	0	1	0	0	x	1	x	x	1
0	1	0	0	1	1	0	x	x	0	1	x
0	1	1	1	0	0	1	x	x	1	x	1
1	0	0	1	0	1	x	0	0	x	1	x
1	0	1	1	0	0	x	0	1	x	1	x
1	1	0	1	1	1	x	0	x	0	1	x
1	1	1	0	1	0	x	1	x	1	x	1

Present State	Next State		
$Q$	$Q^+$	$J$	$K$
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

000

100

010

000

J<sub>0</sub>

$\theta_2 \theta_1$ \ $\theta_0$	0	1
00	1	x
01	1	x
11	1	x
10	1	x

$$J_1 = 1$$

K<sub>0</sub>

$\theta_2 \theta_1$ \ $\theta_0$	0	1
00	x	1
01	x	1
11	x	1
10	x	1

$$K_0 = 1$$

J<sub>1</sub>

$\theta_2 \theta_1$ \ $\theta_0$	0	1
00		1
01	x	x
11	x	x
10		1

$$J_1 = \theta_0$$

K<sub>1</sub>

$\theta_2 \theta_1$ \ $\theta_0$	0	1
00	x	x
01		1
11		1
10	x	x

$$K_1 = \theta_0$$


J<sub>2</sub>

$$J_2 = \theta_1 \theta_0$$

$$K_2 = \theta_1 \theta_0$$

Counter with an arbitrary sequence:

ex


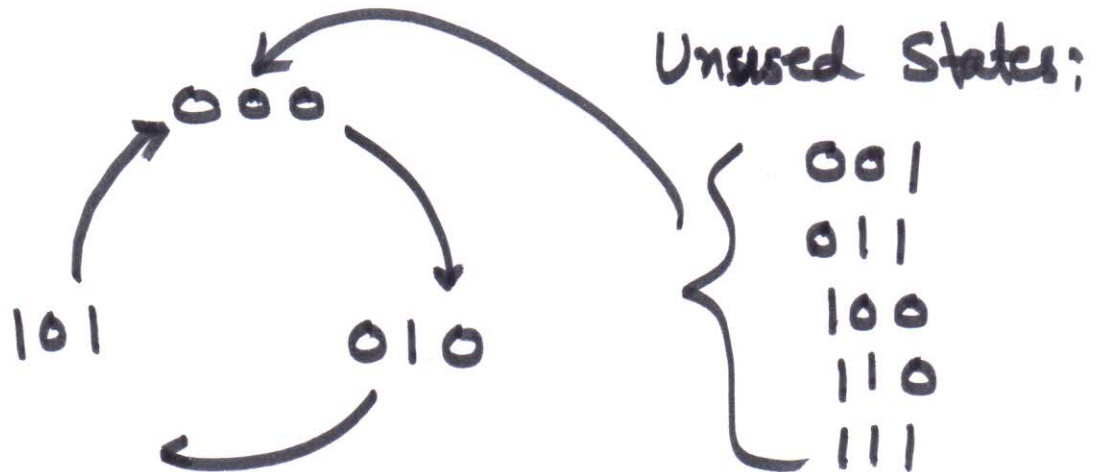


Present State			Next States			1/p					
$Q_2$	$Q_1$	$Q_0$	$Q_2^+$	$Q_1^+$	$Q_0^+$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	0	0	1	0						
0	0	1	0	0	0						
0	1	0	1	0	1						
0	1	1	0	0	0						
1	0	0	0	0	0						
1	0	1	0	0	0						
1	1	0	0	0	0						
1	1	1	0	0	0						

If unused states are ignored.


[illegible]

# Shift Register:

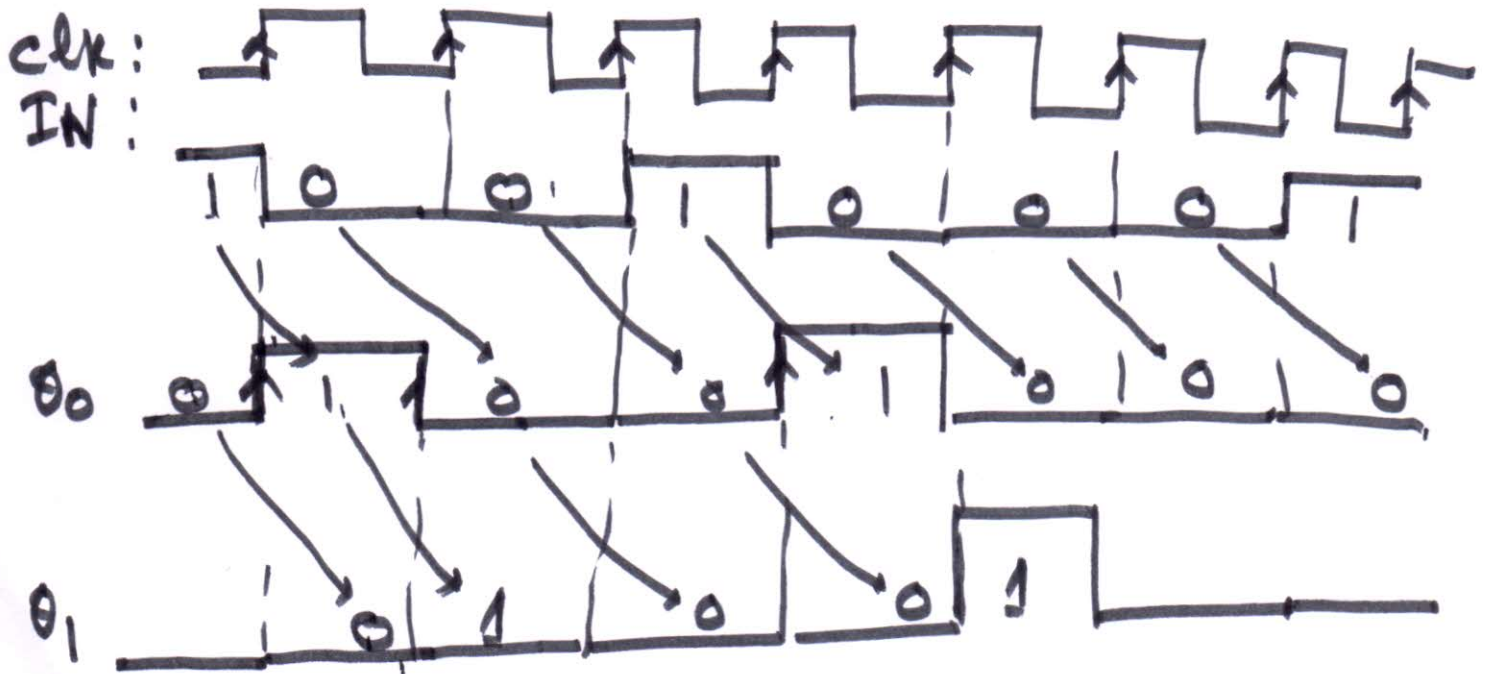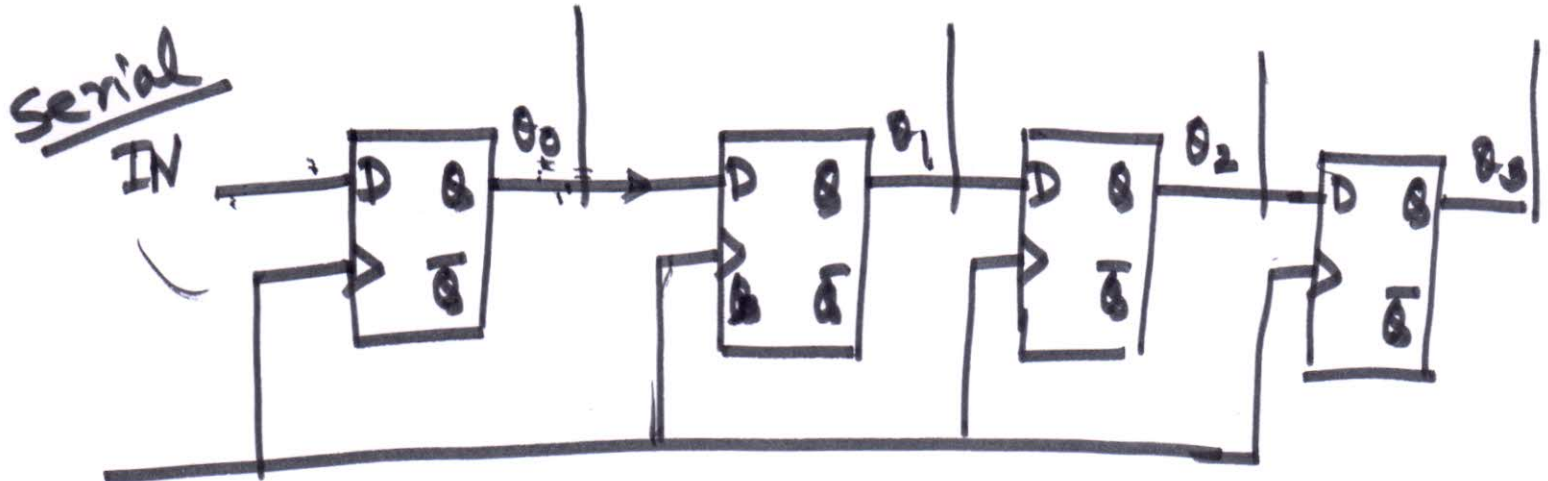



$Q_2$

$Q_3$

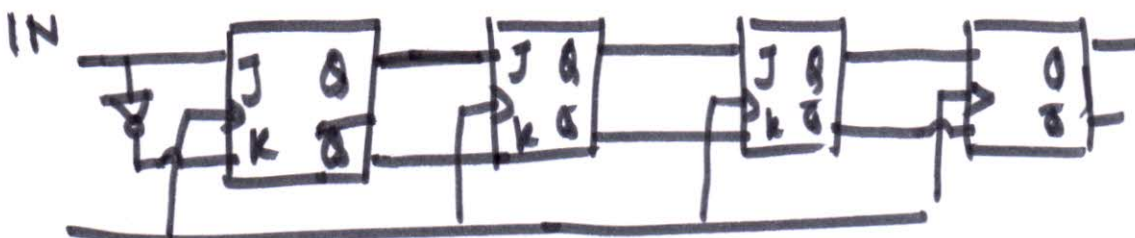




# Ring Counter:

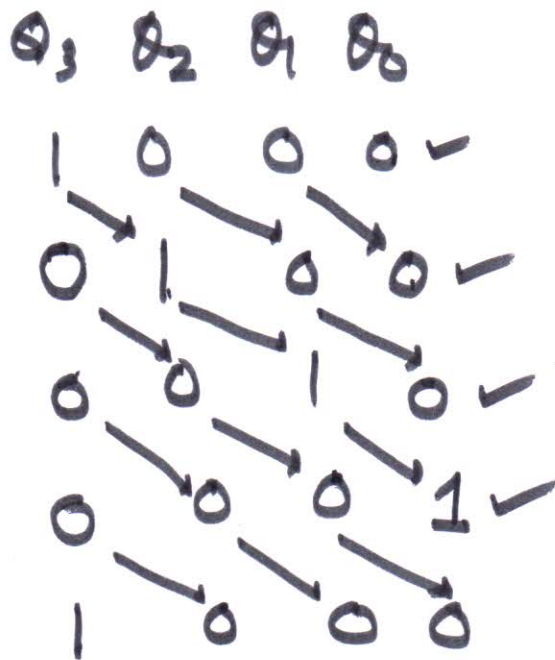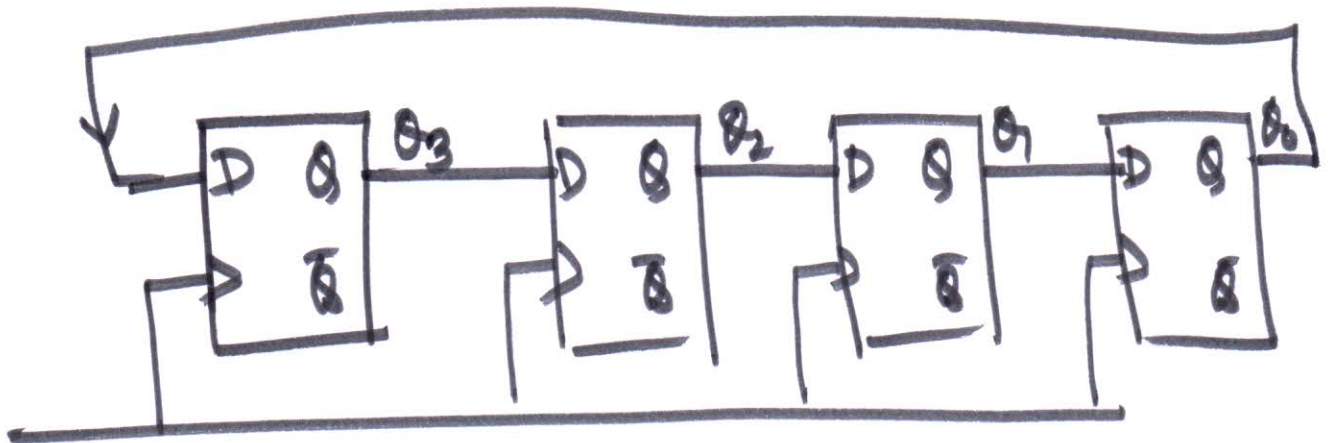

MOD - 4

# Johnson Counter:

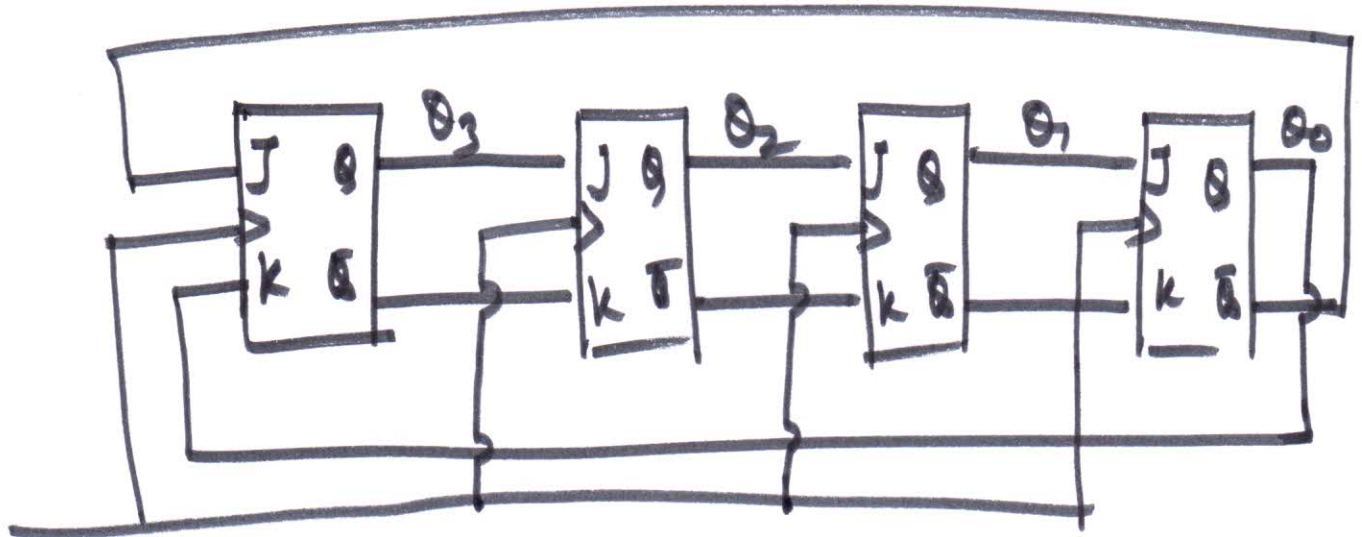

$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1
0	0	0	0

MOD-8

for N-FF  $\rightarrow$  MOD-2N