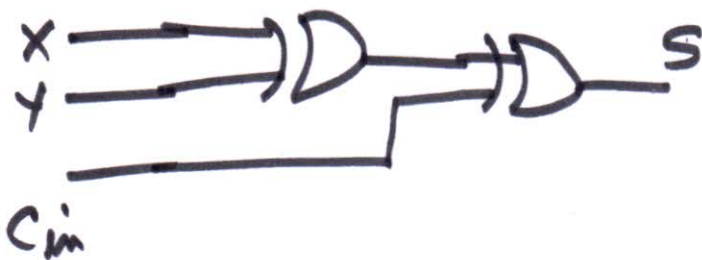


2. Full Adder

Inputs			Output	
X	Y	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

S

	Y C _{in}			
X	00	01	11	10
0		1		1
1	1		1	



$$S = \underline{X\bar{Y}\bar{C}_{in}} + \underline{\bar{X}\bar{Y}C_{in}} + \underline{XYC_{in}} + \underline{\bar{X}Y\bar{C}_{in}}$$

$$= \bar{Y}(\underline{X\bar{C}_{in}} + \underline{\bar{X}C_{in}}) + Y(\underline{XC_{in}} + \underline{\bar{X}\bar{C}_{in}})$$

$$= \bar{Y}(X \oplus C_{in}) + Y \overline{(X \oplus C_{in})}$$

$$= Y \oplus X \oplus C_{in}$$



Full Adder (Cont.)

Count

	$y C_{in}$	00	01	11	10
x	0			1	
	1		1	1	1

xy

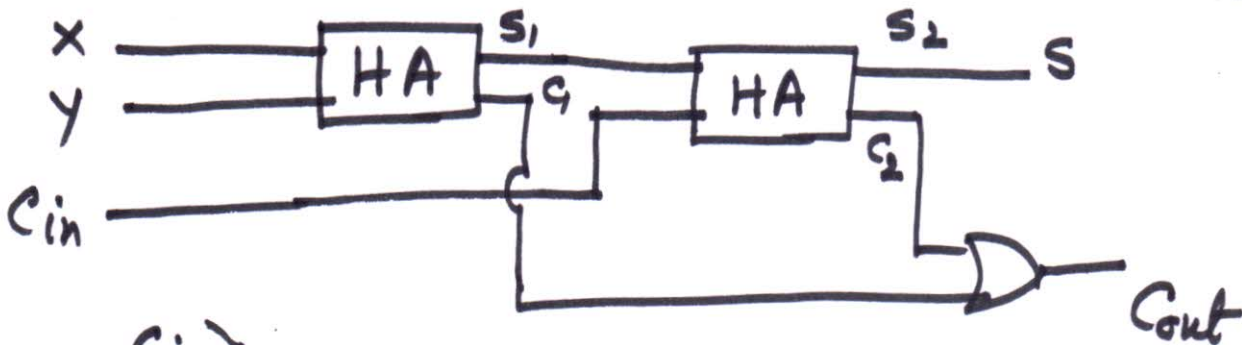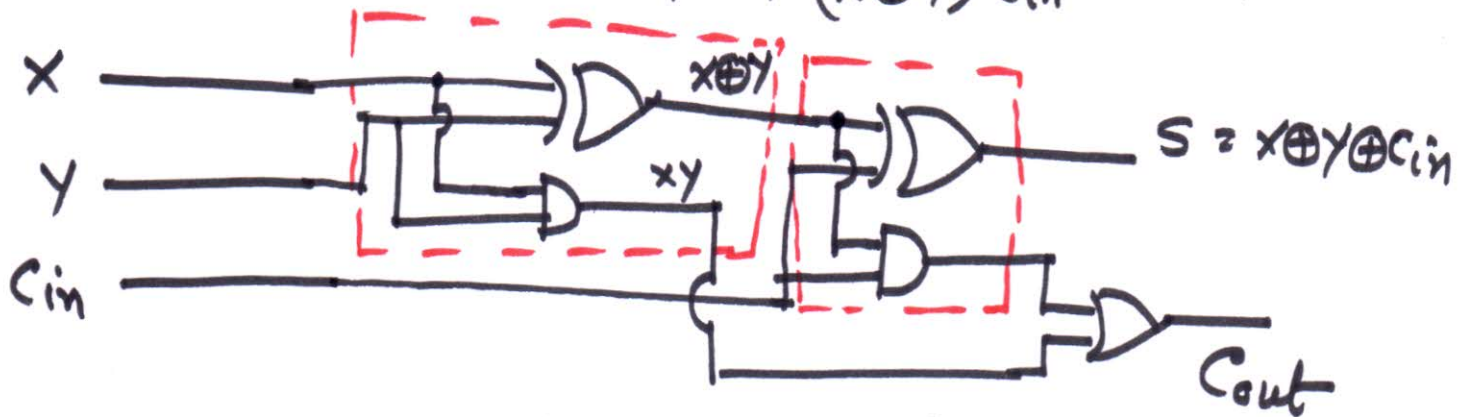
$$\begin{aligned}
 C_{out} &= xy + \bar{x}yC_{in} + x\bar{y}C_{in} \\
 &= xy + (\bar{x}y + x\bar{y})C_{in} \\
 &= xy + (x \oplus y)C_{in}
 \end{aligned}$$



$$\begin{array}{r}
 C_{in} \\
 + X \\
 + Y \\
 \hline
 \end{array}
 \begin{array}{l}
 \\
 S \\
 S \\
 \end{array}$$

Full Adder with NAND Gates:


XOR $Z = x \oplus y$

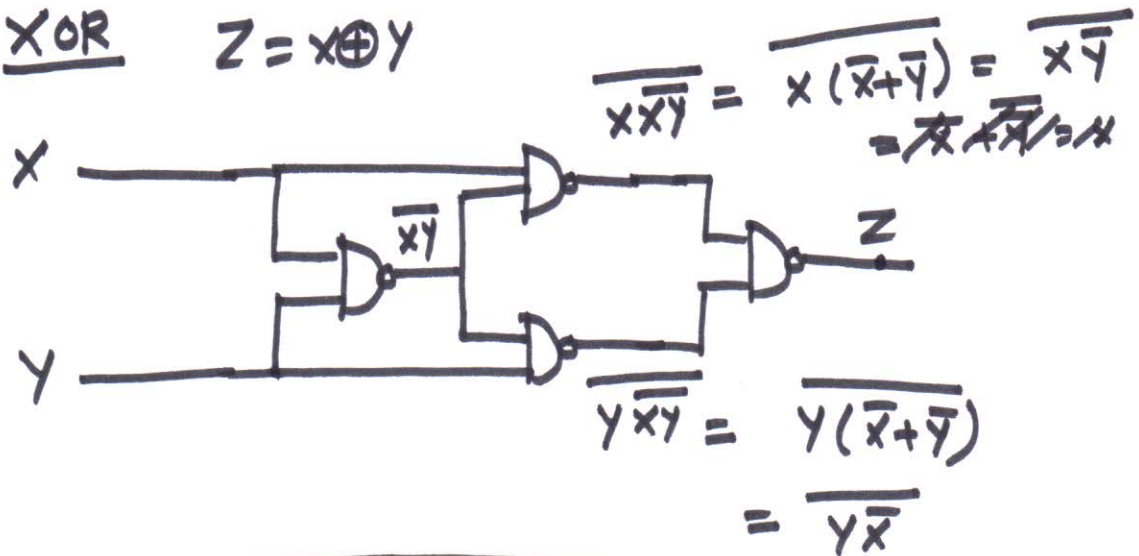


$$Z = \overline{\overline{xy} \cdot \overline{y\bar{x}}}$$

$$= \overline{\overline{xy}} + \overline{\overline{y\bar{x}}}$$



$$= x\bar{y} + y\bar{x} = x \oplus y$$

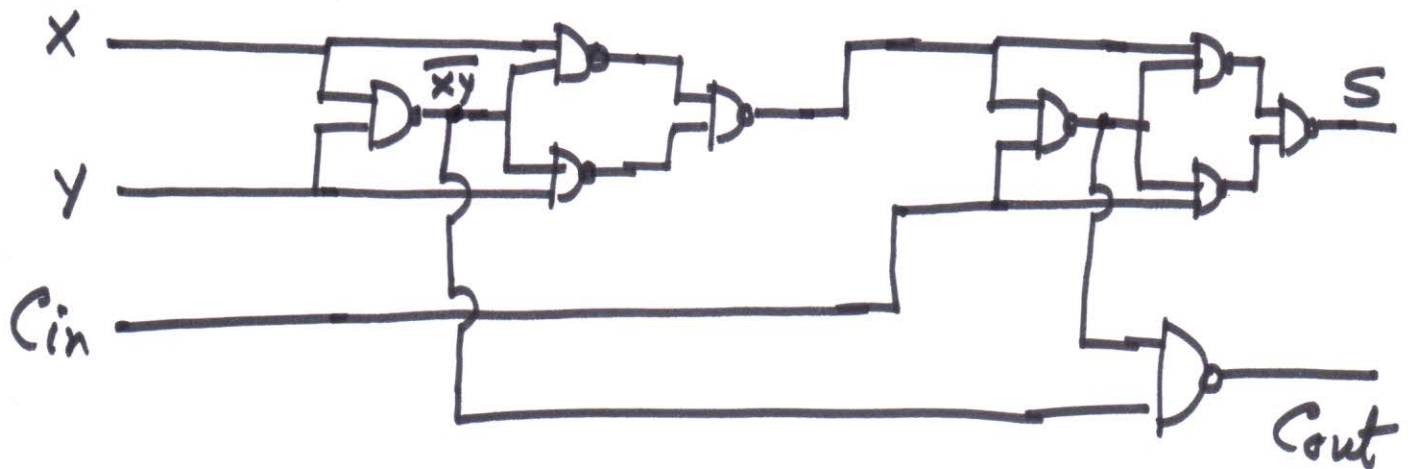

3. Binary Ripple Carry Adder:

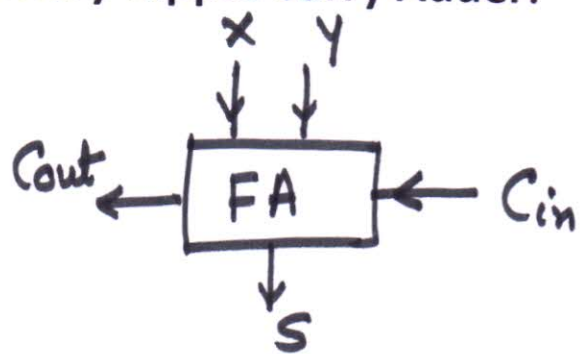
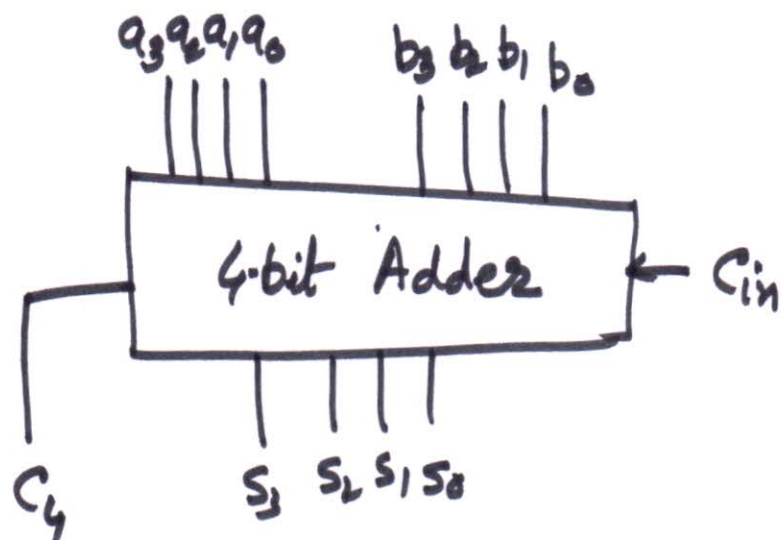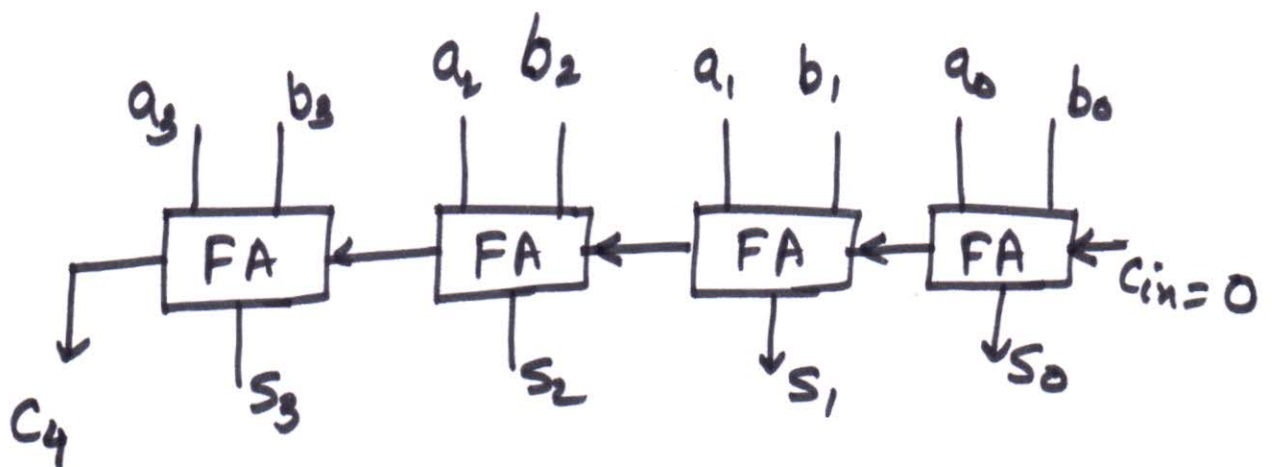
$$\begin{array}{r} a_3 a_2 a_1 a_0 \\ + b_3 b_2 b_1 b_0 \\ \hline \end{array}$$



Binary Subtractor :

1. Half Subtractor


Inputs		Outputs	
X	Y	B	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

D: Difference (X-Y)

B: Borrow

$$D = X \oplus Y$$

$$B = \overline{X}Y$$

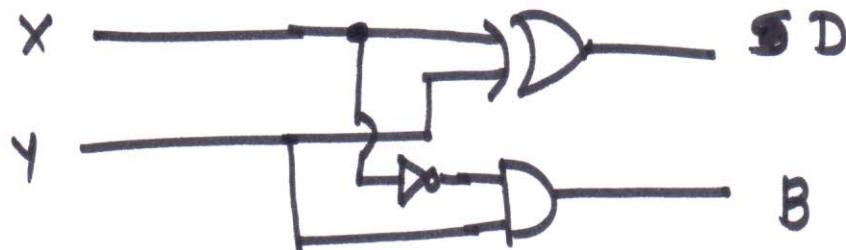

4. Full Subtractor

Inputs			Output	
X	Y	B _{in}	B _{out}	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$X - Y - B_{in}$

D

X \ Y B _{in}	00	01	11	10
0		1		1
1	1		1	

$$D = X \oplus Y \oplus B_{in}$$

B_{out}

X \ Y B _{in}	00	01	11	10
0		1	1	1
1			1	



$\bar{X}Y$

$$\begin{aligned}
 B_{out} &= \bar{X}Y + \bar{X}\bar{Y}B_{in} + XYB_{in} \\
 &= \bar{X}Y + (\bar{X}\bar{Y} + XY)B_{in} \\
 &= \bar{X}Y + \overline{X \oplus Y} B_{in}
 \end{aligned}$$

Adder-Subtractor:

Subtraction of two numbers can be accomplished by adding 2's complement of the subtrahend to the minuend and disregarding the final carry, if any.

Controlled inverter-

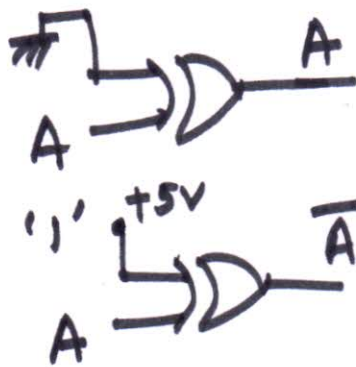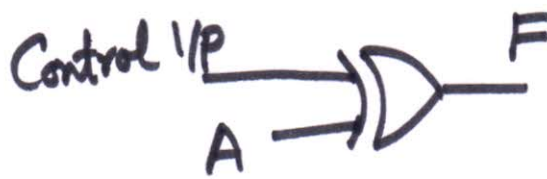

$$\begin{array}{r} a_3 a_2 a_1 a_0 \\ \pm b_3 b_2 b_1 b_0 \end{array}$$

Control 1/p	A	F
{ 0	0	0
	1	1
{ 1	0	1
	1	0

