

Problems on Feedback in Amplifiers

①

7.1

$A = \text{Basic Amplifier Gain} = 10^5$

$A_f = \text{Gain with feedback} = 100$

(i) what is feedback factor β ?

(ii) If A falls to 10^3 , what is new A_f ?

$$A_f = \frac{A}{1 + A\beta} = \frac{10^5}{1 + 10^5 \cdot \beta} = 10^2$$

Find β .

$$\frac{100000}{1 + 100000\beta} = 100$$

$$\therefore 1 + 100000\beta = 1000$$

$$100000\beta = 999$$

$$\therefore \beta = 9.99 \times 10^{-3}$$


$$A_f \text{ at } A = 1000 = \frac{A}{1 + A\beta} = \frac{1000}{1 + 1000 \times 9.99 \times 10^{-3}}$$

$$= \frac{1000}{1 + 0.999 \times 10} = \frac{1000}{\cancel{1.999} \cancel{1.999} 10.999} = 90.99$$

$$\frac{\Delta A_f}{A_f} = \frac{90.99 - 100}{100} = -9\% \text{ for a very large change in } A.$$

7.14

(2)

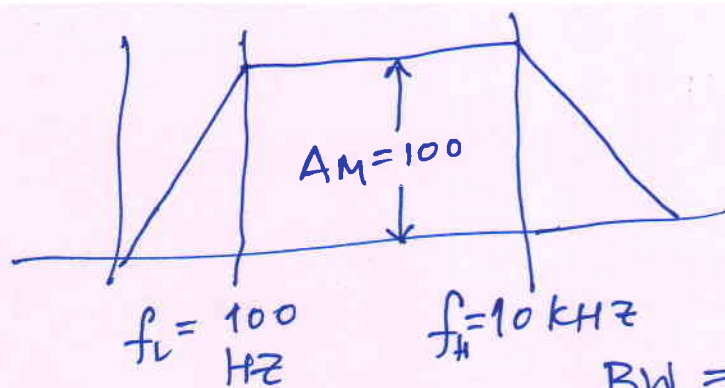Before $F/B = 100$.

$$BW = 10\text{kHz} - 100\text{Hz} = 9900\text{Hz}$$

$$\text{Feedback} = 10$$

Midband gain after negative feedback is applied.
What are f'_{Lf} and f'_{Hf} after feedback is applied.

$$A_{Mf} = \frac{A_M}{1 + A_M \beta}$$

$$\omega_{Hf} = \omega_H (1 + A_M \beta) \quad \text{--- high freq. extended}$$

$$\omega_{Lf} = \frac{\omega_L}{(1 + A_M \beta)} \quad \text{--- lower cutoff freq. reduced to extend BW.}$$

$$10 = \frac{100}{1 + 100 \cdot \beta}$$

$$1 + 100 \cdot \beta = 10$$

$$100 \cdot \beta = 9$$

$$\therefore \beta = \frac{9}{100}$$

$$D = 1 + A\beta = \frac{100}{10} = 10$$

$$\therefore \omega_{Hf} = 10\text{kHz} \times D = 10 \times 10 = 100\text{kHz}$$


$$\omega_{Lf} = \frac{100\text{Hz}}{D} = \frac{100}{10} = 10\text{Hz}$$

$$= \underline{100000 - 10\text{Hz}}$$

Q: 7.21

SERIES - SHUNT F/B

3

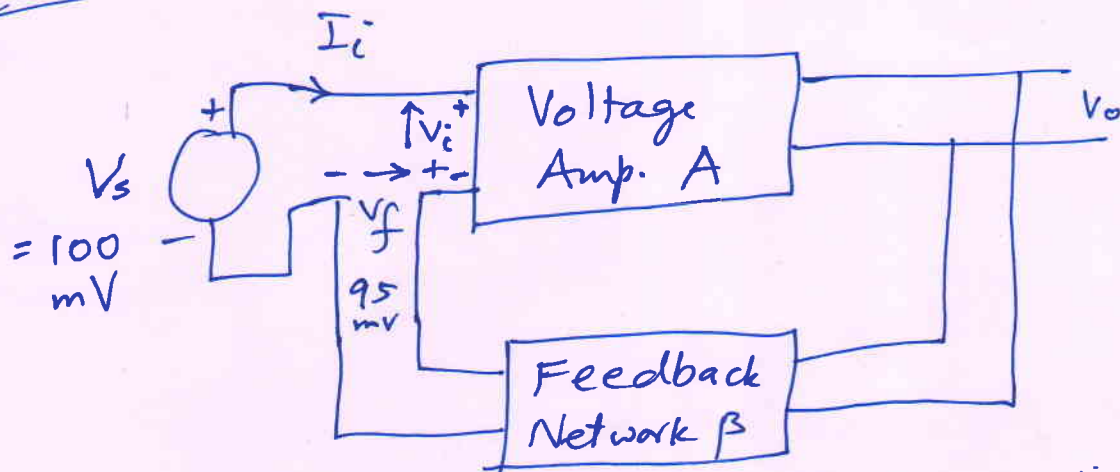

$$V_s = 100 \text{ mV} ; V_f = 95 \text{ mV} ; V_o = 10 \text{ V}$$

What are values of A & β ?

$$V_i = V_s - V_f = 100 - 95 \text{ mV} = 5 \text{ mV}$$

$$V_o = 10 \text{ V} = 10000 \text{ mV}$$


$$\therefore \text{Voltage Gain } A = \frac{V_o}{V_i} = \frac{10000 \text{ mV}}{5 \text{ mV}}$$

$$= \boxed{2000 \text{ V/V}}$$

$$\beta = \frac{V_f}{V_o} = \frac{95 \text{ mV}}{10000 \text{ mV}} = \boxed{0.0095 \text{ V/V}}$$

————— X —————

Q: 7.22

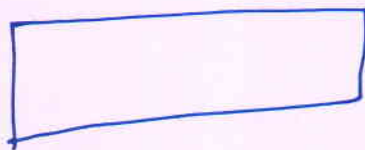


—————>
Next Page

SHUNT-SERIES

Q: 7.22

(4)

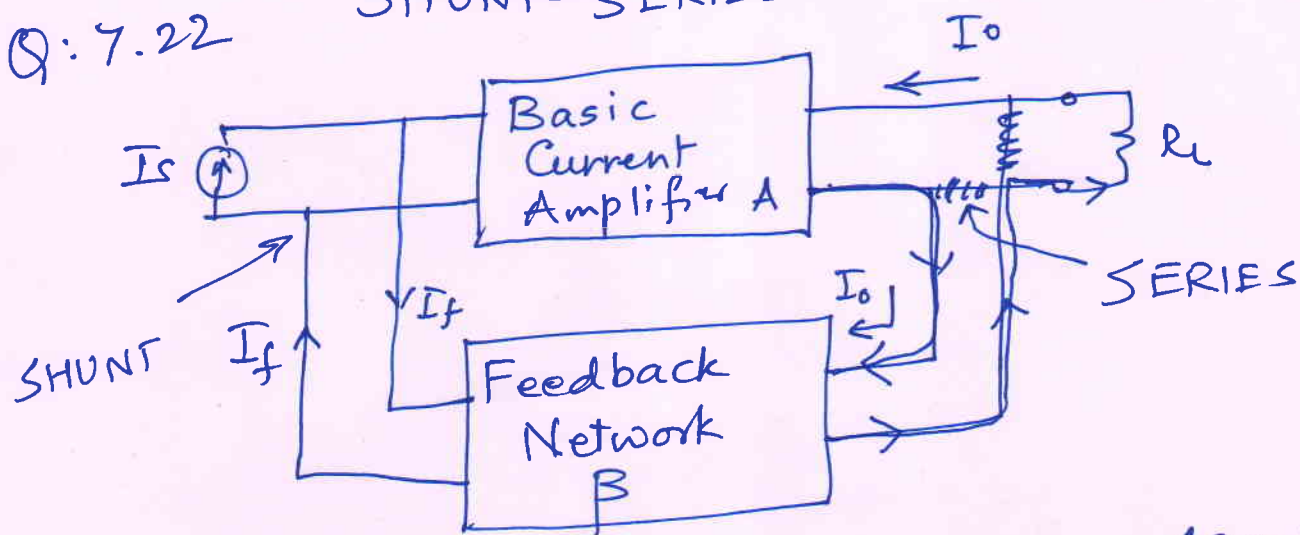

$$I_s = 100 \mu A \quad I_f = 95 \mu A \quad I_o = 10 \text{ mA}$$

Find A & β and mention their units

$$\text{Current Gain of Amplifier} = \frac{\text{Output Current}}{\text{Input Current}}$$

$$= \frac{I_o}{I_s - I_f} = \frac{10 \text{ mA}}{(100 - 95) \mu A}$$


$$= \frac{10,000 \mu A}{5 \mu A} = \boxed{2000 \mu A / \mu A}$$

$$\beta = \frac{I_f}{I_o} = \frac{\cancel{10000 \mu A} \cdot 95 \mu A}{10000 \mu A}$$

$$= \frac{0.095 \text{ mA}}{10 \text{ mA}} = \boxed{0.0095 \text{ mA} / \text{mA}}$$

Q: 7.24

5

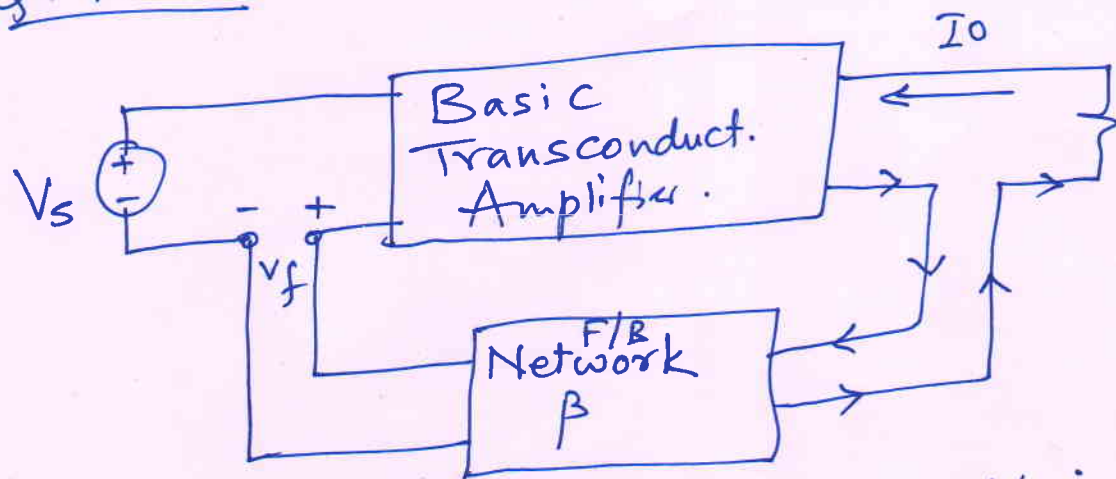

$V_s = 100 \text{ mV}$; $V_f = 95 \text{ mV}$; $I_o = 10 \text{ mA}$
Find A & β and their units.

$$V_i = V_s - V_f = 100 - 95 = 5 \text{ mV}$$

$$A = \text{Transconductance} = \frac{I_o}{V_i} = \frac{10 \text{ mA}}{5 \text{ mV}} = 2 \text{ v}$$

$$= 2 \text{ mhos}$$


$$= 2 \text{ Amps/Volts}$$

$$= 2000 \text{ mV}$$

$$\beta = \frac{V_f}{I_o} = \frac{95 \text{ mV}}{10 \text{ mA}} = 9.5 \text{ ohms}$$

7:27

Series Shunt F/B Amplifier

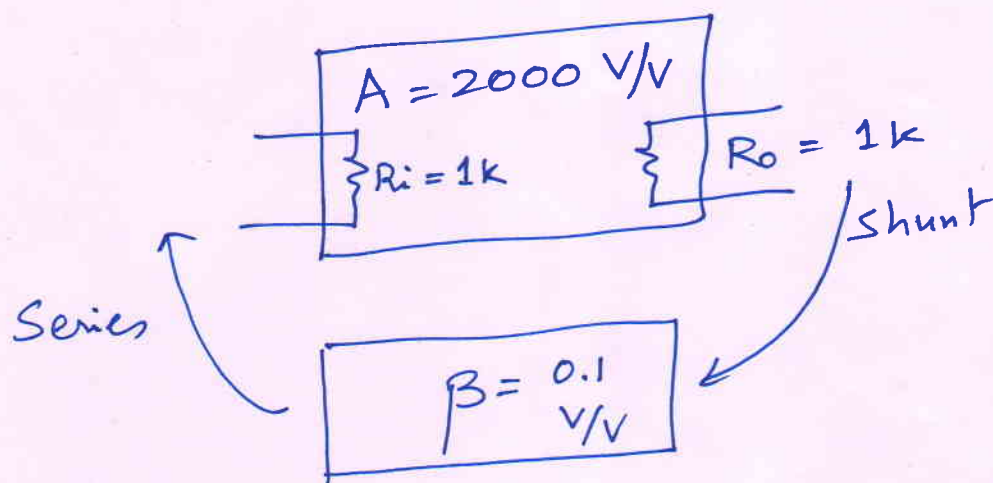

Find A_f , R_{if} and R_{of} .

$$D = 1 + A\beta = 1 + 2000 \times 0.1 = 1 + 200 = 201$$

$$R_{if} = R_i \cdot D = 1\text{k} \times 201 = \boxed{201\text{k}}$$

$$R_{of} = R_o / D = 1\text{k} / 201 \approx 5 \Omega$$

$$A_f = A / D = 2000 / 201 = \boxed{9.95 \text{ V/V}}$$


Gain A_f from approx. formula for validating

$$A_{f \text{ approx}} = \frac{1}{\beta} = \frac{1}{0.1} = 10 \text{ V/V.}$$

The approx. value is pretty close to calculated gain 9.95 \therefore our calculations are right!

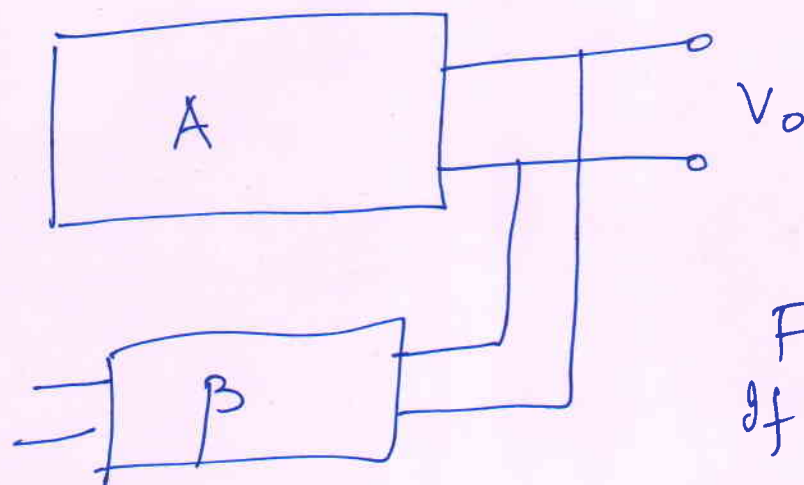Q: 7:28

In Feedback loop, output voltage is Sampled.



Find $A\beta$.
If $R_{of} = 100$, find R_o .

Ratio of R_o after feedback / R_o before feedback = $\frac{1}{80}$

Note that since we are sampling output VOLTAGE, β network will tap 2 points at V_o or $O-O'$, in shunt with R_L or output. This will LOWER output resistance AFTER feedback

$$\therefore \frac{R_{of}}{R_o} = \frac{1}{80} =$$

$$\therefore R_{of} = \frac{R_o}{D} \quad \therefore \boxed{D = 80}$$

$$D = 1 + A\beta = 80 \quad \therefore \boxed{A\beta = 79 = \text{Loop Gain}}$$

$$R_o = R_{of} \cdot D = 100 \times 80 = \boxed{8K}$$