
EXPERIMENT

PHASOR ANALYSIS FOR DIFFERENT

R-L-C CIRCUITS

TASKS

1. R-C Series

- a. Implement the circuit shown in figure 1 on **Breadboard**.

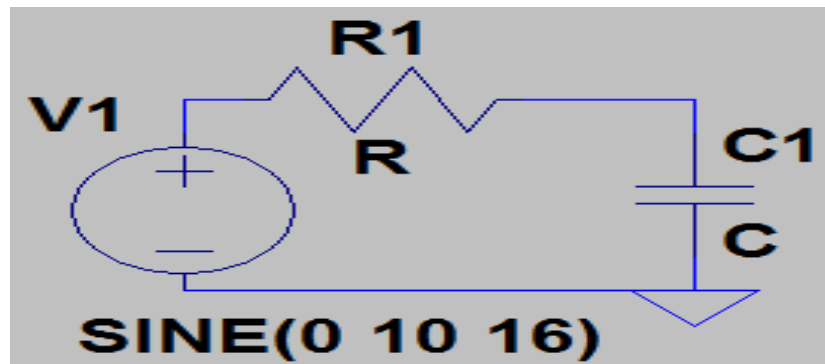


Figure 1.

- b. Case I ($R = (1/X_C)$)
Set $R = 10k$ and $C = 1\mu F$.
Measure V_R, V_C, I_R and I_C using CRO. Express the before said voltages and currents as phasors with respect to the input voltage V_1 .
- c. Case II ($R > (1/X_C)$)
Set $R = 33k$ and $C = 1\mu F$.
Measure V_R, V_C, I_R and I_C using CRO. Express the before said voltages and currents as phasors with respect to the input voltage V_1 .
- d. Case III ($R < (1/X_C)$)
Set $R = 1k$ and $C = 1\mu F$.
Measure V_R, V_C, I_R and I_C using CRO. Express the before said voltages and currents as phasors with respect to the input voltage V_1 .
- e. Implement the circuit shown in figure 1 in **LTSpice** and repeat steps 1(b),(c) and(d).
- f. Do the **hand analysis** for the circuit shown in figure 1 and perform steps 1(b),(c) and(d).

2. R-C parallel

- a. Implement the circuit shown in figure 2 on **Breadboard**.

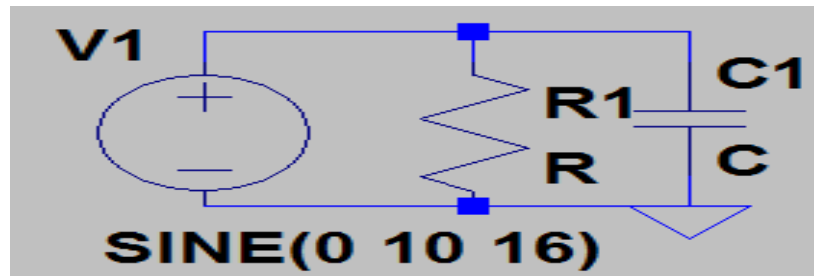


Figure 2.

- b. Set $R=10k$ and $C=1\mu F$.
- c. Measure V_R, V_C, I_R and I_C using CRO. Express the before said voltages and currents as phasors with respect to the input voltage V1.
- d. Implement the circuit shown in figure 2 in **LTSpice** and repeat steps 2(c).
- e. Do the **hand analysis** for the circuit shown in figure 2 and perform steps 2(c).

3. R-L Series

- a. Implement the circuit shown in figure 3 in **LTSpice**.

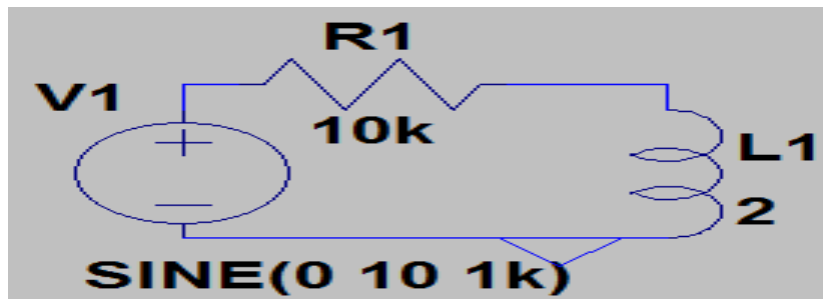


Figure3

- b. Measure V_R, V_C, I_R and I_C . Express the before said voltages and currents as phasors with respect to the input voltage V1.
- c. Do the **hand analysis** for the circuit shown in figure 2 and perform steps 3(b).

4. R-L Parallel

- a. Implement the circuit shown in figure 4 in **LTSpice**.

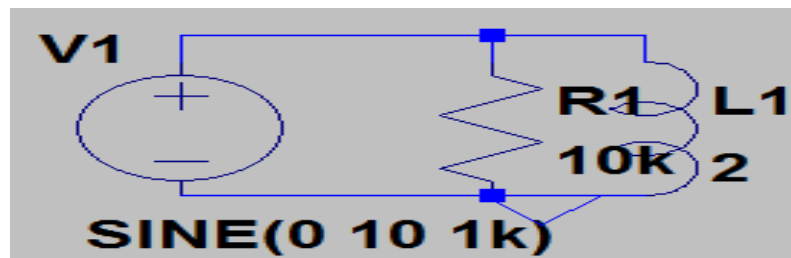


Figure 4

- b. Measure V_R, V_C, I_R and I_C . Express the before said voltages and currents as phasors with respect to the input voltage V_1 .
 - c. Do the **hand analysis** for the circuit shown in figure 4 and perform steps 4(b).
5. Implement the circuit shown in figure 5 on Breadboard.

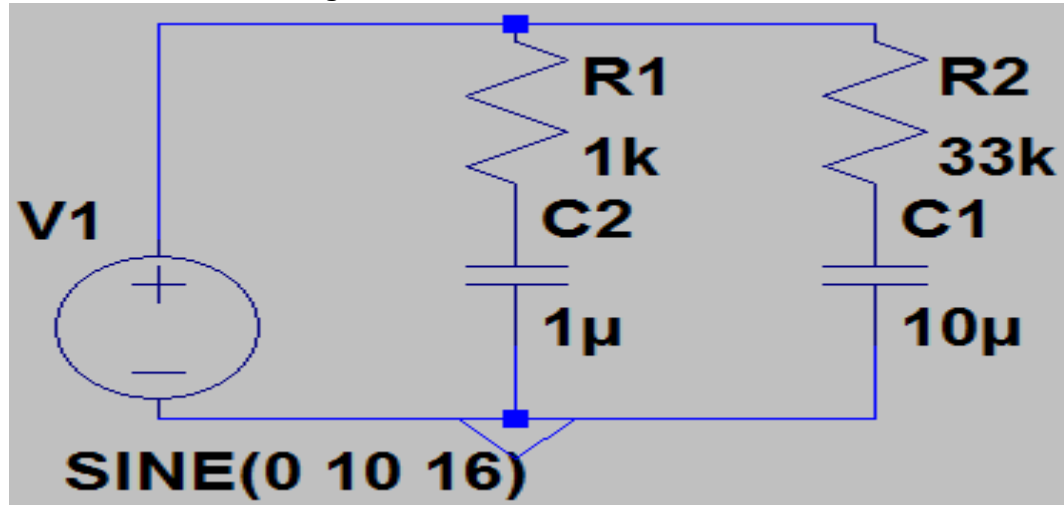


Figure 5

- a. Find out $V_{R1}, V_{R2}, V_{C1}, V_{C2}, I_1$ and I_2 using CRO as phasors with respect to the input voltage V_1 .
 - b. Implement the circuit shown in figure 5 in **LTSpice** and repeat steps 5(a).
 - c. Do the **hand analysis** for the circuit shown in figure 5 and perform steps 5(a).
6. Implement the circuit shown in figure 6 in **LTSpice**.

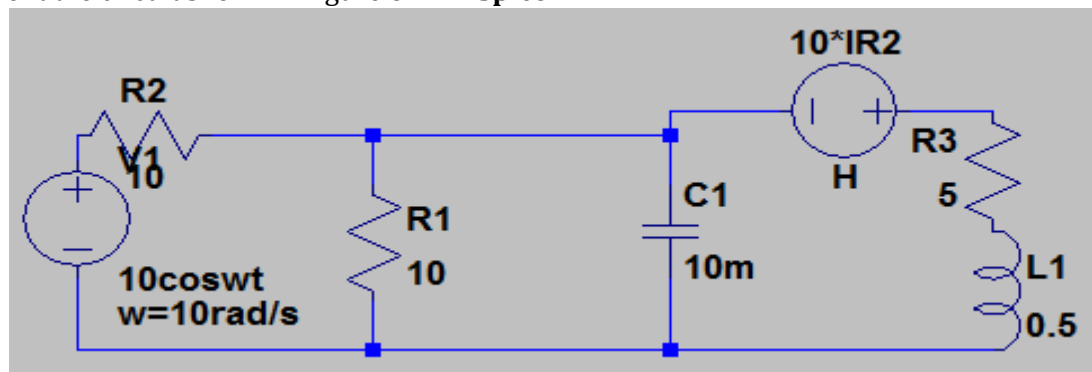


Figure 6

- a. Find voltage across and current through all the components and express them as phasors with respect to the input voltage V_1 .
 - b. Do the **hand analysis** for the circuit shown in figure 6 and perform steps 6(a).

7. Implement the circuit shown in figure 7 in **LTSpice**.

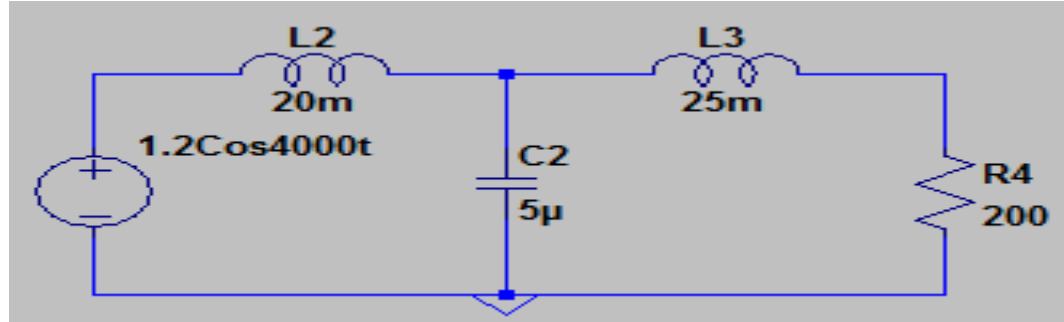


Figure 7

- Find voltage across and current through all the components and express them as phasors with respect to the input voltage $1.2\cos(4000t)$.
- Do the **hand analysis** for the circuit shown in figure 7 and perform steps 6(a).

END
