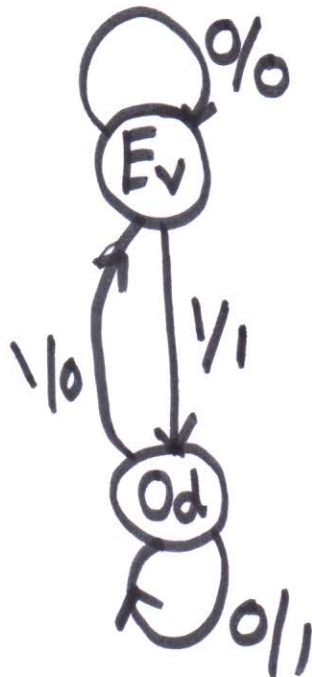


Odd-Even Parity Checker:

1. Using Mealy Machine



State Diagram

Ev : Even state

Od : Odd state

$z = 0$ if sequence is even
 $= 1$ if sequence is odd.

State Transition table


Present States	input		Next states		output	
	$x=0$	$x=1$	$x=0$	$x=1$	$z=0$	$z=1$
Ev	Ev	Od	0	1		
Od	Ev	Od	1	0		

Ev \rightarrow '0'
 Od \rightarrow '1'

Present State q	Input x	Next States q+	Input to FF d	Output z
0	0	0	0	0
0	1	1	1	1
1	0	1	1	1
1	1	0	0	0

$$d = q \oplus x$$


$$z = q \oplus x = d$$

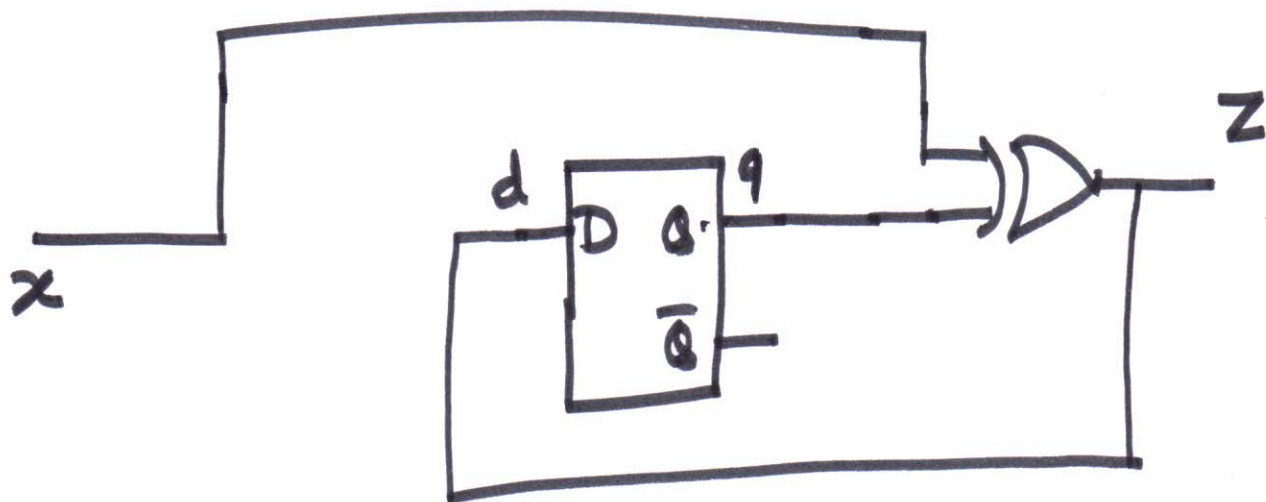

x: 0 1 0 1 0 0 0 1 0 0 1

z: 0 1 1 0 1 1 1 1 0 0

2. Using Moore Machine

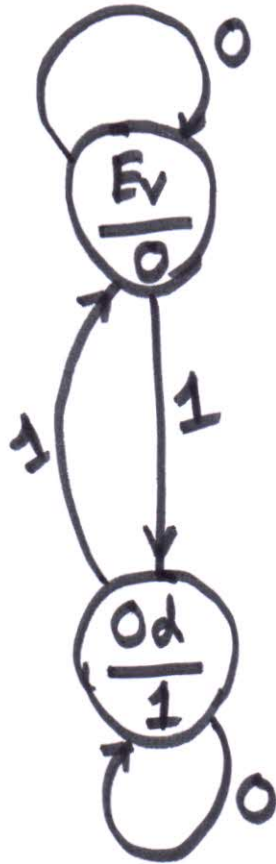

Ev : Even state

Od : Odd state

State Transition Table

Present States	Next states		output
	x=0	x=1	
Ev	Ev	Od	0
Od	Od	Ev	1


Ev → '0'

Od → '1'

Present State (q)	Input (x)	Next state (q')	1/p to FF (d)	output (z)
0	0	0	0	0
0	1	1	1	0
1	0	1	1	1
1	1	0	0	1

$$d = q \oplus x$$

$$z = q$$

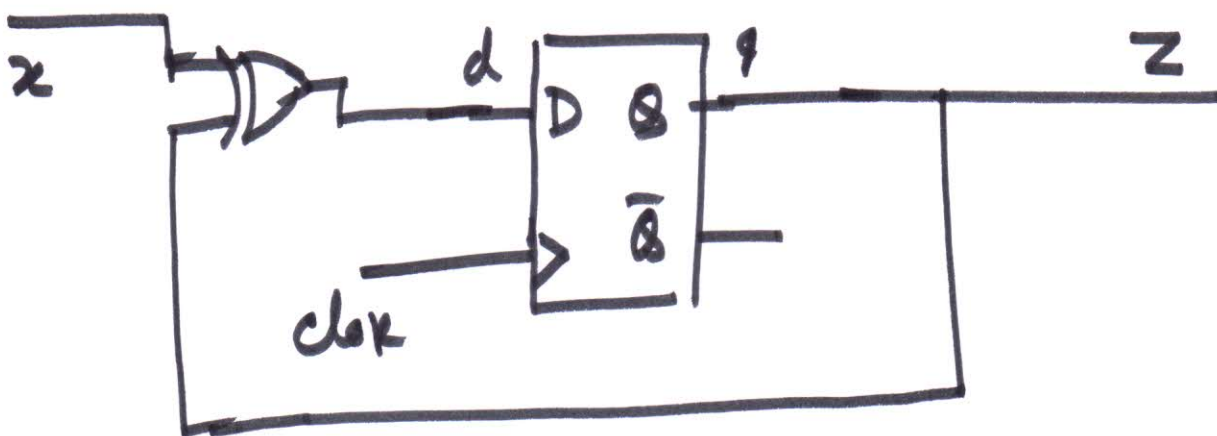


x: 0 1 0 0 1 1 1 0 1 1 0 0

z: 0 0 1 1 1 0 1 0

More examples of Mealy and Moore machines

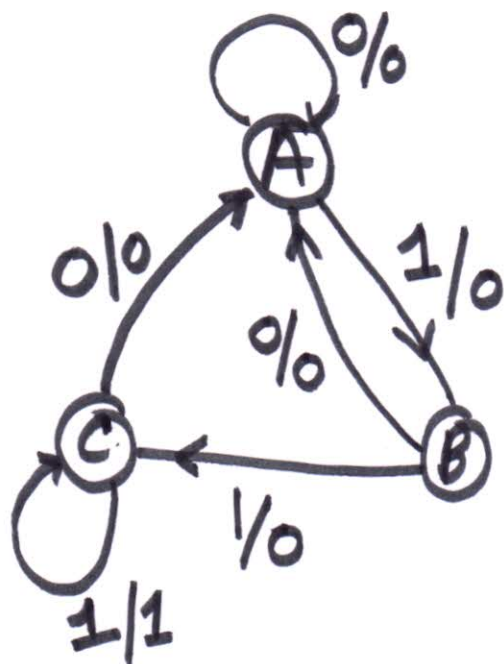1. A Mealy system with one input x and one output z such that $z=1$ iff x has been 1 for three consecutive clock times.



A : no 1's

B : One 1

C : Two ~~1~~ or more 1's

State Transition table

Present States	Next States		Output (z)	
	x=0	x=1	x=0	x=1
A	A	B	0	0
B	A	C	0	0
C	A	C	0	1

A : 0, 0

B : 0 1

C : 1 1

II

Present States		Up (x)	Next States		Flip to FF		Out-put (z)
q_1	q_0		q_1^+	q_0^+	d_1	d_0	
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	0	0	0	0
0	1	1	1	1	1	1	0
1	0	0	x	x	x	x	0
1	0	1	x	x	x	x	0
1	1	0	0	0	0	0	0
1	1	1	1	1	1	1	1

d_1

$q_1, q_0 \backslash x$	0	1
00		
01		1
11		1
10	x	x

d_0

$q_1, q_0 \backslash x$	0	1
00		
01		1
11		1
10	x	x

$$d_1 = q_0 x$$

$$d_0 = x$$

$$z = q_1 q_0 x$$

x: 0 1 0 1 1 1 0 1 1 0 1 1 0

z: 0 0 0 0 0 1 1 0 0 0 0 0 0 1 0