


## Finite State Machine (FSM)

- FSM contains finite number of states where a state specifies a unique internal condition of a system.


- Change of states: *function of present states & present inputs.*
- Output:

- For Mealy Machine- *Output is a function of both present inputs & present states.*
- For Moore Machine-

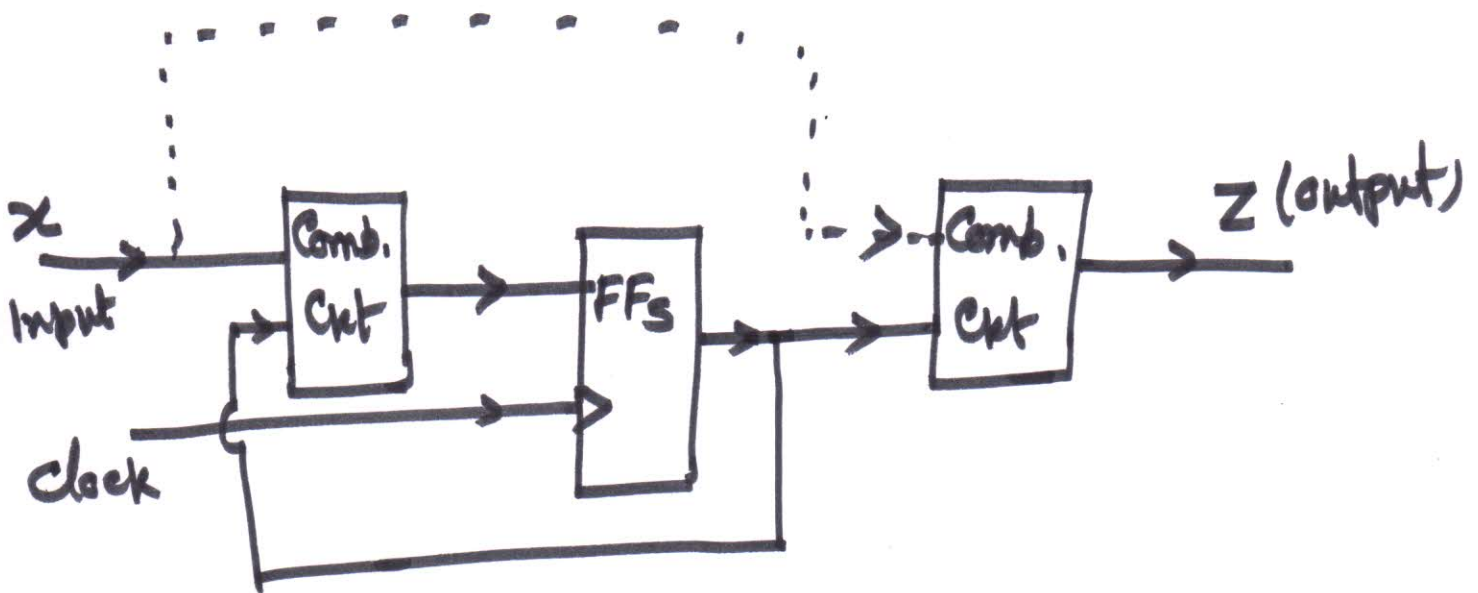*Out is function of present states only.*



Example of Mealy Machine:

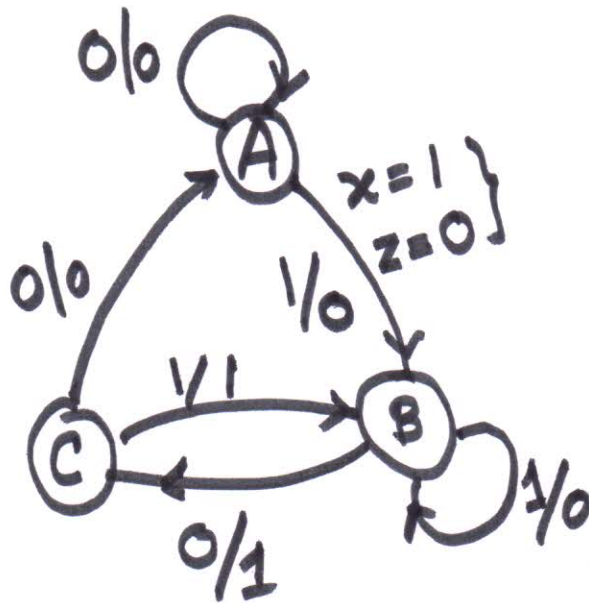

State Diagram

State Transition Table

| Present States | Next States |     | Output (z) |     |
|----------------|-------------|-----|------------|-----|
|                | x=0         | x=1 | x=0        | x=1 |
| A              | A           | B   | 0          | 0   |
| B              | C           | B   | 1          | 0   |
| C              | A           | B   | 0          | 1   |

State Mapping

$q_1, q_0$   
 A  $\rightarrow$  00  
 B  $\rightarrow$  01  
 C  $\rightarrow$  11

TT

| Present States |                | Vp<br>x | Next States                 |                             | Vp of the FFs  |                | Output (z) |
|----------------|----------------|---------|-----------------------------|-----------------------------|----------------|----------------|------------|
| q <sub>1</sub> | q <sub>0</sub> |         | q <sub>1</sub> <sup>+</sup> | q <sub>0</sub> <sup>+</sup> | d <sub>1</sub> | d <sub>0</sub> |            |
| 0              | 0              | 0       | 0                           | 0                           | 0              | 0              | 0          |
| 0              | 0              | 1       | 0                           | 1                           | 0              | 1              | 0          |
| 0              | 1              | 0       | 1                           | 1                           | 1              | 1              | 1          |
| 0              | 1              | 1       | 0                           | 1                           | 0              | 1              | 0          |
| 1              | 1              | 0       | 0                           | 0                           | 0              | 0              | 0          |
| 1              | 1              | 1       | 0                           | 1                           | 0              | 1              | 1          |
| 1              | 0              | 0       | x                           | x                           | x              | x              | 0          |
| 1              | 0              | 1       | x                           | x                           | x              | x              | 0          |


$$\underline{d_0} = \sum m(1, 2, 3, 7) + \sum d(4, 5)$$

| q <sub>1</sub> \ q <sub>0</sub> | 0 | 1 |
|---------------------------------|---|---|
| 0                               | 0 | 1 |
| 1                               | 1 | 1 |
| 1                               | x | x |

$$d_0 = x + \bar{q}_1 q_0$$


$$\underline{d_1} = \bar{q}_1 q_0 x$$

| q <sub>1</sub> \ q <sub>0</sub> | 0 | 1 |
|---------------------------------|---|---|
| 0                               | 0 | 0 |
| 1                               | 1 | 1 |
| 1                               | x | x |

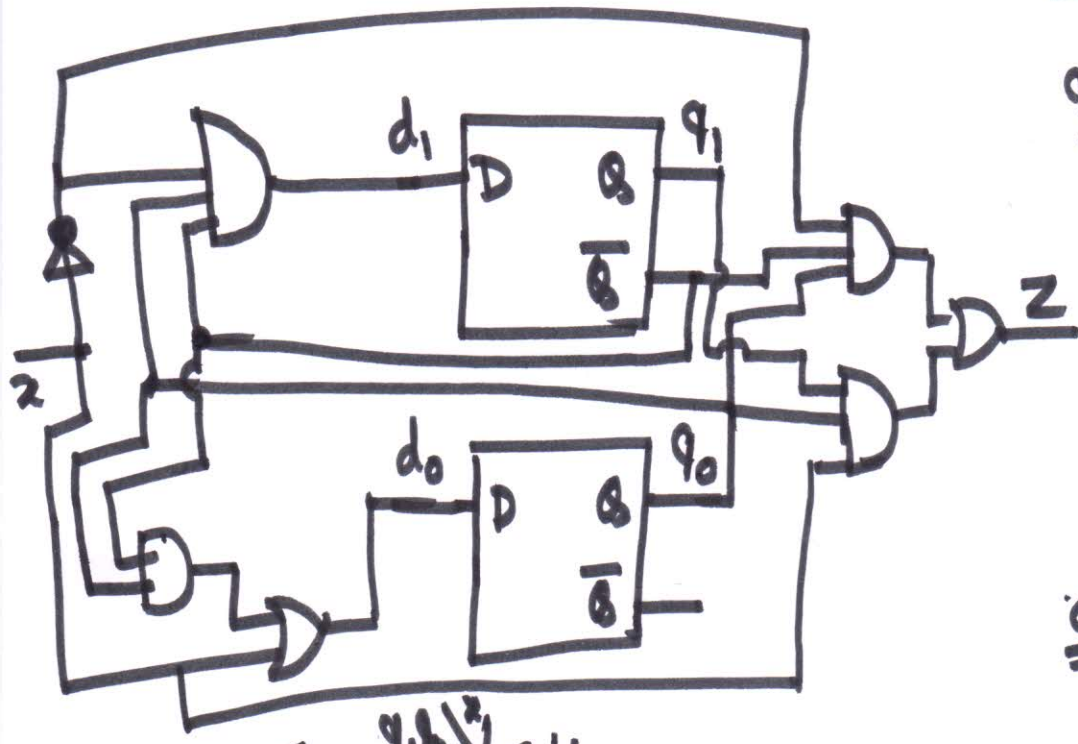

$$\underline{z} = \bar{q}_1 q_0 \bar{x} + q_1 q_0 x$$

Example of Moore Machine:

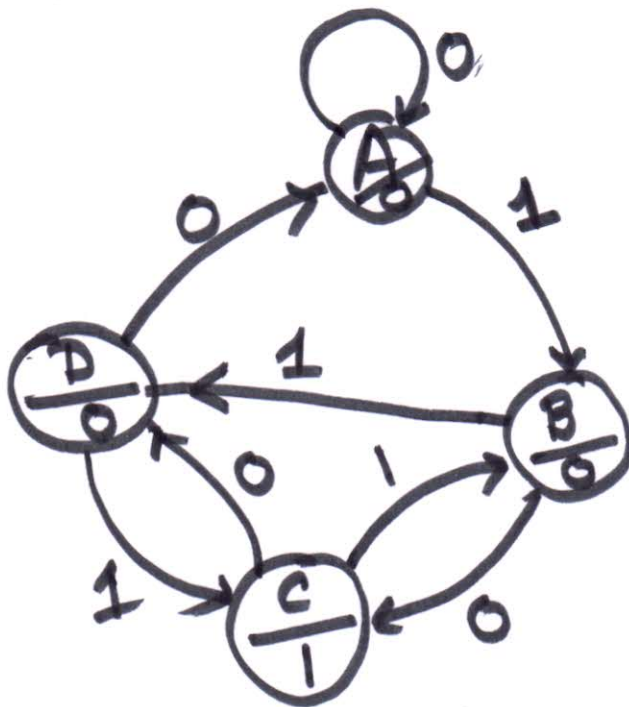

State Transition table

| Present State | Next State |     | output |
|---------------|------------|-----|--------|
|               | x=0        | x=1 |        |
| A             | A          | B   | 0      |
| B             | C          | D   | 0      |
| C             | D          | B   | 1      |
| D             | A          | C   | 0      |