

Basic Electronic Circuits

Credit Structure (L-T-P-Cr): (3-0-3-4.5)

Course Code: EL103

Instructor Introduction:

Name: Dr. Rajib Lochan Das

Qualification: PhD, IIT Kharagpur

Research Interest:

- Graph Signal Processing
- Machine Learning
- Adaptive Signal Processing
- Compressive Sensing
- Image Processing
- Biomedical Signal Processing
- Hardware Implementation of Adaptive Algorithms

Teaching Interest:

- Signals and Systems
- Digital Signal Processing
- Analog Electronics
- Circuit Theory
- Digital Logic Design
- Control Systems
- Adaptive Signal Processing

TOPICS COVERED:

1. Resistive Electric Circuits:

- I. Charge, current and voltage
- II. Ohm's law and ideal sources
- III. Kirchhoff's voltage & current Law
- IV. Node analysis and Mesh analysis
- V. Thevenin & Norton equivalents

2. Electric Circuits with Capacitors and Inductors

- I. First and Second Order Circuits and its D.C Response
- II. Laplace Transform and Sinusoidal Steady-State Analysis of RC, RL and RLC Circuits
- III. Phasor Diagrams, Frequency Response and Filters

3.Two-Port Networks

4.Diode and Transistors


5.Operational Amplifiers

Books:

- * 1. "Fundamentals of Electric Circuits" by Charles K Alexander and Matthew N. O. Sadiku
- 2. "Engineering Circuit Analysis" by W. H. Hayt and J. E. Kemmerley
- ✓ 3. "Network Analysis" by Van Valkenberg
- 4. "Network Analysis & Synthesis" by Franklin S. KUO
- 5. "Introduction to Electric Circuits" by R. C. Dorf and J. A. Svoboda
- ✓ 6. "Microelectronic Circuits: Theory And Applications" by Adel S. Sedra and Kenneth C. Smith
- 7. "Electronic Circuits: Analysis And Design" by Donald A. Neamen
- 8. "Integrated Electronics: Analog and Digital Circuits and Systems" by Jacob Millman and Christos Halkias
- 9. "Design with Operational Amplifiers and Analog Integrated Circuits" by Sergio Franco



Circuit Elements:

1. Resistors

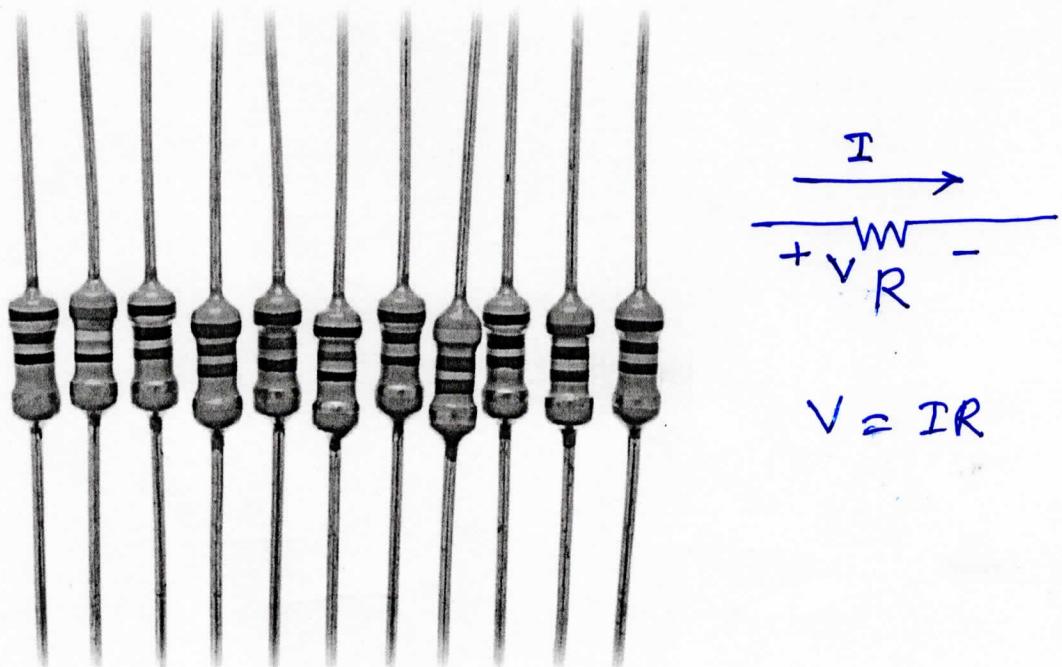


$$V = IR$$


2. Battery (Voltage Source)

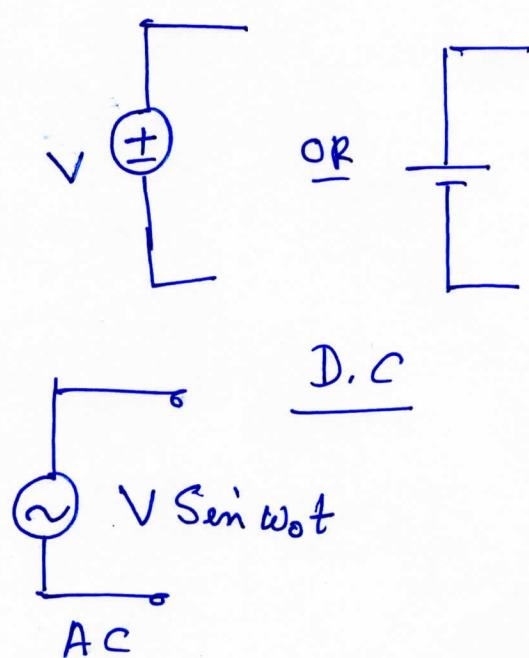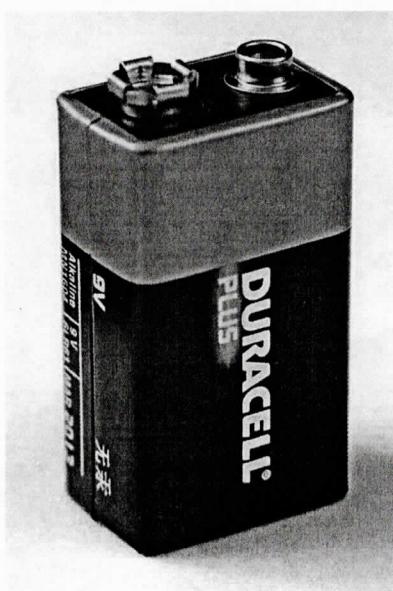

3. Inductors

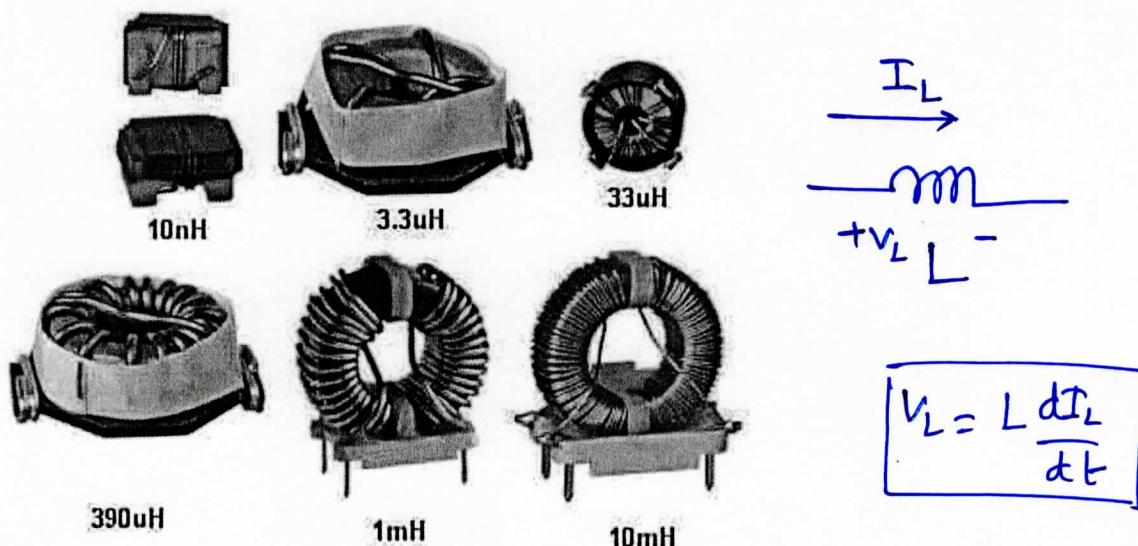

4. Capacitors

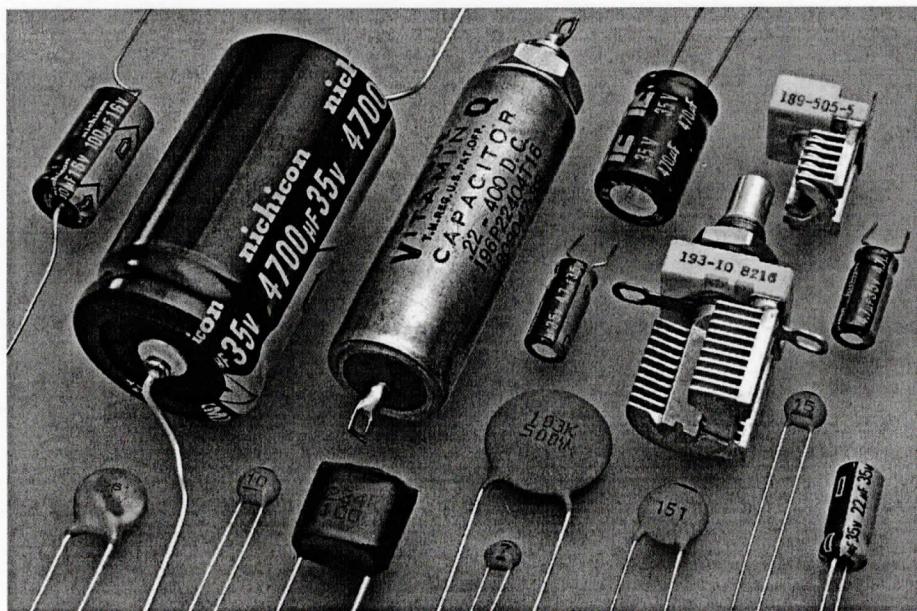


Hand-drawn annotations for a capacitor:



- A vertical line with an arrow pointing up labeled $+C$.
- A horizontal line with an arrow pointing right labeled I_C .
- A hand-drawn symbol consisting of two parallel lines with arrows pointing in opposite directions labeled C .
- The voltage across the capacitor is shown as $+v_C$ at the top and C at the bottom.

$I_C = C \frac{dv_C}{dt}$


5. Diode

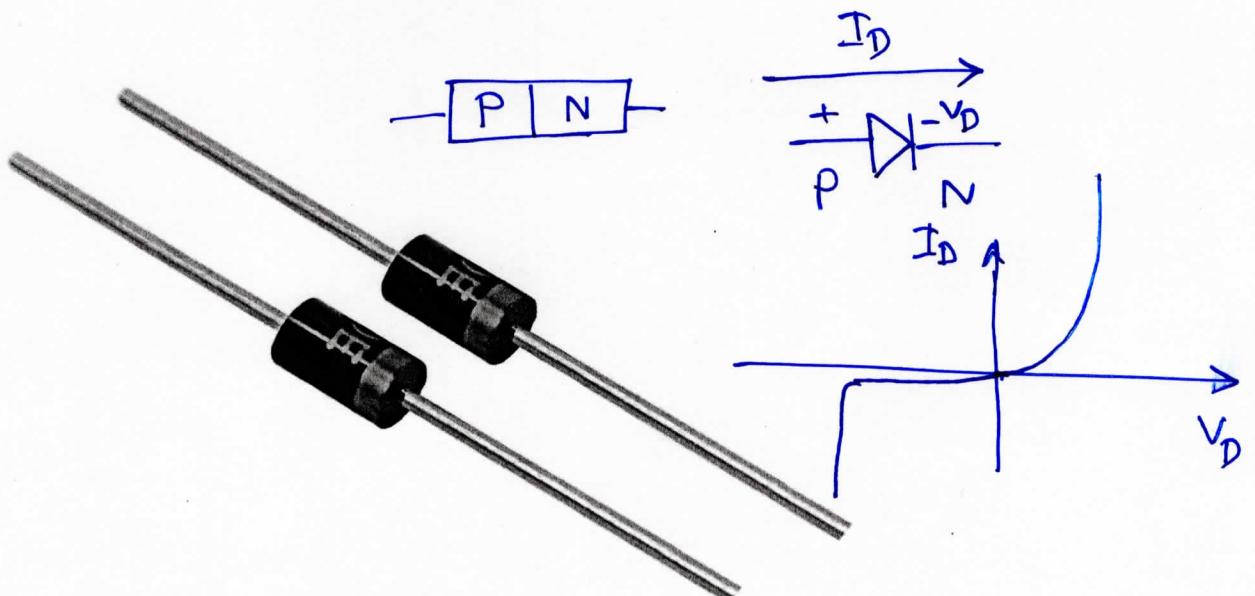


6. Transistors

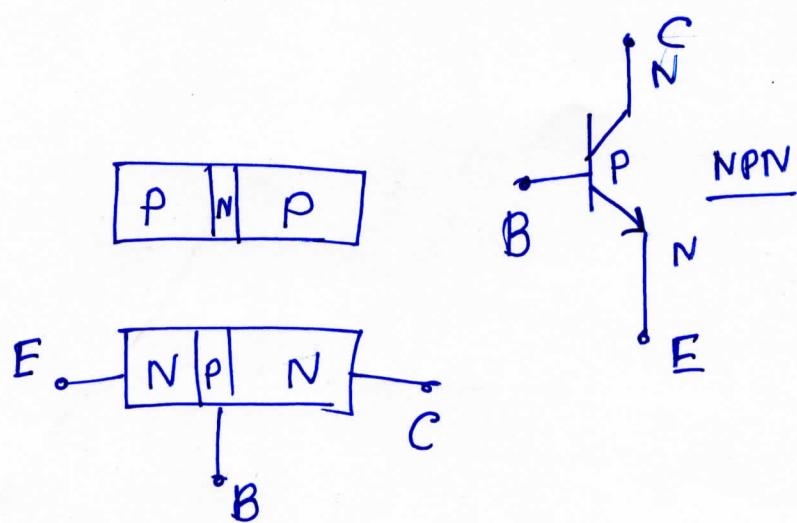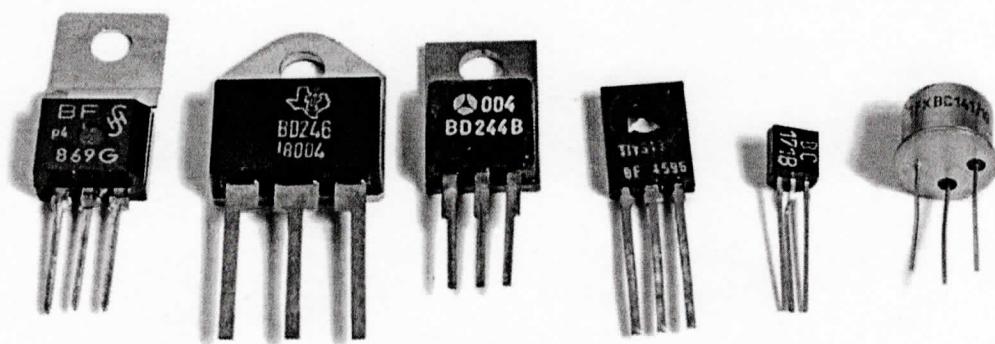


7. Operational Amplifiers

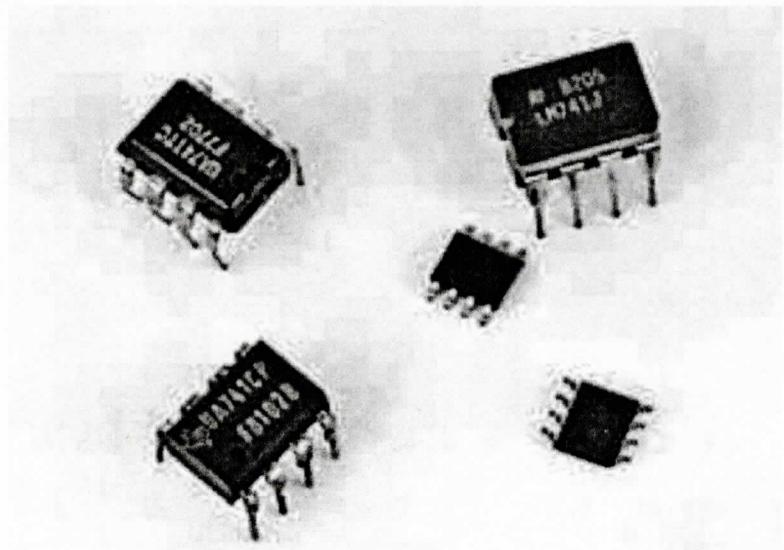


IC 741

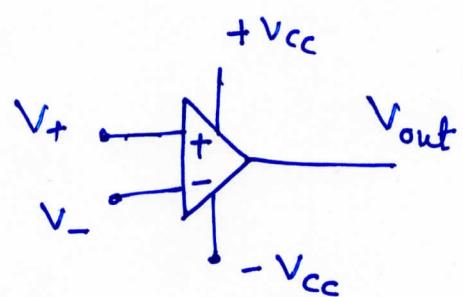

Resistive Circuits

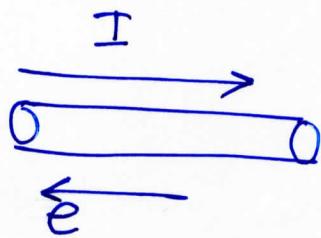


$$I = \frac{dq}{dt}$$

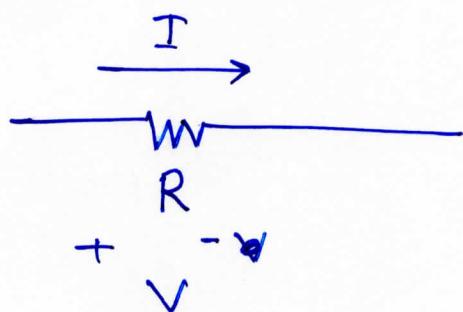

1) Ohm's Law

$$V = IR$$

2) Series Connection of Resistances

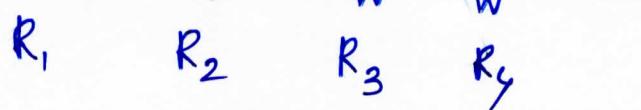


\equiv



$$R_{\text{eq}} = R_1 + R_2 + R_3 + R_4 = \sum_{i=1}^4 R_i$$

3) Parallel Connection

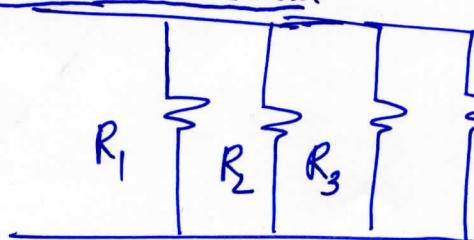


$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_{eq}} \Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2} < \min[R_1, R_2]$$

when $R_1 = R_2 = R$, $R_{eq} = \frac{R}{2}$

Q) Voltage Sources

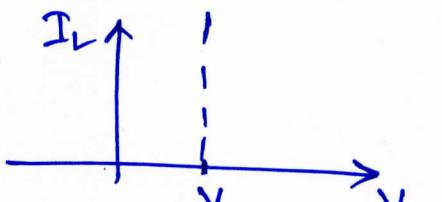

$$V - I_L R_L \text{ or } V = V_L + I_L R_L \quad I_L = \frac{V}{R_L} \quad V_L = V$$

ideal DC voltage source ($R=0$)

Internal Resistance R_s

$$I_L = \frac{V_s}{R_s + R_L}$$

$$V_s = I_s R_s + I_L R_L$$


practical voltage source

$(R \neq 0)$

$$V_L = I L R_L$$

$$V_L = I_L R_L$$

$$R_L \gg R_s$$

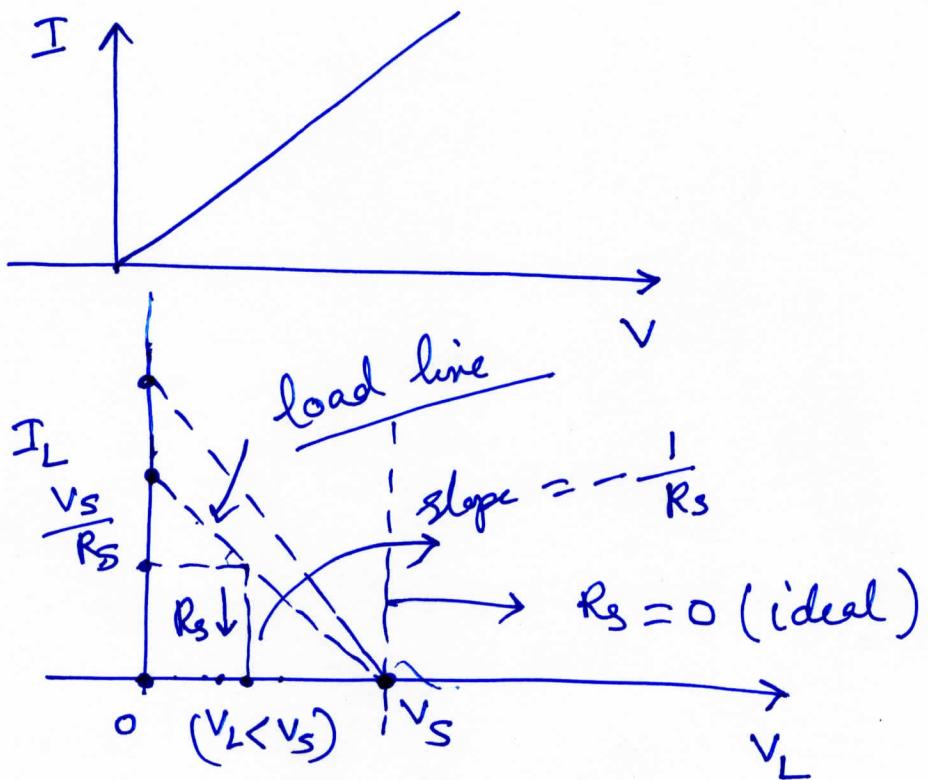


$$V_s = I_L R_s + I_L R_L = I_L R_s + V_L$$

$\Rightarrow \boxed{V_L + I_L R_s = V_s} \rightarrow \text{load line}$


equation

$V_s, R_s \rightarrow \text{Constant}$

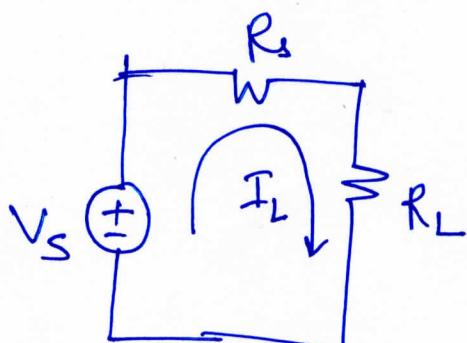



$$I_L = \frac{V_s}{R_s + R_L}$$

Current Source

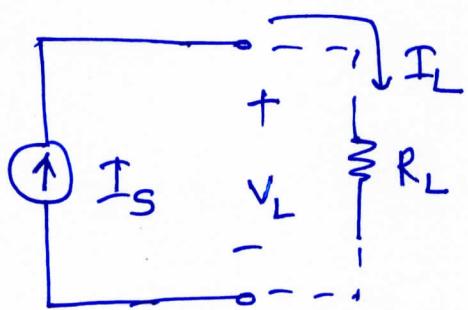


$$I_L = I_s$$

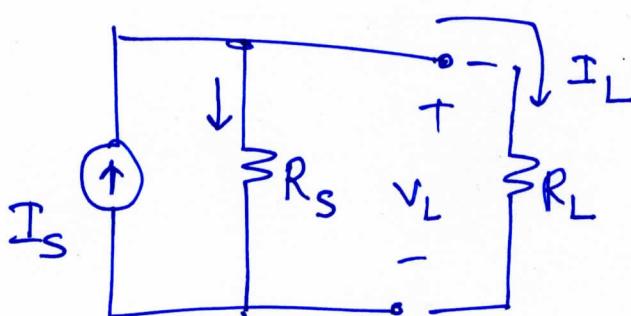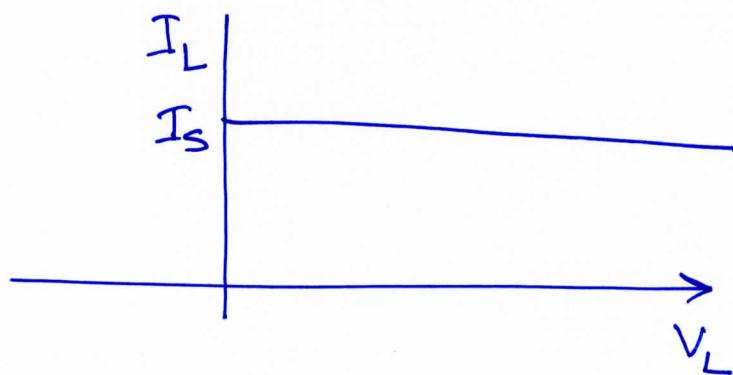DC Current Source ($R_s \rightarrow \infty$)




$$R_s \gg R_L$$

$$I_s = \frac{V_L}{R_s} + I_L$$

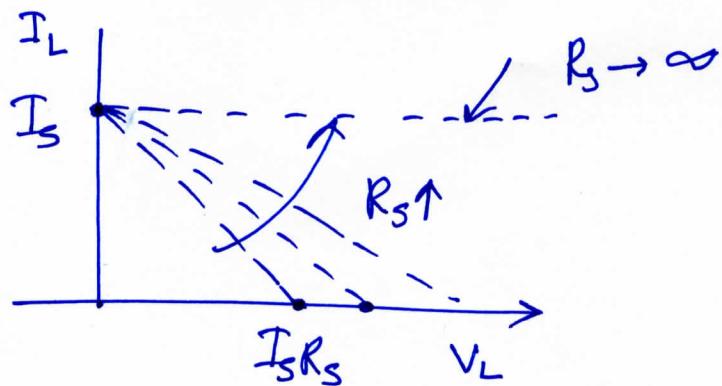

Voltage Divider

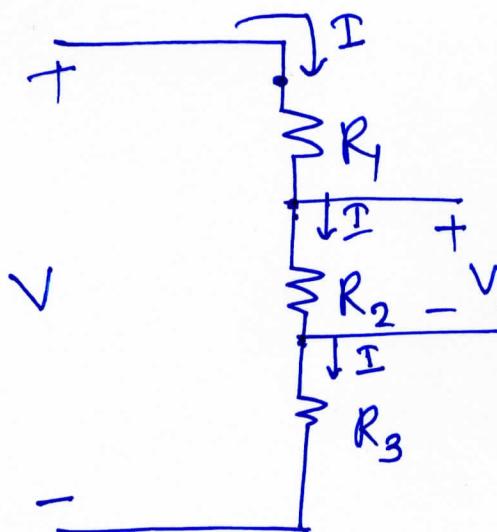


$$I = \frac{V}{R_1 + R_2 + R_3}$$

$$V_2 = I R_2$$

$$= \left(\frac{R_2}{R_1 + R_2 + R_3} \right) \times V$$


$$V_2 \propto R_2$$

~~Ex~~

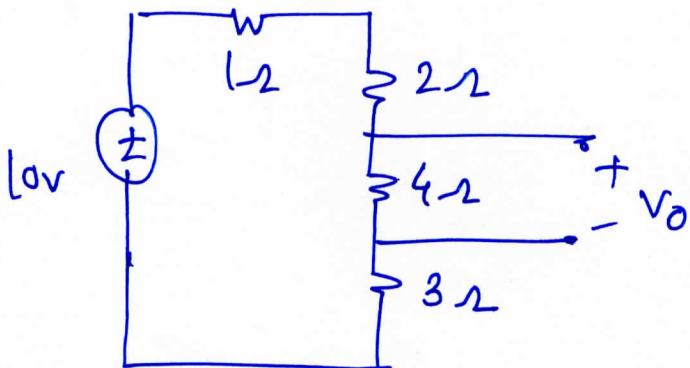

$$\begin{aligned} V_0 &= \frac{4}{1+2+4+3} \times 10 \\ &= \frac{4}{10} \times 10 = 4V \end{aligned}$$

Current Divider

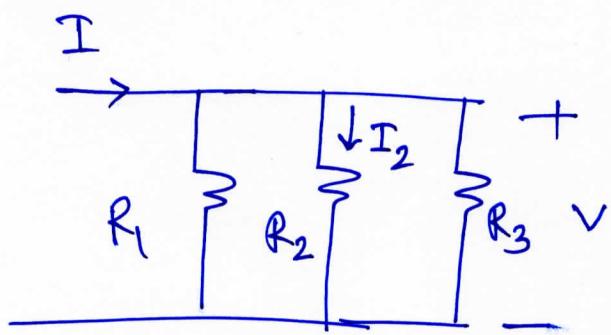

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$= y_1 V + y_2 V + y_3 V$$

where $y_i = \frac{1}{R_i}$,

$$= (y_1 + y_2 + y_3) V \quad i=1, 2, 3$$

$$\Rightarrow V = \frac{I}{y_1 + y_2 + y_3}$$

$$\Rightarrow I_2 = \frac{V}{R_2} = y_2 V$$


$$= y_2 \times \frac{I}{y_1 + y_2 + y_3}$$

$$= \left(\frac{y_2}{y_1 + y_2 + y_3} \right) \times I$$

$$I_2 \propto y_2$$

Ans

For two-resistances

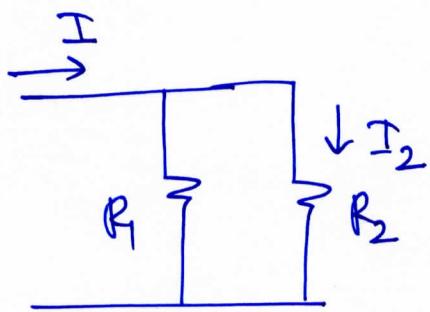


$$I_2 = \frac{y_2}{y_1 + y_2} \times I$$

$$= \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} \times I$$

$$= \frac{R_1}{R_1 + R_2} \times I$$


Ex

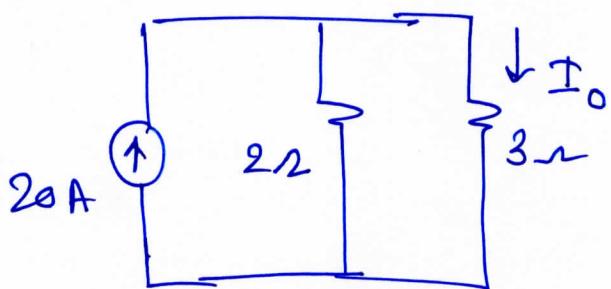

$$I_o = \frac{2}{2+3} \times 20$$

$$= 8A$$


Source Transformation :-

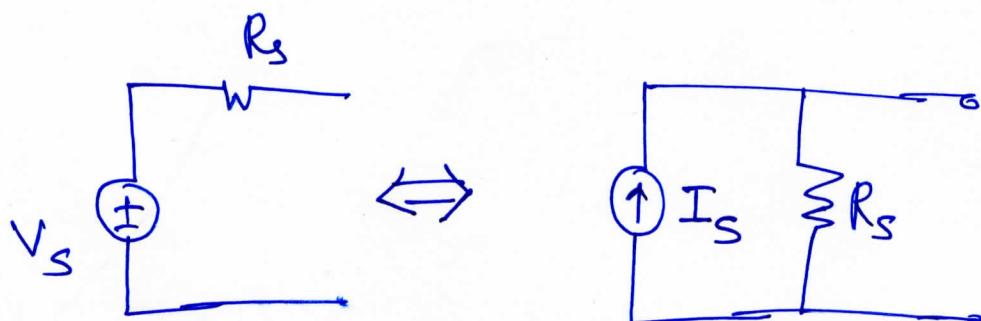

$$V_s = I_s R_s$$

$$I_s = \frac{V_s}{R_s}$$

Ex.1:

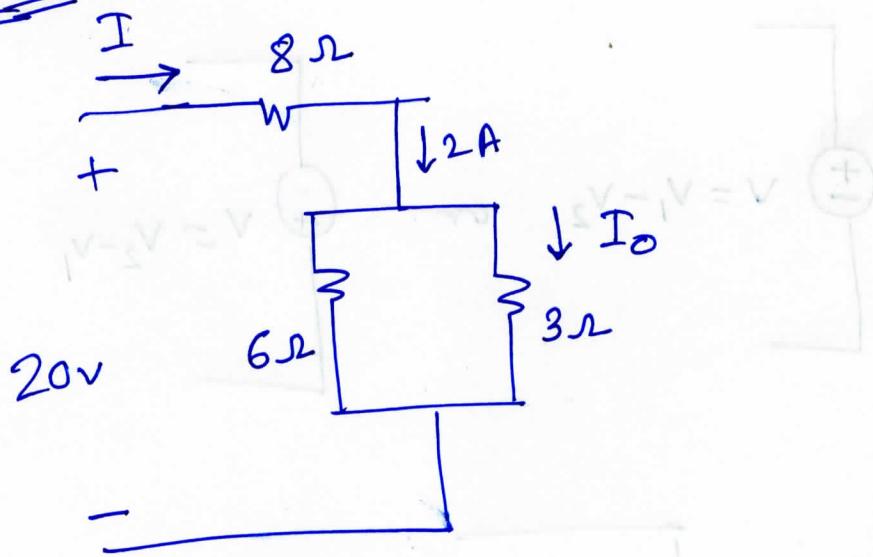


$$6//3$$


$$= \frac{6 \times 3}{6+3} = 2\Omega$$

$$I = \frac{20}{8+2} = 2A$$
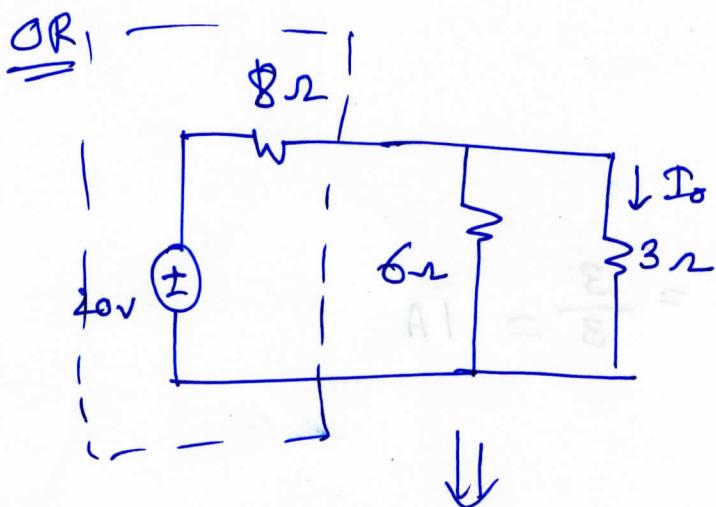
$$I_o = \frac{6}{3+6} \times I = \frac{2}{9} \times 2 = \frac{4}{3} A$$





$$I_s = \frac{20}{8} = \frac{5}{2} A$$

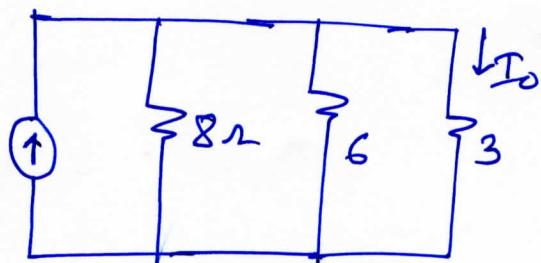

$$I_o = \frac{\frac{1}{3}}{\frac{1}{8} + \frac{1}{6} + \frac{1}{3}} \times \frac{5}{2} = \frac{4}{3} A$$


e.x.


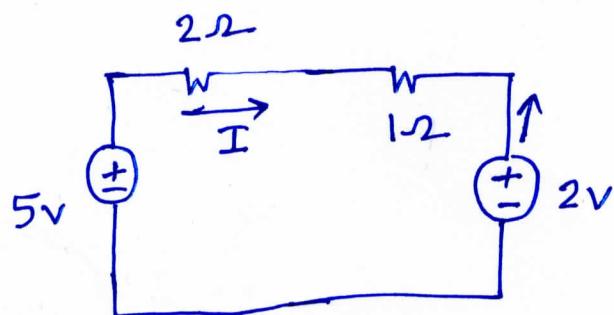
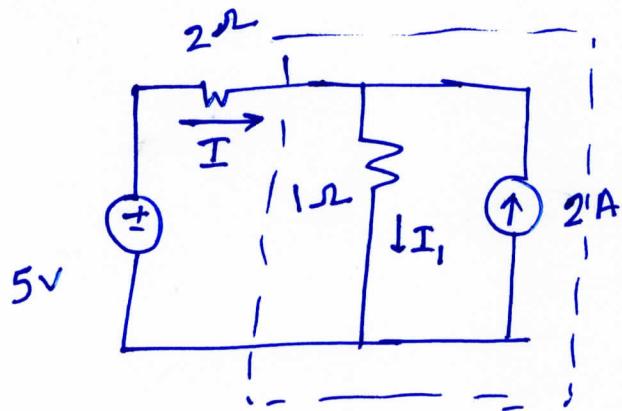


$$I = \frac{5-2}{2+1} = \frac{3}{3} = 1A$$

$$I_1 = 1+2 = 3A$$



Series Connection of voltage sources

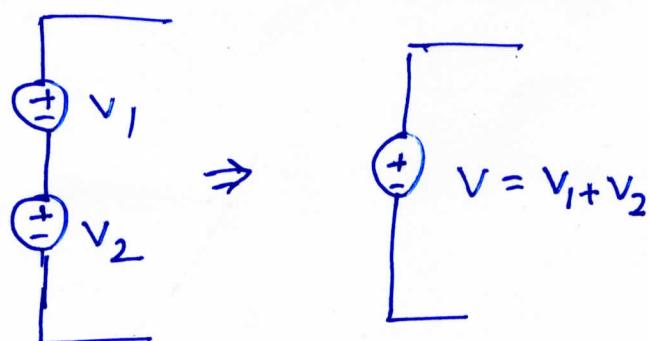

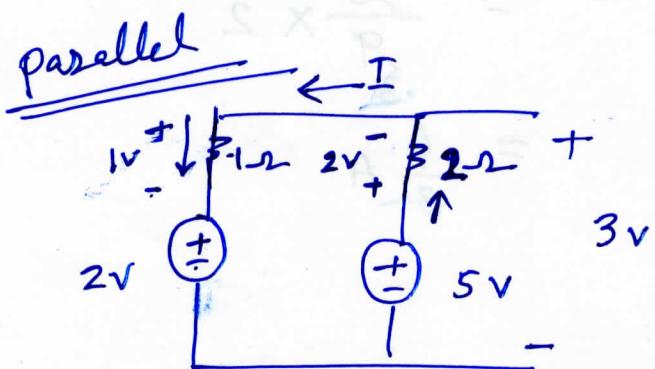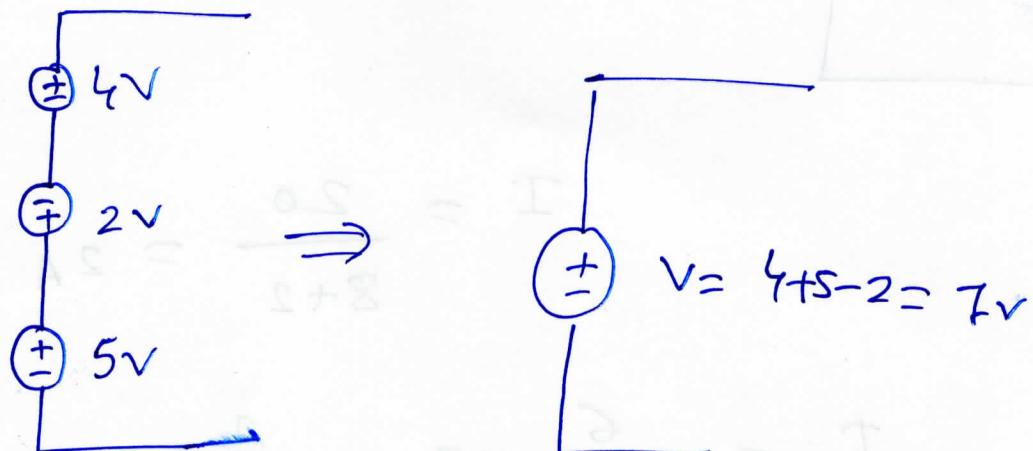
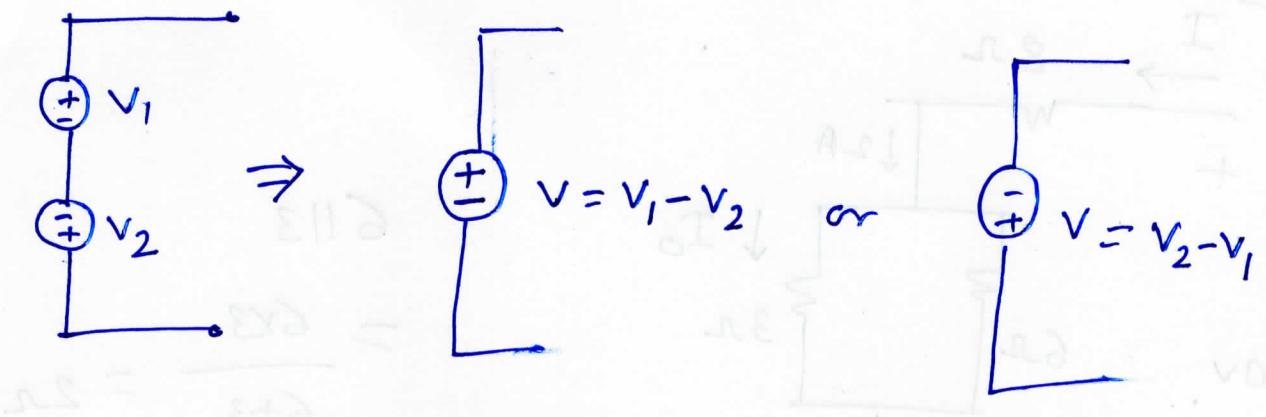




$$I = \frac{5-2}{1+2} = \frac{3}{3} = 1A$$

parallel connection of current sources :


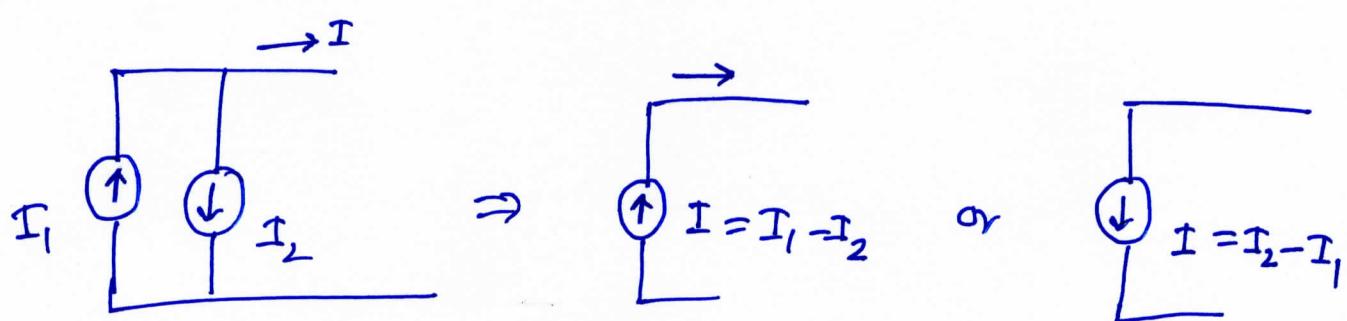
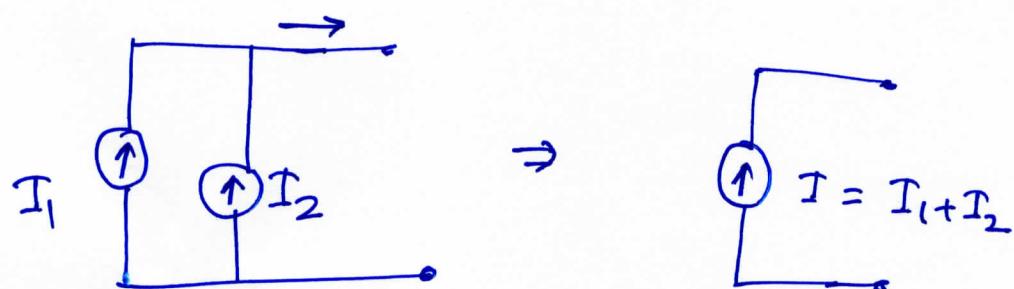


ex:

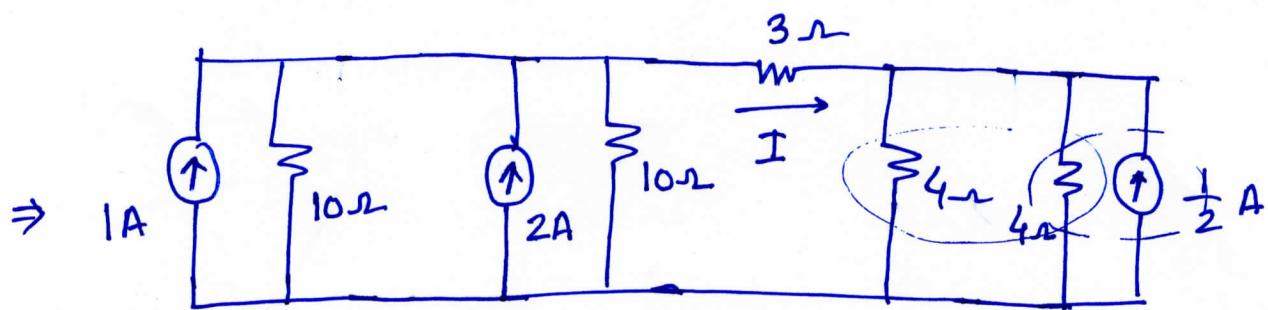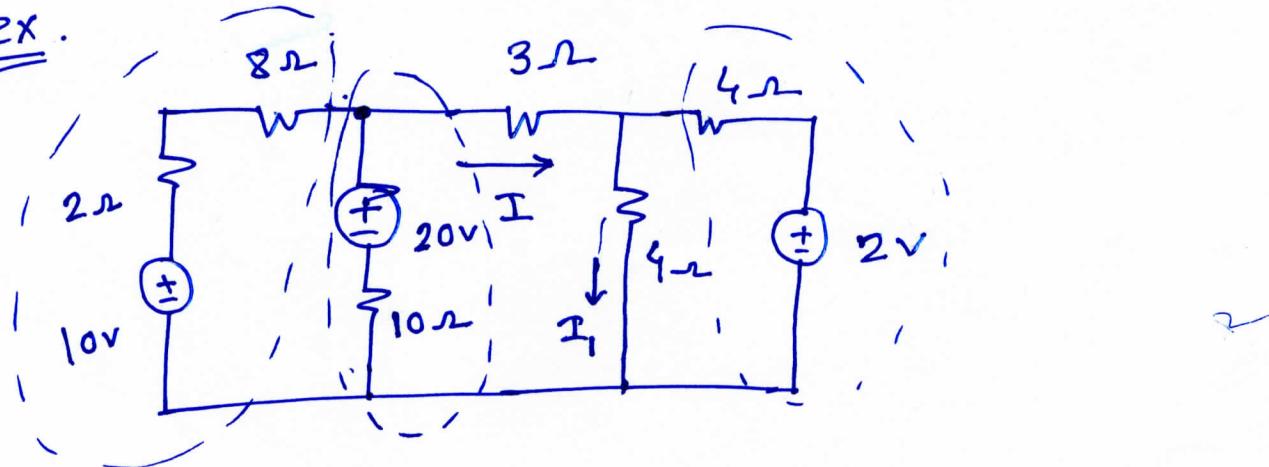

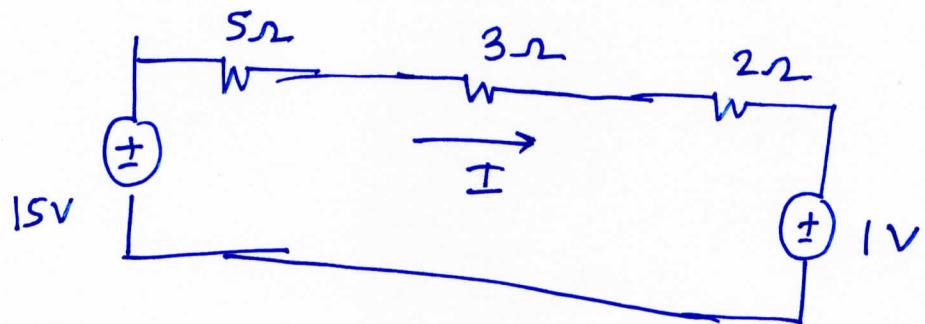
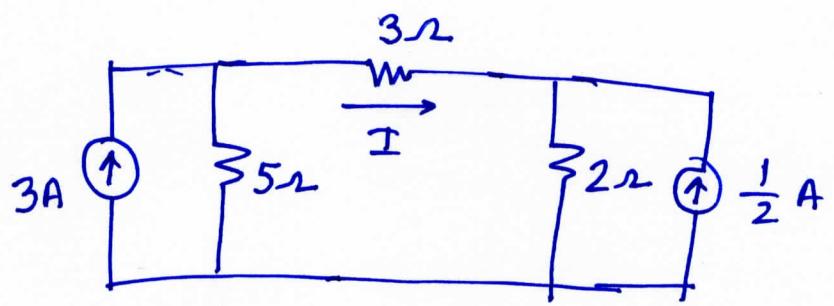

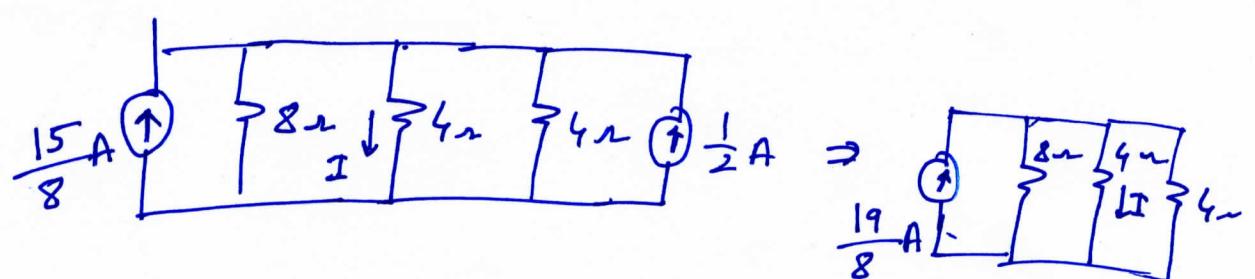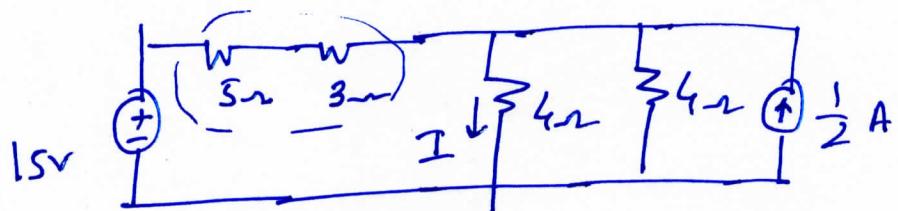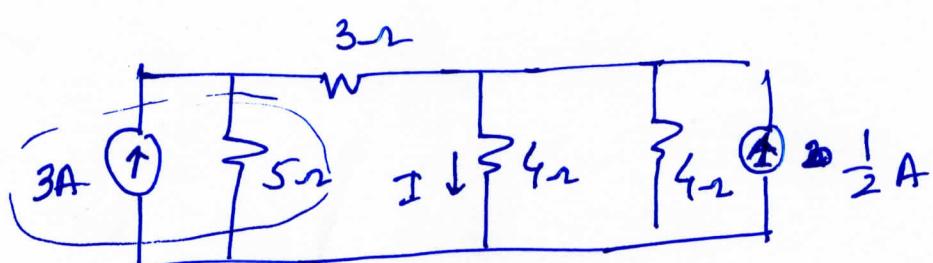
$$I = \frac{15 - 1}{5 + 3 + 2} = \frac{14}{10} = 1.4 A$$




(19)

Dependent Sources

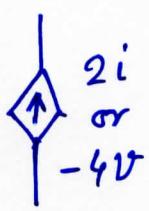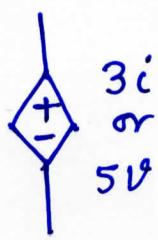

1) Current Controlled Current Source (CCCS):

ex.

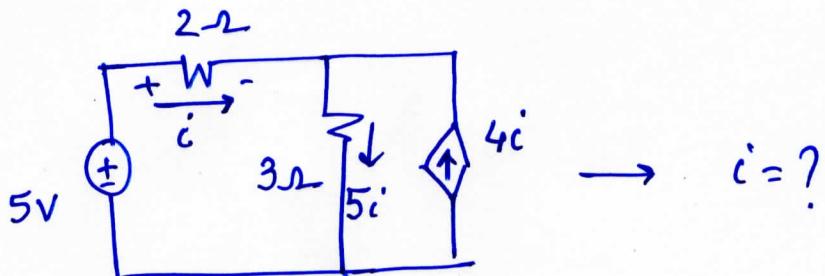


$$5 - 2i - 3 \times 5i = 0$$

$$\Rightarrow 5 - 17i = 0$$

$$\Rightarrow i = \frac{5}{17} \text{ A}$$

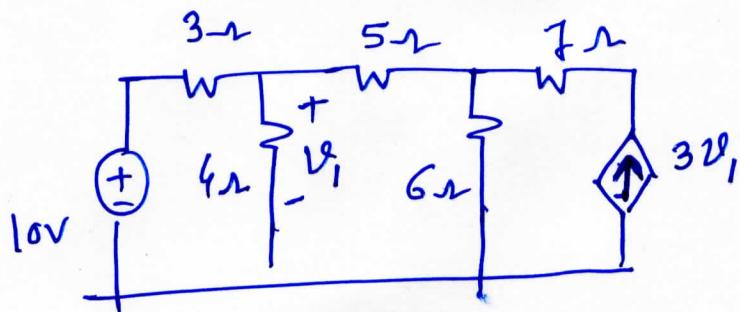
2) Voltage Controlled Current Source (VCCS):






3) Current controlled voltage source (CCVS)

4) Voltage Controlled Voltage Source (VCVS)

ex

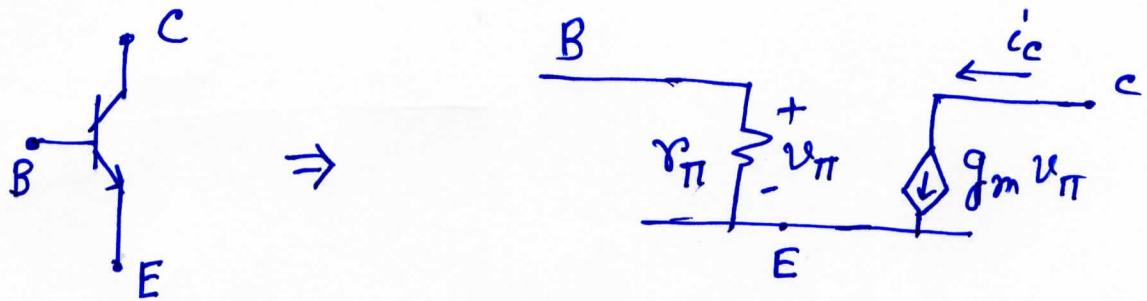

(Small signal mode)
(ac)

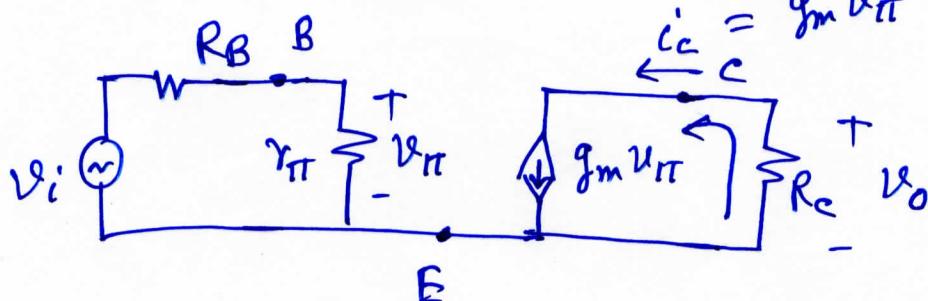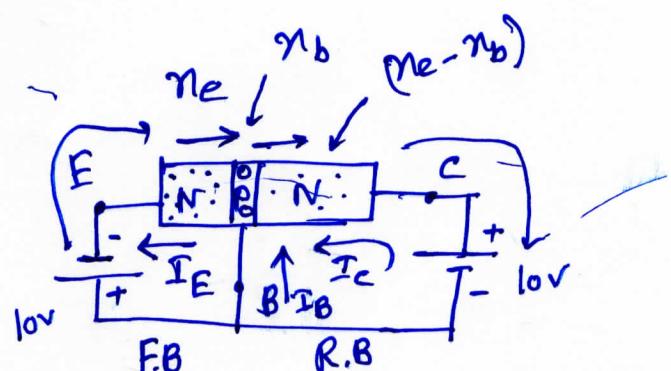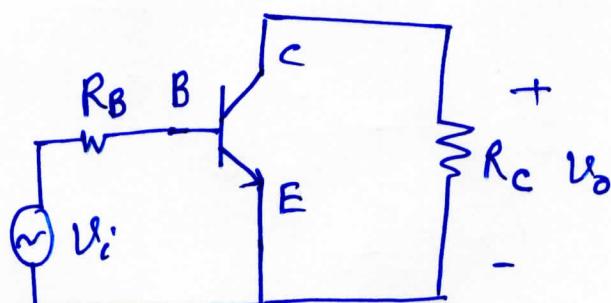

$$\Rightarrow u_{\pi} = \frac{r_{\pi}}{R_B + r_{\pi}} \times u_i$$

$$\text{and } u_o = (-i_c) R_c$$

$$= -g_m u_{\pi} R_c$$


$$= -g_m R_c \frac{r_{\pi}}{R_B + r_{\pi}} u_i$$

$$\Rightarrow \frac{u_o}{u_i} = -\frac{g_m r_{\pi} R_c}{R_B + r_{\pi}} = \text{voltage gain} (\gg 1)$$

$$\frac{i_c}{I_B} = \frac{n_e - n_b}{n_b} = \beta$$


$$I_c = \beta I_B$$

$$I_E = I_B + I_c$$

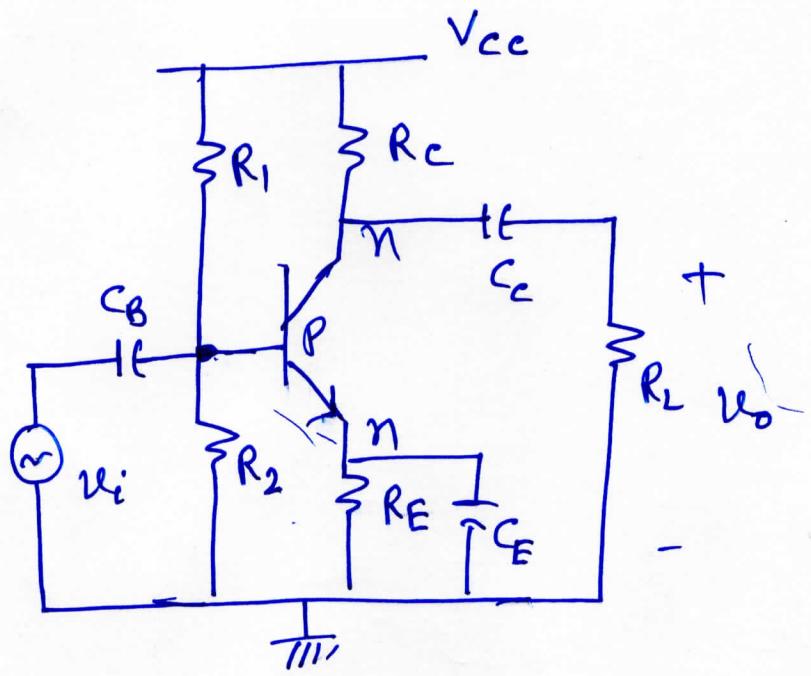

CE

Kirchhoff's Current law (KCL):

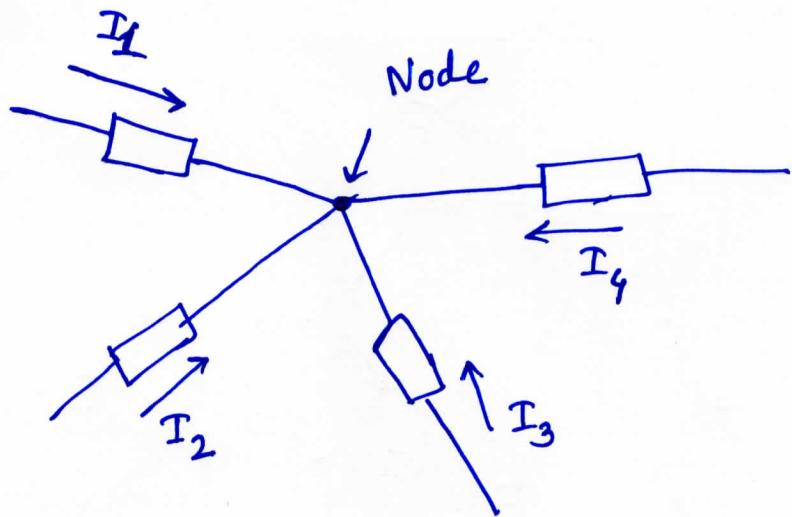


$$I_1 + I_2 + I_3 + I_4 = 0$$

In general,

$$\sum_{i=1}^N I_i = 0$$

Kirchhoff's Voltage law (KVL):

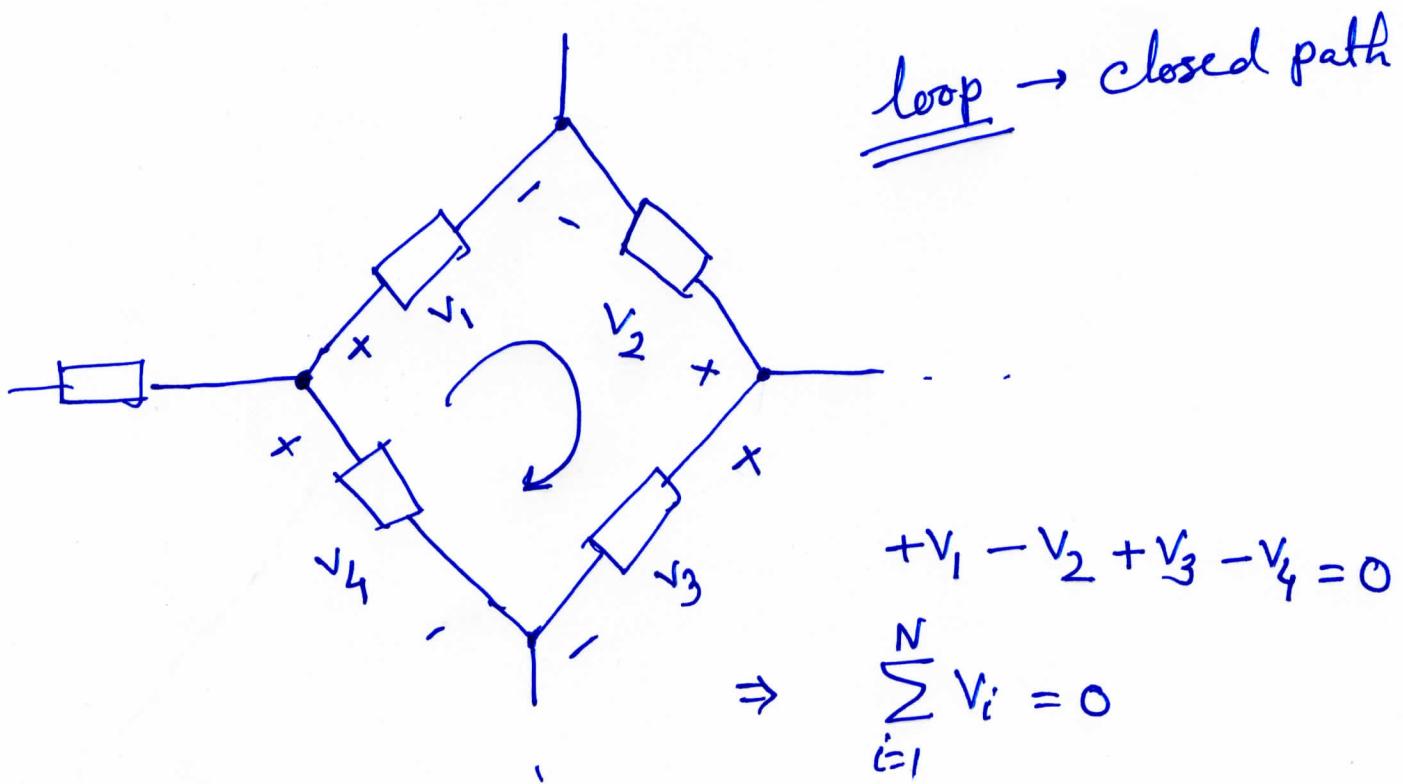


$$+v_1 - v_2 + v_3 - v_4 = 0$$

$$\Rightarrow \sum_{i=1}^N V_i = 0$$

(23)

Node Analysis :-

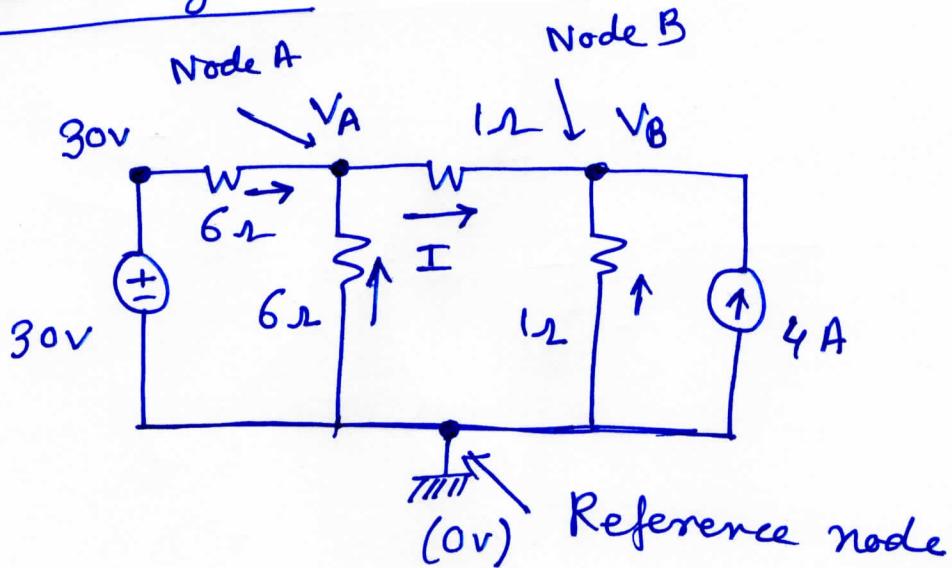

Apply KCL at node A

$$\frac{30 - V_A}{6} + \frac{0 - V_A}{6} + \frac{V_B - V_A}{1} = 0$$

$$\Rightarrow 30 - V_A - V_A + 6V_B - 6V_A = 0$$

$$\Rightarrow 30 - 8V_A + 6V_B = 0$$

$$\Rightarrow 4V_A - 3V_B = 15 \quad \dots \quad (1)$$

Apply KCL at node B

$$\frac{V_A - V_B}{1} + \frac{0 - V_B}{1} + 4 = 0$$


$$\Rightarrow V_A - 2V_B = -4 \quad \dots \quad (2)$$

$$\left. \begin{array}{l} V_A = \frac{42}{5} \\ V_B = \frac{31}{5} \end{array} \right\}$$

$$I = \frac{V_A - V_B}{1} = \frac{42 - 31}{5} = \frac{11}{5} \text{ A}$$

(24)

ex

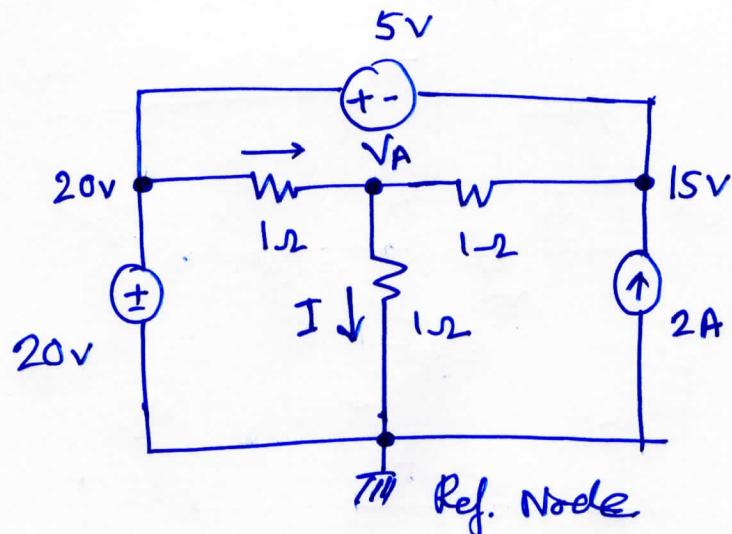

KCL at node A


$$\frac{20 - V_A}{1} + \frac{0 - V_A}{1} + \frac{15 - V_A}{1} = 0$$

$$\Rightarrow 20 + 15 - 3V_A = 0$$

$$\Rightarrow V_A = \frac{35}{3} \text{ V}$$

$$I = \frac{V_A - 0}{1} = \frac{35}{3} \text{ Amp.}$$

ex.

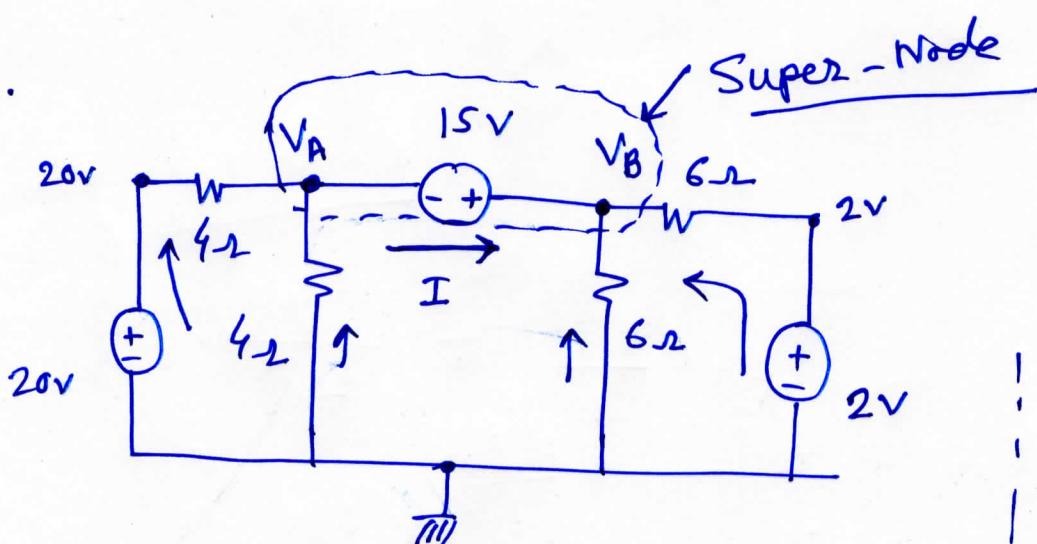

$$\begin{aligned} V_B - V_A &= 15 \\ \Rightarrow V_A + 15 &= V_B \end{aligned}$$

Node A

$$\frac{20 - V_A}{4} + \frac{0 - V_A}{4} - I = 0 \quad | \quad \text{Node B}$$


$$- - \text{(i)} \quad | \quad \frac{2 - V_B}{6} + \frac{0 - V_B}{6} + I = 0 \quad - - \text{(ii)}$$

(25)


Adding (i) & (ii),

$$\frac{20 - V_A}{4} + \frac{0 - V_A}{4} - \cancel{\frac{2 - V_B}{6}} + \frac{0 - V_B}{6} + \cancel{\frac{0 - V_B}{6}} = 0$$
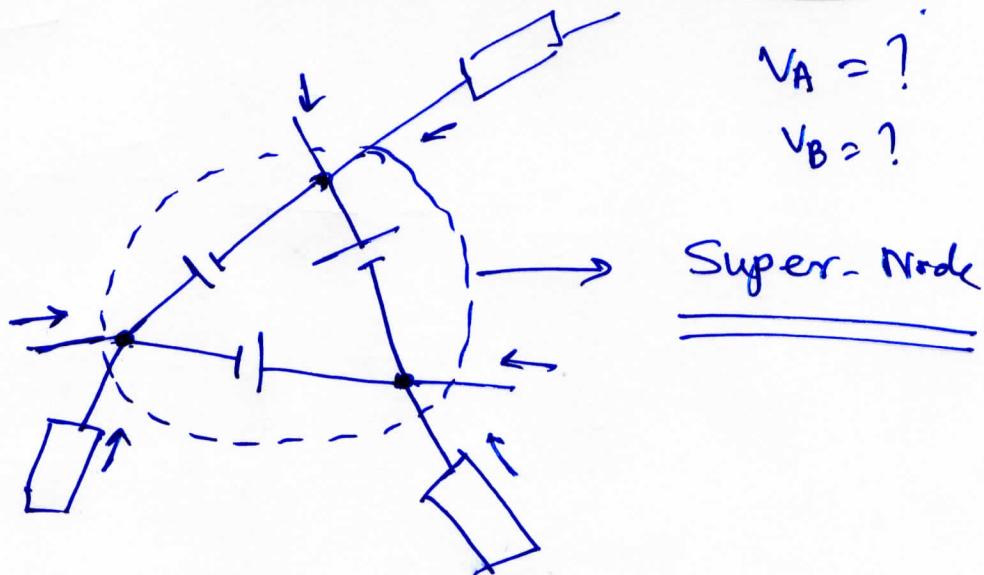
$$\Rightarrow \frac{20 - V_A}{4} + \frac{0 - V_A}{4} + \frac{2 - V_B}{6} + \frac{0 - V_B}{6} = 0$$



Mesh Analysis :-

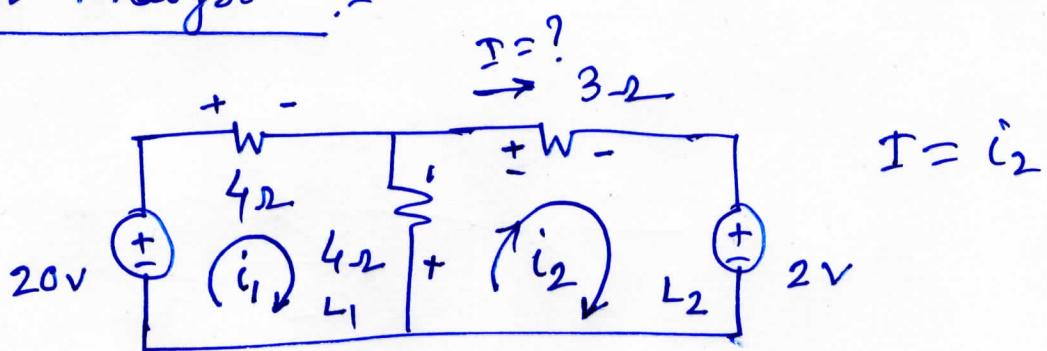

For L_1

$$20 - 4i_1 - 4(i_1 - i_2) = 0$$

For L_2

$$2 + 3i_2 + 4(i_2 - i_1) = 0$$

$$\Rightarrow 8i_1 - 4i_2 = 20$$

$$\Rightarrow 2c_1 - c_2 = 5 \quad \dots \quad (1)$$

Again,

$$2 + 7i_2 - 4i_1 = 0$$

$$\Rightarrow 4i_1 - 7i_2 = 2 \quad \text{--- (1)}$$

$$(i) \times 2 - (ii)$$


$$-2i_2 + 7i_2 = 10 - 2$$

$$\Rightarrow \sin_2 = 8$$

$$\Rightarrow C_2 = 8/5 \text{ A}$$

$$\Rightarrow I = i_2 = 8/5 \text{ A}$$

ex

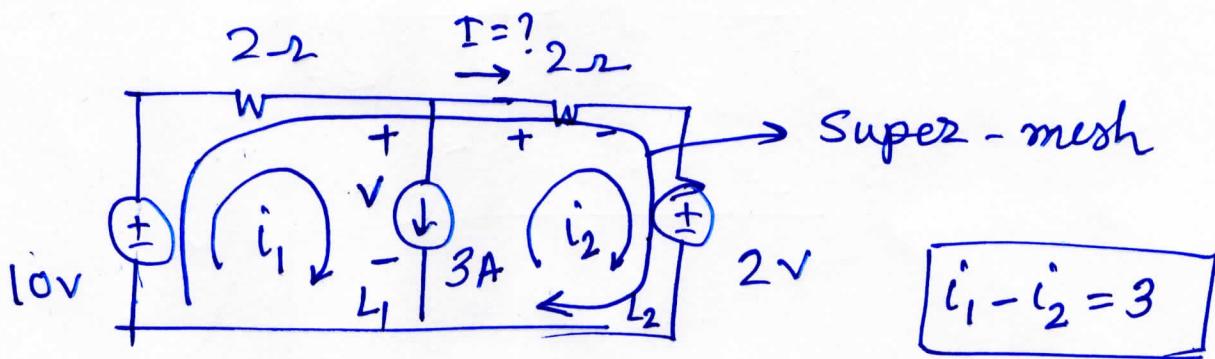


$$\begin{array}{l} \text{L1} \\ \text{L2} \end{array} \quad \left. \begin{array}{l} 10 - 2i_1 - v = 0 \\ v - 2i_2 - 2 = 0 \end{array} \right\} \begin{array}{l} \text{Adding} \\ \boxed{10 - 2i_1} \end{array}$$



$$\text{V} - 2i_2 - 2 = 0 \quad \left\{ \begin{array}{l} 10 - 2i_1 - 2i_2 - 2 = 0 \\ \downarrow \text{KVL for } \underline{\text{bigger loop}} \end{array} \right.$$

Superposition Theorem :-

ex

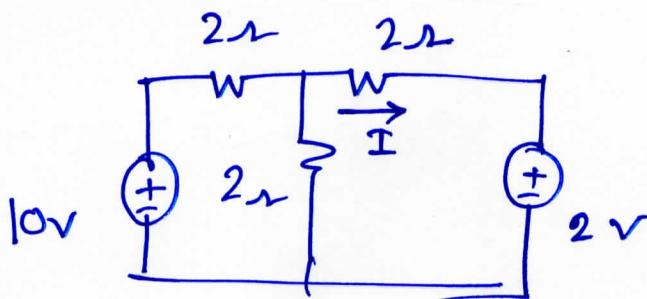

10V is acting

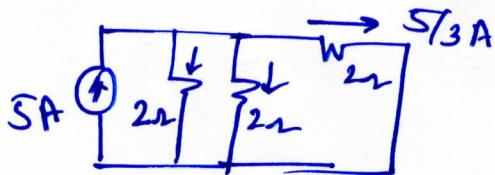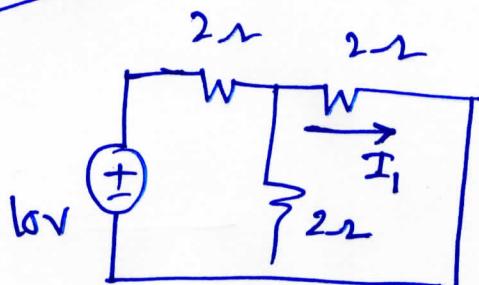

$$\Rightarrow I_1 = 5/3 \text{ A}$$

Replacement

Voltage source

→ shorted

Current source


→ opened

by Superposition theorem,

$$I = I_1 + I_2$$

$$= \frac{5}{3} - \frac{2}{3} = \frac{3}{3} = 1 \text{ A}$$

ex

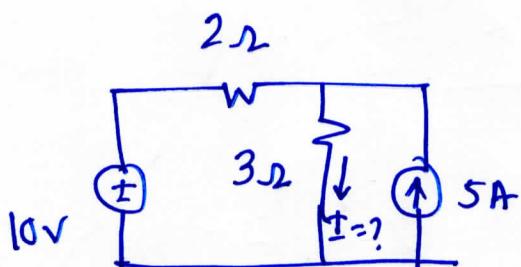

$$\begin{aligned} I &= \frac{10}{5} + \frac{2}{2+3} \times 5 \\ &= 2 + 2 = 4 \text{ A} \end{aligned}$$